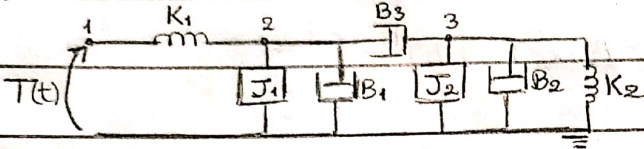



Kevin Chu 10705908

PME3380-Exercícios da Aula 03/09

1) Sistema rotativo - Circuito Mecânico:



Circuito Elétrico:

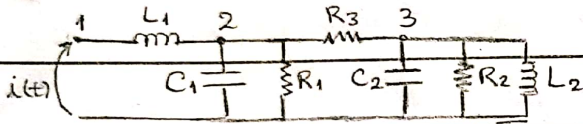


Eq 1: $i(t) = v_1 \left(\frac{1}{L_1 D} \right) - v_2 \left(\frac{1}{L_2 D} \right) \rightarrow T(t) = K_1 \theta_1 - K_2 \theta_2$

Eq 2: $0 = v_2 \left(C_1 D + \frac{1}{L_1 D} + \frac{1}{R_1} + \frac{1}{R_3} \right) - v_1 \left(\frac{1}{L_1 D} \right) - v_3 \left(\frac{1}{R_3} \right) \rightarrow 0 = J_1 \ddot{\theta}_2 + B_1 \dot{\theta}_2 + B_3 \theta_2 + K_1 \theta_1 - K_1 \theta_2 - B_3 \dot{\theta}_3$

Eq 3: $0 = v_3 \left(C_2 D + \frac{1}{L_2 D} + \frac{1}{R_2} + \frac{1}{R_3} \right) - v_2 \left(\frac{1}{R_3} \right) \rightarrow 0 = J_2 \ddot{\theta}_3 + B_3 \dot{\theta}_3 + B_2 \theta_2 + K_2 \theta_3 - B_3 \dot{\theta}_2$

2) a)

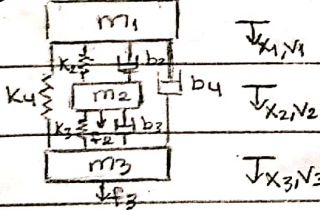

$T = \frac{1}{2} m_1 \dot{x}_1^2 + \frac{1}{2} m_2 \dot{x}_2^2 + \frac{1}{2} m_3 \dot{x}_3^2$

$V = \frac{1}{2} K_1 x_1^2 + \frac{1}{2} K_2 (x_2 - x_1)^2 + \frac{1}{2} K_3 (x_3 - x_2)^2 + \frac{1}{2} K_4 (x_3 - x_1)^2$

$R = \frac{1}{2} b_1 \dot{x}_1^2 + \frac{1}{2} b_2 (\dot{x}_2 - \dot{x}_1)^2 + \frac{1}{2} b_3 (\dot{x}_3 - \dot{x}_2)^2 + \frac{1}{2} b_4 (\dot{x}_3 - \dot{x}_1)^2$

Lagrange: $\frac{d}{dt} \left(\frac{\partial L}{\partial \dot{q}_i} \right) - \frac{\partial L}{\partial q_i} + \frac{\partial R}{\partial \dot{q}_i} = Q$

$q_1 = x_1: \frac{\partial L}{\partial \dot{x}_1} = m_1 \dot{x}_1 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_1} \right) = m_1 \ddot{x}_1$

$\frac{\partial L}{\partial x_1} = -K_1 x_1 + K_2 (x_2 - x_1) + K_3 (x_3 - x_2) + K_4 (x_3 - x_1)$

$\frac{\partial R}{\partial \dot{x}_1} = b_1 \dot{x}_1 - b_2 (\dot{x}_2 - \dot{x}_1) - b_4 (\dot{x}_3 - \dot{x}_1)$

$m_1 \ddot{x}_1 + K_1 x_1 - K_2 (x_2 - x_1) - K_3 (x_3 - x_2) - K_4 (x_3 - x_1) + b_1 \dot{x}_1 - b_2 (\dot{x}_2 - \dot{x}_1) - b_4 (\dot{x}_3 - \dot{x}_1) = 0$

$q_2 = x_2: \frac{\partial L}{\partial \dot{x}_2} = m_2 \dot{x}_2 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_2} \right) = m_2 \ddot{x}_2$

$\frac{\partial L}{\partial x_2} = -K_2 (x_2 - x_1) + K_3 (x_3 - x_2)$

$\frac{\partial R}{\partial \dot{x}_2} = b_2 (\dot{x}_2 - \dot{x}_1) - b_3 (\dot{x}_3 - \dot{x}_2)$

$m_2 \ddot{x}_2 + K_2 (x_2 - x_1) - K_3 (x_3 - x_2) + b_2 (\dot{x}_2 - \dot{x}_1) - b_3 (\dot{x}_3 - \dot{x}_2) = f_2(t)$


$$q_3 = x_3; \frac{\partial L}{\partial \dot{x}_3} = m_3 \dot{x}_3 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_3} \right) = m_3 \ddot{x}_3$$

$$\frac{\partial L}{\partial x_3} = -K_3(x_3 - x_2) - K_4(x_3 - x_1)$$


$$\frac{\partial R}{\partial \dot{x}_3} = b_3(\dot{x}_3 - \dot{x}_2) + b_4(\dot{x}_3 - \dot{x}_1)$$

$$m_3 \ddot{x}_3 + K_3(x_3 - x_2) + K_4(x_3 - x_1) + b_3(\dot{x}_3 - \dot{x}_2) + b_4(\dot{x}_3 - \dot{x}_1) = f_3(t)$$

b)

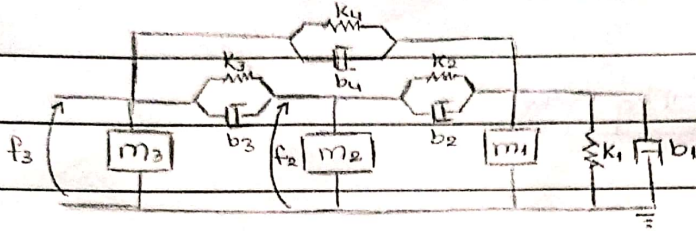

c)

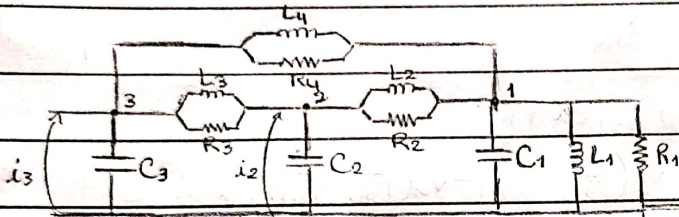

$$\text{No 1: } V_1 \left(C_1 D + \frac{1}{L_1 D} + \frac{1}{L_2 D} + \frac{1}{L_3 D} + \frac{1}{L_4 D} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) - V_2 \left(\frac{1}{L_2 D} + \frac{1}{R_2} \right) - V_3 \left(\frac{1}{L_3 D} + \frac{1}{R_3} \right) = 0$$

$$\text{No 2: } V_2 \left(C_2 D + \frac{1}{L_2 D} + \frac{1}{L_3 D} + \frac{1}{R_2} + \frac{1}{R_3} \right) - V_1 \left(\frac{1}{L_2 D} + \frac{1}{R_2} \right) - V_3 \left(\frac{1}{L_3 D} + \frac{1}{R_3} \right) = i_2$$


$$\text{No 3: } V_3 \left(C_3 D + \frac{1}{L_3 D} + \frac{1}{L_4 D} + \frac{1}{R_3} + \frac{1}{R_4} \right) - V_1 \left(\frac{1}{L_3 D} + \frac{1}{R_3} \right) - V_2 \left(\frac{1}{L_3 D} + \frac{1}{R_3} \right) = i_3$$

$$\text{e) } m_1 \ddot{x}_1 + K_1 x_1 - K_2(x_2 - x_1) - K_3(x_3 - x_2) - K_4(x_3 - x_1) + b_1 \dot{x}_1 - b_2(\dot{x}_2 - \dot{x}_1) - b_4(\dot{x}_3 - \dot{x}_1) = 0$$

$$m_2 \ddot{x}_2 + K_2(x_2 - x_1) - K_3(x_3 - x_2) + b_2(\dot{x}_2 - \dot{x}_1) - b_3(\dot{x}_3 - \dot{x}_2) = f_2$$

$$m_3 \ddot{x}_3 + K_3(x_3 - x_2) + K_4(x_3 - x_1) + b_3(\dot{x}_3 - \dot{x}_2) + b_4(\dot{x}_3 - \dot{x}_1) = f_3$$

3) e)

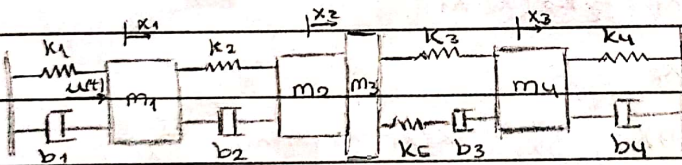

$$T = \frac{1}{2} m_1 \dot{x}_1^2 + \frac{1}{2} (m_2 + m_3) \dot{x}_2^2 + \frac{1}{2} m_4 \dot{x}_3^2$$

$$V = \frac{1}{2} K_1 x_1^2 + \frac{1}{2} K_2 (x_2 - x_1)^2 + \frac{1}{2} K_3 (x_3 - x_2)^2 + \frac{1}{2} K_4 x_3^2 + \frac{1}{2} K_5 (x_3 - x_2)^2$$

$$R = \frac{1}{2} b_1 \dot{x}_1^2 + \frac{1}{2} b_2 (\dot{x}_2 - \dot{x}_1)^2 + \frac{1}{2} b_3 (\dot{x}_3 - \dot{x}_2)^2 + \frac{1}{2} b_4 \dot{x}_3^2$$

$$q_1 = x_1; \frac{\partial L}{\partial \dot{x}_1} = m_1 \dot{x}_1 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_1} \right) = m_1 \ddot{x}_1$$

$$\frac{\partial L}{\partial x_1} = -K_1 x_1 + K_2(x_2 - x_1)$$

$$\frac{\partial R}{\partial \dot{x}_1} = b_1 \dot{x}_1 - b_2(\dot{x}_2 - \dot{x}_1)$$

$$m_1 \ddot{x}_1 + K_1 x_1 - K_2(x_2 - x_1) + b_1 \dot{x}_1 - b_2(\dot{x}_2 - \dot{x}_1) = u(t)$$

$$q_2 = x_2; \frac{\partial L}{\partial \dot{x}_2} = (m_2 + m_3) \dot{x}_2 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_2} \right) = (m_2 + m_3) \ddot{x}_2$$

$$\frac{\partial L}{\partial x_2} = -K_2(x_2 - x_1) + K_3(x_3 - x_2) + K_5(x_3 - x_2)$$

$$\frac{\partial R}{\partial \dot{x}_2} = b_2(\dot{x}_2 - \dot{x}_1) - b_3(\dot{x}_3 - \dot{x}_2)$$



$$(m_2 + m_3) \ddot{x}_2 + K_2(x_2 - x_1) - K_3(x_3 - x_2) - K_5(x_3 - x_2) + b_2(\dot{x}_2 - \dot{x}_1) - b_3(\dot{x}_3 - \dot{x}_2) = 0$$

$q_3 = x_3: \frac{\partial L}{\partial \dot{x}_3} = m_4 \dot{x}_3 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_3} \right) = m_4 \ddot{x}_3$

$\frac{\partial L}{\partial x_3} = -K_3(x_3 - x_2) - K_4 x_3 - K_5(x_3 - x_2)$


$\frac{\partial R}{\partial \dot{x}_3} = b_3(\dot{x}_3 - \dot{x}_2) + b_4 \dot{x}_3$

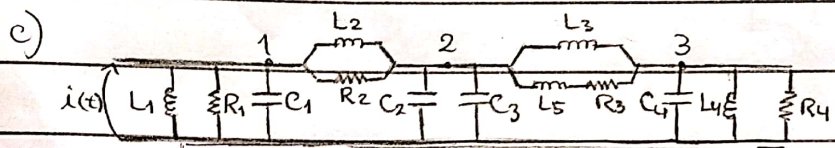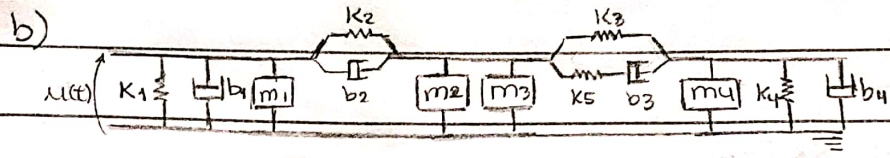$m_4 \ddot{x}_3 + K_3(x_3 - x_2) + K_4 x_3 + K_5(x_3 - x_2) + b_3(\dot{x}_3 - \dot{x}_2) + b_4 \dot{x}_3 = 0$



d) No 1: $V_1(C_1 D + \frac{1}{L_1 D} + \frac{1}{L_2 D} + \frac{1}{R_1} + \frac{1}{R_2}) - V_2(\frac{1}{L_2 D} + \frac{1}{R_2}) = i(t)$
 No 2: $V_2(C_2 D + C_3 D + \frac{1}{L_2 D} + \frac{1}{L_3 D} + \frac{1}{R_2} + \frac{1}{R_3}) - V_1(\frac{1}{L_2 D} + \frac{1}{R_2}) - V_3(\frac{1}{L_3 D} + \frac{1}{L_5 D} + \frac{1}{R_3}) = 0$
 No 3: $V_3(C_3 D + \frac{1}{L_3 D} + \frac{1}{L_4 D} + \frac{1}{R_3} + \frac{1}{R_4}) - V_2(\frac{1}{L_3 D} + \frac{1}{L_5 D} + \frac{1}{R_3}) = 0$

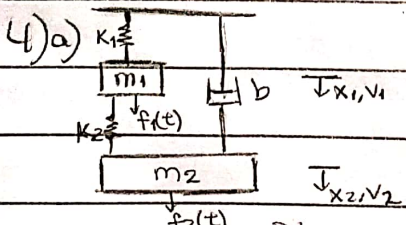e) $m_1 \ddot{x}_1 + k_1 x_1 - k_2(x_2 - x_1) + b_1 \dot{x}_1 - b_2(\dot{x}_2 - \dot{x}_1) = u(t)$
 $(m_2 + m_3) \ddot{x}_2 + k_2(x_2 - x_1) - k_3(x_3 - x_2) - k_5(x_2 - x_2) + b_2(\dot{x}_2 - \dot{x}_1) - b_3(\dot{x}_3 - \dot{x}_2) = 0$
 $m_4 \ddot{x}_3 + k_3(x_3 - x_2) + k_4 x_3 + k_5(x_3 - x_2) + b_3(\dot{x}_3 - \dot{x}_2) + b_4 \dot{x}_3 = 0$





$T = \frac{1}{2} m_1 \dot{x}_1^2 + \frac{1}{2} m_2 \dot{x}_2^2$
 $V = \frac{1}{2} K_1 x_1^2 + \frac{1}{2} K_2 (x_2 - x_1)^2$
 $R = \frac{1}{2} b \dot{x}_2^2$

$q_1 = x_1: \frac{\partial L}{\partial \dot{x}_1} = m_1 \dot{x}_1 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_1} \right) = m_1 \ddot{x}_1; \frac{\partial L}{\partial x_1} = -K_1 x_1 + K_2(x_2 - x_1); \frac{\partial R}{\partial \dot{x}_1} = 0$

$m_1 \ddot{x}_1 + k_1 x_1 - k_2(x_2 - x_1) = f_1(t)$


$q_2 = x_2: \frac{\partial L}{\partial \dot{x}_2} = m_2 \dot{x}_2 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_2} \right) = m_2 \ddot{x}_2; \frac{\partial L}{\partial x_2} = -K_2(x_2 - x_1); \frac{\partial R}{\partial \dot{x}_2} = b \dot{x}_2$

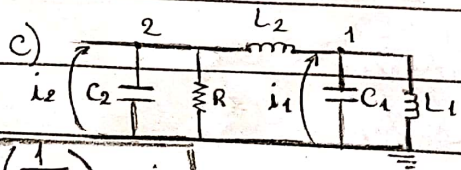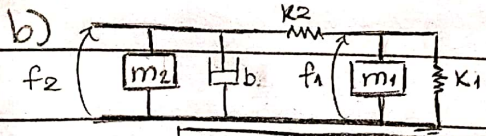$m_2 \ddot{x}_2 + k_2(x_2 - x_1) + b \dot{x}_2 = f_2(t)$



d) No 1: $V_1(C_1 D + \frac{1}{L_1 D} + \frac{1}{L_2 D}) - V_2(\frac{1}{L_2 D}) = i_1$
 No 2: $V_2(C_2 D + \frac{1}{L_2 D} + \frac{1}{R}) - V_1(\frac{1}{L_2 D}) = i_2$

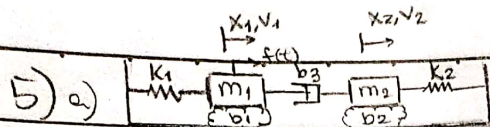e) $m_1 \ddot{x}_1 + k_1 x_1 - k_2(x_2 - x_1) = f_1$
 $m_2 \ddot{x}_2 + k_2(x_2 - x_1) + b \dot{x}_2 = f_2$





$$T = \frac{1}{2} m_1 \dot{x}_1^2 + \frac{1}{2} m_2 \dot{x}_2^2; \quad V = \frac{1}{2} k_1 x_1^2 + \frac{1}{2} k_2 x_2^2; \quad R = \frac{1}{2} b_1 \dot{x}_1^2 + \frac{1}{2} b_2 \dot{x}_2^2 + \frac{1}{2} b_3 (\dot{x}_2 - \dot{x}_1)^2$$

$$q_1 = x_1: \frac{\partial L}{\partial x_1} = m_1 \dot{x}_1 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_1} \right) = m_1 \ddot{x}_1; \quad \frac{\partial L}{\partial x_1} = -k_1 x_1; \quad \frac{\partial R}{\partial \dot{x}_1} = b_1 \dot{x}_1 - b_3 (\dot{x}_2 - \dot{x}_1)$$

$$m_1 \ddot{x}_1 + k_1 x_1 + b_1 \dot{x}_1 - b_3 (\dot{x}_2 - \dot{x}_1) = f(t)$$

$$q_2 = x_2: \frac{\partial L}{\partial x_2} = m_2 \dot{x}_2 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_2} \right) = m_2 \ddot{x}_2; \quad \frac{\partial L}{\partial x_2} = -k_2 x_2; \quad \frac{\partial R}{\partial \dot{x}_2} = b_2 \dot{x}_2 + b_3 (\dot{x}_2 - \dot{x}_1)$$
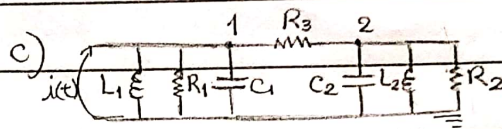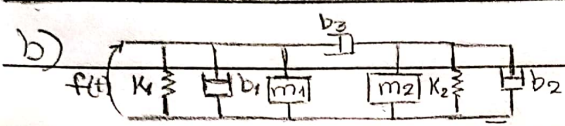
$$m_2 \ddot{x}_2 + k_2 x_2 + b_2 \dot{x}_2 + b_3 (\dot{x}_2 - \dot{x}_1) = 0$$




$$d) \text{No } 1: V_1 \left(C_1 D + \frac{1}{L_1 D} + \frac{1}{R_1} + \frac{1}{R_3} \right) - V_2 \frac{1}{R_3} = i(t)$$

$$\text{No } 2: V_2 \left(C_2 D + \frac{1}{L_2 D} + \frac{1}{R_2} + \frac{1}{R_3} \right) - V_1 \frac{1}{R_3} = 0$$

$$e) m_1 \ddot{x}_1 + k_1 x_1 + b_1 \dot{x}_1 - b_3 (\dot{x}_2 - \dot{x}_1) = f(t)$$
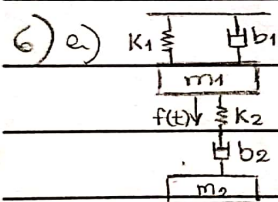
$$m_2 \ddot{x}_2 + k_2 x_2 + b_2 \dot{x}_2 + b_3 (\dot{x}_2 - \dot{x}_1) = 0$$



$$T = \frac{1}{2} m_1 \dot{x}_1^2 + \frac{1}{2} m_2 \dot{x}_2^2$$

$$V = \frac{1}{2} k_1 x_1^2 + \frac{1}{2} k_2 (x_2 - x_1)^2$$

$$R = \frac{1}{2} b_1 \dot{x}_1^2 + \frac{1}{2} b_2 (\dot{x}_2 - \dot{x}_1)^2$$

$$q_1 = x_1: \frac{\partial L}{\partial x_1} = m_1 \dot{x}_1 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_1} \right) = m_1 \ddot{x}_1; \quad \frac{\partial L}{\partial x_1} = -k_1 x_1 + k_2 (x_2 - x_1); \quad \frac{\partial R}{\partial \dot{x}_1} = b_1 \dot{x}_1 - b_2 (\dot{x}_2 - \dot{x}_1)$$



$$m_1 \ddot{x}_1 + k_1 x_1 - k_2 (x_2 - x_1) + b_1 \dot{x}_1 - b_2 (\dot{x}_2 - \dot{x}_1) = f(t)$$

$$q_2 = x_2: \frac{\partial L}{\partial x_2} = m_2 \dot{x}_2 \Rightarrow \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_2} \right) = m_2 \ddot{x}_2; \quad \frac{\partial L}{\partial x_2} = 0; \quad \frac{\partial R}{\partial \dot{x}_2} = b_2 (\dot{x}_2 - \dot{x}_1)$$

$$m_2 \ddot{x}_2 + b_2 (\dot{x}_2 - \dot{x}_1) = 0$$

$$q_3 = x_3: \frac{\partial L}{\partial x_3} = 0; \quad \frac{\partial L}{\partial x_3} = -k_2 (x_3 - x_1); \quad \frac{\partial R}{\partial \dot{x}_3} = -b_2 (\dot{x}_2 - \dot{x}_3)$$
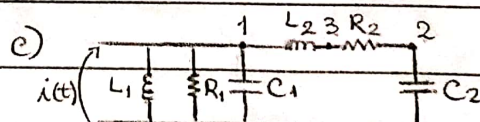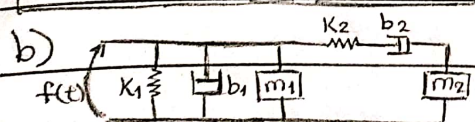
$$k_2 (x_3 - x_1) - b_2 (\dot{x}_2 - \dot{x}_3) = 0$$



$$d) \text{No } 1: V_1 \left(C_1 D + \frac{1}{L_1 D} + \frac{1}{R_1} + \frac{1}{R_3} \right) - V_3 \left(\frac{1}{L_2 D} \right) = i(t)$$

$$\text{No } 2: V_2 \left(C_2 D + \frac{1}{R_2} \right) - V_3 \left(\frac{1}{R_2} \right) = 0$$


$$\text{No } 3: V_3 \left(\frac{1}{L_2 D} + \frac{1}{R_2} \right) - V_1 \frac{1}{L_2 D} - V_2 \frac{1}{R_2} = 0$$

$$e) m_1 \ddot{x}_1 + k_1 x_1 - k_2 (x_3 - x_1) + b_1 \dot{x}_1 - b_2 (\dot{x}_2 - \dot{x}_3) = f(t)$$


$$m_2 \ddot{x}_2 + b_2 (\dot{x}_2 - \dot{x}_3) = 0$$

$$k_2 (x_3 - x_1) - b_2 (\dot{x}_2 - \dot{x}_3) = 0$$

7) Circuito mecânico:

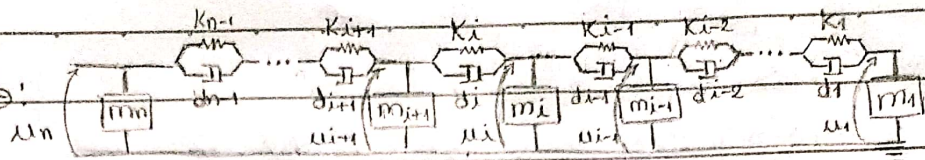

Circuito elétrico:

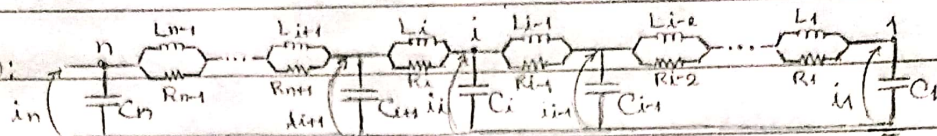


Nó n: $V_n(C_n D + \frac{1}{L_{n-1} D} + \frac{1}{R_{n-1}}) - V_{n-1}(\frac{1}{L_{n-1} D} + \frac{1}{R_{n-1}}) = i_n$

Nó i: $V_i(C_i D + \frac{1}{L_i D} + \frac{1}{L_{i-1} D} + \frac{1}{R_i} + \frac{1}{R_{i-1}}) - V_{i+1}(\frac{1}{L_i D} + \frac{1}{R_i}) - V_{i-1}(\frac{1}{L_{i-1} D} + \frac{1}{R_{i-1}}) = i_i$


Nó 1: $V_1(C_1 D + \frac{1}{L_1 D} + \frac{1}{R_1}) - V_2(\frac{1}{L_1 D} + \frac{1}{R_1}) = i_1$

$$\begin{cases} m_n \ddot{x}_n + d_{n-1} \dot{x}_n + k_{n-1} x_n - d_{n-1} \dot{x}_{n-1} - k_{n-1} x_{n-1} = u_n(t) \\ m_i \ddot{x}_i + (d_i + d_{i-1}) \dot{x}_i + (k_i + k_{i-1}) x_i - d_i \dot{x}_{i+1} - k_i x_{i+1} - d_{i-1} \dot{x}_{i-1} - k_{i-1} x_{i-1} = u_i(t) \\ m_1 \ddot{x}_1 + d_1 \dot{x}_1 + k_1 x_1 - d_1 \dot{x}_2 - k_1 x_2 = u_1(t) \end{cases}$$


8)

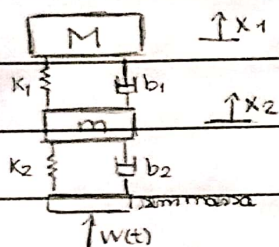

a) Circuito mecânico:

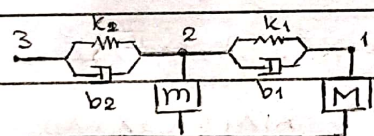

Circuito elétrico:

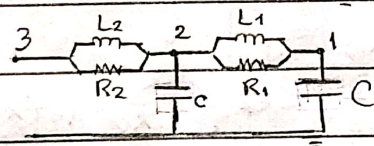


Nó 1: $V_1(C D + \frac{1}{L_1 D} + \frac{1}{R_1}) - V_2(\frac{1}{L_1 D} + \frac{1}{R_1}) = 0$

Nó 2: $V_2(C D + \frac{1}{L_1 D} + \frac{1}{L_2 D} + \frac{1}{R_1} + \frac{1}{R_2}) - V_1(\frac{1}{L_1 D} + \frac{1}{R_1}) - V_3(\frac{1}{L_2 D} + \frac{1}{R_2}) = 0$

Nó 3: $V_3(\frac{1}{L_2 D} + \frac{1}{R_2}) - V_2(\frac{1}{L_2 D} + \frac{1}{R_2}) = 0$

$$\begin{cases} M \ddot{x}_1 + b_1 \dot{x}_1 + k_1 x_1 - b_1 \dot{x}_2 - k_1 x_2 = 0 \\ m \ddot{x}_2 + b_1 \dot{x}_2 + b_2 \dot{x}_2 + k_1 x_2 + k_2 x_2 - b_1 \dot{x}_1 - k_1 x_1 - b_2 \dot{w}(t) - k_2 w(t) = 0 \\ b_2 \dot{w}(t) + k_2 w(t) - b_2 \dot{x}_2 - k_2 x_2 = 0 \end{cases}$$

b) Circuito elétrico:

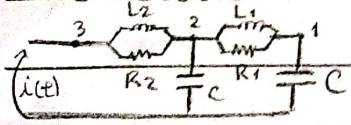

Nó 1: $V_1(C D + \frac{1}{L_1 D} + \frac{1}{R_1}) - V_2(\frac{1}{L_1 D} + \frac{1}{R_1}) = 0$

Nó 2: $V_2(C D + \frac{1}{L_1 D} + \frac{1}{L_2 D} + \frac{1}{R_1} + \frac{1}{R_2}) - V_1(\frac{1}{L_1 D} + \frac{1}{R_1}) - V_3(\frac{1}{L_2 D} + \frac{1}{R_2}) = 0$

Nó 3: $V_3(\frac{1}{L_2 D} + \frac{1}{R_2}) - V_2(\frac{1}{L_2 D} + \frac{1}{R_2}) = i(t)$

$$\begin{cases} M \ddot{x}_1 + b_1 \dot{x}_1 + k_1 x_1 - b_1 \dot{x}_2 - k_1 x_2 = 0 \\ m \ddot{x}_2 + b_1 \dot{x}_2 + b_2 \dot{x}_2 + k_1 x_2 + k_2 x_2 - b_1 \dot{x}_1 - k_1 x_1 - b_2 \dot{x}_3 - k_2 x_3 = 0 \\ b_2 \dot{x}_3 + k_2 x_3 - b_2 \dot{x}_2 - k_2 x_2 = w(t) \end{cases}$$