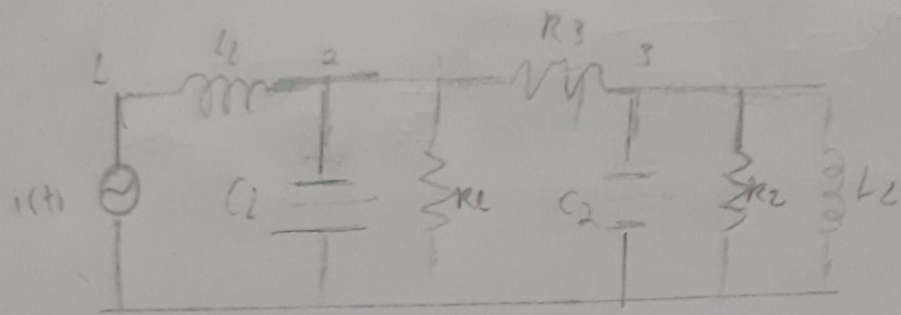


1-



$$\text{Nó 1: } V_1 \left(\frac{1}{L_1 D} \right) - V_2 \left(\frac{1}{L_1 D} \right) = i(t)$$

$$\text{Nó 2: } V_2 \left(C_1 D + \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{L_1 D} \right) - V_1 \left(\frac{1}{L_1 D} \right) - V_3 \left(\frac{1}{R_3} \right) = 0$$

$$\text{Nó 3: } V_3 \left(C_2 D + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{L_2 D} \right) - V_2 \left(\frac{1}{R_3} \right) = 0$$

Usando a utulizao:

$$1 - k_1 (\theta_1 - \theta_2) = T/H$$

$$2 - J \ddot{\theta}_2 + (B_1 + B_3) \dot{\theta}_2 + k_1 \theta_2 - k_1 \theta_1 - B_3 \dot{\theta}_3 = 0$$

$$3 - J_2 \ddot{\theta}_3 + (B_2 + B_3) \dot{\theta}_3 + k_2 \theta_3 - B_3 \dot{\theta}_2 = 0$$

2- Por Lagrange:

$$T = \frac{1}{2} (m_1 \dot{x}_1^2 + m_2 \dot{x}_2^2 + m_3 \dot{x}_3^2)$$

$$V = m_1 g x_1 + m_2 g x_2 + m_3 g x_3 + \frac{1}{2} (k_1 x_1^2 + k_2 (x_2 - x_1)^2 + k_3 (x_3 - x_2)^2 + k_4 (x_3 - x_1)^2)$$


$$R = \frac{1}{2} (b_1 \dot{x}_1^2 + b_2 (\dot{x}_2 - \dot{x}_1)^2 + b_3 (\dot{x}_3 - \dot{x}_1)^2 + b_4 (\dot{x}_3 - \dot{x}_2)^2)$$

$$P/x_1 \rightarrow m_1 \ddot{x}_1 + (k_1 + k_2 + k_3 + k_4) x_1 + (b_1 + b_2 + b_4) \dot{x}_1 = k_2 x_2 + b_2 \dot{x}_2 + k_4 x_3 + b_4 \dot{x}_3$$


$$P/x_2 \rightarrow m_2 \ddot{x}_2 + (k_2 + k_3) x_2 + (b_2 + b_3) \dot{x}_2 = k_2 x_1 + b_2 \dot{x}_1 + k_3 x_3 + b_3 \dot{x}_3 + f_2(t)$$

$$P/x_3 \rightarrow m_3 \ddot{x}_3 + (k_3 + k_4) x_3 + (b_3 + b_4) \dot{x}_3 = k_3 x_2 + b_3 \dot{x}_2 + k_4 x_1 + b_4 \dot{x}_1 + f_3(t)$$

b) Mecânica

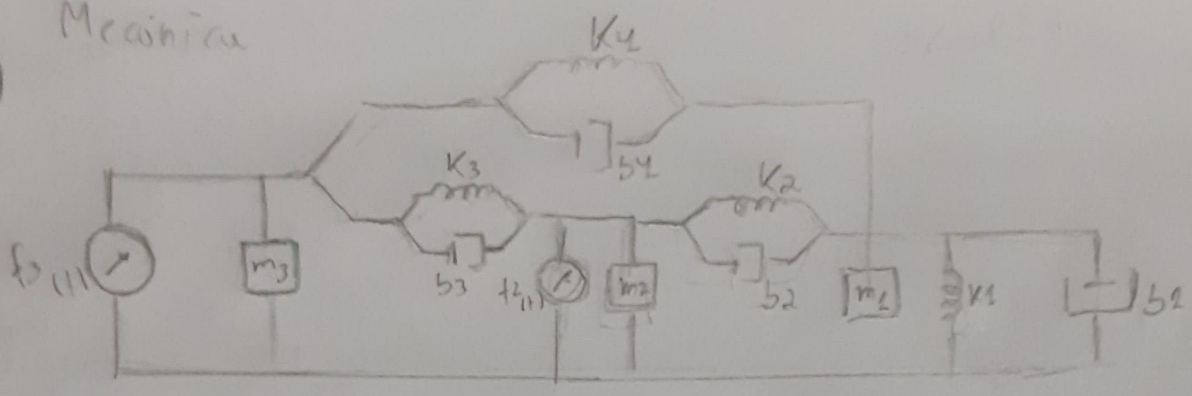

c) Circuito Eléctrico equivalente.

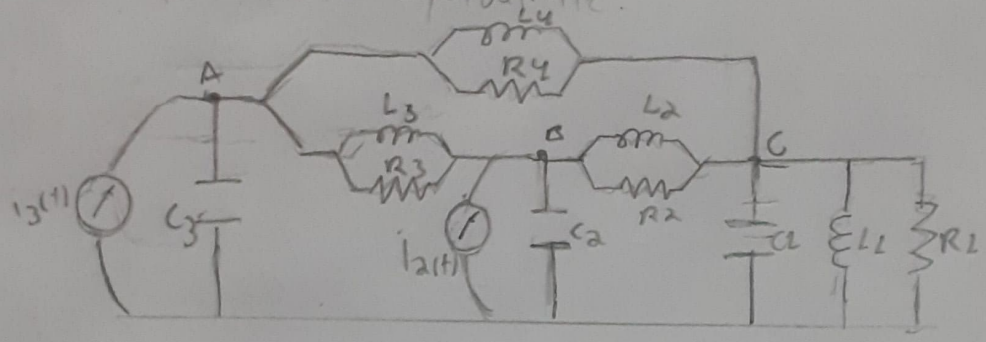

$$N^o A: V_A \left(C_3 D + \frac{1}{R_3} + \frac{1}{L_3 D} + \frac{1}{R_4} + \frac{1}{L_4 D} \right) - V_C \left(\frac{1}{R_4} + \frac{1}{L_4 D} \right) - V_B \left(\frac{1}{R_3} + \frac{1}{L_3 D} \right) = i_3(t)$$

$$N^o B: V_B \left(C_2 D + \frac{1}{R_2} + \frac{1}{L_2 D} + \frac{1}{R_3} + \frac{1}{L_3 D} \right) - V_C \left(\frac{1}{R_2} + \frac{1}{L_2 D} \right) - V_A \left(\frac{1}{R_3} + \frac{1}{L_3 D} \right) = i_2(t)$$


$$N^o C: V_C \left(C_1 D + \frac{1}{R_1} + \frac{1}{L_1 D} + \frac{1}{R_2} + \frac{1}{L_2 D} + \frac{1}{R_4} + \frac{1}{L_4 D} \right) - V_B \left(\frac{1}{R_2} + \frac{1}{L_2 D} \right) - V_A \left(\frac{1}{R_4} + \frac{1}{L_4 D} \right) = 0$$

e) Equações

$$N^o A: m_3 \ddot{x}_3 + (b_3 + b_4) \dot{x}_3 + (K_3 + K_4) x_3 = f_3(t) + b_4 \dot{x}_2 + K_4 x_1 + b_3 \dot{x}_2 + K_3 x_2$$

$$N^o B: m_2 \ddot{x}_2 + (b_2 + b_3) \dot{x}_2 + (K_2 + K_4) x_2 = f_2(t) + b_2 \dot{x}_1 + K_2 x_1 + b_3 \dot{x}_3 + K_3 x_3$$
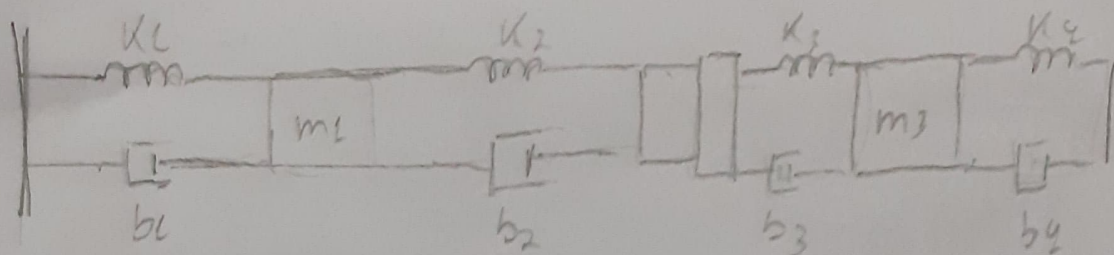
$$N^o C: m_1 \ddot{x}_1 + (b_1 + b_2 + b_4) \dot{x}_1 + (K_1 + K_2 + K_4) x_1 = b_2 \dot{x}_2 + K_2 x_2 + b_4 \dot{x}_3 + K_4 x_3$$



a) P Lagrange:

$$T = \frac{1}{2} (m_1 \dot{x}_1^2 + m_2 \dot{x}_2^2 + m_3 \dot{x}_3^2)$$

$$V = \frac{1}{2} (k_1 x_1^2 + k_2 (x_2 - x_1)^2 + k_3 (x_3 - x_2)^2 + k_4 x_3^2)$$

$$R = \frac{1}{2} (b_1 \dot{x}_1^2 + b_2 (\dot{x}_2 - \dot{x}_1)^2 + b_3 (\dot{x}_3 - \dot{x}_2)^2 + b_4 \dot{x}_3^2)$$


Equations:

$$m_1 \ddot{x}_1 + (b_1 + b_2) \dot{x}_1 - b_2 \dot{x}_2 + (k_1 + k_2) x_1 - k_2 x_2 = u$$


$$m_2 \ddot{x}_2 - b_2 \dot{x}_1 + (b_2 + b_3) \dot{x}_2 - b_3 \dot{x}_3 - k_2 x_1 + (k_2 + k_3) x_2 - k_3 x_3 = 0$$

$$m_3 \ddot{x}_3 - b_3 \dot{x}_2 + (b_3 + b_4) \dot{x}_3 - k_3 x_2 + (k_3 + k_4) x_3 = 0$$

b)

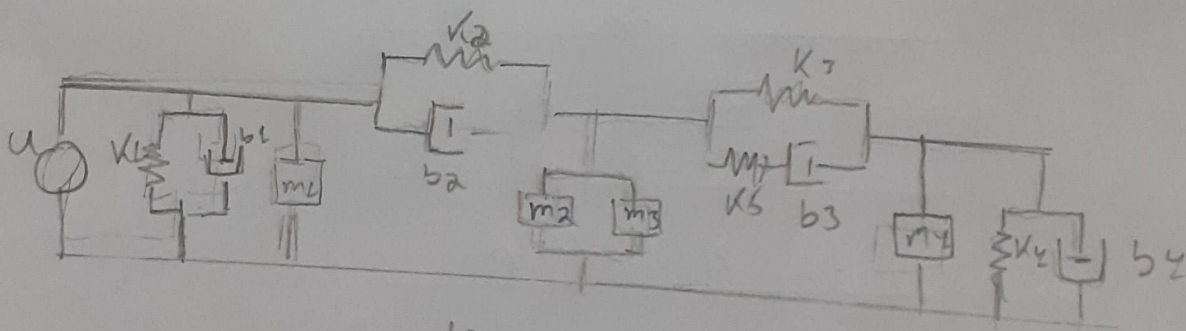


c)

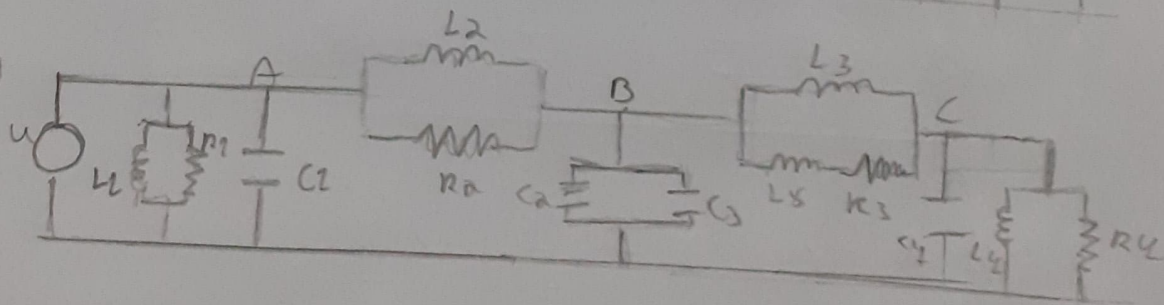

$$\text{Node A: } \left(\frac{1}{L_1 D} + \frac{1}{R_1} + C_1 D + \frac{1}{L_2 D} + \frac{1}{R_2} \right) V_A - \left(\frac{1}{L_2 D} + \frac{1}{R_2} \right) V_B = u(t)$$

$$\text{Node B: } \left(\frac{1}{L_2 D} + \frac{1}{R_2} + C_2 D + \frac{1}{L_3 D} + \frac{1}{L_4 D} + \frac{1}{R_3} \right) V_B - \left(\frac{1}{L_2 D} + \frac{1}{R_2} \right) V_A - \left(\frac{1}{L_3 D} + \frac{1}{L_4 D} + \frac{1}{R_3} \right) V_C = 0$$
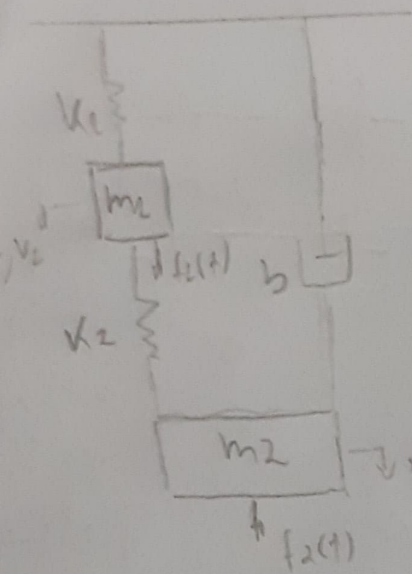
$$\text{Node C: } \left(\frac{1}{L_3 D} + \frac{1}{L_4 D} + \frac{1}{R_3} + \frac{1}{L_4 D} + \frac{1}{R_4} + C_3 D \right) V_C - \left(\frac{1}{L_3 D} + \frac{1}{L_4 D} + \frac{1}{R_3} \right) V_B = 0$$



$$T = \frac{1}{2} (m_1 \dot{x}_1^2 + m_2 \dot{x}_2^2)$$

$$V = \frac{1}{2} (k_1 x_1^2 + k_2 (x_2 - x_1)^2)$$

$$R = \frac{1}{2} b \dot{x}_2^2$$

$$p/x_1 \rightarrow \frac{\partial L}{\partial \dot{x}_1} = m_1 \dot{x}_1 \quad \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_1} \right) = m_1 \ddot{x}_1$$



$$\frac{\partial L}{\partial x_1} = -k_1 x_1 - k_2 (x_2 - x_1) \quad \frac{\partial R}{\partial \dot{x}_1} = 0$$

$$L = T - V$$

$$m_1 \ddot{x}_1 + k_1 x_1 + k_2 (x_2 - x_1) = f_1(t)$$

$$p/x_2 \rightarrow \frac{\partial L}{\partial \dot{x}_2} = m_2 \dot{x}_2 \quad \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_2} \right) = m_2 \ddot{x}_2 \quad \frac{\partial L}{\partial x_2} = -k_2 (x_2 - x_1) \quad \frac{\partial R}{\partial \dot{x}_2} = b \dot{x}_2$$
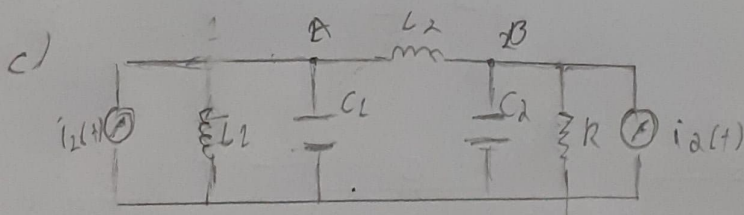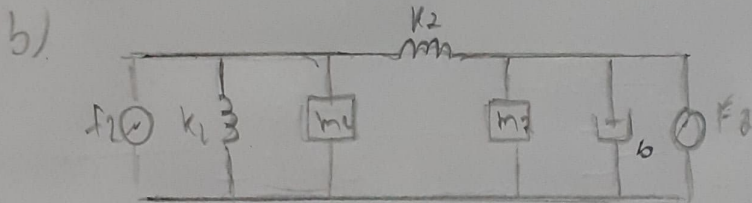
$$m_2 \ddot{x}_2 + k_2 (x_2 - x_1) + b \dot{x}_2 = 0$$




$$d) \text{ Ns' A: } V_1 \left(C_1 D + \frac{1}{L_1 D} + \frac{1}{L_2 D} \right) - V_2 \frac{1}{L_2 D} = i_2(t)$$

$$\text{Ns' B: } V_2 \left(C_2 D + \frac{1}{R} + \frac{1}{L_2 D} \right) - V_1 \frac{1}{L_2 D} = i_a(t)$$

$$e) \text{ Ns' A: } m_1 \ddot{x}_1 + (k_1 + k_2) x_1 = f_1(t) + k_2 x_2$$

$$\text{Ns' B: } m_2 \ddot{x}_2 + b \dot{x}_2 + k_2 x_2 = f_2(t) + k_2 x_1$$



5.

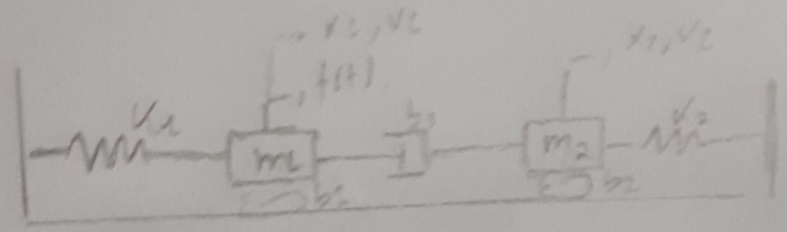

$$T = \frac{1}{2} (m_1 \dot{x}_1^2 + m_2 \dot{x}_2^2) \quad V = \frac{1}{2} (k_1 x_1^2 + k_2 x_2^2) \quad K = \frac{1}{2} (b_1 \dot{x}_1^2 + b_2 \dot{x}_2^2 + b_3 (\dot{x}_1 - \dot{x}_2)^2)$$

$$P/x_1 = m_1 \ddot{x}_1 + k_1 x_1 + (b_2 + b_3) \dot{x}_1 = b_3 \dot{x}_2 + f(t)$$
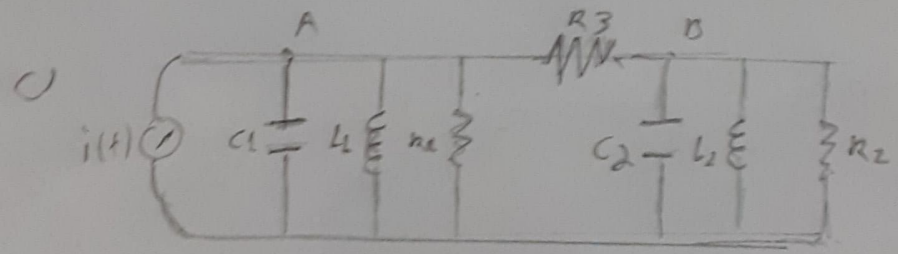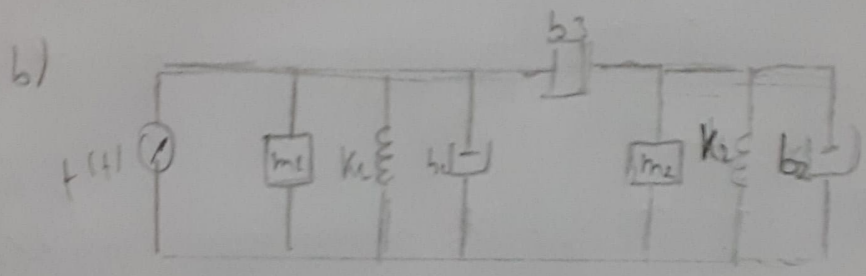
$$P/x_2 = m_2 \ddot{x}_2 + k_2 x_2 + (b_2 + b_3) \dot{x}_2 = b_3 \dot{x}_1$$




d) Ns A: $V_1 (C_2 D + \frac{1}{R_2} + \frac{1}{L_2 D} + \frac{1}{R_3}) - V_2 \frac{1}{R_3} = i(t)$

Ns B: $V_2 (C_2 D + \frac{1}{R_2} + \frac{1}{L_2 D} + \frac{1}{R_3}) - V_1 \frac{1}{R_3} = 0$

e) A: $m_1 \ddot{x}_1 + (b_2 + b_3) \dot{x}_1 + k_1 x_1 = f(t) + b_3 \dot{x}_2$

B: $m_2 \ddot{x}_2 + (b_2 + b_3) \dot{x}_2 + k_2 x_2 = b_3 \dot{x}_1$

6.

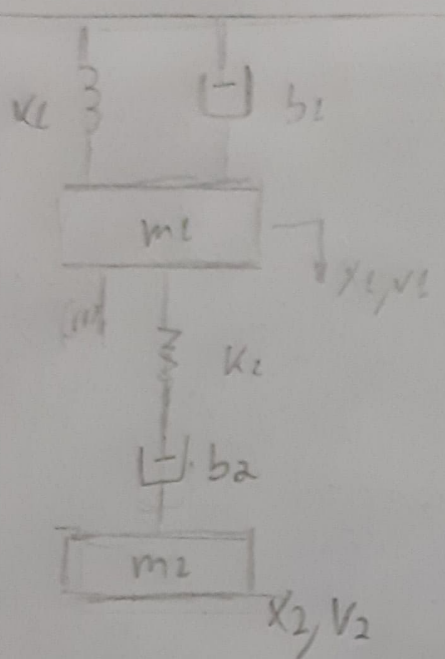

$$T = \frac{1}{2} (m_1 \dot{x}_1^2 + m_2 \dot{x}_2^2)$$

$$V = \frac{1}{2} (k_1 x_1^2 + k_2 (x_2 - x_1)^2)$$

$$R = \frac{1}{2} (b_1 \dot{x}_1^2 + b_2 (\dot{x}_2 - \dot{x}_1)^2)$$

$\mathcal{P}/x_1 =$

$$\frac{\partial L}{\partial x_1} = m_1 \ddot{x}_1 \quad \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_1} \right) = m_1 \dot{x}_1 \quad \frac{\partial L}{\partial x_1} = -k_1 x_1 + k_2 (x_2 - x_1)$$

$$\frac{\partial R}{\partial \dot{x}_1} = b_1 \dot{x}_1 \quad \rightarrow \quad m_1 \ddot{x}_1 + (k_1 + k_2) x_1 + b_1 \dot{x}_1 = f(t) + k_2 x_2$$

$\mathcal{P}/x_2 =$

$$\frac{\partial L}{\partial x_2} = m_2 \ddot{x}_2 \quad \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}_2} \right) = m_2 \dot{x}_2 \quad \frac{\partial L}{\partial x_2} = 0 \quad \frac{\partial R}{\partial \dot{x}_2} = b_2 (\dot{x}_2 - \dot{x}_1)$$


$$m \ddot{x}_2 + b_2 \dot{x}_2 = b_1 \dot{x}_1$$

\mathcal{P}/x_3


$$\frac{\partial L}{\partial x_3} = 0 \quad \frac{\partial L}{\partial x_3} = -k_2 (x_3 - x_1) \quad \frac{\partial R}{\partial \dot{x}_3} = -b_2 (\dot{x}_2 - \dot{x}_3)$$

$$k_2 \dot{x}_3 + b_2 \dot{x}_3 = k_2 x_1 + b_2 \dot{x}_2$$

b)

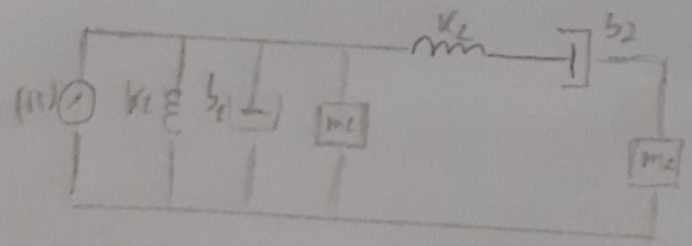

c)

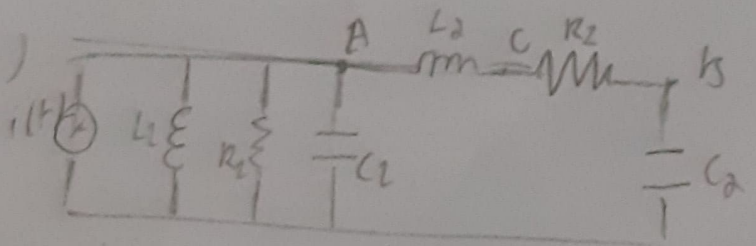

di N₅ A: $V_1 \left(C_2 D + \frac{1}{R_2} + \frac{1}{L_2 D} \right) - V_2 \frac{1}{L_2 D} = i(t)$

N₅ B: $V_2 \left(C_2 D + \frac{1}{R_2} \right) - V_3 \frac{1}{R_2} = 0$



N₅ C: $V_3 \left(\frac{1}{R_2} + \frac{1}{L_2 D} \right) - V_1 \frac{1}{L_2 D} - V_2 \frac{1}{R_2} = 0$

a) $m_1 \ddot{x}_1 + b_1 \dot{x}_1 + (k_1 + k_2)x_1 = f(t) + k_2 x_3$

$m_2 \ddot{x}_2 + b_2 \dot{x}_2 = b_2 \dot{x}_3$

$b_2 \dot{x}_3 + k_2 x_3 = k_2 x_2 + b_2 \dot{x}_2$




7.

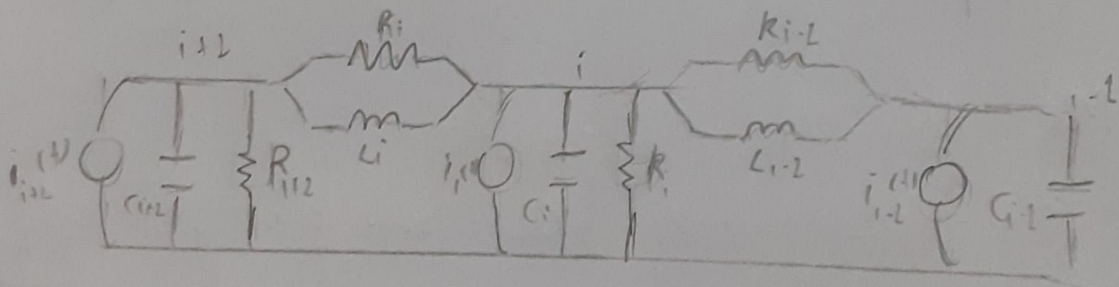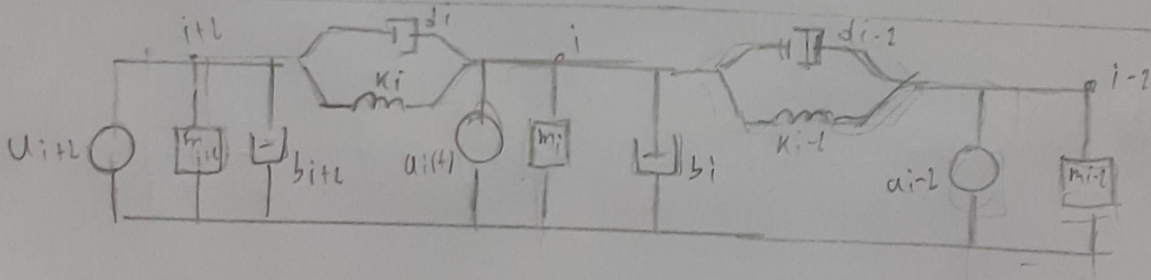

$$E_0: V_i \left(C_i D + \frac{1}{R_i} + \frac{1}{L_i D} + \frac{1}{L_{i-2} D} + \frac{1}{R_i} + \frac{1}{R_{i-2}} \right) - V_{i-2} \left(\frac{1}{R_{i-2}} + \frac{1}{L_{i-2} D} \right) - V_{i+2} \left(\frac{1}{R_i} + \frac{1}{L_i D} \right) = i_i(t)$$

For analysis
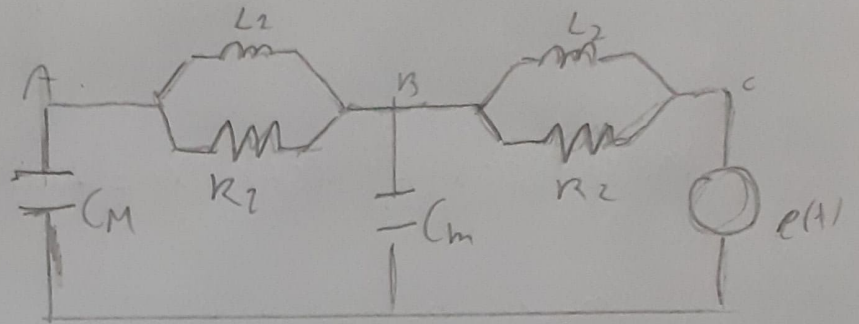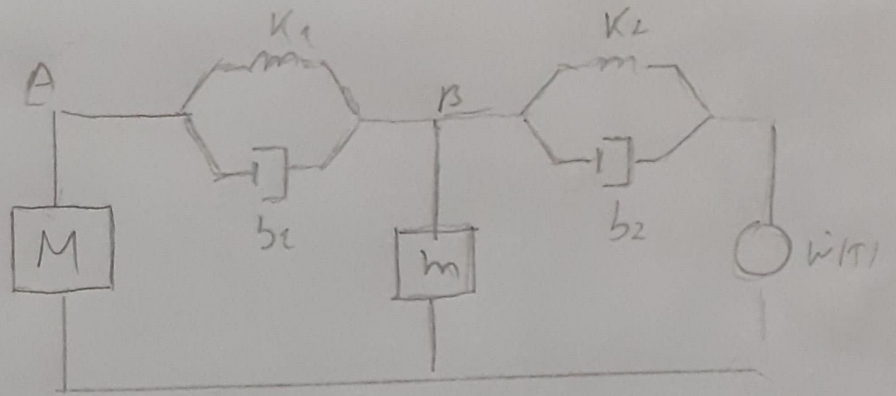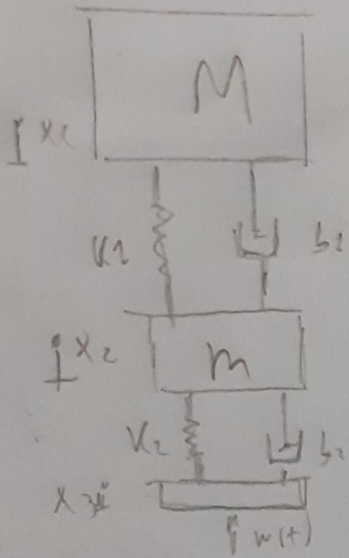
$$m_i \ddot{x}_i + (b_i + d_i + d_{i-2}) \dot{x}_i + (k_i + k_{i-2}) x_i = u_i(t) - m_{i+2} \ddot{x}_{i+2} + b_{i-2} \dot{x}_{i-2} + b_i \dot{x}_{i+2} + k_{i-2} x_{i-2} + k_i x_{i+2}$$



$$NS' A: V_2 \left(C_m D + \frac{1}{L_1 D} + \frac{1}{R_1} \right) - V_2 \left(\frac{1}{L_1 D} + \frac{1}{R_2} \right) = 0$$

$$NS' B: V_2 \left(C_m D + \frac{1}{L_1 D} + \frac{1}{L_2 D} + \frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \left(\frac{1}{L_1 D} + \frac{1}{R_1} \right) - e(t) \left(\frac{1}{L_2 D} + \frac{1}{R_2} \right) = 0$$

$$M \ddot{x}_1 + k_1 x_1 - k_2 x_2 + b_1 \dot{x}_1 - b_1 \dot{x}_2 = 0$$

$$m \ddot{x}_2 + k_1 x_2 + k_2 x_2 - k_1 x_1 - k_2 \omega(t) + b_1 \dot{x}_2 + b_2 \dot{x}_2 - b_1 \dot{x}_1 - b_2 \omega(t) = 0$$

b) Mechanical circuits, $i(t) \leftrightarrow \dot{w}(t) \rightarrow w(t)$

$$NS' A: V_2 \left(C_m D + \frac{1}{L_1 D} + \frac{1}{R_1} \right) - V_2 \left(\frac{1}{L_1 D} + \frac{1}{R_1} \right) = 0$$

$$NS' B: V_2 \left(C_m D + \frac{1}{L_1 D} + \frac{1}{L_2 D} + \frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \left(\frac{1}{L_1 D} + \frac{1}{R_1} \right) - V_3 \left(\frac{1}{L_2 D} + \frac{1}{R_2} \right) = 0$$

$$NS' C: V_3 \left(\frac{1}{L_2 D} + \frac{1}{R_2} \right) - V_2 \left(\frac{1}{L_2 D} + \frac{1}{R_2} \right) = i(t)$$

$$m \ddot{x}_1 + k_1 x_1 - k_2 x_2 + b_1 \dot{x}_1 - b_1 \dot{x}_2 = 0$$

$$m \ddot{x}_2 + k_1 x_2 + k_2 x_2 - k_1 x_1 - k_2 \omega(t) + b_1 \dot{x}_2 + b_2 \dot{x}_2 - b_1 \dot{x}_1 - b_2 \omega(t) = 0$$

$$k_2 x_2 - k_2 \omega(t) + b_2 \dot{x}_2 - b_2 \omega(t) = \omega(t)$$