
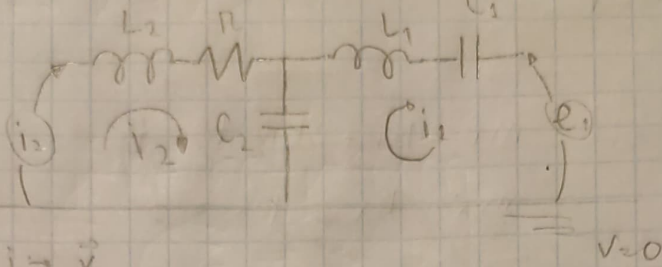


Enzo C Zugliani - 10333741

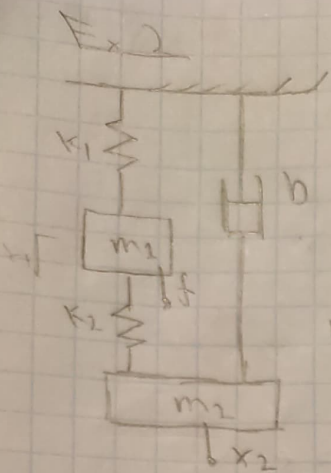

$v \rightarrow \dot{x}, i \rightarrow \dot{q}$   
 • Malha 2:

$$L_2 D \cdot i_2 + R i_2 + (i_2 - i_1) \cdot \frac{1}{C_2 D} = 0 \Rightarrow$$

$$\Rightarrow m_2 D v_2 + b \cdot v_2 + (v_2 - v_1) \cdot \frac{K_2}{D} = 0 \Rightarrow$$

$$\Rightarrow m_2 \ddot{x}_2 + b \dot{x}_2 + (x_2 - x_1) \cdot K_2 = 0,$$


• Malha 1:

$$\cdot -(i_1 - i_2) \cdot \frac{1}{C_2 D} + L_1 D i_1 + i_1 \cdot \frac{1}{C_1 D} = e_1 \Rightarrow$$


$$\Rightarrow (v_1 - v_2) \cdot \frac{K_2}{D} + m_1 v_1 D + v_1 \cdot \frac{K_1}{D} = f \Rightarrow$$

$$\Rightarrow (x_1 - x_2) \cdot K_2 + m_1 \dot{x}_1 + x_1 \cdot K_1 = f,$$

Ex 3

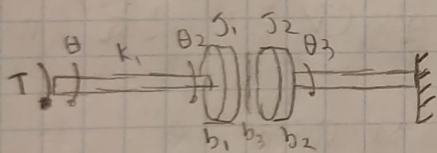

$f \rightarrow v, \dot{v} \rightarrow i$

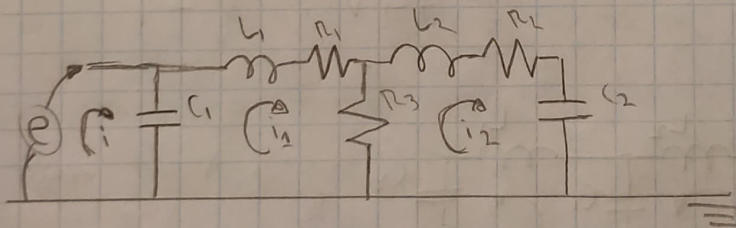

$x = \theta_1$   
 $x_1 = \theta_2$   
 $x_2 = \theta_3,$

• Malha 2:

$$\cdot e - (i - i_2) \cdot \frac{1}{C_1 D} = 0$$

$$\Rightarrow f - (v - v_1) \cdot \frac{K_1}{D} = 0 \Rightarrow (x - x_1) K_1 = f,$$

• Malha 1:

$$\cdot (i_1 - i) \cdot \frac{1}{C_2 D} + L_1 D i_1 + R_1 i_1 + (i_1 - i_2) \cdot R_3 = 0$$

$$\Rightarrow (v_1 - v) \cdot \frac{K_1}{D} + m_1 \cdot D \cdot v_1 + b \cdot v_2 + (v_1 - v_2) \cdot b_3 = 0$$


$$\Rightarrow (x_1 - x) \cdot K_1 + m_1 \dot{x}_1 + b \cdot v_1 + (v_1 - v_2) \cdot b_3 = 0,$$

• Malha 2:

$$(i_2 - i_3) \cdot R_3 + i_2 \cdot D \cdot L_2 + R_2 i_2 + \frac{1}{C_2 D} i_2 = 0$$

$$\Rightarrow (v_2 - v_1) \cdot b_3 + m_2 \ddot{x}_2 + b_2 \dot{x}_2 + k_2 \cdot x_2 = 0$$

• Ex "3"

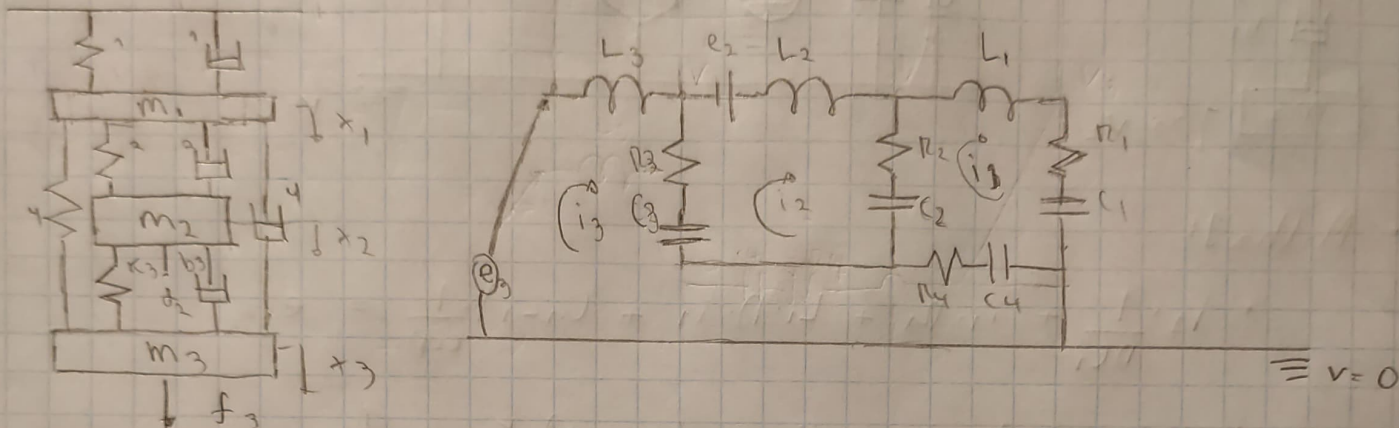

• Malha 1:

$$L_1 \cdot D \cdot i_1 + R_1 i_1 + \frac{1}{C_1 D} i_1 + (i_1 - i_3) \cdot (R_4 + \frac{1}{C_4 D}) + (i_1 - i_2) (R_2 + \frac{1}{C_2 D}) = 0$$

$$\Rightarrow m_1 \ddot{x}_1 + b_1 \dot{x}_1 + k_1 x_1 + (x_1 - x_3) b_4 + (x_1 - x_3) k_4 + (x_1 - x_2) b_2 + (x_1 - x_2) k_2 = 0$$

• Malha 2:

$$L_2 \cdot D \cdot i_2 + (i_2 - i_1) (R_2 + \frac{1}{C_2 D}) + (i_2 - i_3) (R_3 + \frac{1}{C_3 D}) = e_2$$

$$\Rightarrow m_2 \ddot{x}_2 + (x_2 - x_1) b_2 + (x_2 - x_1) k_2 + (x_2 - x_3) b_3 + (x_2 - x_3) k_3 = f_2$$



• Malha 3:

$$L_3 \cdot D \cdot i_3 + (i_3 - i_2) (R_3 + \frac{1}{C_3 D}) + (i_3 - i_1) (R_4 + \frac{1}{C_4 D}) = e_3$$

$$\Rightarrow m_3 \ddot{x}_3 + (x_3 - x_2) b_3 + (x_3 - x_2) k_3 + (x_3 - x_1) b_4 + (x_3 - x_1) k_4 = f_3$$

Ex 6

$$f \rightarrow V, \vec{v} + i$$

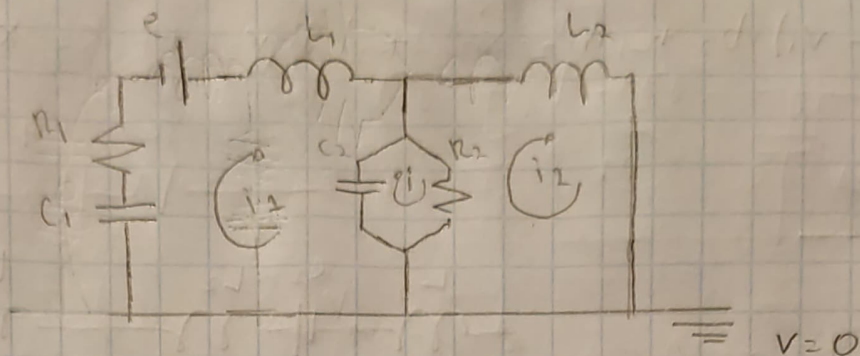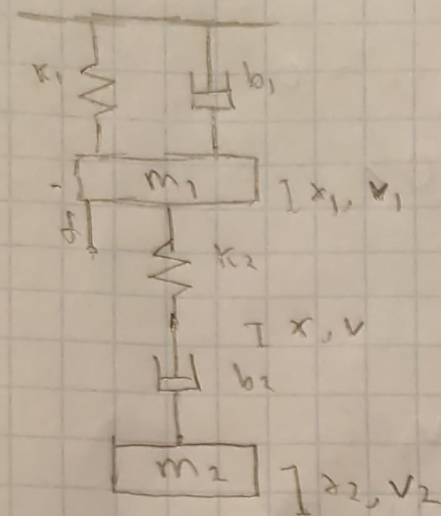

• Mathe 1:

$$i_2 \cdot \frac{1}{C_2} + i_1 \cdot R_1 + L_1 \cdot D \cdot i_1 + (i_1 - i_2) \cdot \frac{1}{C_1} = e$$

$$\Rightarrow x_1 \cdot k_1 + \dot{x}_1 \cdot b_1 + m_1 \ddot{x}_1 + (x_1 - x_2) \cdot k_2 = f$$

• Mathe 2:

$$i_2 \cdot L_2 \cdot D + (i_2 - i_1) \cdot R_2 = 0$$


$$\Rightarrow m_2 \ddot{x}_2 + (\dot{x}_2 - \dot{x}_1) \cdot b_2 = 0$$

• Mathe "i"


$$(i - i_2) R_2 + (i - i_1) \cdot \frac{1}{C_1} = 0$$

$$\Rightarrow (\dot{x} - \dot{x}_2) b_2 + (x - x_1) \cdot k_2 = 0$$

Ex 7

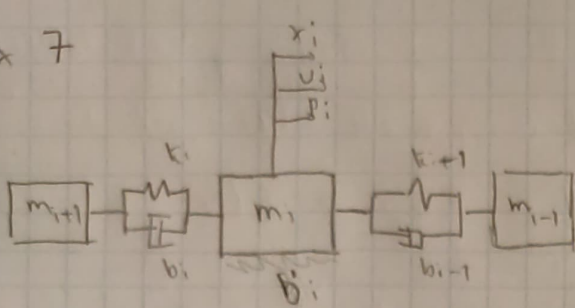

Circuit analógico:

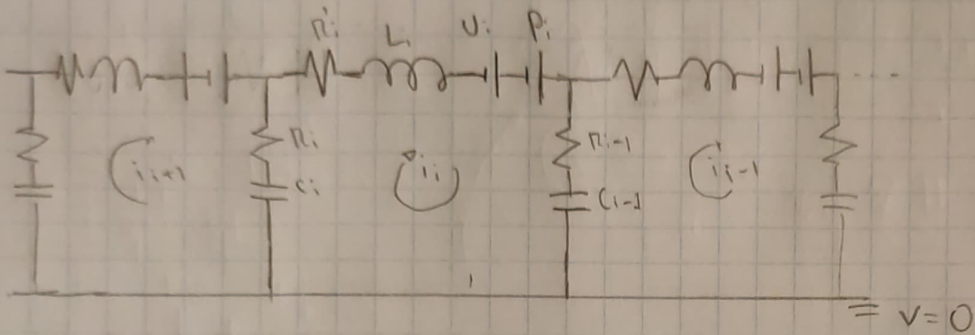


Malha  $i_i$ :

$$i_i \cdot R_i + L_i \cdot D \cdot i_i - v_i - P_i + (i_i - i_{i-1}) \cdot \left( R_{i-1} + \frac{1}{C_{i-1} D} \right) + (i_i - i_{i+1}) \cdot \left( R_i + \frac{1}{C_i D} \right) = 0$$

$$\Rightarrow \dot{x}_i \cdot b_i + m_i \ddot{x}_i + (x_i - x_{i-1}) b_{i-1} + (x_i - x_{i+1}) \cdot k_{i+1} + (x_i - x_{i+1}) b_i + (x_i - x_{i-1}) k_i = v_i + m_i \cdot g \cdot \text{sen} \theta$$

Ex 8

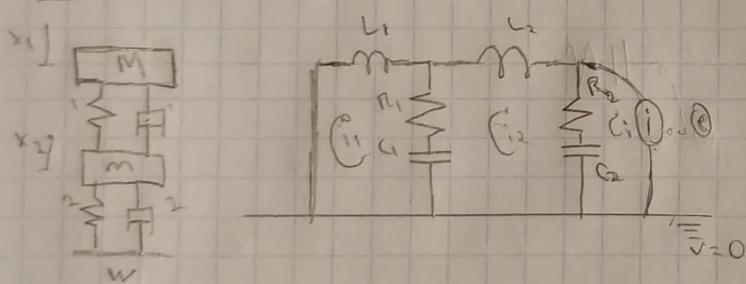

$f \rightarrow v; \quad \dot{v} \rightarrow i$

Malha 1:

$$i_1 \cdot L_1 D + (i_1 - i_2) \cdot \left( R_1 + \frac{1}{C_1 D} \right) = 0$$

$$\Rightarrow m_1 \ddot{x}_1 + (x_1 - x_2) b_1 + (x_1 - x_2) k_1 = 0 \quad (J)$$

Malha 2:

$$i_2 L_2 D + (i_2 - i_1) \left( R_2 + \frac{1}{C_2 D} \right) + (i_2 - i_1) \left( R_1 + \frac{1}{C_1 D} \right) = 0$$

$$\Rightarrow m_2 \ddot{x}_2 + (x_1 - x_2) b_2 + (\dot{x}_1 - \dot{x}_2) k_2 + (x_2 - x_1) b_1 + (x_2 - x_1) k_1 = 0$$

b) w forço; Equações (J) e a mesma.

Malha 2:

$$i_2 L_2 D + i_2 R_2 + i_2 \frac{1}{C_2 D} + (i_2 - i_1) \left( R_2 + \frac{1}{C_2 D} \right) = e$$

$$\Rightarrow m_2 \ddot{x}_2 + b_2 \dot{x}_2 + k_2 x_2 + (x_2 - x_1) b_1 + (x_2 - x_1) k_1 = w$$