
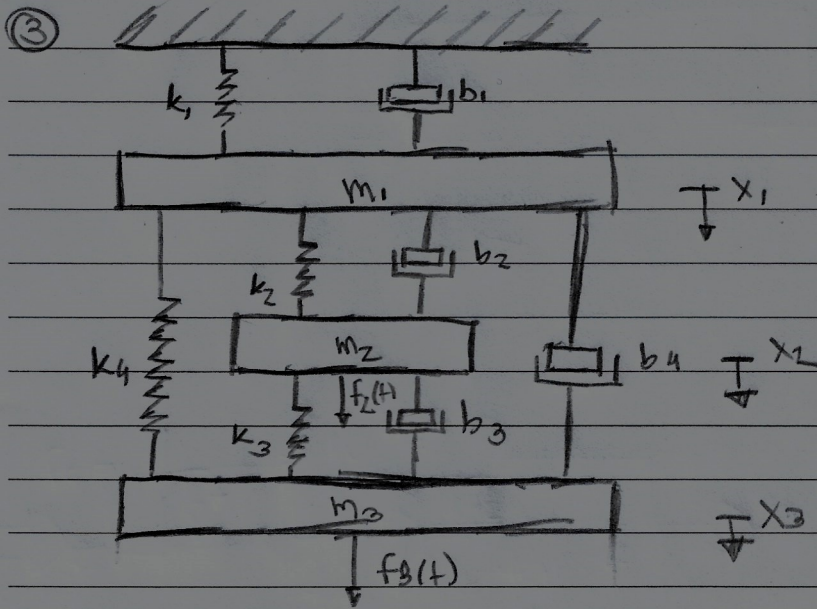


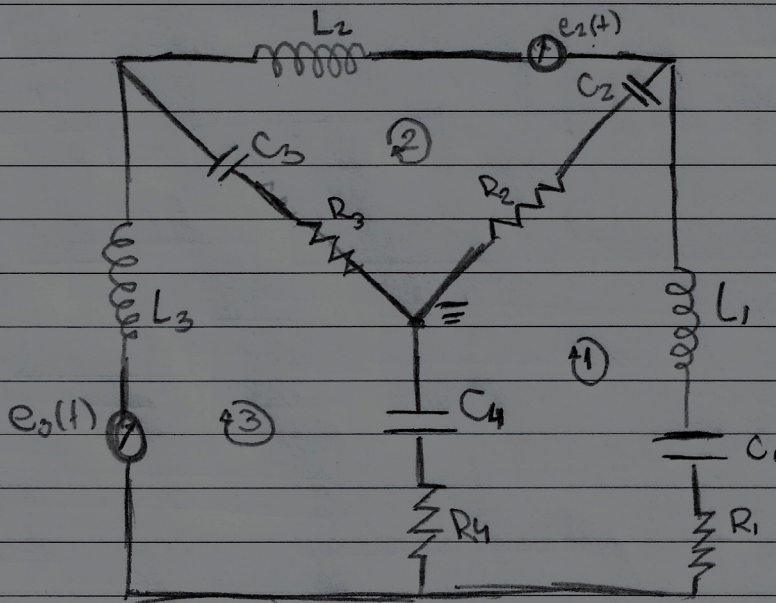Rodrigo Yukio Tamaki Rodriguez - 10772709



Circuito elétrico



①

Mathe 1

1)

$$L_1 \ddot{x}_1 + \frac{1}{C_1 D} \dot{x}_1 + R_1 \dot{x}_1 + R_4 (x_1 - x_3) + \frac{1}{C_4 D} (x_1 - x_3) + R_2 (x_1 - x_2) + \frac{1}{C_2 D} (x_1 - x_2) = 0$$

2)

$$L_2 \ddot{x}_2 + \frac{1}{C_2 D} (x_2 - x_1) + R_2 (x_2 - x_1) + R_3 (x_2 - x_3) + \frac{1}{C_3 D} (x_2 - x_3) = e_2(t)$$


$$3) L_3 \ddot{x}_3 + \frac{1}{C_3 D} (x_3 - x_2) + R_3 (x_3 - x_2) + \frac{1}{C_4 D} (x_3 - x_1) + R_4 (x_3 - x_1) = e_3(t)$$

Por analogia


$$\begin{cases} m_1 \ddot{x}_1 + k_1 x_1 + b_1 \dot{x}_1 + b_4 (\dot{x}_1 - \dot{x}_3) + k_4 (x_1 - x_3) + b_2 (\dot{x}_1 - \dot{x}_2) + k_2 (x_1 - x_2) = 0 \\ m_2 \ddot{x}_2 + k_2 (x_2 - x_1) + b_2 (\dot{x}_2 - \dot{x}_1) + b_3 (\dot{x}_2 - \dot{x}_3) + k_3 (x_2 - x_3) = f_2(t) \\ m_3 \ddot{x}_3 + k_3 (x_3 - x_2) + b_3 (\dot{x}_3 - \dot{x}_2) + k_4 (x_3 - x_1) + b_4 (\dot{x}_3 - \dot{x}_1) = f_3(t) \end{cases}$$

(2)

⑥

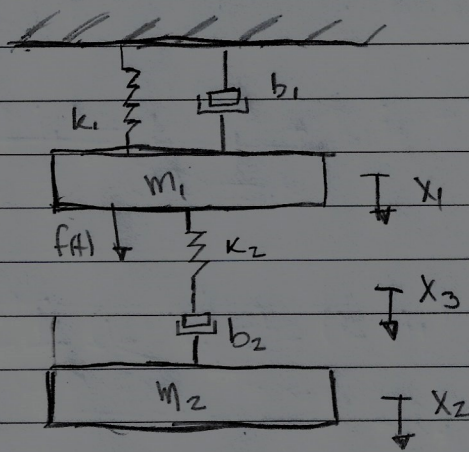

Circuito elétrico

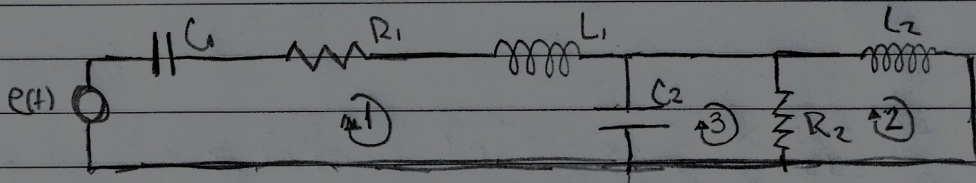

1),


$$\frac{1}{C_1} i_1 + R_1 i_1 + L_1 D i_1 + \frac{1}{C_2 D} (i_1 - i_3) = e(t)$$

$$2) \quad L_2 D i_2 + R_2 (i_2 - i_3) = 0$$


$$3) \quad R_2 (i_3 - i_2) + \frac{C_2}{C_2 D} (i_3 - i_1) = 0$$

$$\begin{cases} k_1 x_1 + b_1 \dot{x}_1 + m_1 \ddot{x}_1 + k_2 (x_1 - x_3) = e(t) \\ m_2 \ddot{x}_2 + b_2 (\dot{x}_2 - \dot{x}_3) = 0 \\ k_2 (x_3 - x_1) + b_2 (\dot{x}_3 - \dot{x}_2) = 0 \end{cases}$$

③

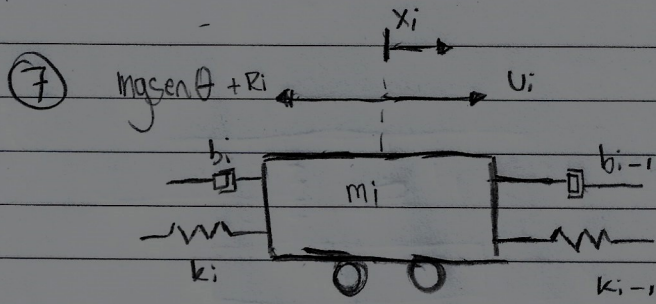


Circuito elétrico

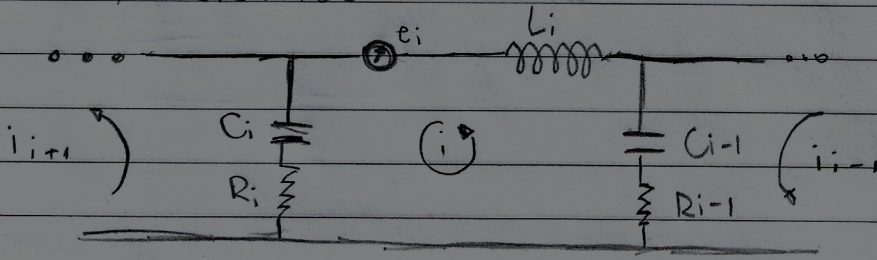


ii)

$$L_i \frac{d i_i}{dt} + \frac{1}{C_i} (i_i - i_{i-1}) + R_{i-1} (i_i - i_{i-1}) + R_i (i_i - i_{i+1}) + \frac{1}{C_i} (i_i - i_{i+1})$$
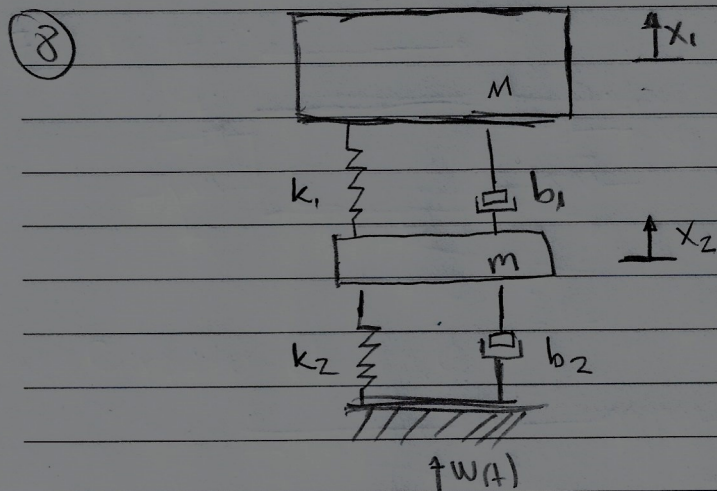
$$m_i \ddot{x}_i + k_{i+1} (x_i - x_{i+1}) + b_{i+1} (\dot{x}_i - \dot{x}_{i+1}) + b_i (\dot{x}_i - \dot{x}_{i-1}) + k_i (x_i - x_{i-1}) = u_i - m_i g \sin \theta - R_i$$



Circuito elétrico

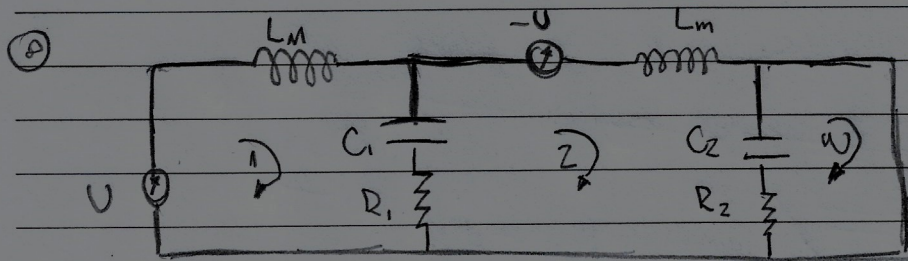

$$1) \quad L_m D i_1 + \frac{1}{C_1 D} (i_1 - i_2) + R_1 (i_1 - i_2) = U$$

$$2) \quad L_m D i_2 + \frac{1}{C_2 D} (i_2 - i_w) + R_2 (i_2 - i_w) + R_1 (i_2 - i_1) + \frac{1}{C_1 D} (i_2 - i_1) = -U$$

$$w) \quad R_2 (i_w - i_2) + \frac{1}{C_2 D} (i_w - i_2) = 0$$

$$M \ddot{x}_1 + k_1 (x_1 - x_2) + b_1 (\dot{x}_1 - \dot{x}_2) = U$$

$$m \ddot{x}_2 + k_1 (x_2 - x_1) + b_1 (\dot{x}_2 - \dot{x}_1) + k_2 (x_2 - w) + b_2 (\dot{x}_2 - \dot{w}) = -U$$

$$b_2 (\dot{w} - \dot{x}_2) + k_2 (w - x_2) = 0$$

5

$$\begin{aligned} \textcircled{b} \quad & | \quad c: M\ddot{x}_1 + k_1(x_1 - x_2) + b_1(\dot{x}_1 - \dot{x}_2) = U \\ & | \quad m\ddot{x}_2 + k_2(x_2 - x_3) + b_2(\dot{x}_2 - \dot{x}_3) + b_1(\dot{x}_2 - \dot{x}_1) + k_1(x_2 - x_1) = -U + W \\ & | \quad b_2(\dot{x}_3 - \dot{x}_2) + k_2(x_3 - x_2) = 0 \end{aligned}$$

 $\textcircled{6}$