
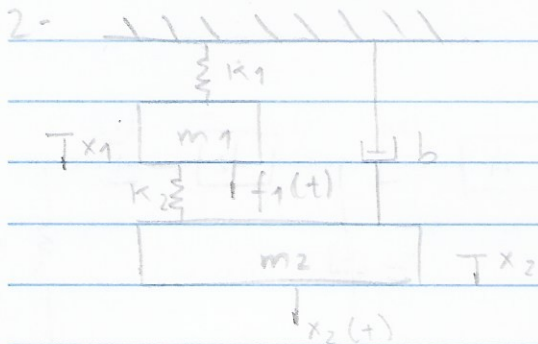


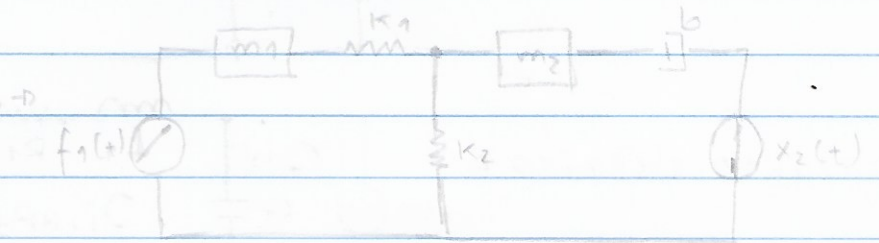
Victor Manoel Ferreira Rosa da Costa 10772713
Analogia tipo 1



circuito mecânico \rightarrow



circuito elétrico \rightarrow

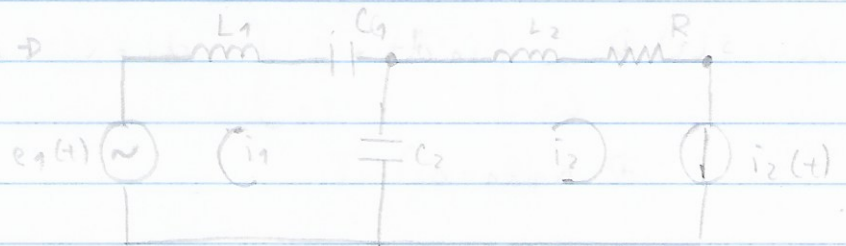

$$V_{L1} + V_{C1} + V_{C2} = e_1(t) \Rightarrow$$


$$\Rightarrow L_1 \frac{di_1}{dt} + \frac{1}{C_1} \int i_1 dt + \frac{1}{C_2} \int i_2 dt - \frac{1}{C_2} \int i_1 dt = e_1(t) \Rightarrow$$

$$\Rightarrow L_1 \ddot{q}_1 + \frac{q_1}{C_1} + \frac{q_1}{C_2} - \frac{q_2}{C_2} = e_1(t) \Rightarrow m_1 \ddot{x}_1 + k_1 x_1 + k_2 (x_1 - x_2) = f_1(t)$$


$$V_{L2} + V_R + V_{C2} = 0 \Rightarrow$$

$$\Rightarrow L_2 \frac{di_2}{dt} + R i_2 + \frac{1}{C_2} \int i_2 dt - \frac{1}{C_2} \int i_1 dt = 0 \Rightarrow$$

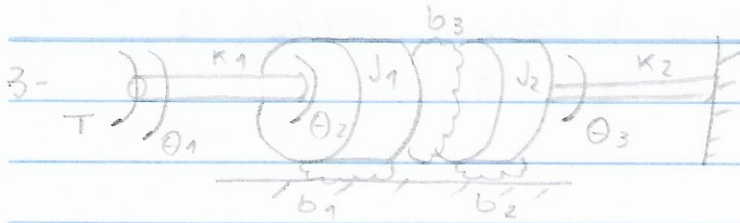
$$\Rightarrow L_2 \dot{q}_2 + R q_2 + \frac{q_2}{C_2} - \frac{q_1}{C_2} = 0 \Rightarrow m_2 \dot{x}_2 + b x_2 + k_2 (x_2 - x_1) = 0$$



circuito mecánico \rightarrow

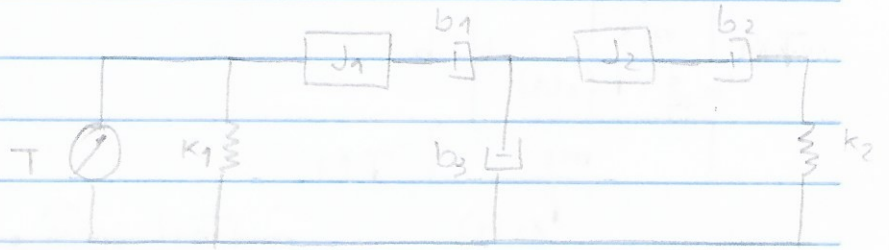

circuito eléctrico \rightarrow

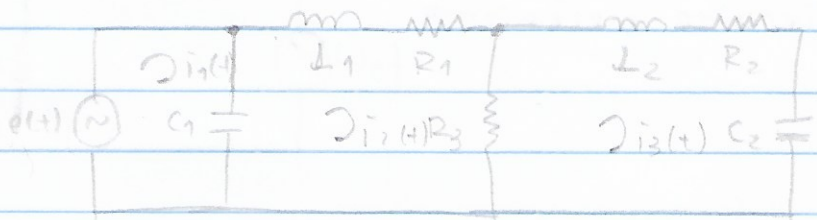

$$V_{C1} = e(t) \Rightarrow \frac{1}{C_1} \int i_1 dt - \frac{1}{C_1} \int i_2 dt = e(t) \Rightarrow q_1 - q_2 = e(t) \Rightarrow$$

$$\Rightarrow k_1(\theta_1 - \theta_2) = T$$

$$V_{L1} + V_{R1} + V_{C1} + V_{R3} = 0 \Rightarrow$$

$$\Rightarrow L_1 \frac{di_2}{dt} + R_1 i_2 + \frac{1}{C_1} \int i_2 dt - \frac{1}{C_1} \int i_1 dt + R_3 i_2 - R_3 i_3 = 0 \Rightarrow$$

$$\Rightarrow L_1 \dot{q}_2 + R_1 q_2 + q_2 - q_1 + R_3 q_2 - R_3 q_3 = 0 \Rightarrow$$

$$\Rightarrow J_1 \ddot{\theta}_2 + b_1 \dot{\theta}_2 + b_3(\dot{\theta}_2 - \dot{\theta}_1) = -k_1(\theta_2 - \theta_1) \Rightarrow$$

$$\Rightarrow J_1 \ddot{\theta}_2 + b_1 \dot{\theta}_2 + b_3(\dot{\theta}_2 - \dot{\theta}_3) = T$$

$$V_{L2} + V_{R2} + V_{C2} + V_{R3} = 0 \Rightarrow$$

$$\Rightarrow L_2 \frac{di_3}{dt} + R_2 i_3 + \frac{1}{C_2} \int i_3 dt + R_3 i_3 - R_3 i_2 = 0 \Rightarrow$$

$$\Rightarrow L_2 \dot{q}_3 + R_2 q_3 + q_3 + R_3 q_3 - R_3 q_2 = 0 \Rightarrow$$

$$\Rightarrow J_2 \ddot{\theta}_3 + b_2 \dot{\theta}_3 + b_3(\dot{\theta}_3 - \dot{\theta}_2) + k_3 \theta_3 = 0$$




$$V_{L3} + V_{C3} + V_{R3} + V_{L4} + V_{R4} = e_3(t) \Rightarrow$$

$$\Rightarrow L_3 \frac{di_3}{dt} + R_3 i_3 - R_3 i_2 + R_4 i_3 - R_4 i_1 + \frac{1}{C_3} \int i_3 dt - \frac{1}{C_3} \int i_2 dt + \frac{1}{C_4} \int i_3 dt -$$


$$- \frac{1}{C_4} \int i_2 dt = e_3(t) \Rightarrow$$

$$\Rightarrow m_3 \ddot{x}_3 + b_3 (x_3 - x_2) + b_4 (x_3 - x_1) + K_3 (x_2 - x_3) + K_4 (x_3 - x_2) = f_3(t)$$


6-

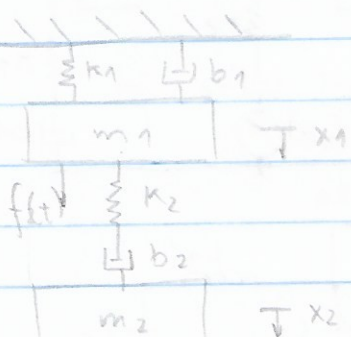

circuito mecánico \Rightarrow

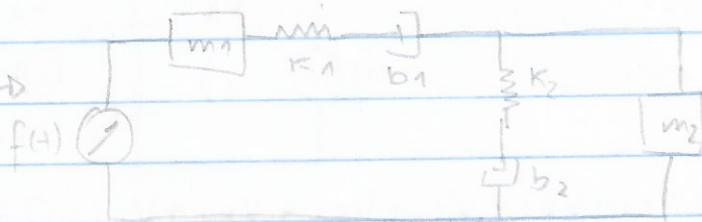

circuito electrónico \Rightarrow

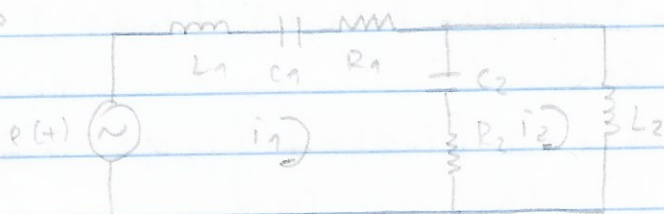

$$V_{L1} + V_{C1} + V_{R1} + V_{C2} + V_{R2} = e(t) \Rightarrow$$

$$\Rightarrow L_1 \frac{di_1}{dt} + R_1 i_1 + R_2 i_1 - R_2 i_2 + \frac{1}{C_1} \int i_1 dt + \frac{1}{C_2} \int i_1 dt - \frac{1}{C_2} \int i_2 dt = e(t) \Rightarrow$$



$$\Rightarrow m_1 \ddot{x}_1 + b_1 \dot{x}_1 + b_2 (x_1 - x_2) + K_1 x_1 + K_2 (x_1 - x_2) = f(t)$$

$$V_{L2} + V_{C2} + V_{R2} = 0 \Rightarrow$$


$$\Rightarrow L_2 \frac{di_2}{dt} + R_2 i_2 - R_2 i_1 + \frac{1}{C_2} \int i_2 dt - \frac{1}{C_2} \int i_1 dt = 0 \Rightarrow$$

$$\Rightarrow m_2 \ddot{x}_2 + b_2 (x_2 - x_1) + K_2 (x_2 - x_1) = 0$$

Lista →

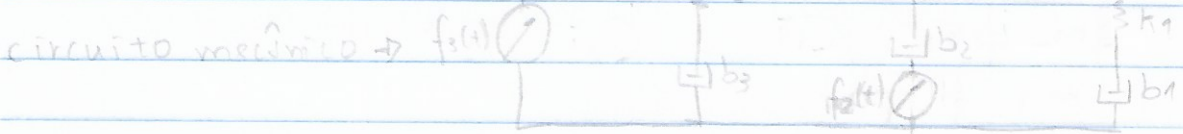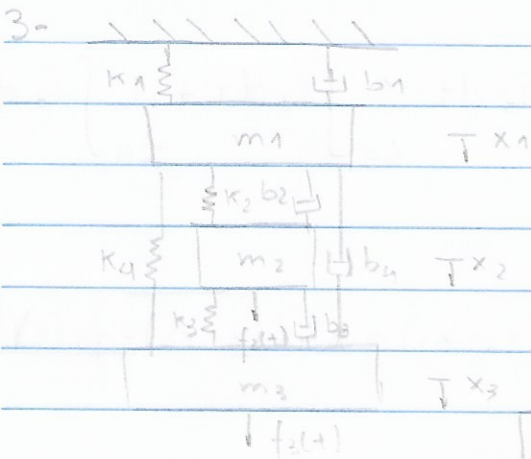

circuito elétrico →

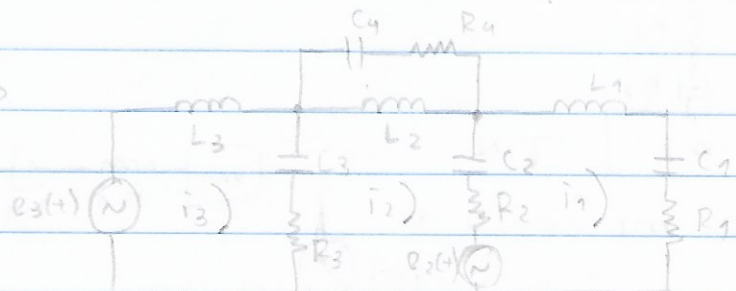

$$V_{L1} + V_{C1} + V_{R1} + V_{C2} + V_{R2} + V_{R4} + V_{C4} = 0 \Rightarrow$$

$$\Rightarrow L_1 \frac{di_1}{dt} + \frac{1}{C_1} \int i_1 dt + R_1 i_1 + \frac{1}{C_2} \int i_2 dt - \frac{1}{C_2} \int i_2 dt + R_2 i_1 - R_2 i_2 +$$

$$+ R_4 i_1 - R_4 i_2 + \frac{1}{C_4} \int i_2 dt - \frac{1}{C_4} \int i_3 dt = 0 \Rightarrow$$


$$\Rightarrow m_1 \ddot{x}_1 + b_1 \dot{x}_1 + b_2(x_1 - \dot{x}_2) + b_4(x_1 - \dot{x}_3) + k_2(x_1 - x_2) + k_4(x_1 - x_3) =$$

$$V_{L2} + V_{C2} + V_{R2} + V_{C3} + V_{R3} = e_2(t) \Rightarrow$$


$$\Rightarrow L_2 \frac{di_2}{dt} + R_2 i_2 - R_2 i_1 + R_3 i_2 - R_3 i_3 + \frac{1}{C_2} \int i_2 dt - \frac{1}{C_2} \int i_1 dt +$$

$$+ \frac{1}{C_3} \int i_2 dt - \frac{1}{C_3} \int i_3 dt = e_2(t) \Rightarrow$$
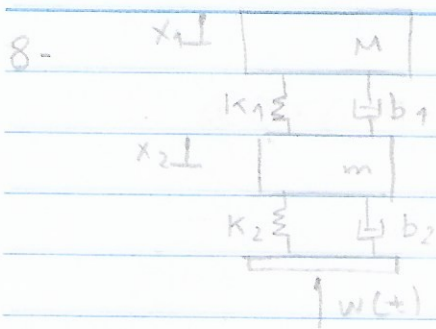
$$\Rightarrow m_2 \ddot{x}_2 + b_2(x_2 - \dot{x}_1) + b_3(x_2 - \dot{x}_3) + k_2(x_2 - x_1) + k_3(x_2 - x_3) = f_2(t)$$



a) $w(t)$ -displacement

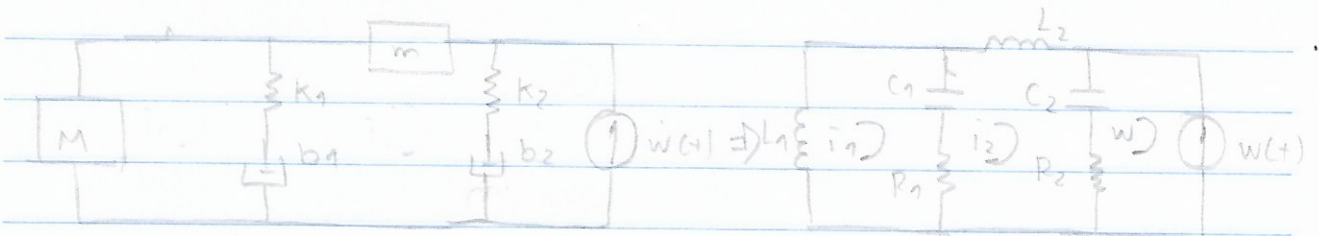

$$V_{L1} + V_{C1} + V_{R1} = 0 \Rightarrow$$

$$\Rightarrow L_1 \frac{di_1}{dt} + R_1 i_1 - R_1 i_2 + \frac{1}{C_1} \int i_1 dt - \frac{1}{C_1} \int i_2 dt = 0 \Rightarrow$$


$$\Rightarrow M \ddot{x}_1 + b_1 (x_1 - x_2) + k_1 (x_1 - x_2) = 0$$

$$V_{L2} + V_{C2} + V_{R2} + V_{C1} + V_{R1} = 0 \Rightarrow$$

$$\Rightarrow L_2 \frac{di_2}{dt} + R_2 i_2 - R_1 i_1 + R_2 i_2 - R_2 w + \frac{1}{C_2} \int i_2 dt - \frac{1}{C_1} \int i_1 dt +$$

$$+ \frac{1}{C_2} \int i_2 dt - \frac{1}{C_2} \int w dt = 0 \Rightarrow m \ddot{x}_2 + b_1 (x_2 - x_1) + b_2 (x_2 - w(t)) + k_1 (x_2 - x_1) + k_2 (x_2 - w(t)) = 0$$

b) $w(t)$ -force

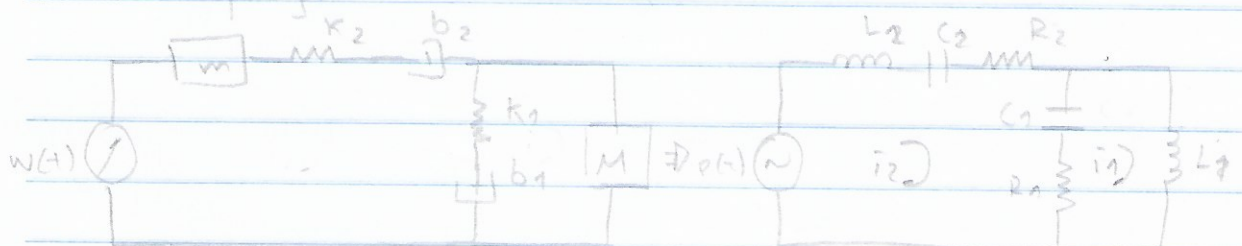

$$V_{L2} + V_{C2} + V_{R2} + V_{C1} + V_{R1} = e(t) \Rightarrow$$

$$\Rightarrow L_2 \frac{di_2}{dt} + R_2 i_2 + R_1 i_2 - R_1 i_1 + \frac{1}{C_2} \int i_2 dt + \frac{1}{C_1} \int i_2 dt - \frac{1}{C_1} \int i_1 dt = e(t) \Rightarrow$$

$$\Rightarrow m \ddot{x}_2 + b_2 \dot{x}_2 + b_1 (x_2 - x_1) + k_2 x_2 + k_1 (x_2 - x_1) = w(t)$$



$$V_{L1} + V_{C1} + V_{B1} = 0 \Rightarrow$$

$$\Rightarrow L_1 \frac{di_1}{dt} + \frac{1}{C_1} \int i_1 dt - \frac{1}{C_1} \int i_2 dt + R_1 i_1 - R_1 i_2 = 0 \Rightarrow$$

$$\Rightarrow M \ddot{x}_1 + b_1 (x_1 - x_2) + k_1 (x_1 - x_2) = 0$$