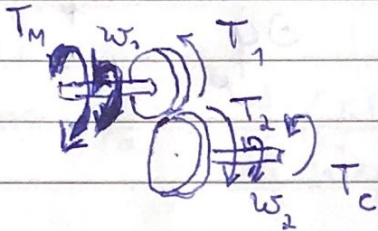


Carolina Carvalho Silva - 10705933

- Exercícios do dia 15/09 -



Eixo 1:

$$J_1 \dot{\omega}_1 + B_1 \omega_1 + T_1 = T_M \quad (1)$$

⊗

Eixo 2:

$$J_2 \dot{\omega}_2 + B_2 \omega_2 + T_c = T_2$$

$$\Rightarrow J_2 \dot{\omega}_2 + B_2 \omega_2 + T_c = T_1 \cdot n \quad (2)$$


De (1):  $T_1 = -J_1 \dot{\omega}_1 - B_1 \omega_1 + T_M$   
 $= -J_1 n \dot{\omega}_2 - B_1 n \omega_2 + T_M \quad (3)$

Substituindo (3) em (2):

$$J_2 \dot{\omega}_2 + B_2 \omega_2 + T_c = (-J_1 n \dot{\omega}_2 - B_1 n \omega_2 + T_M) n$$

$$\Rightarrow (J_2 + J_1 n^2) \dot{\omega}_2 + (B_2 + B_1 n^2) \omega_2 + (T_c - T_M n) = 0$$

Analogia do tipo 2:

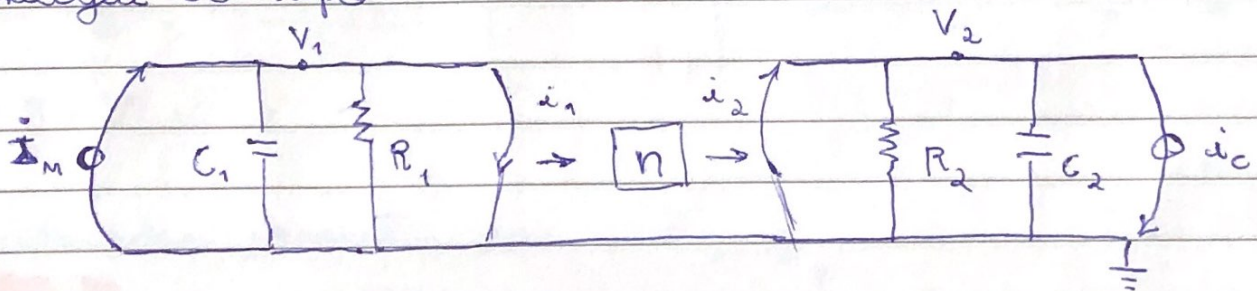


$$1: V_1 \left( C_1 D + \frac{1}{R_1} \right) = i_m - i_1$$

$$2: V_2 \left( C_2 D + \frac{1}{R_2} \right) = i_2 - i_c$$

$$\begin{cases} J_1 \dot{\omega}_1 + B_1 \omega_1 = T_M - T_1 \\ J_2 \dot{\omega}_2 + B_2 \omega_2 = T_2 - T_C \end{cases}$$


Analogia tipo 1:

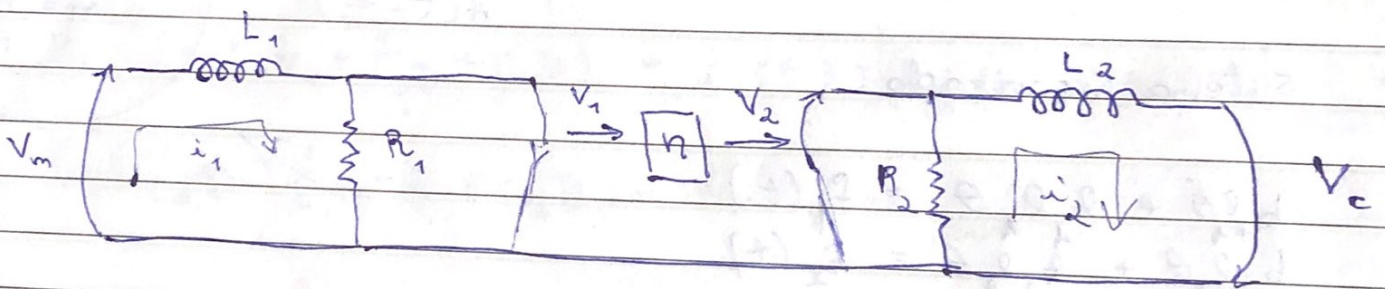


Malha 1:  $L_1 D \cdot i_1 + R_1 i_1 = V_m - V_1$

Malha 2:  $R_2 i_2 + L_2 D i_2 = V_2 - V_c$


$$\begin{cases} J_1 \dot{\omega}_1 + B_1 \omega_1 = T_M - T_1 \\ J_2 \dot{\omega}_2 + B_2 \omega_2 = T_2 - T_C \end{cases}$$

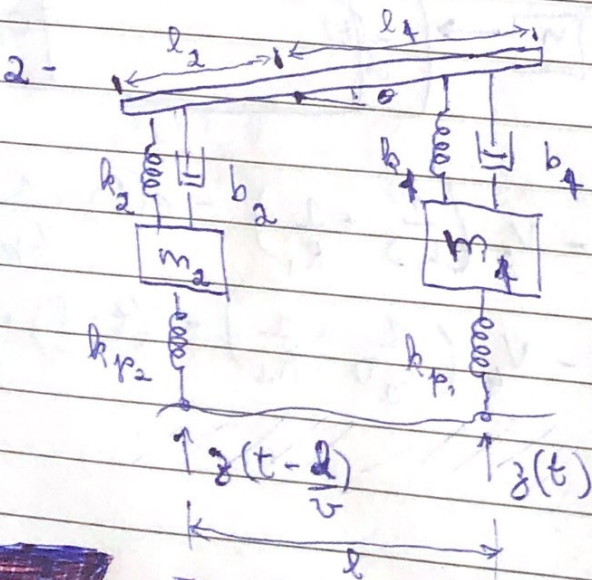

Sistema 1:

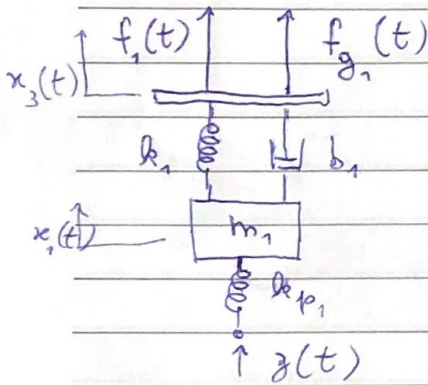

Sistema 2:

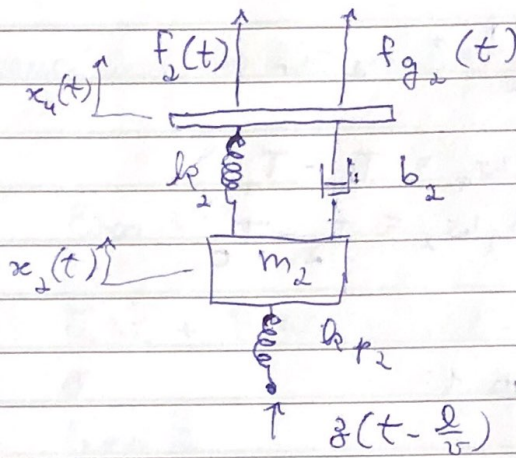

$$n = \frac{l_1}{l_2}$$

$$F_1 l_1 \theta_1 = F_2 l_2 \theta_2$$

$$\frac{l_1}{l_2} = \frac{F_1}{F_2}$$

$$\therefore n = \frac{F_1}{F_2}$$

Sistema linearizado:


$$b_1 l_1 \dot{\theta} + k_1 l_1 \theta = f_1(t)$$

$$b_2 l_2 \dot{\theta} + k_2 l_2 \theta = f_2(t)$$

$$b_1 \dot{x}_G - b_1 x_1 + k_1 x_G - k_1 x_1 = f_{g1}(t)$$

$$b_2 \dot{x}_G - b_2 x_2 + k_2 x_G - k_2 x_2 = f_{g2}(t)$$

Analogia 2:

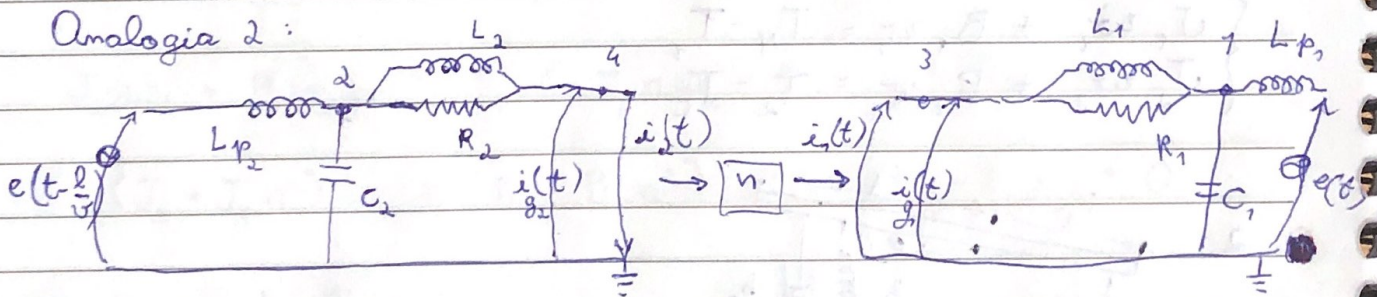

$$\text{No } 1: V_1 \left( \frac{1}{L_1 D} + \frac{1}{R_1} + \frac{1}{L_2 D} + C_1 D \right) - V_3 \left( \frac{1}{L_1 D} + \frac{1}{R_1} \right) - e(t) \cdot \frac{1}{L_2 D} = 0$$

$$\text{No } 2: V_2 \left( \frac{1}{L_2 D} + \frac{1}{R_2} + \frac{1}{L_1 D} + C_2 D \right) - V_4 \left( \frac{1}{L_2 D} + \frac{1}{R_2} \right) - e(t - l/v) \cdot \frac{1}{L_1 D} = 0$$

$$\text{Nó 3: } V_3 \left( \frac{1}{L_1 D} + \frac{1}{R_1} \right) - i_1(t) - i_{g_1}(t) = 0$$

$$\text{Nó 4: } V_4 \left( \frac{1}{L_2 D} + \frac{1}{R_2} \right) - i_{g_2}(t) - i_2(t) = 0$$

$$\Rightarrow \begin{cases} V_3 \left( \frac{1}{L_1 D} + \frac{1}{R_1} \right) = i_1(t) + i_{g_1}(t) \\ V_4 \left( \frac{1}{L_2 D} + \frac{1}{R_2} \right) = i_2(t) + i_{g_2}(t) \end{cases}$$

Substituindo nos nós 1 e 2:

$$\left\{ V_1 \left( \frac{1}{L_1 D} + \frac{1}{R_1} + \frac{1}{L_{p_1} D} + C_1 D \right) - i_1(t) - i_{g_1}(t) - e(t) \cdot \frac{1}{L_{p_1} D} = 0 \right.$$

$$\left. V_2 \left( \frac{1}{L_{p_2} D} + \frac{1}{L_2 D} + \frac{1}{R_2} + C_2 D \right) - i_2(t) - i_{g_2}(t) - e(t - \frac{l}{v}) \cdot \frac{1}{L_{p_2} D} = 0 \right.$$

$$\left\{ v_1 \left( \frac{k_1}{D} + b_1 + \frac{k_{p_1}}{D} + m_1 D \right) - f_1(t) - f_{g_1}(t) - \dot{z}(t) \cdot \frac{k_{p_1}}{D} = 0 \right.$$

$$\left. v_2 \left( \frac{k_{p_2}}{D} + \frac{k_2}{D} + b_2 + m_2 D \right) - f_2(t) - f_{g_2}(t) - \dot{z}(t - \frac{l}{v}) \cdot \frac{k_{p_2}}{D} = 0 \right.$$

$$\begin{cases} m_1 \ddot{x}_1 + b_1 \dot{x}_1 + (k_1 + k_{p_1}) x_1 = f_1(t) + f_{g_1}(t) + k_{p_1} \dot{z}(t) \\ m_2 \ddot{x}_2 + b_2 \dot{x}_2 + (k_2 + k_{p_2}) x_2 = f_2(t) + f_{g_2}(t) + k_{p_2} \dot{z}(t - \frac{l}{v}) \end{cases}$$

$$f_1 l_1 + f_{g_1} l_1 + f_{g_2} l_1 - f_2 l_2 = J_g \ddot{z}$$