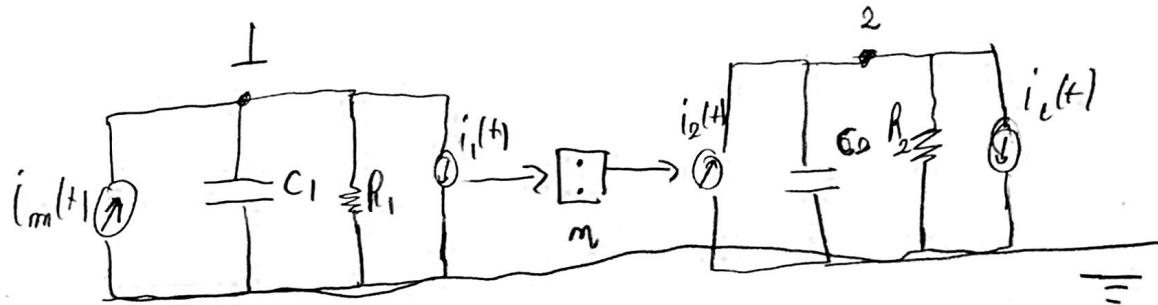


Gabriel Rodrigues Camargo - 10772460
PME 3380 -

Excs aula 15/09

① a) Por analogia tipo 2, temos o circuito:



Nó 1 e 2:


$$\begin{cases} V_1 \left(C_1 D + \frac{1}{R_1} \right) = i_m (+) - i_1 (+) \\ V_2 \left(C_2 D + \frac{1}{R_2} \right) = i_2 (+) - i_c (+) \end{cases} \quad \text{onde pelo transformador: } i_2 = m i_1,$$

(P1 sistema mecanico)

$$\begin{cases} \ddot{\theta}_1 (J_1 D + B_1) = T_m - T_1 \\ \ddot{\theta}_2 (J_2 D + B_2) = T_2 - T_c \end{cases} \Rightarrow \begin{cases} J_1 \ddot{\theta}_1 + B_1 \dot{\theta}_1 = T_m - T_1 \\ J_2 \ddot{\theta}_2 + B_2 \dot{\theta}_2 = T_2 - T_c \end{cases}$$

$$\text{onde } T_2 = T_1 m \Rightarrow \dot{\theta}_1 = m \dot{\theta}_2$$

b) Por analogia 1:

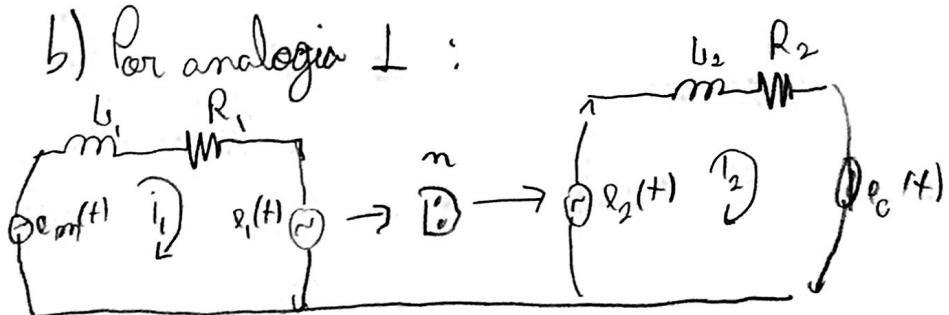

Equações:

$$i_1 (L_1 D + R_1) = e_m (+) - e_1 (+) \quad \text{com } e_2 (+) = e_1 (+)$$

$$i_2 (L_2 D + R_2) = e_c (+) - e_2 (+)$$


P/ sistema mecânico :

$$\begin{cases} \dot{\theta}_1 (\bar{J}_1 D + B_1) = T_m - \bar{T}_1 \\ \dot{\theta}_2 (\bar{J}_2 D + B_2) = T_2 - T_c \end{cases} \Rightarrow \begin{cases} \bar{J}_1 \ddot{\theta}_1 + B_1 \dot{\theta}_1 = T_m - \bar{T}_1 \\ \bar{J}_2 \ddot{\theta}_2 + B_2 \dot{\theta}_2 = T_2 - T_c \end{cases}$$

Com



$$T_2 = m \bar{T}_1 \xrightarrow{\text{logo}} \dot{\theta}_1 = m \dot{\theta}_2$$

②

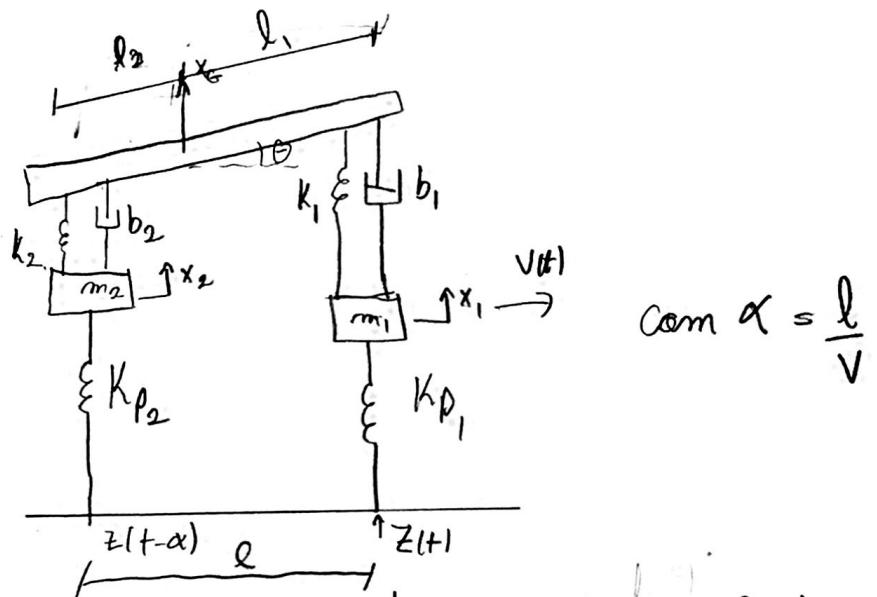

$$\text{Com } \alpha = \frac{l}{V}$$

Separando em 2:

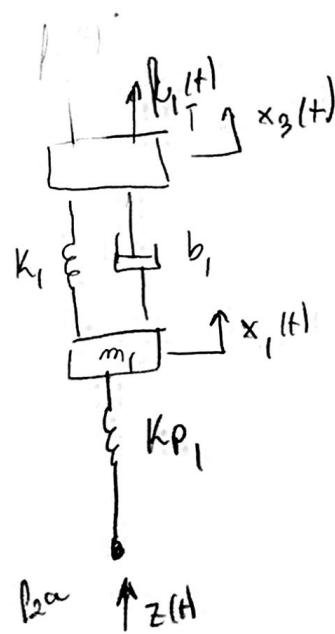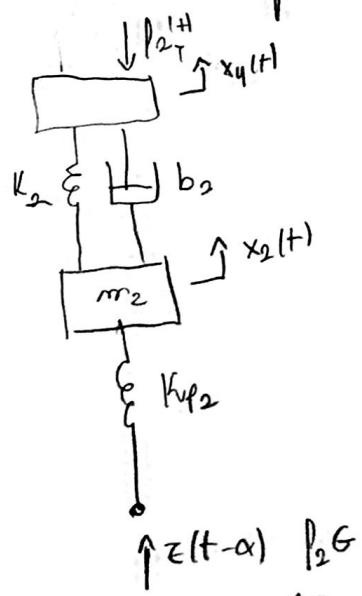


$$f_{2T}^{(4)} = l_2 \underbrace{(k_2 \theta + b_2 \dot{\theta})}_{\underbrace{P_2 G}_{f_2 a}} - \left(b_2 (\dot{x}_G - \dot{x}_2) + k_2 (x_G - x_2) \right)$$

$$f_{1T}^{(4)} = l_1 \underbrace{(k_1 \theta + b_1 \dot{\theta})}_{\underbrace{P_1 G}_{f_1 a}} + b_1 (\dot{x}_G - \dot{x}_1) + k_1 (x_G - x_1)$$

As potências transferidas nesse caso precisam ser iguais:

$$P_{1a} \cdot V_{1a} = P_{2a} \cdot V_{2a} \Rightarrow P_{1a} l_1 \dot{\theta} = P_{2a} l_2 \dot{\theta} \Rightarrow m = \frac{l_1}{l_2} = \frac{P_{2a}}{P_{1a}}$$

Círculo análogo por analogia tipo 2:

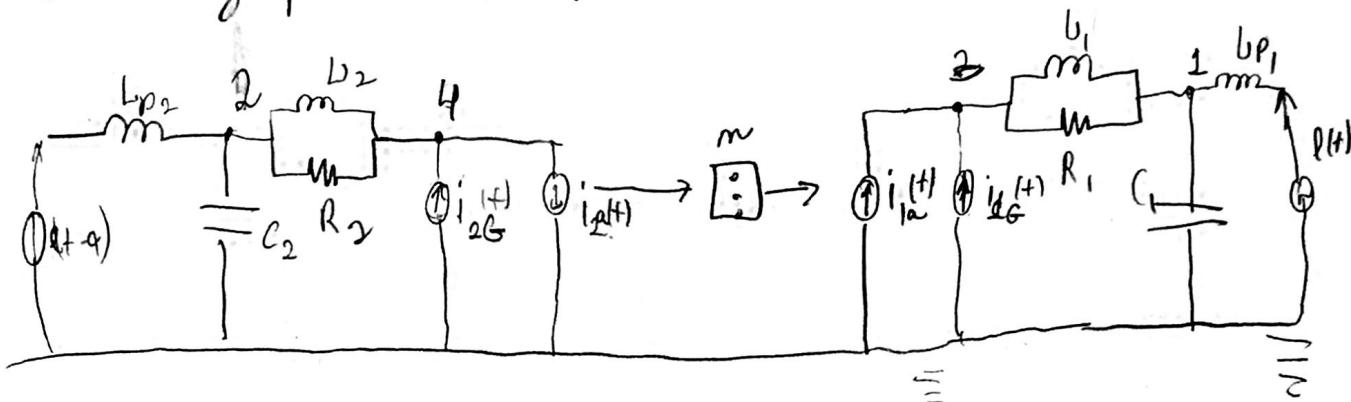

P/ més 1, 2, 3 e 4:

$$V_1 \left(C_1 D + \frac{1}{R_1} + \frac{1}{L_1 D} + \frac{1}{L_{1p} D} \right) - e(t+) \cdot \frac{1}{L_{1p} D} = V_3 \left(\frac{1}{R_1} + \frac{1}{L_1 D} \right) = 0$$

$$V_3 \left(\frac{1}{R_1} + \frac{1}{L_1 D} \right) - (i_{1a}(t+) + i_{1G}(t+)) = 0$$

$$V_4 \left(\frac{1}{R_2} + \frac{1}{L_2 D} \right) + i_{2a}(t+) - i_{2G}(t+) = 0$$

$$V_2 \left(C_2 D + \frac{1}{R_2} + \frac{1}{L_2 D} + \frac{1}{L_{2p} D} \right) - e(t+\alpha) \cdot \frac{1}{L_{2p} D} - V_4 \left(\frac{1}{R_2} + \frac{1}{L_2 D} \right) = 0$$

Fazendo substituições apropriadas:

$$\left\{ V_1 \left(C_1 D + \frac{1}{R_1} + \frac{1}{L_1 D} + \frac{1}{L_{1p} D} \right) = i_{1a}(t+) + i_{1G}(t+) + \frac{e(t)}{L_{1p} D} \right.$$

$$\left. V_2 \left(C_2 D + \frac{1}{R_2} + \frac{1}{L_2 D} + \frac{1}{L_{2p} D} \right) = -i_{2a}(t+) + i_{2G}(t+) + \frac{e(t-\phi)}{L_{2p} D} \right.$$

Analogia mecânica:

$$\begin{cases} m_1 \ddot{x}_1 + b_1 \dot{x}_1 + (k_1 + k_1 p)x_1 = f_{1a}(t) + f_{G1}(t) + k_1 p z(t) \\ m_2 \ddot{x}_2 + b_2 \dot{x}_2 + (k_2 + k_2 p)x_2 = f_{2a}(t) + f_{G2}(t) + k_2 p z(t-\alpha) \end{cases}$$

↓
Encontramos as outras posições por:

$$\begin{cases} P_{2T}(t) + P_{1T}(t) = M \ddot{x}_G \\ P_{2T} l_2 + P_{1T} l_1 = J_G \ddot{\theta} \end{cases}$$

③ Demonstrar eq dif ρ / ω_2 da caixa de transmissão:

$$J_2 \ddot{\omega}_2 + B_2 \omega_2 + T_C = T_2$$

$$J_1 \ddot{\omega}_1 + B_1 \omega_1 + T_1 = T_m$$

Com potências iguais:

$$T_1 \omega_1 = T_2 \omega_2 \Rightarrow m = \frac{\omega_1}{\omega_2} = \frac{T_2}{T_1}$$

Substituindo essa definição e isolando T_1 :

$$J_2 \ddot{\omega}_2 + B_2 \omega_2 + T_C = m T_1$$

$$T_1 = T_m - (J_1 \ddot{\omega}_1 + B_1 \omega_1)$$

Substituindo:

$$J_2 \ddot{\omega}_2 + B_2 \omega_2 + T_C = m (T_m - J_1 \ddot{\omega}_1 + B_1 \omega_1)$$

Com $\dot{\omega}_1 = m \dot{\omega}_2$:

$$J_2 \ddot{\omega}_2 + B_2 \omega_2 + J_1 m^2 \ddot{\omega}_2 + B_1 m^2 \omega_2 + T_C = m T_m$$

$$(J_2 + m^2 J_1) \ddot{\omega}_2 + (B_2 + m^2 B_1) \omega_2 + T_C = m T_m$$

$$\boxed{J_{eq2} \ddot{\omega}_2 + B_{eq2} \omega_2 + T_C = m T_m}$$