
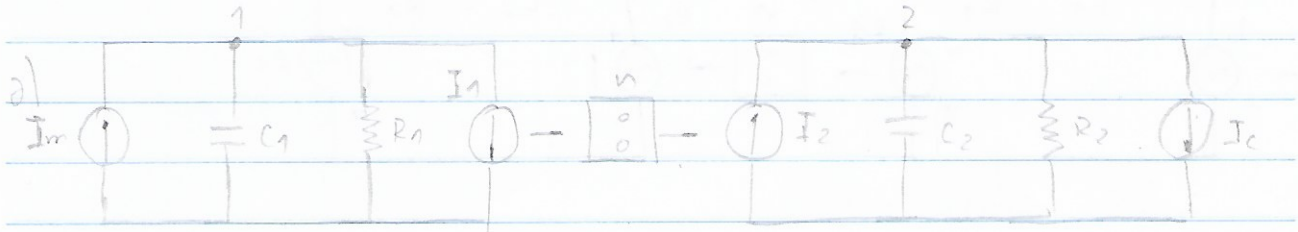


Transformadores

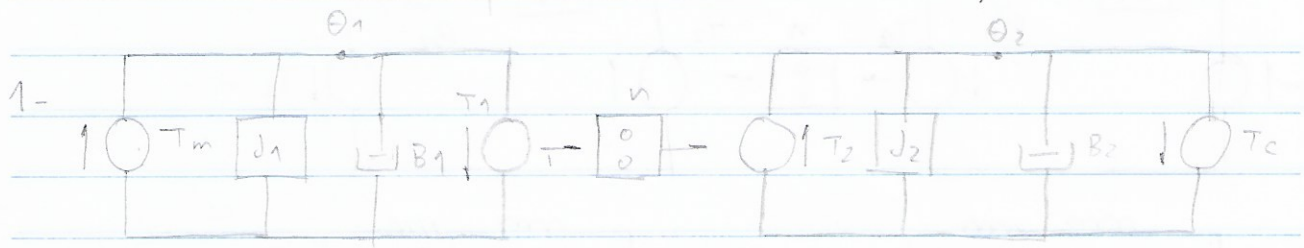

$$V_1 (C_1 D + R_1) = I_m - I_1 \Rightarrow \dot{\theta}_1 (J_1 D + B_1) = T_m - T_1 \Rightarrow$$

$$\Rightarrow J_1 \ddot{\theta}_1 + B_1 \dot{\theta}_1 = T_m - T_1$$

$$V_2 (C_2 D + R_2) = I_2 - I_c \Rightarrow \dot{\theta}_2 (J_2 D + B_2) = T_2 - T_c \Rightarrow$$

$$\Rightarrow J_2 \ddot{\theta}_2 + B_2 \dot{\theta}_2 = T_2 - T_c$$

$$T_1 = T_2 \Rightarrow J_1 \ddot{\theta}_1 + B_1 \dot{\theta}_1 + T_2 = T_m \Rightarrow$$



$$\Rightarrow J_1 \ddot{\theta}_1 + B_1 \dot{\theta}_1 + \frac{1}{n} (J_2 \ddot{\theta}_2 + B_2 \dot{\theta}_2 + T_c) = T_m$$

$$\dot{\theta}_2 = \dot{\theta}_1 \Rightarrow \dot{\theta}_1 \left(J_1 + \frac{J_2}{n^2} \right) + \dot{\theta}_1 \left(B_1 + \frac{B_2}{n^2} \right) + \frac{T_c}{n} = T_m \Rightarrow$$

$$\Rightarrow \left| J_{eq1} \dot{\theta}_1 + B_{eq1} \dot{\theta}_1 + \frac{T_c}{n} = T_m \right|$$

$$J_2 \ddot{\theta}_2 + B_2 \dot{\theta}_2 + T_c = T_1 n \Rightarrow J_2 \ddot{\theta}_2 + B_2 \dot{\theta}_2 + T_c = n (-J_1 \ddot{\theta}_1 - B_1 \dot{\theta}_1 + T_m) \Rightarrow$$
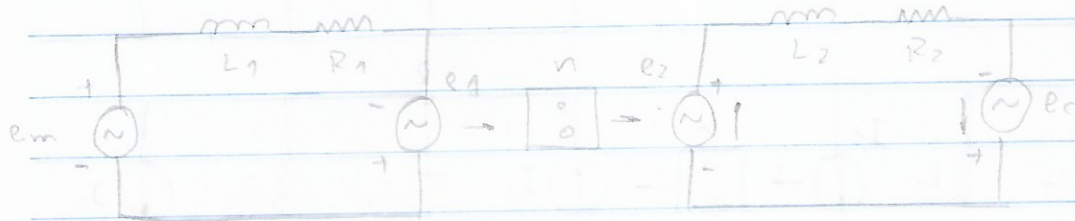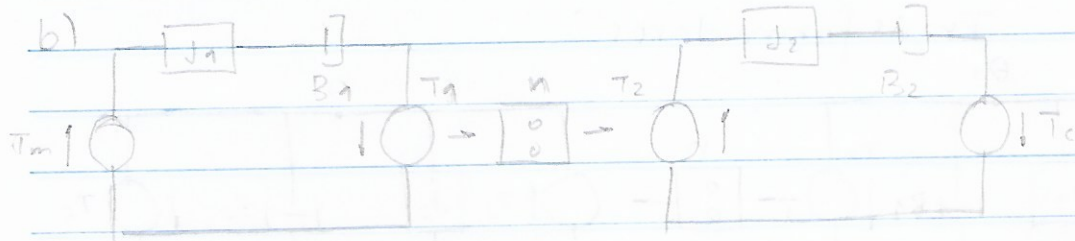
$$\Rightarrow \dot{\theta}_2 (J_2 + J_1 n^2) + \dot{\theta}_2 (B_2 + B_1 n^2) + T_c = n T_m$$



$$V_{L1} + V_{R1} = e_m - e_1 \Rightarrow L_1 \frac{dI_1}{dt} + R_1 I_1 = e_m - e_1 \Rightarrow$$

$$\Rightarrow J_1 \ddot{\theta}_1 + B_1 \dot{\theta}_1 = T_m - T_1$$

$$V_{L2} + V_{R2} = e_2 - e_c \Rightarrow L_2 \frac{dI_2}{dt} + R_2 I_2 = e_2 - e_c \Rightarrow$$

$$\Rightarrow J_2 \ddot{\theta}_2 + B_2 \dot{\theta}_2 = T_2 - T_c$$

$$n = \dot{\theta}_1 = I_2$$

$$\dot{\theta}_2 = T_1$$

$$J_{eq1} \ddot{\theta}_1 + B_{eq1} \dot{\theta}_1 + T_c = T_m$$

$$J_{eq2} \ddot{\theta}_2 + B_{eq2} \dot{\theta}_2 + T_c = n T_m$$