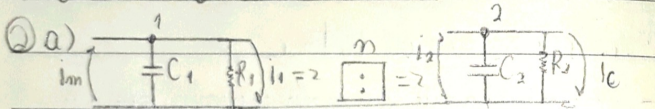


Exercício Guia - 15/09/2020


① $J_1 \dot{\omega}_1 + B_1 \omega_1 + T_1 = T_m$
 $J_2 \dot{\omega}_2 + B_2 \omega_2 + T_c = T_2 = m T_1$
 $J_2 \dot{\omega}_2 + B_2 \omega_2 + T_c = m(T_m - J_1 \dot{\omega}_1 - B_1 \omega_1)$
 $J_2 \dot{\omega}_2 + B_2 \omega_2 + T_c = m(T_m - J_1 m \dot{\omega}_2 - B_1 m \omega_2)$
 $\dot{\omega}_2 (J_2 + m^2 J_1) + \omega_2 (B_2 + m^2 B_1) + T_c = m T_m$
 $J_2 m \dot{\omega}_2 + B_2 m \omega_2 + T_c = T_m \cdot m$



• Malha 1: $(C_1 D + \frac{1}{R_1}) V_1 = i_m - i_1$
 • Malha 2: $(C_2 D + \frac{1}{R_2}) V_2 = i_2 - i_c$

$J_1 \dot{\omega}_1 + B_1 \omega_1 = T_m - T_1$


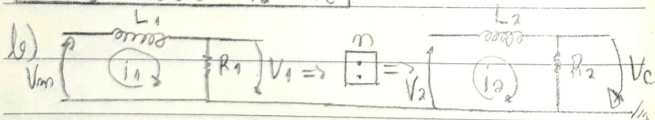
$J_2 \dot{\omega}_2 + B_2 \omega_2 = T_2 - T_c$



• Malha 1: $L_1 D i_1 + R_1 i_1 = V_m - V_1$

• Malha 2: $L_2 D i_2 + R_2 i_2 = V_2 - V_c$

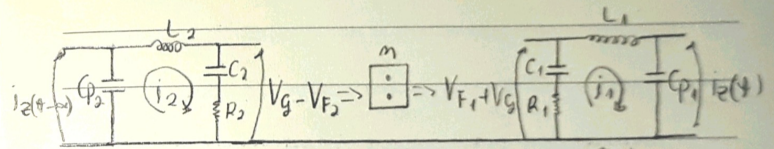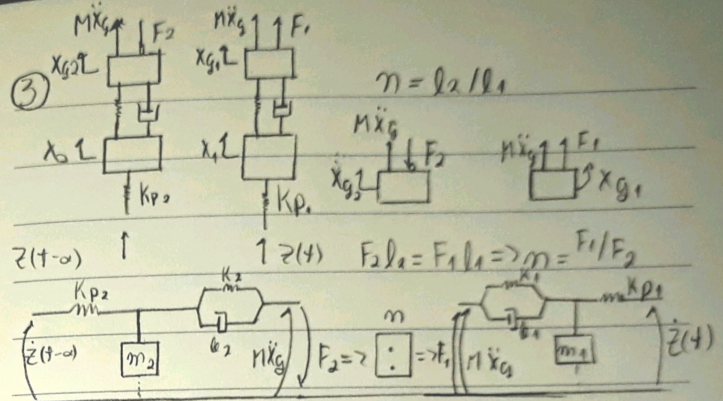$J_1 \dot{\omega}_1 + B_1 \omega_1 = T_m - T_1$; $J_2 \dot{\omega}_2 + B_2 \omega_2 = V_2 - V_c$



• Malha 1: $i_1 (L_1 D + R_1 + \frac{1}{C_1 D} + \frac{1}{C_2 D}) - i_2 (t) (\frac{1}{C_2 D}) = V_{F_1} + V_G$
 • Malha 2: $i_2 (L_2 D + R_2 + \frac{1}{C_2 D} + \frac{1}{C_1 D}) - i_1 (t) (\frac{1}{C_1 D}) = V_G - V_{F_2}$
 $m_1 \ddot{x}_1 + b_1 \dot{x}_1 + k_1 x_1 + k_p x_1 - k_p \cdot z(t) = F_1 + M \ddot{x}_G$
 $m_2 \ddot{x}_2 + b_2 \dot{x}_2 + k_2 x_2 + k_p x_2 - k_p \cdot z(t-\omega) = -F_2 + M \ddot{x}_G$