

Aplicando I: $J_1 \dot{w}_1 = T_m - T_1 - B_1 w_1$ ②

Aplicando II: $J_2 \dot{w}_2 + B_2 w_2 + T_c = T_2$ ③


aplicando I em III e reescrevendo II

$J_2 \dot{w}_2 + B_2 w_2 + T_c = T_m$ ④

$T_1 = T_m - J_1 m \dot{w}_2 - B_1 m w_2$ ⑤; aplicado V em ④;

$J_2 \dot{w}_2 + B_2 w_2 + T_c = T_m - J_1 m^2 \dot{w}_2 - B_1 m^2 w_2$
 $\Rightarrow (J_2 + J_1 m^2) \dot{w}_2 + (B_2 + B_1 m^2) w_2 + T_c = T_m$

Solução por analogia tipo 2:

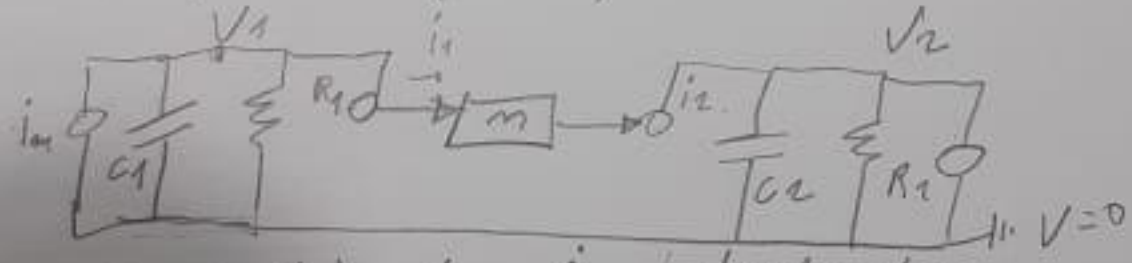


$V_1 (C_1 D + \frac{1}{R_1}) = i_m - i_1$
 $V_2 (C_2 D + \frac{1}{R_2}) = i_2 - i_2$

transformadores
 $i_2 = m i_1$
 $V_2 = V_1 / m$

reescrevendo

$$\left. \begin{aligned} J_1 \dot{w}_1 + B_1 w_1 &= T_m - T_1 \\ J_2 \dot{w}_2 + B_2 w_2 &= T_2 - T_c \end{aligned} \right\} \begin{aligned} T_2 &= m T_1 \\ w_2 &= w_1 / m \text{ (atenção)} \end{aligned}$$

analogia 1

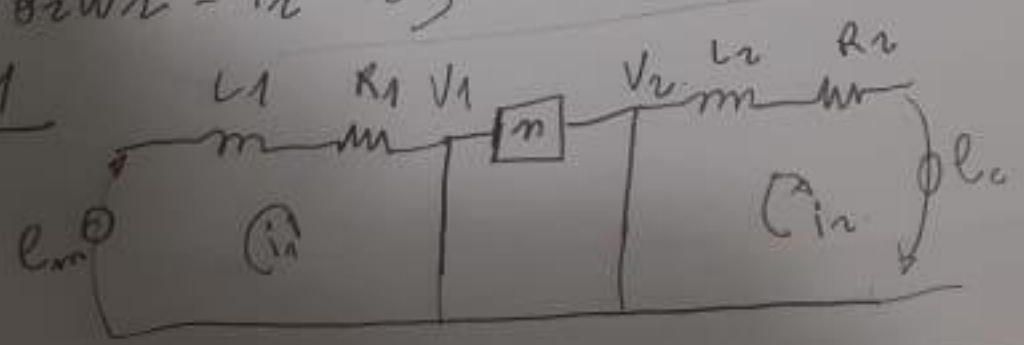


todas malhas em 1:
 $L_1 D i_1 + R_1 i_1 = E_m - V_1$
 malhas em 2.

transformadores
 $V_2 = n V_1$
 $i_2 = \frac{i_1}{n}$

em 2: $L_2 D i_2 + R_2 i_2 = V_2 - E_m$

relacionando por analogia


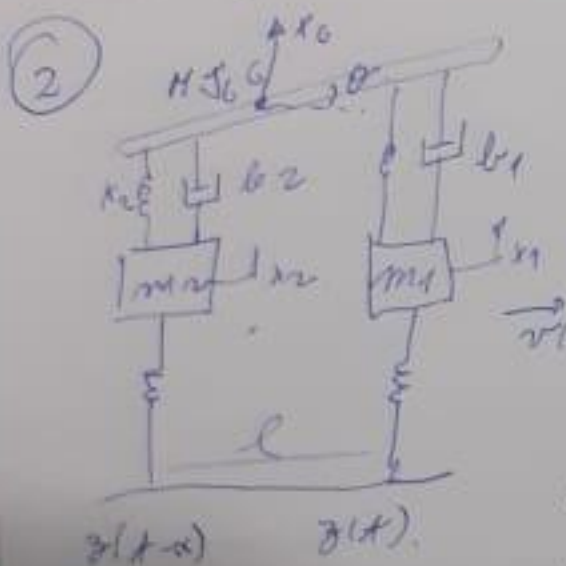
$B_1 u_1 + B_2 u_1 = T_1 - T_2$ com $T_2 = n T_1$
 $B_2 u_2 + B_1 u_2 = T_2 - T_1$ $u_2 = \frac{u_1}{n}$



separar os 2 sistemas de 1/4 curso ligados por um transf que introduz o mov de fuga em.



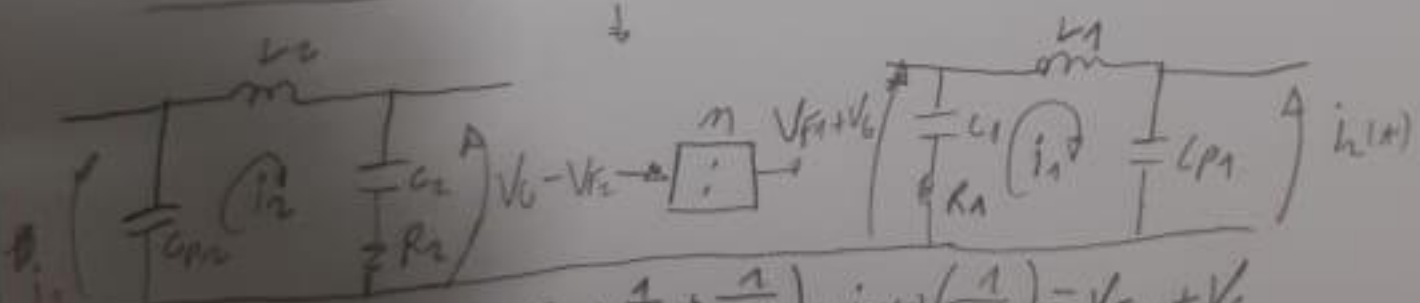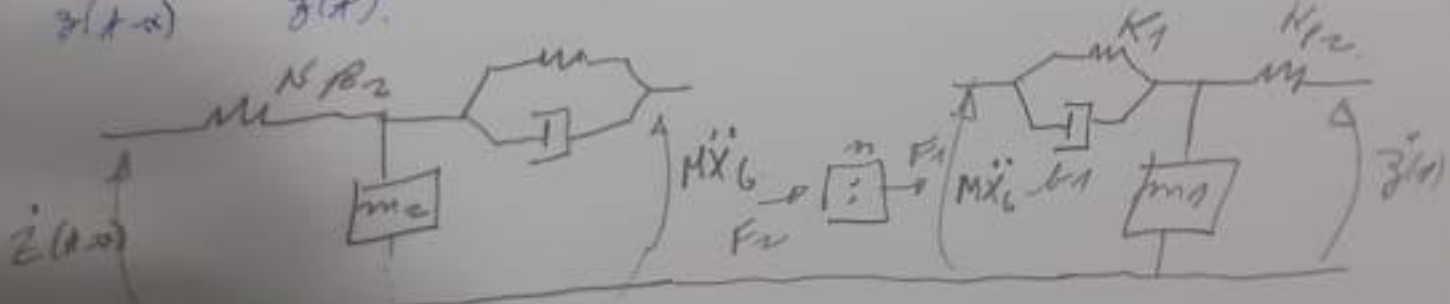$F_2 b_2 = F_1 b_1 \rightarrow n = \frac{F_1}{F_2}$



malha 1: $i_1 (L_1 D + R_1 + \frac{1}{C_1 D} + \frac{1}{C_2 D}) + i_2(t) (\frac{1}{C_2 D}) = V_{F1} + V_0$
 malha 2: $i_2 (L_2 D + R_2 + \frac{1}{C_2 D} + \frac{1}{C_1 D}) - i_1(t-2) (\frac{1}{C_2 D}) = V_0 - V_{F2}$
 fided: $m_1 \ddot{x}_1 + b_1 \dot{x}_1 + K_1 x_1 + K_{p1} x_1 - K_{p1} z(t) = F_1 + M \ddot{x}_0$
 $m_2 \ddot{x}_2 + b_2 \dot{x}_2 + K_2 x_2 + K_{p2} x_2 - K_{p2} z(t-d) = -F_2 + M \ddot{x}_0$

$$(3) J_1 \dot{\omega}_1 + B_1 \omega_1 + T_1 = T_m$$

$$J_2 \dot{\omega}_2 + B_2 \omega_2 + T_c = T_2 - m T_1$$

$$J_2 \dot{\omega}_2 + B_2 \omega_2 + T_c = m (T_m - J_1 \dot{\omega}_1 - B_1 \omega_1)$$

$$J_2 \dot{\omega}_2 + B_2 \omega_2 + T_c = m (T_m - J_1 m \dot{\omega}_1 - B_1 m \omega_1)$$

$$\dot{\omega}_2 (J_2 + m^2 J_1) + \omega_2 (B_2 + m^2 B_1) + T_c = m T_m$$

$$J_{eq} \dot{\omega}_2 + B_{eq} \omega_2 + T_c = T_m$$

600'0