

Henrique Silva Barbosa - 10769323

1) Por sistema mecânico:

$$\begin{cases} J_1 \dot{\omega}_1 + B_1 \omega_1 = T_m - T_1 \\ J_2 \dot{\omega}_2 + B_2 \omega_2 = T_2 - T_c \end{cases}$$

$$P_1 = P_2 ; \quad T_1 \omega_1 = T_2 \omega_2$$

$$T_2 = \frac{T_1 \omega_1}{\omega_2} \rightarrow T_2 = \eta T_1$$


$$J_2 \dot{\omega}_2 + B_2 \omega_2 + T_c = \eta (T_m - J_1 \dot{\omega}_1 - B_1 \omega_1)$$

$$J_2 \dot{\omega}_2 + B_2 \omega_2 + T_c = \eta (T_m - J_1 \eta \dot{\omega}_2 - B_2 \eta \omega_2)$$

$$\dot{\omega}_2 (J_2 + \eta^2 J_1) + \omega_2 (B_2 + \eta^2 B_1) + T_c = \eta T_m$$


$J_{eq,2} \dot{\omega}_2 + B_{eq,2} \omega_2 + T_c = T_m \cdot \eta$

2a) Por analogia:

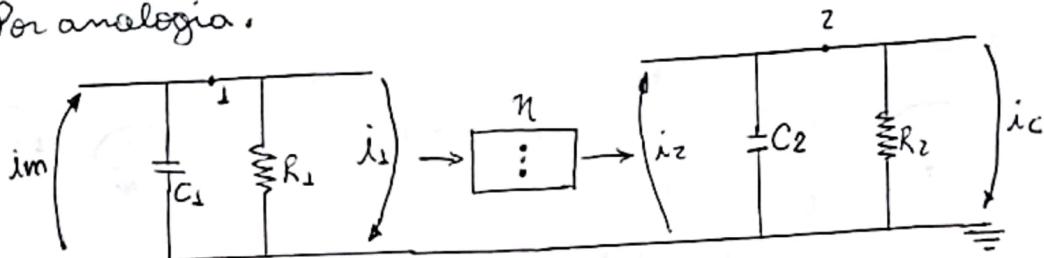

Nó 1: $(C_1 D + \frac{1}{R_1}) V_1 = i_m \cdot i_1$; Nó 2: $(C_2 D + \frac{1}{R_2}) V_2 = i_2 - i_c$

$J_1 \dot{\omega}_1 + B_1 \omega_1 = T_m - T_1$
 $J_2 \dot{\omega}_2 + B_2 \omega_2 = T_2 - T_c$

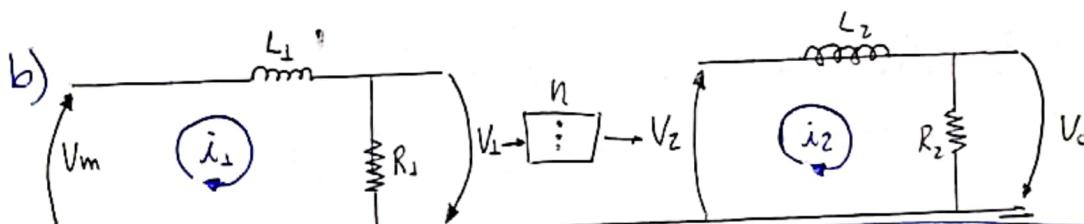


Malha 1: $L_1 D i_1 + R_1 i_1 = V_m - V_1$

Malha 2: $L_2 D i_2 + R_2 i_2 = V_2 - V_c$


$J_1 \dot{\omega}_1 + B_1 \omega_1 = T_m - T_1$
 ~~$J_2 \dot{\omega}_2 + B_2 \omega_2 = T_2 - T_c$~~

3)

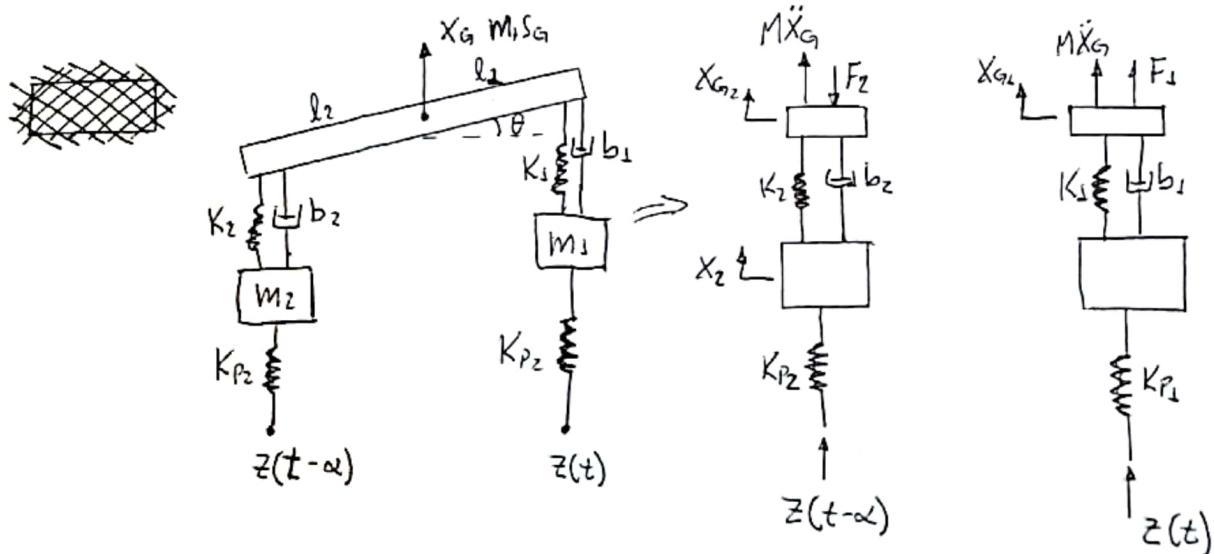


$$\eta = \frac{l_2}{l_1} \quad F_2 l_2 = F_1 l_1 \rightarrow \eta = \frac{F_1}{F_2}$$

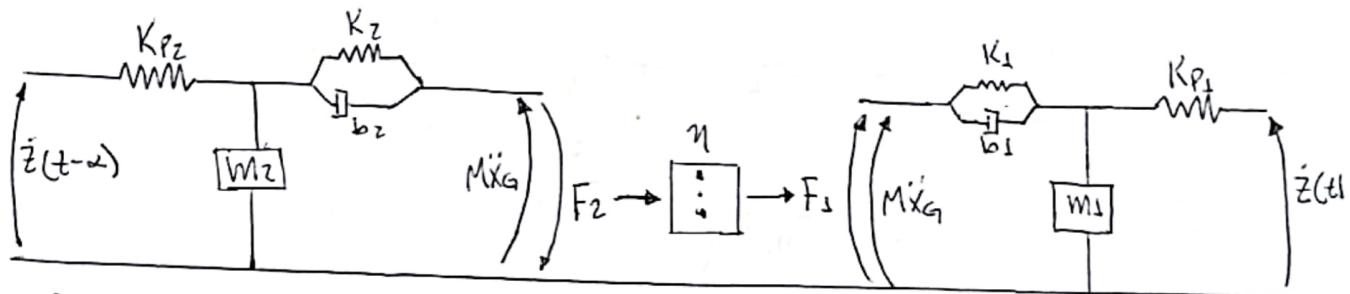• Por hipótese: $\theta \approx 0^\circ \therefore \sin \theta \approx \theta$; $\cos \theta = 1$



Analogia

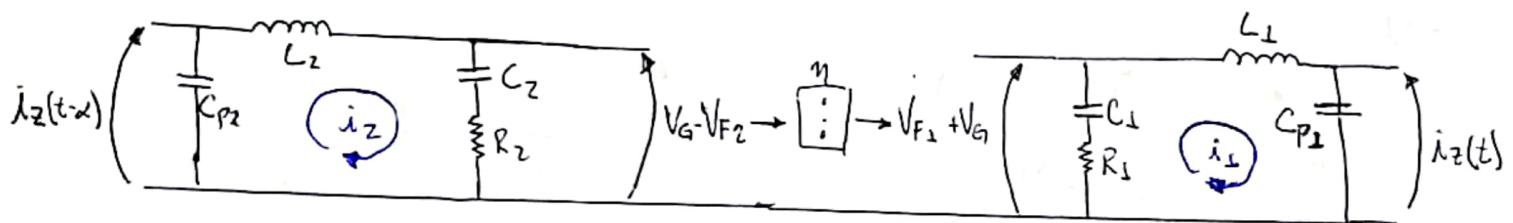

$$\text{Malha 1: } i_1 \left(L_1 D + R_1 + \frac{1}{C_1 D} + \frac{1}{C_{p1} D} \right) - i_2(t) \left(\frac{1}{C_{p1} D} \right) = V_{F1} - V_G$$

$$\text{Malha 2: } i_2 \left(L_2 D + R_2 + \frac{1}{C_2 D} + \frac{1}{C_{p2} D} \right) - i_2(t-\omega) \left(\frac{1}{C_{p2} D} \right) = V_G - V_{F2}$$

$$\boxed{\begin{aligned} M_1 \ddot{x}_1 + b_1 \dot{x}_1 + K_1 x_1 + K_{p1} x_1 - K_{p1} z(t) &= F_1 + M \ddot{x}_G \\ M_2 \ddot{x}_2 + b_2 \dot{x}_2 + K_2 x_2 + K_{p2} x_2 - K_{p2} z(t-\omega) &= -F_2 + M \ddot{x}_G \end{aligned}}$$