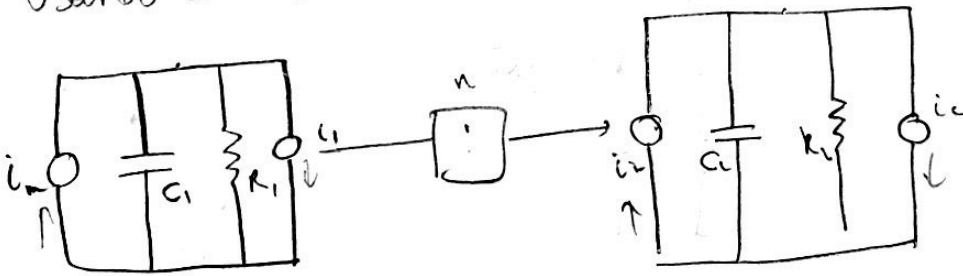


Usando analogia tipo 2:



nó 1: $(v_1 - 0)(C_1 D + \frac{1}{R_1}) = i_m - i_1$; nó 2: $(v_1 - 0)(C_1 D + \frac{1}{R_1}) = i_1 - i_c$

transformador: $i_2 = n i_1$


Usando a analogia tipo 2:

nó 1: $J_1 \ddot{\theta}_1 + k_1 \theta_1 = T_m - T_1$; nó 2: $J_2 \ddot{\theta}_2 + k_2 \theta_2 = T_c - T_e$

pel analogia (transformador) $\theta_2 = \frac{1}{n} \theta_1$

Item b: Resolver por analogia tipo 1.

Por analogia 1, o sistema elétrico fica

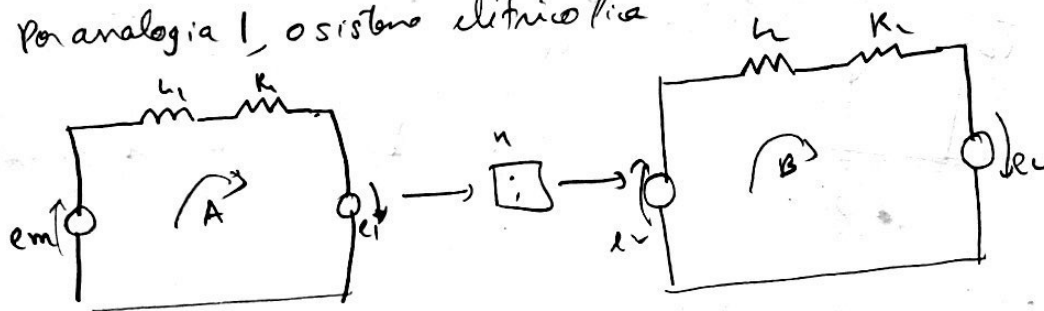

Circ. A:

$e_m(t) - L_1 D i_1 - R_1 i_1 - e_1(t) = 0$

Circ. B:

$e_2 - L_2 D i_2 - R_2 i_2 - e_1 = 0$

transformador $e_2 = n e_1$




Por analogia:

Ⓐ $T_m - J_1 \ddot{\theta}_1 - b_1 \dot{\theta}_1 - T_1 = 0 \Rightarrow J_1 \ddot{\theta}_1 + b_1 \dot{\theta}_1 = T_m - T_1$



Transf. $T_L = n T_1$

Ⓑ $T_L - J_2 \ddot{\theta}_L - b_2 \dot{\theta}_L - T_c = 0 \Rightarrow J_2 \ddot{\theta}_L + b_2 \dot{\theta}_L = T_L - T_c$

Exercício 2 - separar em 2 sistemas

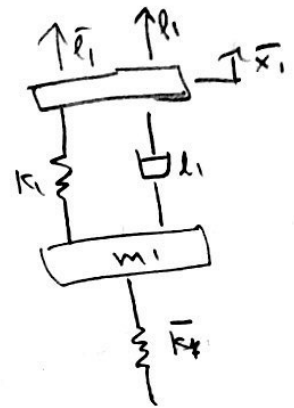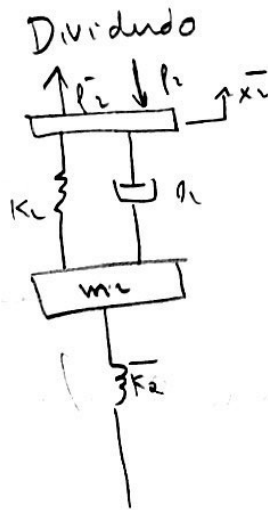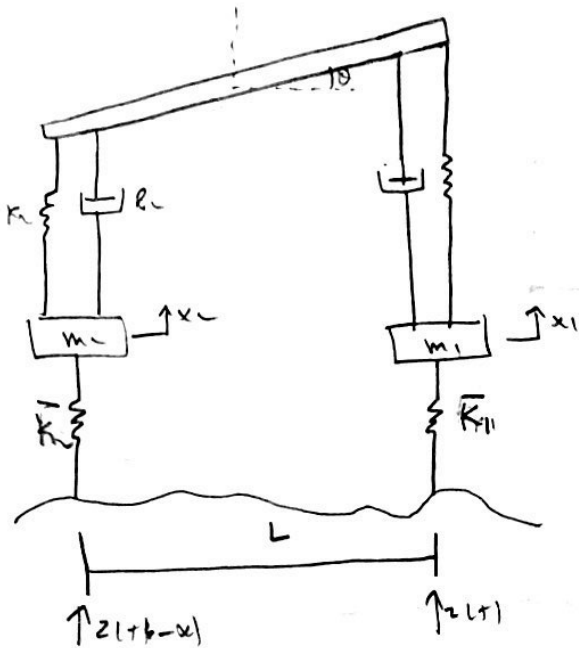

Por analogia h102; lianes can:

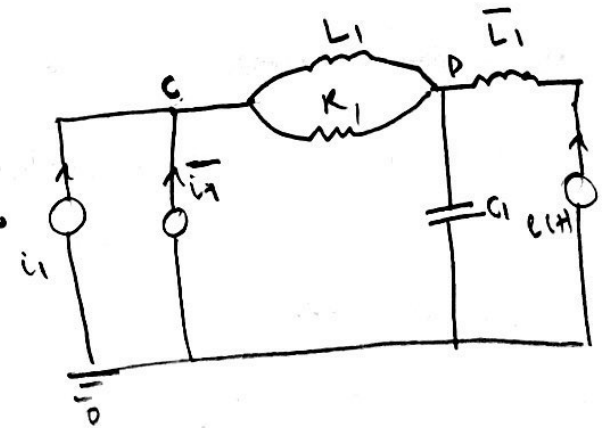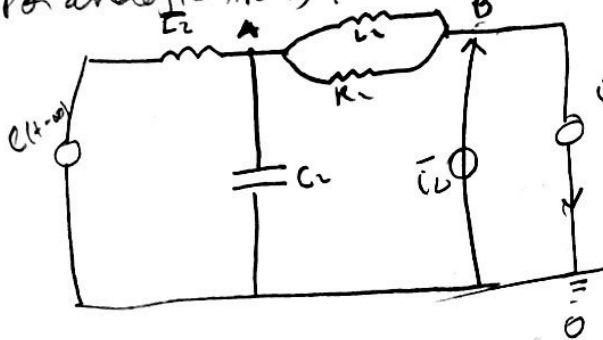

Nó A:

$$(V_A - 0)(C_2 D) + (V_A - e(t-x)) \left(\frac{1}{L_2 D} \right) + (V_A - V_B) \left(\frac{1}{L_1 D} + \frac{1}{R_1} \right) = 0$$

Nó D:

$$(V_D - 0)(C_1 D) + (V_D - e(t)) \left(\frac{1}{L_1 D} \right) + (V_D - V_C) \left(\frac{1}{L_1 D} + \frac{1}{R_1} \right) = 0$$

Nó B:

$$V_B \left(\frac{1}{L_1 D} + \frac{1}{R_1 D} \right) = \bar{i}_2 - i_2$$

Nó C:

$$V_C \left(\frac{1}{L_1 D} + \frac{1}{R_1} \right) = i_1 + \bar{i}_1$$

Ficamos com

no A:

$$V_A \left(C_2 D + \frac{1}{L_2 D} + \frac{1}{R_2} + \frac{1}{L_2 D} \right) - e(+x) \frac{1}{L_2 D} = \bar{u}_2 - \dot{u}_2$$

no D

$$V_D \left(C_1 D + \frac{1}{L_1 D} + \frac{1}{R_1} + \frac{1}{L_1 D} \right) - e(+x) \frac{1}{L_1 D} = \dot{u}_1 + \bar{u}_1$$

Isso gera:

$$\begin{cases} m_1 \ddot{x}_1 + b_1 \dot{x}_1 + (k_1 + \bar{k}_1) x_1 - \bar{k}_1 z(+x) = f_1 + \bar{f}_1 \\ m_2 \ddot{x}_2 + b_2 \dot{x}_2 + (k_2 + \bar{k}_2) x_2 - \bar{k}_2 z(+x) = -f_2 + \bar{f}_2 \end{cases}$$

temos que

$$f_1 = b_1 (k_1 \dot{x}_1 + b_1 \dot{x}_1) ; f_2 = b_2 (k_2 \dot{x}_2 + b_2 \dot{x}_2)$$

$$\bar{f}_1 = (x_G - x_1) k_1 + b_1 (x_G - \dot{x}_1) \quad \bar{f}_2 = (x_G - x_2) k_2 + b_2 (x_G - \dot{x}_2)$$