

Francisco Samuel Amâncio Lima  
10771584

①

Sem perdas na transmissão  $\Rightarrow T_2 = T_1 \cdot \frac{\omega_1}{\omega_2} = n T_1$  (I)

e sabendo que:


$$\left. \begin{array}{l} J_1 \cdot \dot{\omega}_1 + B_1 \cdot \omega_1 + T_1 = T_m \quad \text{(II)} \\ J_2 \cdot \dot{\omega}_2 + B_2 \cdot \omega_2 + T_c = T_2 \quad \text{(III)} \end{array} \right\}$$

Juntando as três equações:

$$J_2 \cdot \dot{\omega}_2 + B_2 \cdot \omega_2 + T_c = T_m \cdot n - (J_1 \cdot \dot{\omega}_2 n^2 + B_1 \cdot \omega_2 n^2)$$

$$(J_2 + J_1 \cdot n^2) \dot{\omega}_2 + (B_2 + n^2 B_1) \omega_2 + T_c = n T_m$$


A) Analogia tipo ②

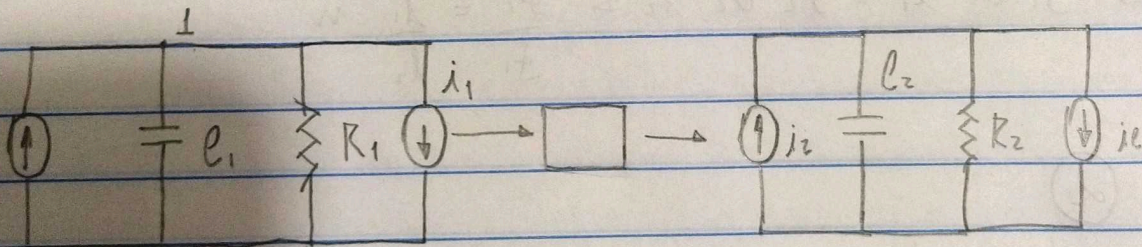

$$\text{nó 1: } i_n - V_1 \left( C_1 D + \frac{1}{R_1} \right) = i_1 \Rightarrow J_1 \cdot \ddot{\theta}_1 + B_1 \cdot \dot{\theta}_1 = T_m - T_1$$

$$\text{nó 2: } i_2 - V_2 \left( C_2 D + \frac{1}{R_2} \right) = i_e \Rightarrow T_2 = J_2 \ddot{\theta}_2 + B_2 \cdot \dot{\theta}_2 + T_c$$

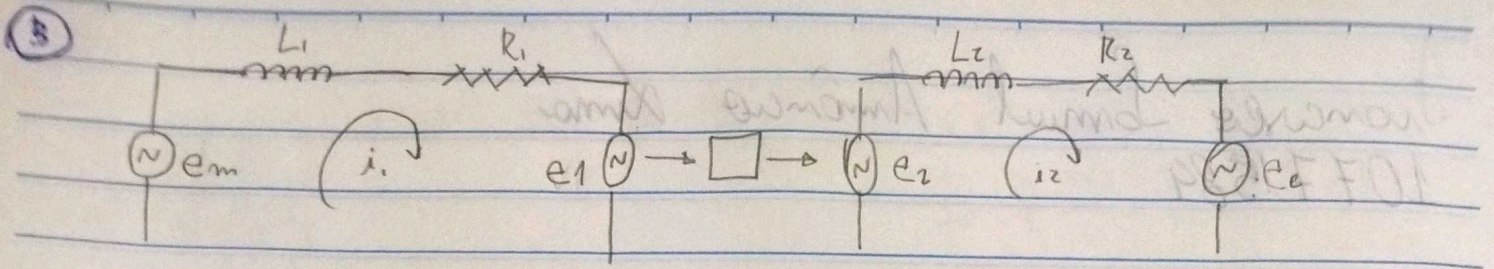
$$\text{transformador: } V_1 \cdot i_1 = V_2 \cdot i_2 \Rightarrow \frac{\dot{\theta}_1}{\dot{\theta}_2} = n$$



malha  $i_1$ :  $e_m = e_1 + i_1(L_1 D + R_1) = 0 \Rightarrow J_1 \cdot \ddot{\theta}_1 + B_1 \cdot \dot{\theta}_1 = T_m - T_1$

malha  $i_2$ :  $e_c = e_2 + i_2(L_2 D + R_2) = 0 \Rightarrow J_2 \cdot \ddot{\theta}_2 + R_2 \cdot \dot{\theta}_2 = T_2 - T_c$

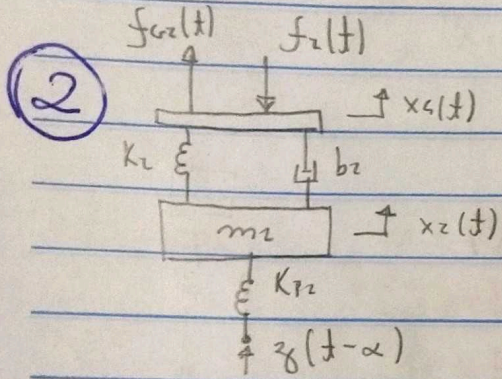transform.:  $e_1 i_1 = e_2 i_2 \Rightarrow \dot{\theta}_1 = n \dot{\theta}_2$



$$f_1 = h_1(k_1 \theta + b_1 \dot{\theta})$$

$$f_2 = h_2(k_2 \theta + b_2 \dot{\theta})$$


$$q_1 = b_1(\dot{x}_G - \dot{x}_1) + k_1(x_G - x_1)$$

$$q_2 = b_2(\dot{x}_G - \dot{x}_2) + k_2(x_G - x_2)$$

Com  $P = F \cdot v$

e  $P_1 = P_2 \Rightarrow f_1 \cdot \dot{\theta}_1 \cdot l_1 = f_2 \cdot \dot{\theta}_2 \cdot l_2 \Rightarrow \frac{f_2}{f_1} = \frac{l_1}{l_2} = n$

Analogia tipo 2

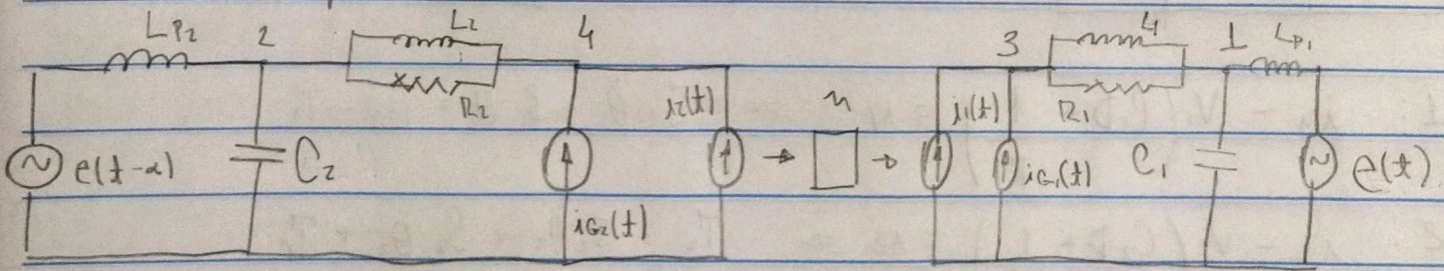

no 1:  $V_1 \left( C_2 D + \frac{1}{R_1} + \frac{1}{L_2 D} + \frac{1}{L_1 D} \right) - V_3 \left( \frac{1}{R_1} + \frac{1}{L_1 D} \right) = e(t) \frac{1}{L_1 D}$

no 2:  $V_2 \left( C_2 D + \frac{1}{R_2} + \frac{1}{L_2 D} + \frac{1}{L_1 D} \right) - e(t - \alpha) \frac{1}{L_2 D} - V_4 \left( \frac{1}{L_2 D} + \frac{1}{R_2} \right) = 0$

no 3:  $i_1(t) + i_{g_1}(t) = V_3 \left( \frac{1}{R_1} + \frac{1}{L_2 D} \right)$

no 4:

$$x_2(t) + V_1 \left( \frac{1}{k_2} + \frac{1}{L_2 D} \right) = i c_2(t)$$

Da eq. 2 um 4:

Da eq. 3 um 1:

$$\left\{ \begin{array}{l} m_2 \ddot{x}_2 + b_2 \dot{x}_2 + (k_2 + k_{2p}) x_2 = k_{2p} z(t) - f_2(t) + f_{02}(t) \\ m_1 \ddot{x}_1 + b_1 \dot{x}_1 + (k_1 + k_{1p}) x_1 = k_{1p} z(t) + f_1(t) + f_{01}(t) \end{array} \right.$$