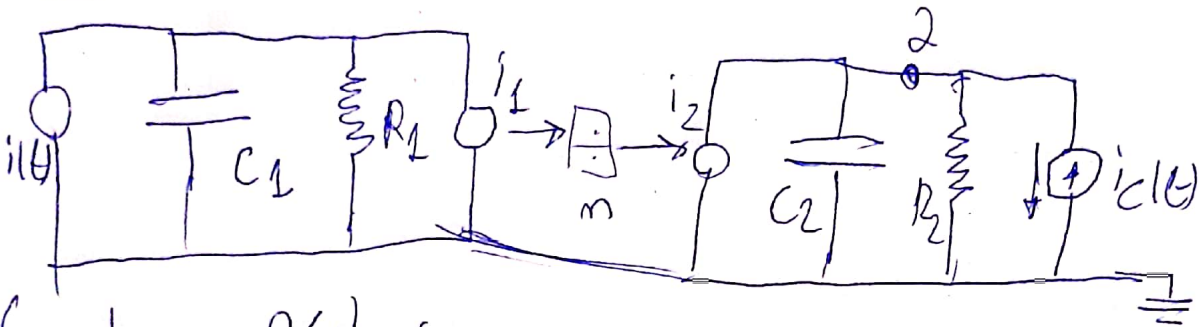


Nome: Paulo Mateus Corrêa Vianna

Nusp: 10772741

① Realizando a analogia tipo 2:
 (a)



Sistema elétrico:

$$\text{Nó 1: } V_1 \left(C_1 D + \frac{1}{R_1} \right) = i_m - i_1 \quad i_2 = m i_1 \rightarrow V_2 = \frac{V_1}{m}$$

$$\text{Nó 2: } V_2 \left(C_2 D + \frac{1}{R_2} \right) = i_2 - i_c$$


Sistema mecânico:

$$\text{Nó 1: } u_1 (J_1 D + B_1) = T_m - T_2 \rightarrow J_1 \ddot{\theta}_1 + B_1 \dot{\theta}_1 = T_m - T_2$$

$$\text{Nó 2: } u_2 (J_2 D + B_2) = T_2 - T_c \rightarrow J_2 \ddot{\theta}_2 + B_2 \dot{\theta}_2 = T_2 - T_c$$

$$T_2 = m T_1 \rightarrow \theta_2 = \frac{\theta_1}{m}$$

② Realizando analogia tipo 1:

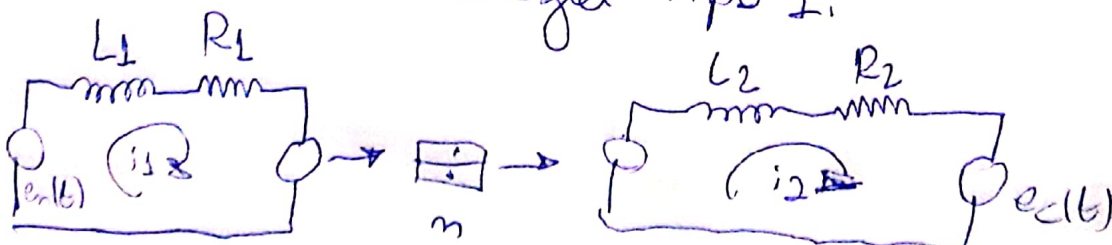

Malha 1: $(L_1 D + R_1) i_1 = e_m - e_1$

Malha 2: $(L_2 D + R_2) i_2 = e_2 - e_c$

Circuito elétrico

$e_2 = m e_1$

$T_2 = m T_1$
Malha 1: $(S_1 D + B_1) \omega_1 = t_m - T_1$

Sistema Mecânico

Malha 2: $(S_2 D + B_2) \omega_2 = T_2 - T_c$

$\rightarrow S_1 \ddot{\theta}_1 + B_1 \dot{\theta}_1 = t_m - T_1$


$S_2 \ddot{\theta}_2 + B_2 \dot{\theta}_2 = T_2 - T_c$

$\theta_2 = \frac{\theta_1}{n}$

Nó 3: $V_3 \left(\frac{1}{R_1} + \frac{1}{L_1 D} \right) = i_1(t) + i_{g3}(t)$

Nó 4: $V_4 \left(\frac{1}{R_2} + \frac{1}{L_2 D} \right) = i_2(t) + i_{g4}(t)$

② Analogia do tipo 2

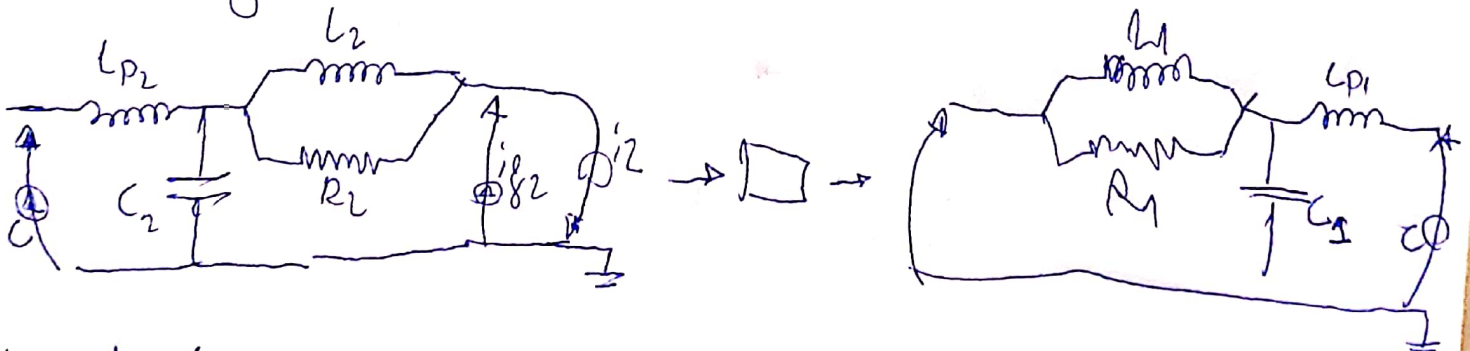

Nó 1: $V_1 \left(C_2 D + \frac{1}{R_1} + \frac{1}{L_1 D} + \frac{1}{L_{p2} D} \right) - e(t) - \frac{1}{L_{p2} D} - V_3 \left(\frac{1}{R_1} + \frac{1}{L_1 D} \right) = 0$

Nó 2: $V_2 \left(C_2 D + \frac{1}{R_2} + \frac{1}{L_2 D} + \frac{1}{L_{p2} D} \right) - e(t) \frac{1}{L_{p2} D} - V_4 \left(\frac{1}{R_2} + \frac{1}{L_2 D} \right) = 0$

Após reorganizar, obtenhas as expressões:

$$\begin{cases} m_1 \ddot{x}_1 + b_1 \dot{x}_1 + (k_1 + k_{1p}) x_1 = k_{1p} z(t) + F_1(t) + F_{gm}(t) \\ m_2 \ddot{x}_2 + b_2 \dot{x}_2 + (k_2 + k_{2p}) x_2 = k_{2p} z(t - \omega) - F_2(t) + F_{g2}(t) \end{cases}$$

$$\begin{aligned} \textcircled{3} \quad \begin{cases} \zeta_1 \omega_1 + B_1 \omega_1 + T_1 = T_m & T_e = m T_1 \quad \omega_1 = m \omega_2 \\ \zeta_2 \omega_2 + B_2 \omega_2 + T_c = T_e & T_1 = T_m - \zeta_1 \omega_1 - B_1 \omega_1 \end{cases} \end{aligned}$$

$$\zeta_2 \omega_2 + B_2 \omega_2 + T_c = m (T_m - \zeta_1 \omega_1 - B_1 \omega_1)$$

$$\zeta_2 \omega_2 + B_2 \omega_2 + T_c = m (T_m - \zeta_1 m \omega_2 - B_1 m \omega_2)$$

$$(\zeta_2 + m \zeta_1) \omega_2 + (B_2 + m^2 B_1) \omega_2 + T_c = m T_m$$

$$\boxed{\zeta_{eq} \omega_2 + B_{eq} \omega_2 + T_c = m T_m}$$