

$$3) I_S \cdot R_S + V_Z = V_{in} \quad I_{out} \cdot R_L + I_S \cdot R_S = V_{in} \quad \text{no limit, } I_Z = 0$$

$$I_S (R_L + R_S) = V_{in} \quad I_{out} = I_S$$

$$I_S R_S + V_Z = I_S (R_L + R_S)$$

$$\frac{V_Z}{R_L} = I_S \rightarrow I_S = 8 \text{ mA}$$

$$\rightarrow V_{in} = I_S R_S + V_Z$$

$$| V_{in} = 14,64 \text{ V} |$$

$$4) V_{out} = V_Z + "XX" = V_{Z_{ENERG}} + r_Z I_Z + "XX" \quad R = \frac{V_{out} - V_Z}{I_Z} = \frac{7,1 - 2,1}{1}$$


$$V_{out} = 7 + 0,1$$

$$| V_{out} = 7,1 \text{ V} |$$

$$| R = 5 \text{ k}\Omega |$$

↳ Error!

Ex 22/09 - Henrique Kuhlmann 10772672

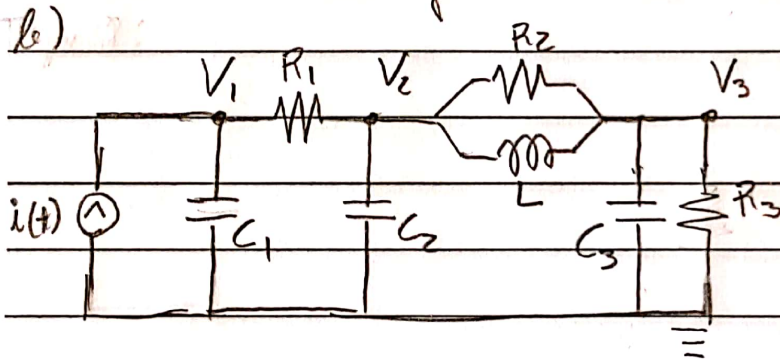

$$V \sim \rho g h \quad l \sim a$$

$$I \sim i' = \frac{l}{\rho L}$$

$$R \sim \frac{\rho g l}{A}$$

$$C \sim \frac{A}{\rho g}$$

$$c) 1) V_1 (C_1 D + 1/R_1) - V_2/R_1 = i_1(t)$$

$$2) V_2 (C_2 D + 1/R_1 + 1/R_2 + 1/L D) - V_1/R_1 - V_3 (1/R_2 + 1/L D) = 0$$

$$3) V_3 (C_3 D + 1/R_3 + 1/R_2 + 1/L D) - V_2 (1/R_2 + 1/L D) = 0$$

$$1) A_1 \dot{h}_1 + h_1/R_1 - h_2/R_1 = Q_i(t)$$

$$2) A_2 \dot{h}_2 + h_2 (1/R_1 + 1/R_2) + \frac{g a}{l} \int h_2 dt - h_1/R_1 - h_3/R_3 - \frac{g a}{l} \int h_3 dt = 0$$

$$3) A_3 \dot{h}_3 + h_3 (1/R_2 + 1/R_3) + \frac{g a}{l} \int h_3 dt - h_2/R_2 - \frac{g a}{l} \int h_2 dt = 0$$

