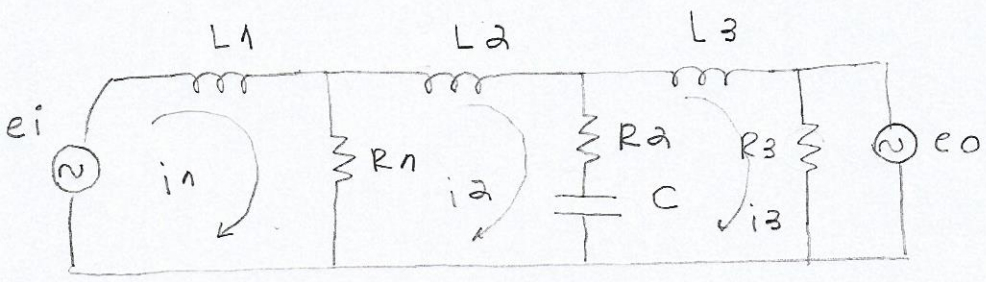


1) Circuito análogo do tipo 1:



Equacionamento:

malha 1:

$$e_i = L_1 D i_1 + R_1 (i_1 - i_2)$$

malha 2:

$$L_2 D i_2 + R_1 (i_2 - i_1) + R_2 (i_2 - i_3) + \frac{(i_2 - i_3)}{C D} = 0$$

malha 3:

$$L_3 D i_3 + R_2 (i_3 - i_2) + \boxed{R_3 (i_3)} + \frac{(i_3 - i_2)}{C D} = 0$$

Analogamente:

$$Q_i = C f_1 D h_1 + \frac{(h_1 - h_2)}{R_1}$$

$$C f_2 D h_2 + \frac{(h_2 - h_1)}{R_1} + \frac{(h_2 - h_3)}{R_2} + \frac{(h_2 - h_3)}{L f D} = 0$$

$$C f_3 D h_3 + \frac{(h_3 - h_2)}{R_2} + Q_o + \frac{(h_3 - h_2)}{L f D} = 0$$

onde:

$$C f_1 = \frac{A_1}{\rho g}$$


$$C f_2 = \frac{A_2}{\rho g}$$

$$C f_3 = \frac{A_3}{\rho g}$$

$$L f = \frac{\rho \cdot l}{a}$$



2) Analogia do tipo a

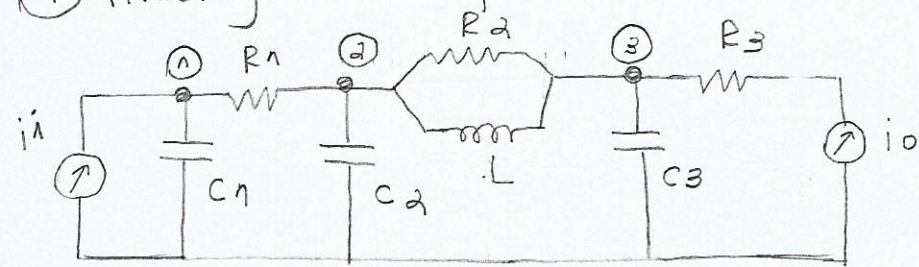

$$\underbrace{V_3/R_3 = i_o}_{h_3/R_3 = Q_0}$$

$$V_1 \left( C_1 D + \frac{1}{R_1} \right) - V_2 \left( \frac{1}{R_1} \right) = i$$

$$V_2 \left( C_2 D + \frac{1}{R_2} + \frac{1}{L D} \right) - V_3 \left( \frac{1}{R_2} + \frac{1}{L D} \right) = 0$$

$$V_3 \left( C_3 D + \frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{L D} \right) - V_2 \left( \frac{1}{R_2} + \frac{1}{L D} \right) = 0$$

analogamente:

$$h_1 \left( C_{f1} D + \frac{1}{R_1} \right) - h_2 \left( \frac{1}{R_1} \right) = Q$$

$$h_2 \left( C_{f2} D + \frac{1}{R_2} + \frac{1}{L_f D} \right) - h_3 \left( \frac{1}{R_2} + \frac{1}{L_f D} \right) = 0$$

$$h_3 \left( C_{f3} D + \frac{1}{R_2} + \frac{1}{L_f D} \right) - h_2 \left( \frac{1}{R_2} + \frac{1}{L_f D} \right) = -Q_0$$