

Desconhecemos as tensões em 1, 2, 3 e 4 - Método Prático

Nó 1: $V_1 (C_1 D + \frac{1}{R_1}) - V_2 \frac{1}{R_1} = i_1(t)$

Nó 2: $V_2 (C_2 D + \frac{1}{R_1} + \frac{1}{R_2}) - V_1 \frac{1}{R_1} - V_3 \frac{1}{R_2} = 0$

Nó 3: $V_3 (C_3 D + \frac{1}{R_2} + \frac{1}{R_3}) - V_2 \frac{1}{R_2} - V_4 \frac{1}{R_3} = 0$

Nó 4: $V_4 (C_4 D + \frac{1}{R_3} + \frac{1}{R_4}) - V_3 \frac{1}{R_3} = i_0(t)$

$P \rightarrow V ; Q \rightarrow i$



Aplicando analogia


① $\frac{A_1}{s} \frac{dp_1}{dt} + \frac{1}{s} p_1 - \frac{1}{s} p_2 = Q_1(t)$

② $\frac{A_2}{s} \frac{dp_2}{dt} + (\frac{1}{s} p_1 + \frac{1}{s} p_2) - \frac{p_1}{s} - \frac{p_4}{s} = 0$

④ $p_4 (\frac{1}{s}) + \frac{a}{s} \int p_4 dt - \frac{p_2}{s} - \frac{p_3}{s} = 0$

③ $\frac{A_3}{s} \frac{dp_3}{dt} + \frac{1}{s} p_3 + \frac{a}{s} \int p_3 dt - \frac{a}{s} \int p_4 dt = Q_3(t)$

Analogia tipo 1

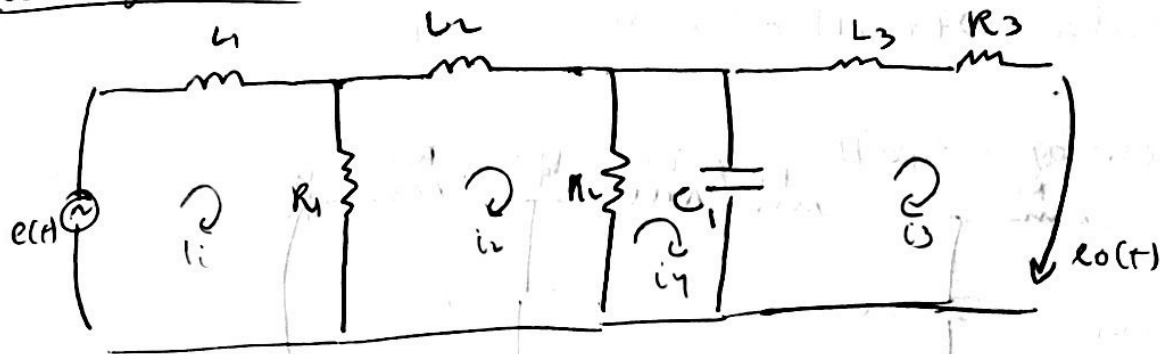

$$\text{malha 1: } e(t) - L_1 D i_1 - R_1 (i_1 - i_2) = 0 \rightarrow L_1 D i_1 + R_1 (i_1 - i_2) = e(t)$$

$$\text{malha 2: } -L_2 D i_2 - R_1 (i_2 - i_1) - R_2 (i_2 - i_3) = 0 \rightarrow L_2 D i_2 + R_1 (i_2 - i_1) + R_2 (i_2 - i_3)$$

$$\text{malha 3: } e_o(t) - (L_3 D + R_3) i_3 - \frac{1}{C_1 D} (i_3 - i_4) = 0 \rightarrow (L_3 D + R_3) i_3 + \frac{1}{C_1 D} (i_3 - i_4) = e_o(t)$$

$$\text{malha 4: } -R_2 (i_4 - i_2) - \frac{1}{C_1 D} (i_4 - i_3) = 0 \Rightarrow R_2 (i_4 - i_2) + \frac{1}{C_1 D} (i_4 - i_3) = 0$$

Para analogia tipo 1:

$$\textcircled{1} \frac{A_1}{s g} \frac{d p_1}{dt} + \frac{1}{s g R_1} p_1 - \frac{1}{s g R_1} p_2 = q(t)$$

$$\textcircled{2} \frac{A_2}{s g} \frac{d p_2}{dt} + \frac{1}{s g R_1} (p_2 - p_1) + \frac{1}{s g R_2} (p_2 - p_4) = 0$$

$$\textcircled{3} \frac{A_3}{s g} \frac{d p_3}{dt} + \frac{1}{s g R_3} p_3 + \frac{a}{s l} \int p_3 dt - \frac{a}{s l} \int p_4 dt = q_o(t)$$

$$\textcircled{4} \frac{1}{s g R_2} (p_4 - p_2) + \frac{a}{s l} \left[\int p_4 dt - \int p_3 dt \right] = 0$$

As equações tanto no analogia como 1 são equivalentes !!!