

PSI3213 – CIRCUITOS ELÉTRICOS II

Solução da Lista 5: Potência e energia em Regime Permanente Senoidal

1 –	Cargas	P(kW)	Q(kVAr)	$ P_{ap} $ (kVA)	$\cos \psi$
	C1	8	6	10	0,8 atr.
	C2	12	-16	20	0,6 ad.
	C3	5	10	11,18	0,45 atr.
		<u>25</u>	<u>0</u>		

Carga 1: $P = |P_{ap}| \cos \psi \rightarrow |P_{ap}| = 10 \text{ kVA}$
 $Q = |P_{ap}| \sin \psi \rightarrow Q = 6 \text{ kVAr} \quad (> 0 \text{ ind.})$

Carga 2: $P = |P_{ap}| \cos \psi = 12 \text{ kW}$
 $Q = |P_{ap}| \sin \psi = -16 \text{ kVAr}$

Carga 3: $Y = \frac{1}{Z} = \frac{1}{2,5 + j5} = 0,08 - j0,16$

$$P_{ap} = G |V|^2 - j B |V|^2 = 5 + j10$$

$$P_{ap} \text{ total} = (25 + j0) \text{ kVA}$$

$$|P_{ap}| = |V| |I_L| \rightarrow |I_L| = 25000/250 = 100 \text{ Aef}$$

Como $Q_t = 0 \rightarrow \hat{I}_L = 100 \angle 0^\circ$

$$\hat{V}_p = 100(0,05 + j0,5) = 5 + j50$$

$$\hat{V}_s = \hat{V}_p + 250 \angle 0^\circ = 255 + j50 = 259,86 \angle 11,09^\circ$$


$$v_s(t) = 367,49 \cos(377t + 11,09^\circ) \text{ (V,s)}$$

Potência real nas cargas:

$$\begin{aligned} P_1 &= 8 \text{ kW} \\ P_2 &= 12 \text{ kW} \\ P_3 &= 5 \text{ kW} \end{aligned}$$

Potência real na linha: $0,05 \cdot |I_L|^2 = 0,5 \text{ kW}$

2 –

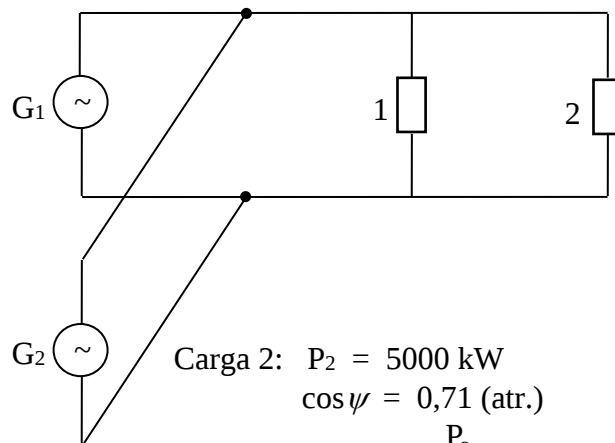

Carga 1: $P_1 = 3000 \text{ kW}$
 $\cos \psi = 1$
 $Q_1 = 0$

Carga 2: $P_2 = 5000 \text{ kW}$
 $\cos \psi = 0,71 \text{ (atr.)}$
 $Q_2 = \frac{P_2}{\cos \psi} \sin \psi = 4959,2 \text{ kVAr}$

Gerador $G_1 \rightarrow P_{G1} = 5000 \text{ kW}$
 $\cos \psi = 0,8 \text{ (atr.)}$
 (convenção de gerador)

$$Q_{G1} = \frac{P_{G1}}{0,8} \sin \psi = 3750 \text{ kVAr}$$

Teorema da conservação das potências:

$$\begin{aligned} P_1 + P_2 &= P_{G1} + P_{G2} \rightarrow P_{G2} = 3000 \text{ kW} \\ \underbrace{Q_1 + Q_2}_{\text{conv. receptor}} &= \underbrace{Q_{G1} + Q_{G2}}_{\text{conv. gerador}} \rightarrow Q_{G2} = 1209,2 \text{ kVAr} \end{aligned}$$

$$\tan \psi_2 = \frac{1209,2}{3000} = \frac{Q_{G2}}{P_{G2}} = 0,40$$

$$\cos \psi_2 = 0,93 \text{ (atr.)} \leftarrow \text{conv. gerador !}$$

3 – a) $P_{\text{ap total}} = 300 + j100 = P_{\text{ap1}} + P_{\text{ap2}}$

$$|P_{\text{ap total}}| = \sqrt{(300)^2 + (100)^2} = 316,23 = |V| |I| \rightarrow |I| = 1,58 \text{ Aef}$$

$$P_{\text{total}} = R(\omega) |I|^2 \rightarrow R(\omega) = 300/(1,58)^2 = 120 \Omega$$

$$Q_{\text{total}} = X(\omega) |I|^2 \rightarrow X(\omega) = 100/(1,58)^2 = 40 \Omega \rightarrow Z = 120 + j40 \Omega$$

b) $P_1 = R_1 |I|^2 \rightarrow R_1 = 40 \Omega$
 $Q_1 = X_1 |I|^2 \rightarrow X_1 = 80 \Omega$
 $Z_1 = 40 + j80 \Omega$

$P_2 = R_2 |I|^2 \rightarrow R_2 = 80 \Omega$
 $Q_2 = X_2 |I|^2 \rightarrow X_2 = -40 \Omega$
 $Z_2 = 80 - j40 \Omega$

4 – Gerador de Thévenin equivalente:

Tensão em aberto: Divisor de tensão :

$$\hat{E}_0 = \frac{100 \angle 0^\circ \cdot j3}{25 + j10 + j3} = \frac{300 \angle 90^\circ}{28,18 \angle 27,5^\circ}$$

$$\hat{E}_0 = 10,65 \angle 62,5^\circ$$


$$\text{Impedância : } Z_0 = (25 + j10) // j3 = \frac{(25 + j10) j3}{25 + j13}$$

$$Z_0 = 2,87 \angle 84,3^\circ = 0,28 + j2,85 \Omega$$

Condição de máxima transferência de potência ativa à carga Z_L :

$$\text{a) } Z_L = Z_0^* = 0,28 - j2,85 \Omega$$

$$\text{b) } P_{\text{máx}} = \frac{|E_0|^2}{4R} = \frac{(10,65)^2}{4 \cdot 0,28} = 101,3 \text{ W}$$

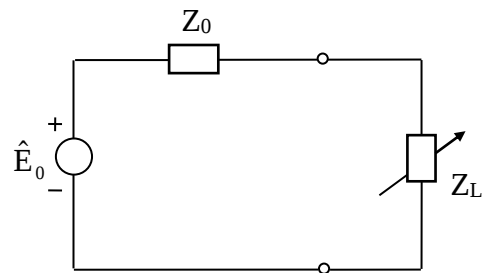

5 – a)	P (kW)	Q(kVAr)	$\cos \psi$	$ P_{\text{ap}} / (\text{kVA})$
A	5	0	1	5
B	5	6,67	0,6 atr.	8,33
C	3,72	5,58	0,55 atr.	6,71
	<u>13,72</u>	<u>12,25</u>		

$$\text{Carga C: } Y = \frac{1}{4 + j6} = 0,0769 - j0,1154 \text{ S}$$

$$P_{\text{ap}} = 0,0769 |V|^2 + 0,1154 |V|^2 = 3,72 + j5,58 \text{ kVA}$$

$$P_{\text{ap total}} = 13,72 + j12,25 \text{ kVA}$$

$$P_{\text{total}} = 13,72 \text{ kW} \quad Q_{\text{total}} = 12,25 \text{ kVAr}$$

$$\text{b) } \hat{I}_A = \frac{5000}{110} \angle 0^\circ = 45,45 \angle 0^\circ \text{ Aef}$$


$$\hat{I}_B = \frac{8333}{110} \angle -53,13^\circ = 75,75 \angle -53,13^\circ \text{ Aef}$$

$$\hat{I}_C = \frac{220 \angle 0^\circ}{4 + j6} = 30,51 \angle -56,31^\circ \text{ Aef}$$

$$\hat{I}_a = \hat{I}_A + \hat{I}_C = 67,34 \angle -22,15^\circ \text{ Aef}$$

$$\hat{I}_b = -(\hat{I}_B + \hat{I}_C) = 106,23 \angle 125,96^\circ \text{ Aef}$$
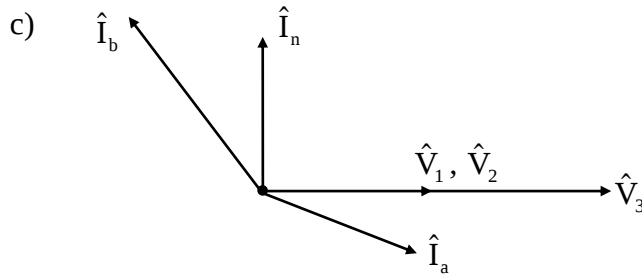
$$\hat{I}_n = \hat{I}_A - \hat{I}_B = 60,6 \angle 90^\circ \text{ Aef}$$



6 –


Cargas	P (kW)	Q (kVAr)	cos ϕ	$ P_{ap} $ (kVA)
i	250	0	1	250
ii	1500	726,48	0,9 at.	1666,67
iii	1000	750	0,8 at.	1250
iv	700	-339,02	0,9 ad.	777,78

$$\Sigma P = 3450 \text{ kW}$$

$$\Sigma Q = 1137,45 \text{ kVAr}$$

a) $P_{ap t} = 3450 + j 1137,45 \text{ kVA}$

$$\cos \phi_t = \frac{P_t}{|P_{ap t}|} = \frac{3450}{3632,67} = 0,95 \text{ atrasado}$$

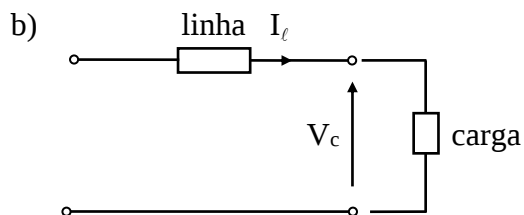


Mesmo aquecimento $\rightarrow$ mesma $|I_\ell|$

$$P_t = V_c I_\ell \cos \phi_t = 3450 \text{ kW}$$

Para $\cos \phi_t' = 1$, mantendo fixos V_c e $I_\ell \rightarrow$

$$\rightarrow P_t' = V_c I_\ell = \frac{3450}{0,95} = 3632,67 \text{ kW}$$

7 – Por análise de malhas:

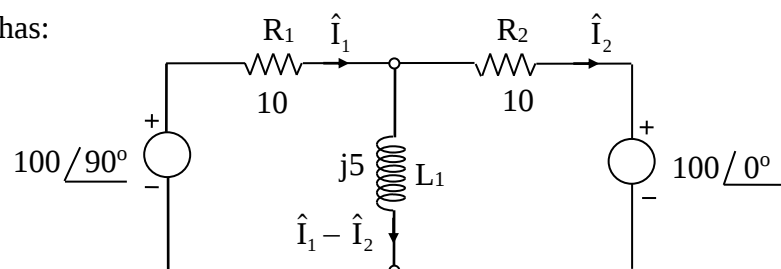

2ª LK :

$$10 \hat{I}_1 + j5 (\hat{I}_1 - \hat{I}_2) = 100 \angle 90^\circ$$

$$j5(\hat{I}_1 - \hat{I}_2) - 10\hat{I}_2 = 100\angle 0^\circ \quad \text{que fornece o sistema:}$$

$$\begin{bmatrix} 10 + j5 & -j5 \\ j5 & -10 - j5 \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \end{bmatrix} = \begin{bmatrix} 100\angle 90^\circ \\ 100 \end{bmatrix}$$

Resolvendo :

$$\hat{I}_1 = 5\angle 90^\circ \text{ Aef} \quad \hat{I}_2 = 11,18\angle -206,56^\circ \text{ Aef}$$

$$P_{ap\ g1} = 100\angle 90^\circ \cdot \hat{I}_1^* = 500 + j0 \text{ VA fornecida}$$

$$P_{ap\ g2} = 100\angle 0^\circ \cdot (-\hat{I}_2^*) = 1000 + j500 \text{ VA fornecida}$$

$$P_{R1} = R_1 \cdot |\hat{I}_1|^2 = 10 \cdot 25 = 250 \text{ W}$$


$$P_{R2} = R_2 \cdot |\hat{I}_2|^2 = 10 \cdot (11,18)^2 = 1250 \text{ W}$$

$$Q_{L1} = 5 \cdot (|\hat{I}_1 - \hat{I}_2|)^2 = 500 \text{ Var}$$

$$\text{Portanto: } P_{g1} + P_{g2} = P_{R1} + P_{R2} = 1500 \text{ W}$$

$$Q_{g1} + Q_{g2} = Q_{L1} = 500 \text{ Var}$$

8 –

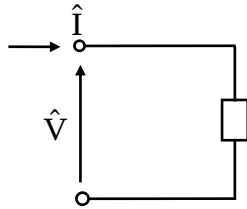

$$\text{a) Sabe-se que: } P_{ap} = \hat{V} \cdot \hat{I}^* = P + jQ \rightarrow$$

$$\rightarrow \hat{I}^* = \frac{P + jQ}{\hat{V}}$$

$$\rightarrow \hat{I} = \frac{P - jQ}{\hat{V}^*} = \frac{P}{\hat{V}^*} - j \frac{Q}{\hat{V}^*}$$

(aplicando-se propriedades dos números complexos)

$$\text{b) } \hat{I}_a = \hat{I}_1 + \hat{I}_2 \quad \text{Carga 1: } P = 12 \text{ kW} \quad \hat{V} = \hat{E}_1 = 127\angle 0^\circ$$

$$Q = \sqrt{P_{ap}^2 - P^2} = 21.931,71 \text{ Var}$$

$$\rightarrow \hat{I}_1 = \frac{12.000}{127} - \frac{j 21.931,71}{127} \quad (\text{item a})$$

$$\hat{I}_1 = 196,85\angle -61,31^\circ \text{ Aef}$$

$$\text{Carga 2: } Q = -12.000 \text{ kVar} \quad P = \sqrt{P_{ap}^2 - Q^2} = 48.538,64 \text{ W}$$

$$\hat{V} = \hat{E}_1 + \hat{E}_2 = 127\angle 60^\circ \text{ Vef}$$

$$\hat{I}_2 = \frac{48.538,64}{127\angle -60^\circ} + \frac{j 12.000}{127\angle -60^\circ} = 393,69\angle 73,89^\circ \text{ Aef}$$

$$\hat{I}_a = \hat{I}_1 + \hat{I}_2 = 289,41\angle 45,25^\circ \text{ Aef}$$

$$\begin{aligned}
 \text{c) } P_{\text{ap g1}} &= 25,88 - j 26,10 \text{ kVA} \\
 \text{Carga 1} &\longrightarrow P_1 = 12 \text{ kW} & Q_1 &= 21,93 \text{ kVAr} \\
 \text{Carga 1'} &\longrightarrow P_{1'} = 12 \text{ kW} & Q_{1'} &= 21,93 \text{ kVAr} \\
 \\
 \text{Carga 2} &\longrightarrow P_2 = 48,54 \text{ kW} & Q_2 &= -12 \text{ kVAr}
 \end{aligned}$$

Pela conservação das potências:

$$\begin{aligned}
 P_{\text{g2}} &= P_1 + P_{1'} + P_2 - 25,88 = 46,66 \text{ kW} \\
 Q_{\text{g2}} &= Q_1 + Q_{1'} + Q_2 + 26,10 = 57,96 \text{ kVAr}
 \end{aligned}$$

Portanto:

$$P_{\text{ap g2}} = 46,66 + j 57,96 \text{ kVA} \text{ fornecida.}$$