

Figure 9-1

Basic structure of a  $2^n \times b$  ROM.

<i>Inputs</i>			<i>Outputs</i>			
<i>A2</i>	<i>A1</i>	<i>A0</i>	<i>D3</i>	<i>D2</i>	<i>D1</i>	<i>D0</i>
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Table 9-1

Truth table for a 3-input, 4-output combinational logic function.

 


Figure 9-2

A 2-to-4 decoder with output-polarity control.

 


Figure 9-3

Connections to build the 2-to-4 decoder using an  $8 \times 4$  ROM that stores Table 9-1.

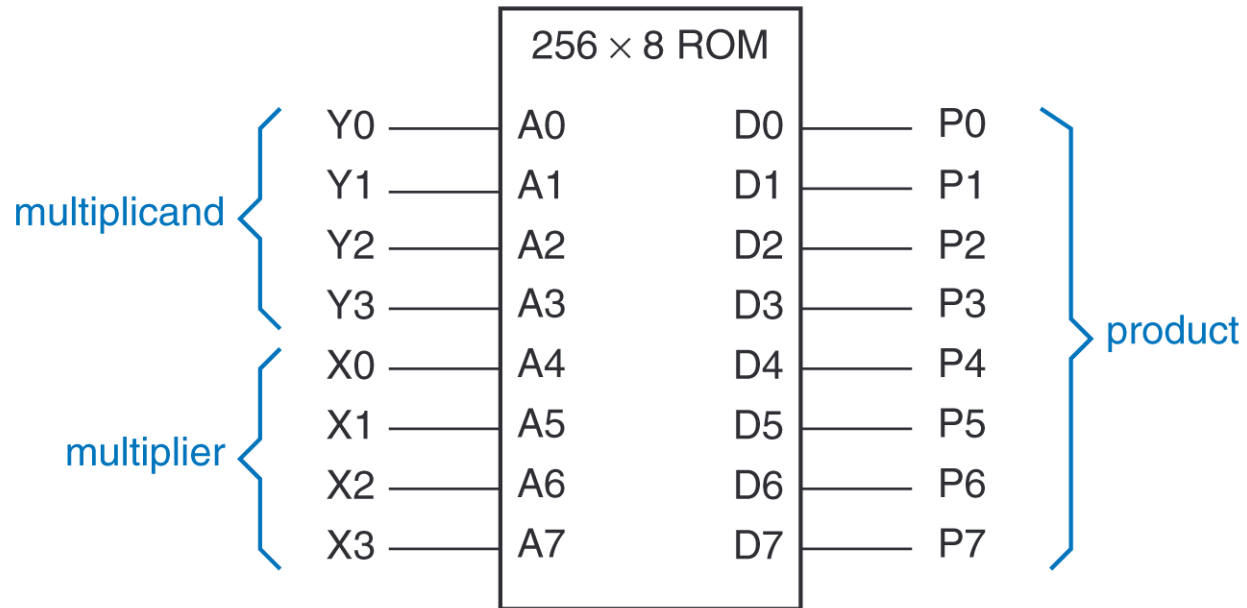


Figure 9-4

Connections to perform a  $4 \times 4$  unsigned binary multiplication using a  $256 \times 8$  ROM.

---

```
00: 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
10: 00 01 02 03 04 05 06 07 08 09 0A 0B 0C 0D 0E 0F
20: 00 02 04 06 08 0A 0C 0E 10 12 14 16 18 1A 1C 1E
30: 00 03 06 09 0C 0F 12 15 18 1B 1E 21 24 27 2A 2D
40: 00 04 08 0C 10 14 18 1C 20 24 28 2C 30 34 38 3C
50: 00 05 0A 0F 14 19 1E 23 28 2D 32 37 3C 41 46 4B
60: 00 06 0C 12 18 1E 24 2A 30 36 3C 42 48 4E 54 5A
70: 00 07 0E 15 1C 23 2A 31 38 3F 46 4D 54 5B 62 69
80: 00 08 10 18 20 28 30 38 40 48 50 58 60 68 70 78
90: 00 09 12 1B 24 2D 36 3F 48 51 5A 63 6C 75 7E 87
A0: 00 0A 14 1E 28 32 3C 46 50 5A 64 6E 78 82 8C 96
B0: 00 0B 16 21 2C 37 42 4D 58 63 6E 79 84 8F 9A A5
C0: 00 0C 18 24 30 3C 48 54 60 6C 78 84 90 9C A8 B4
D0: 00 0D 1A 27 34 41 4E 5B 68 75 82 8F 9C A9 B6 C3
E0: 00 0E 1C 2A 38 46 54 62 70 7E 8C 9A A8 B6 C4 D2
F0: 00 0F 1E 2D 3C 4B 5A 69 78 87 96 A5 B4 C3 D2 E1
```

---

Table 9-3

Hexadecimal text file specifying the contents of a  $4 \times 4$  multiplier ROM.

---

```

#include <stdio.h>

/* Procedure to print d as a hex digit. */
void PrintHexDigit(int d)
{
    if (d<10) printf("%c", '0'+d);
    else printf("%c", 'A'+d-10);
}

/* Procedure to print i as two hex digits. */
void PrintHex2(int i)
{
    PrintHexDigit((i / 16) % 16);
    PrintHexDigit(i % 16);
}

void main()
{
    int x, y;

    for (x=0; x<=15; x++) {
        PrintHex2(x*16); printf(":");
        for (y=0; y<=15; y++) {
            printf(" ");
            PrintHex2(x*y);
        }
        printf("\n");
    }
}

```

---

Table 9-4

Program to generate the text file specifying the contents of a  $4 \times 4$  multiplier ROM.

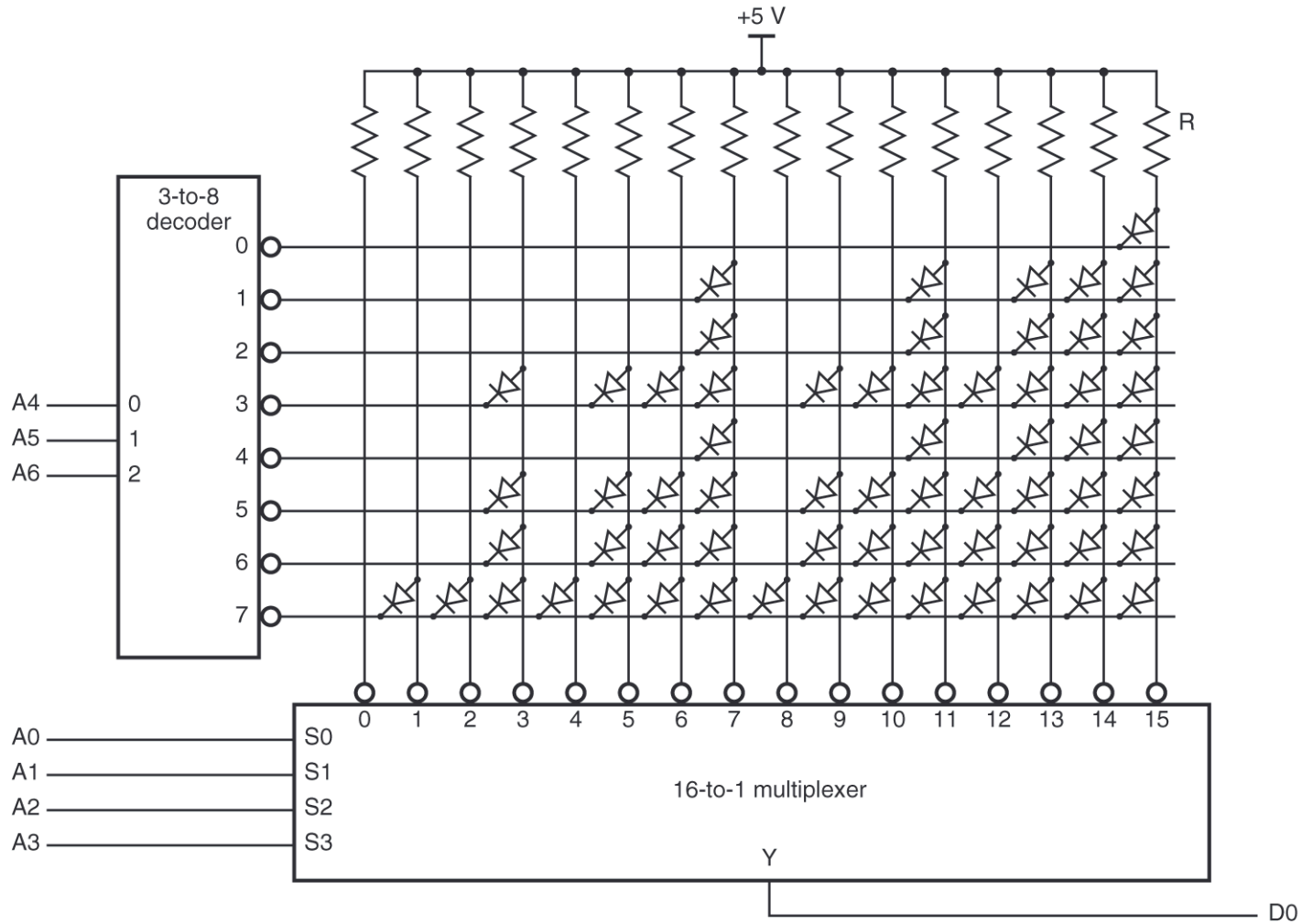


Figure 9-7  
Internal structure of a  $128 \times 1$  ROM using two-dimensional decoding.



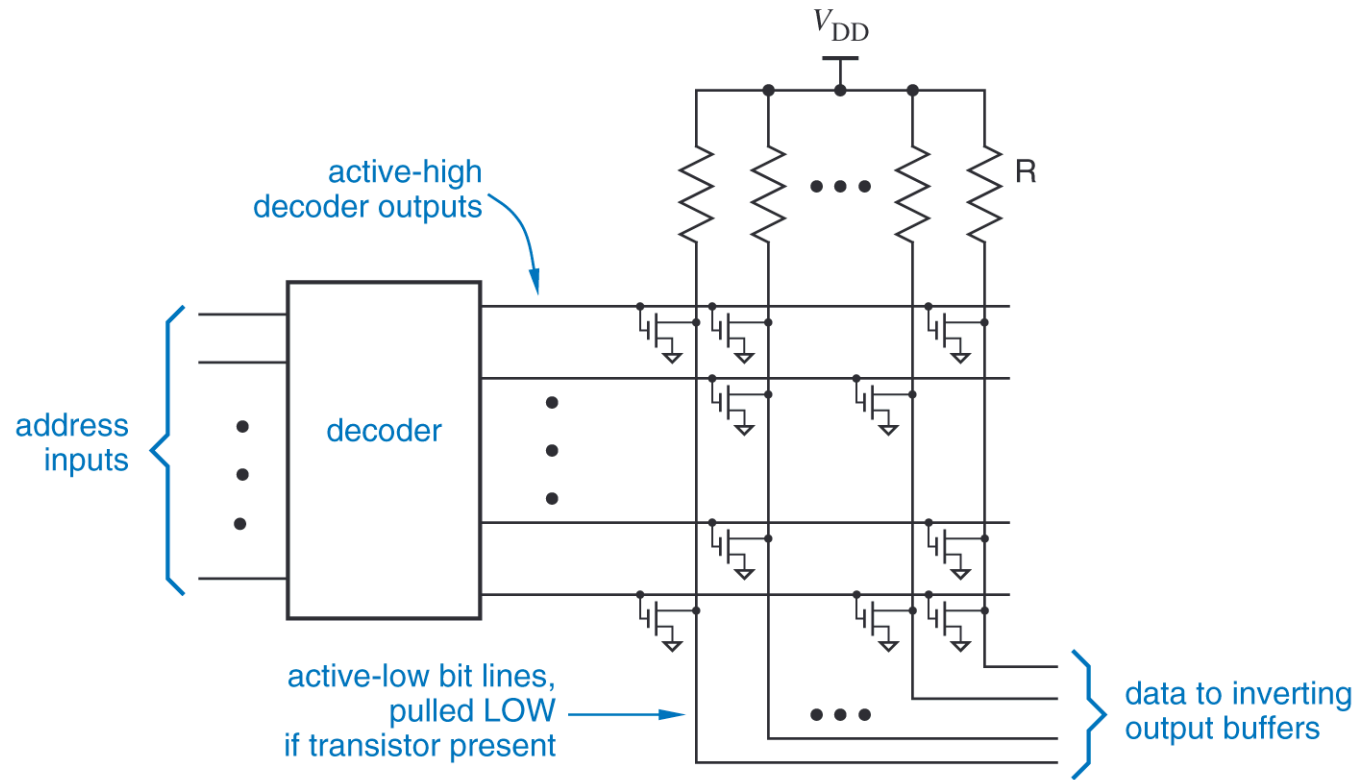


Figure 9-8  
MOS transistors as storage elements in a ROM.

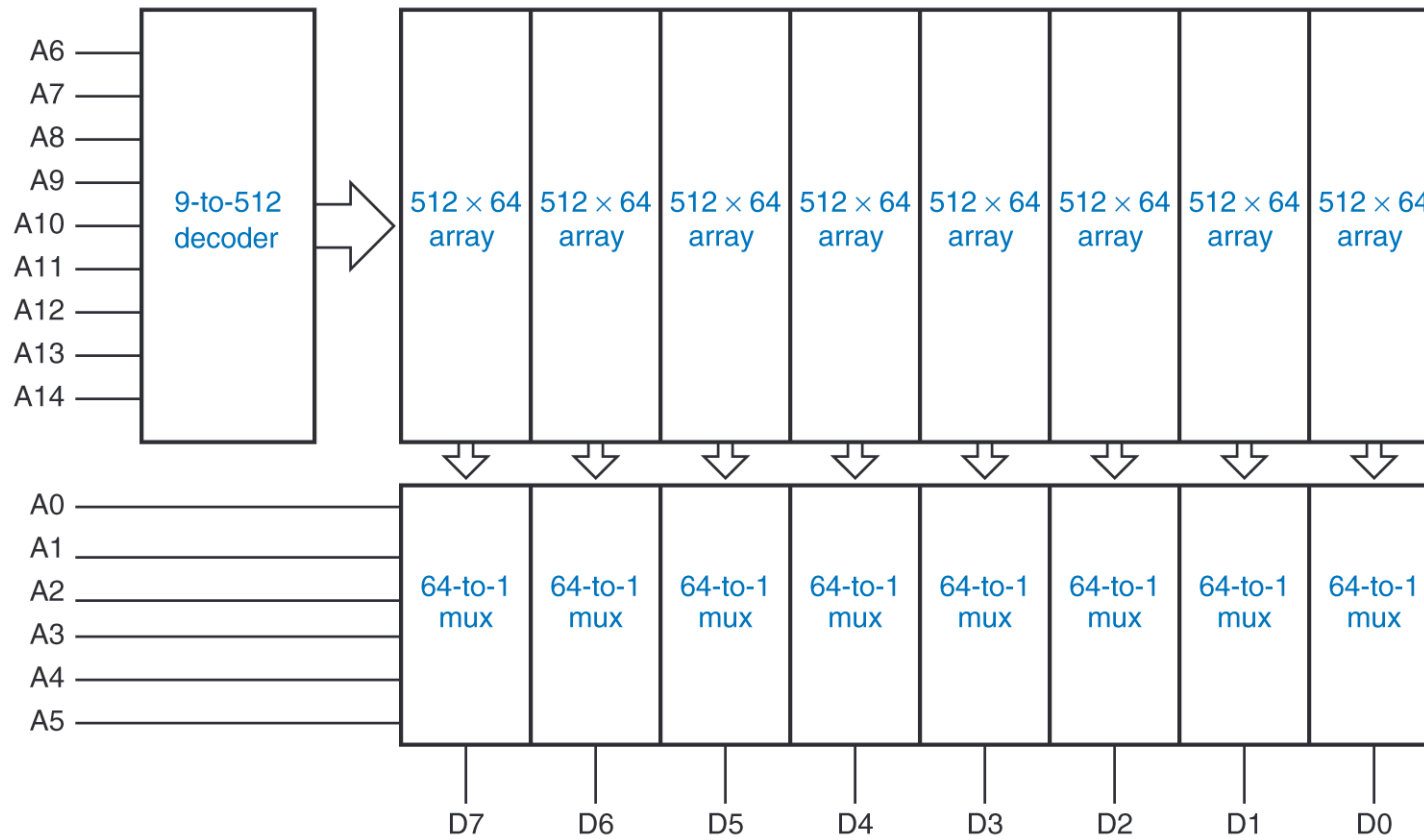


Figure 9-9  
Possible layout of a 32K x 8 ROM.

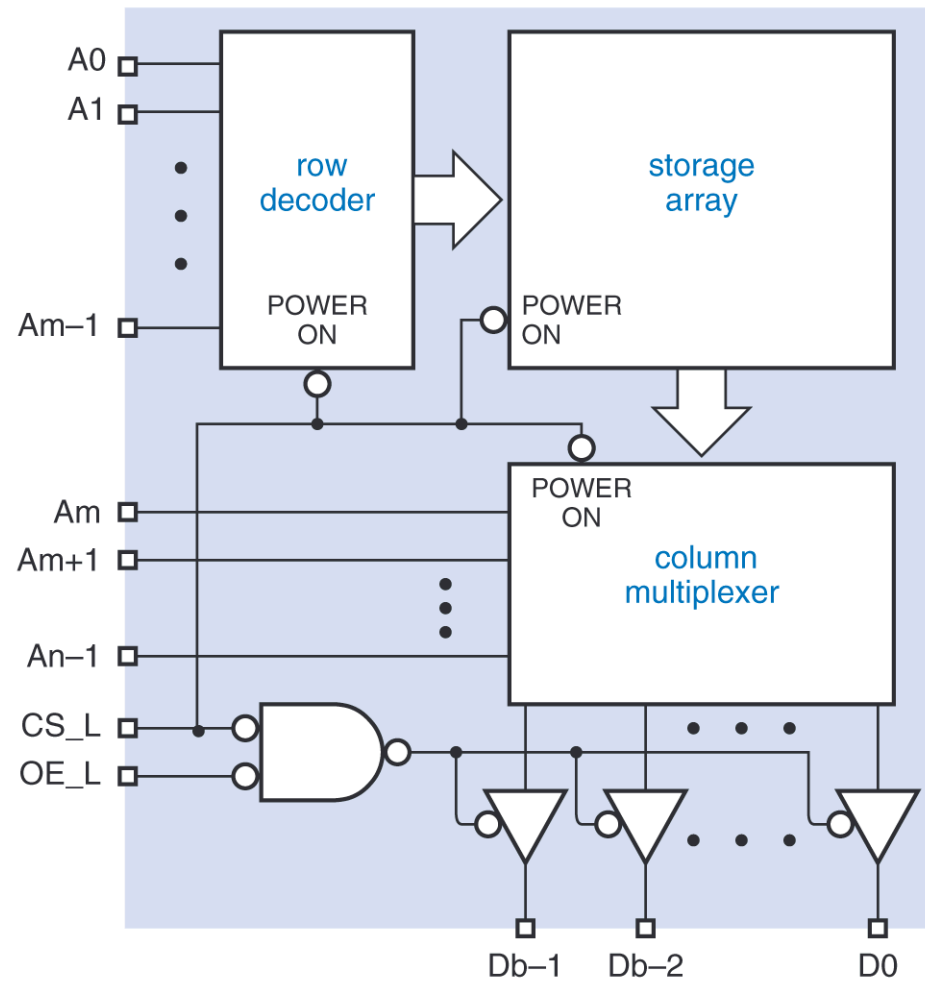


Figure 9-13

Internal ROM structure, showing use of control inputs.

 


Figure 9-15  
Format of a  $\mu$ -law PCM byte.

 


Figure 9-16

Block diagram of a digital attenuator using discrete components.

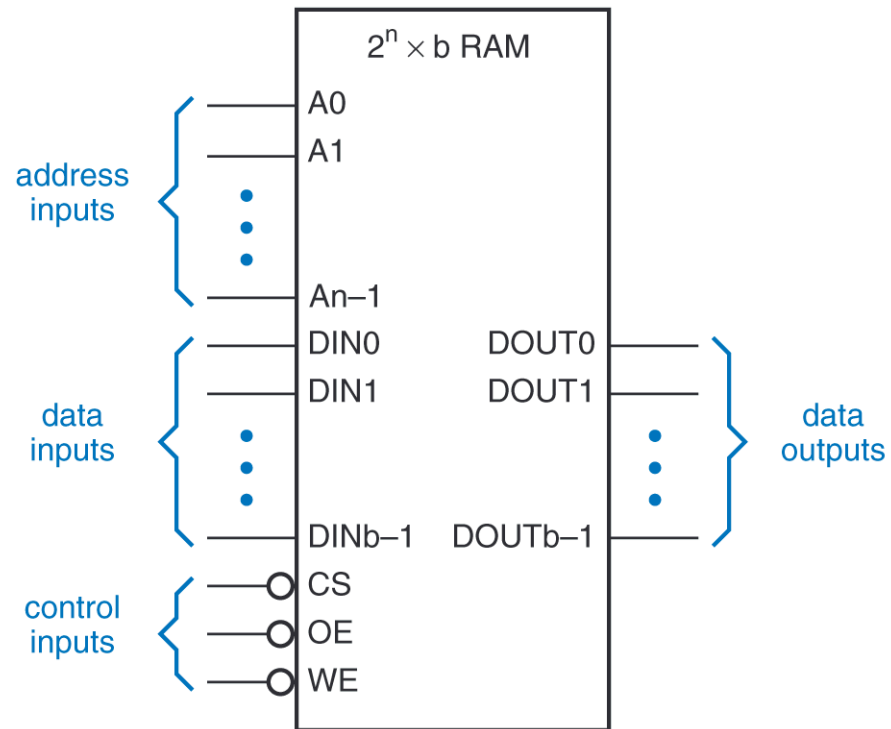


Figure 9-19

Basic structure of a  $2^n \times b$  RAM.

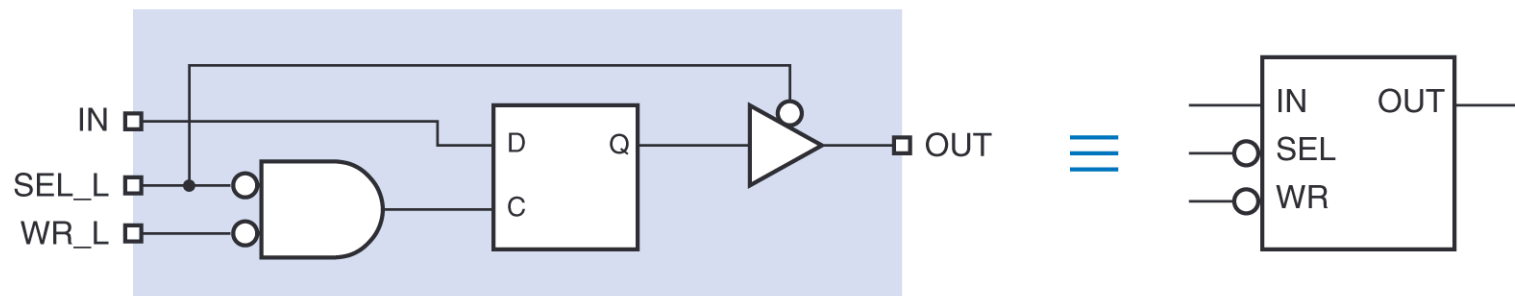


Figure 9-20

Functional behavior of a static-RAM cell.

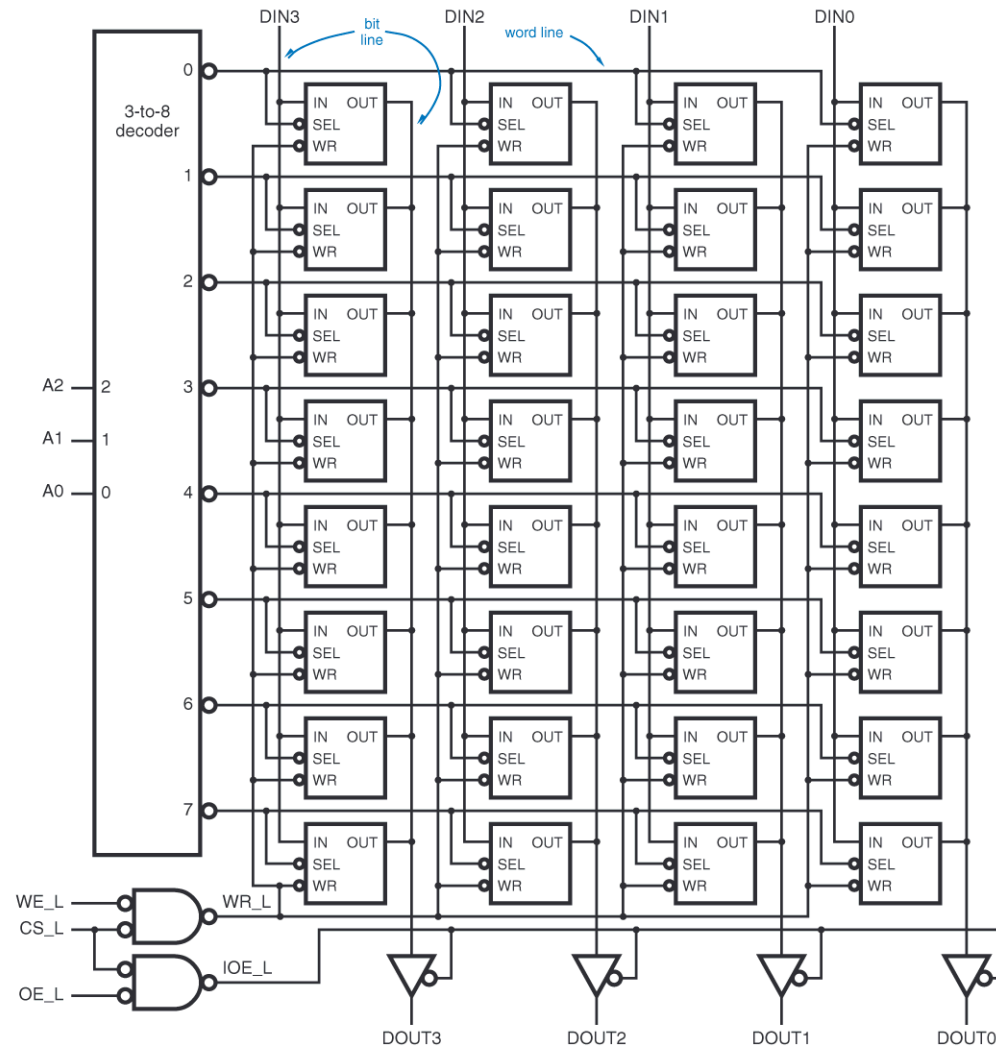


Figure 9-21

Internal structure of an  $8 \times 4$  static RAM.

From *Digital Design: Principles and Practices*, Fourth Edition, John F. Wakerly, ISBN 0-13-186389-4.  
 ©2006, Pearson Education, Inc., Upper Saddle River, NJ. All rights reserved.



 


Figure 9-25

Output-buffer control in an SRAM with a bidirectional data bus.

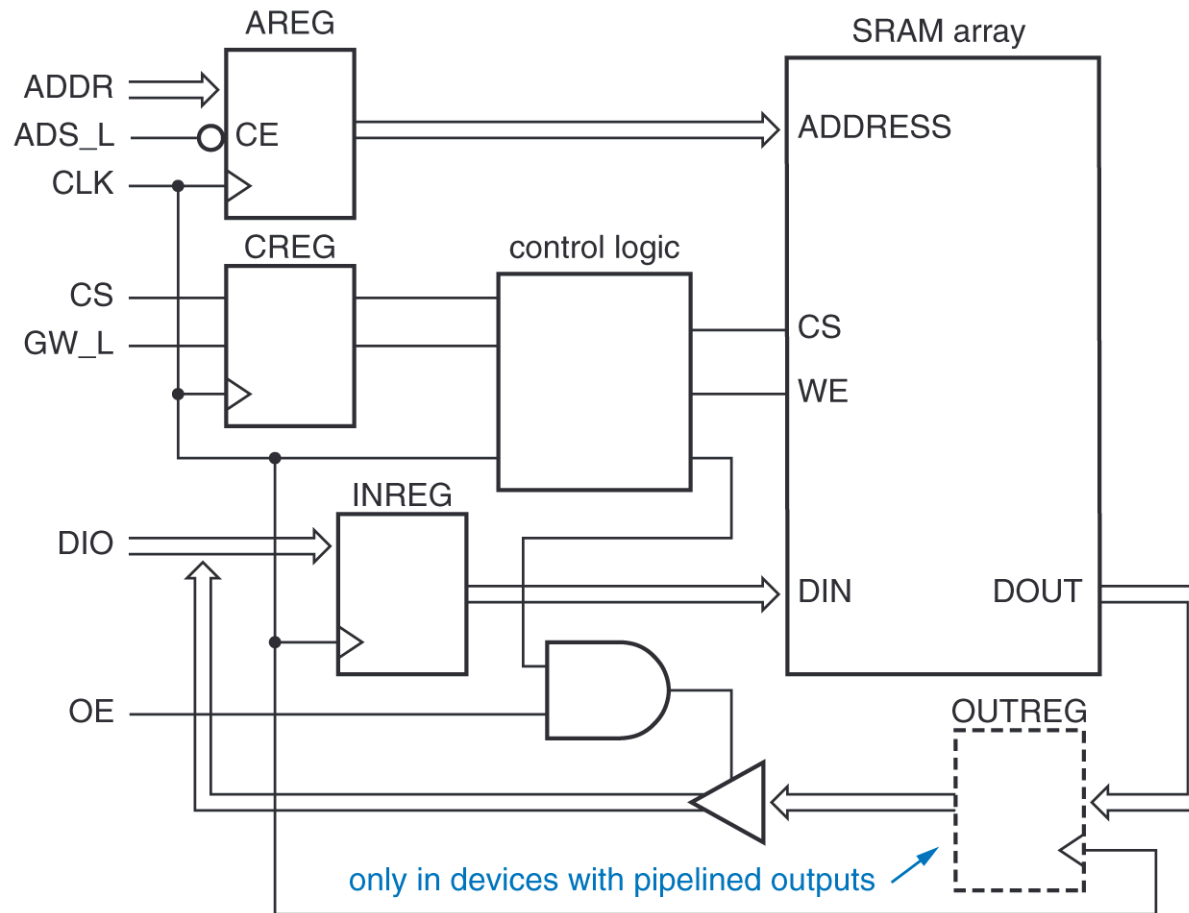


Figure 9-26

Internal structure of a synchronous SRAM.

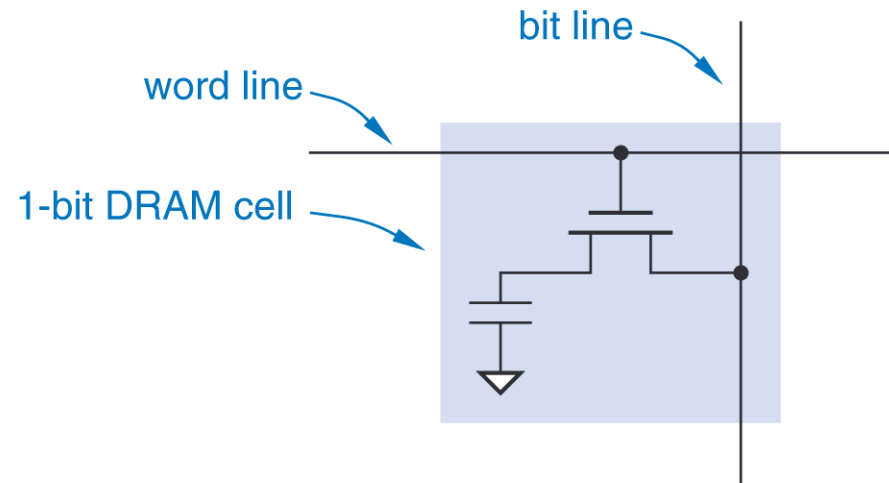


Figure 9-31  
Storage cell for one bit in a DRAM.

 


Figure 9-32

Voltage stored in a DRAM cell after writing and refresh operations.

<b>Command Name</b>	<b>Description</b>
NOP	No operation
ACTV	Row-address strobe and activate bank
READ	Column address and read command
READA	Read with auto-precharge
WRIT	Column address and read command
WRITA	Write with auto-precharge
REF	Auto refresh
PRE	Precharge

Table 9-8  
Commonly used SDRAM commands.

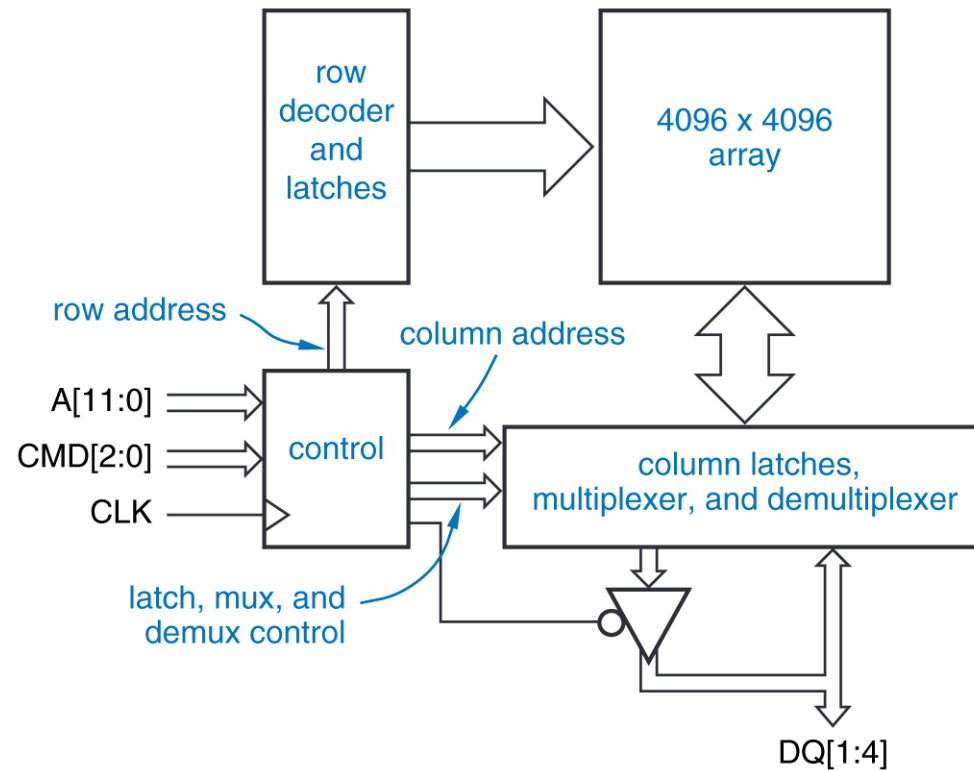


Figure 9-33  
SDRAM internal structure.

 


Figure 9-44  
General FPGA chip architecture.

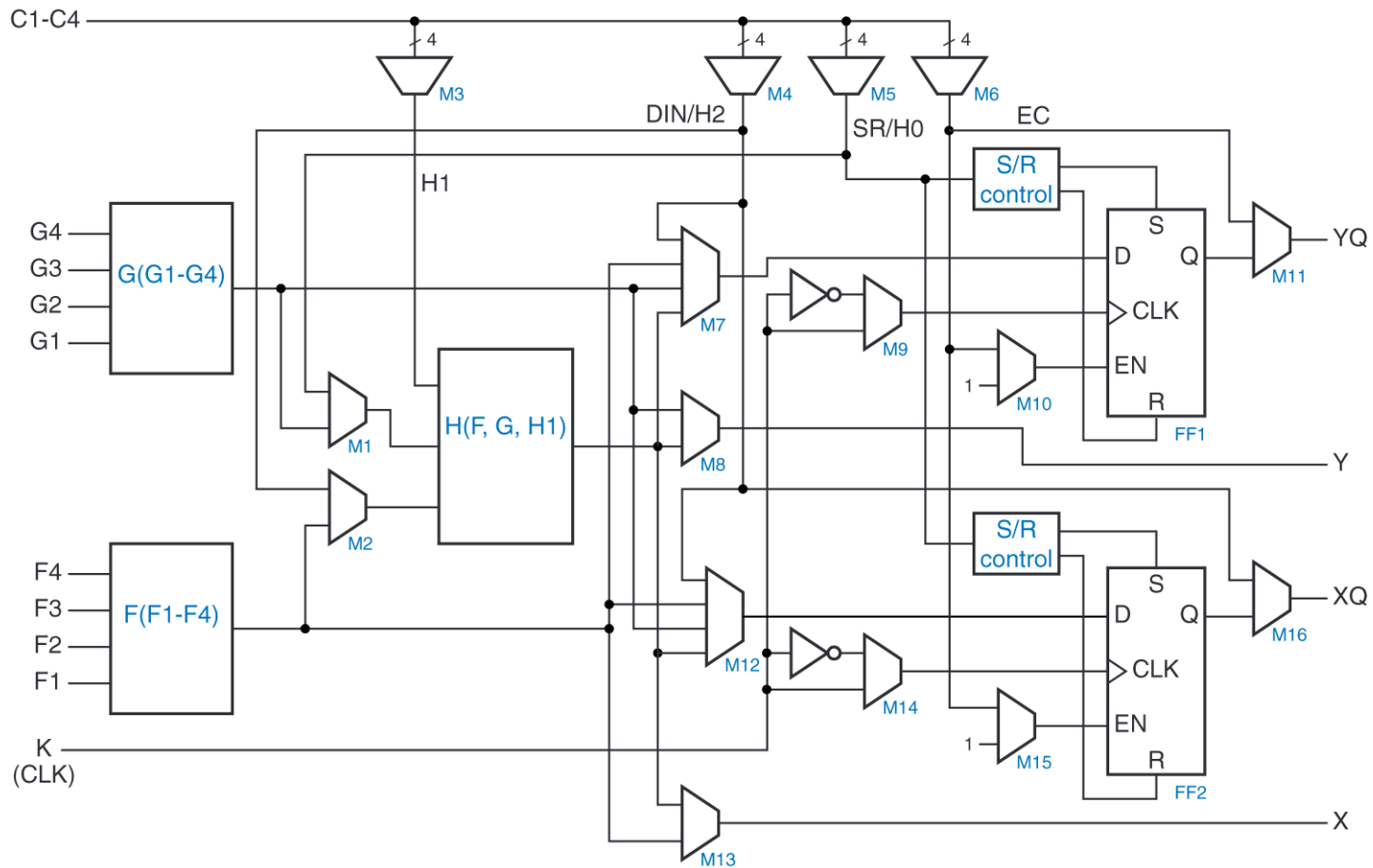


Figure 9-45  
XC4000 configurable logic block.

From *Digital Design: Principles and Practices*, Fourth Edition, John F. Wakerly, ISBN 0-13-186389-4.  
©2006, Pearson Education, Inc., Upper Saddle River, NJ. All rights reserved.



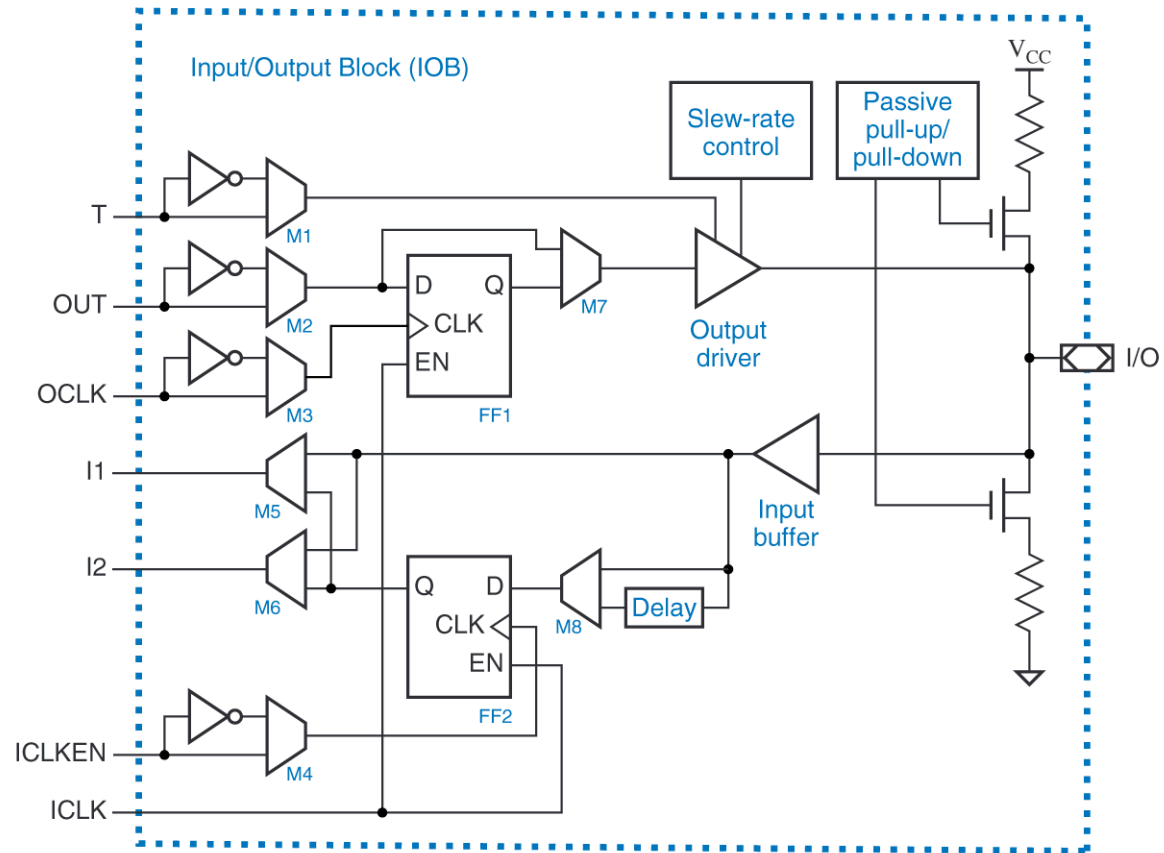


Figure 9-46  
XC4000 I/O block.

From *Digital Design: Principles and Practices*, Fourth Edition, John F. Wakerly, ISBN 0-13-186389-4.  
©2006, Pearson Education, Inc., Upper Saddle River, NJ. All rights reserved.

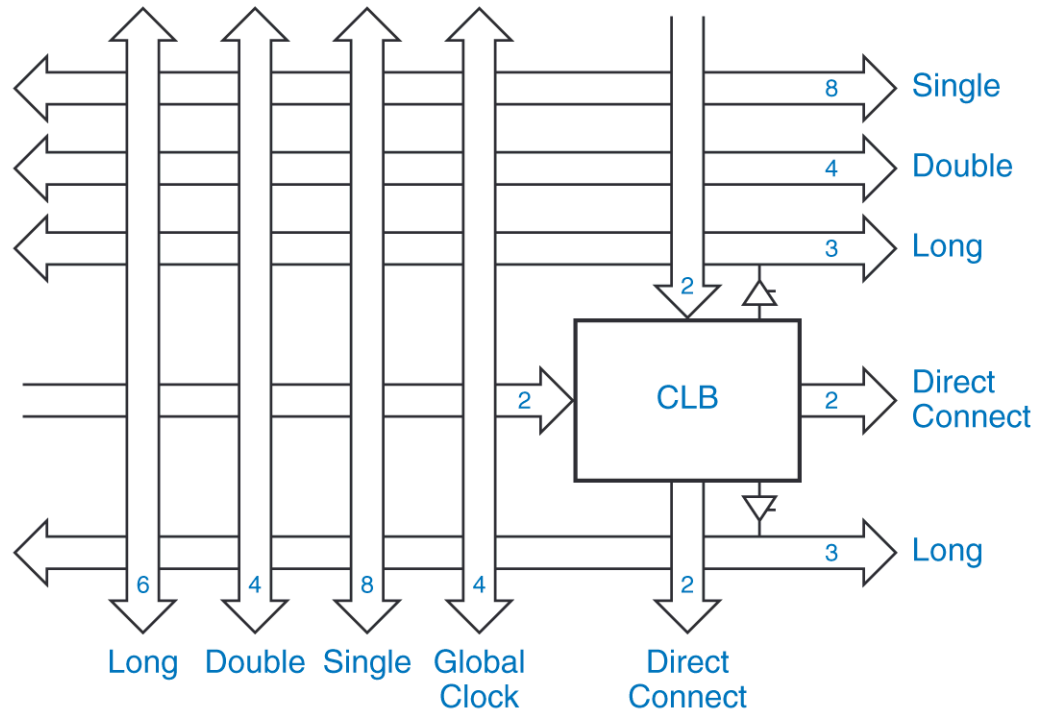


Figure 9-47

XC4000 general interconnect structure.

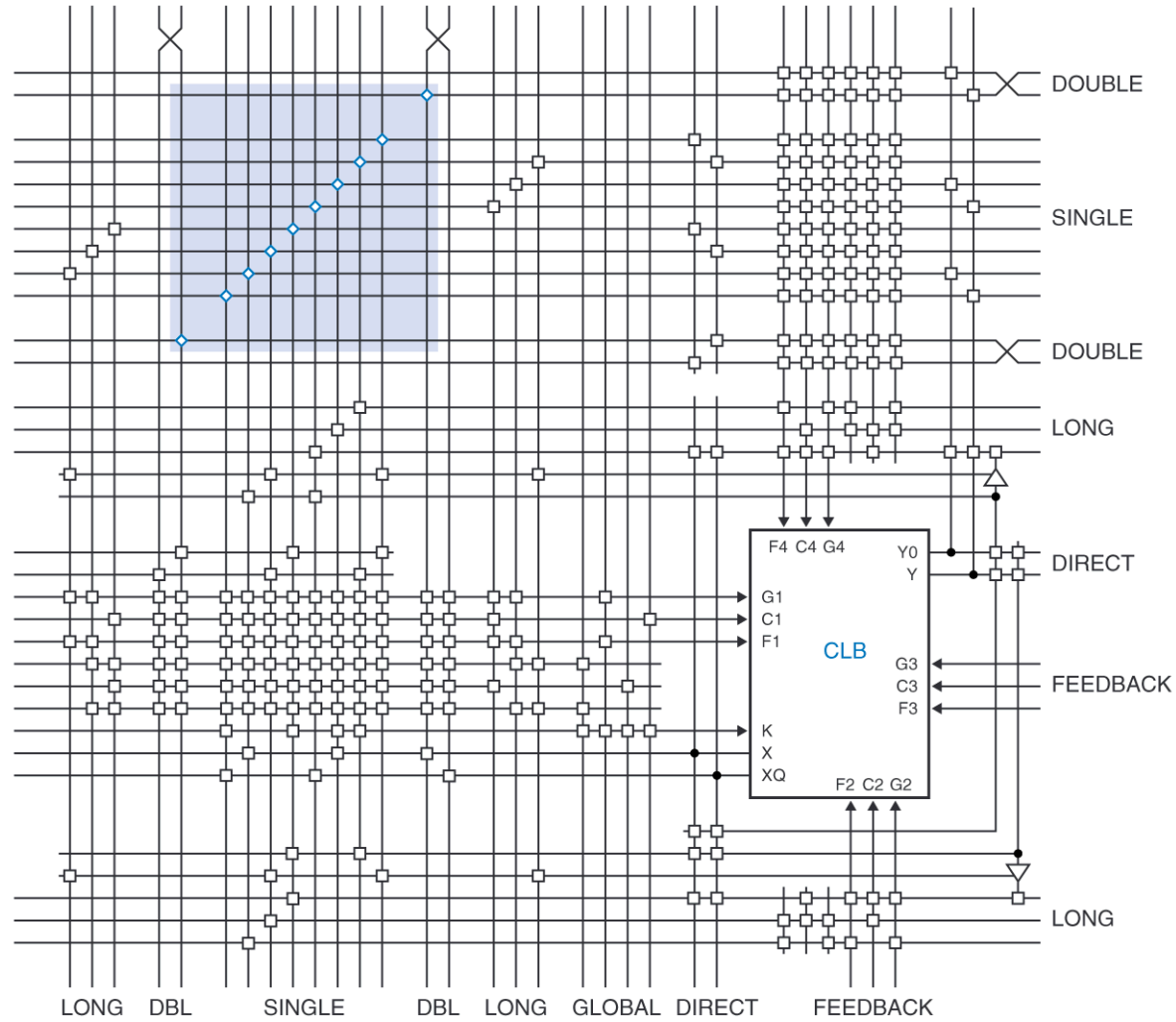


Figure 9-48

XC4000 CLB and wire connection details.

From *Digital Design: Principles and Practices*, Fourth Edition, John F. Wakerly, ISBN 0-13-186389-4.  
 ©2006, Pearson Education, Inc., Upper Saddle River, NJ. All rights reserved.



 



Figure 9-49

 XC4000 programmable connections: (a) programmable switch matrix (PSM);  
 (b) programmable switch element (PSE); (c) a few possible connections.



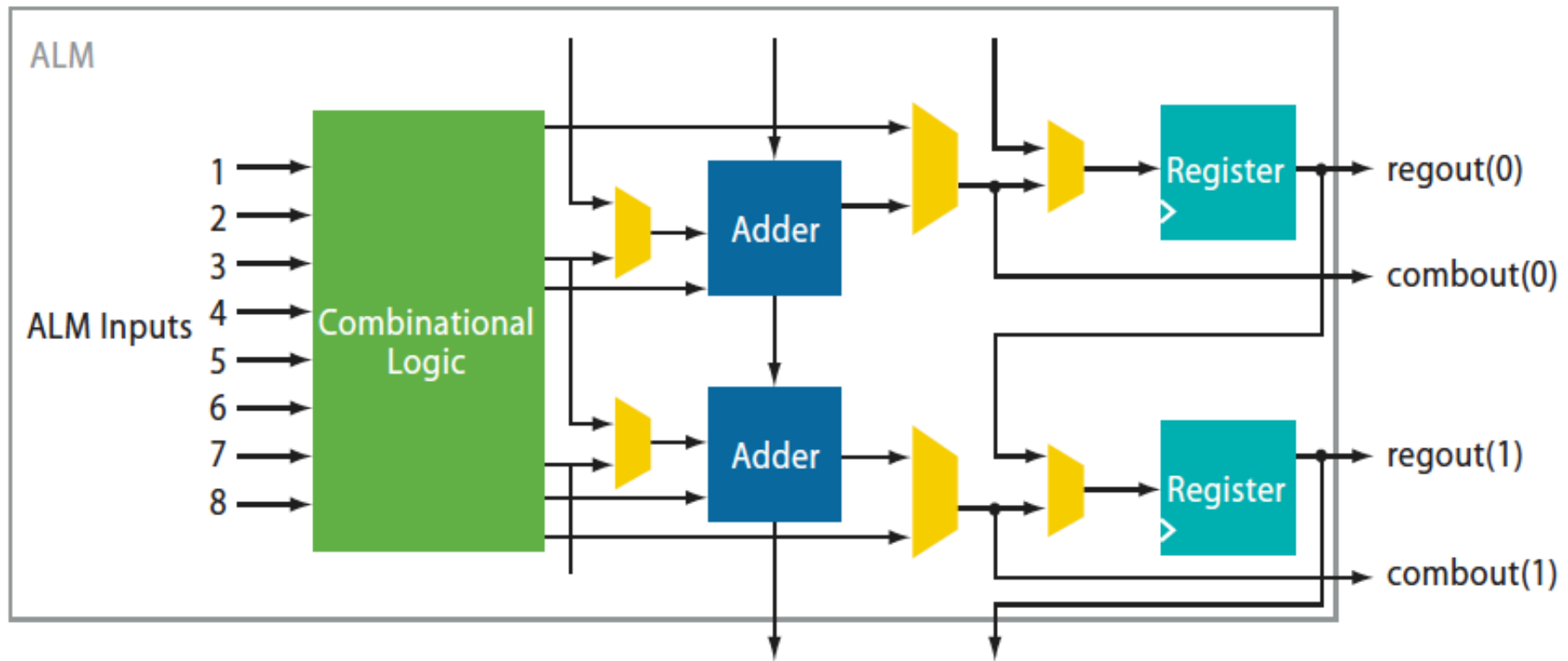

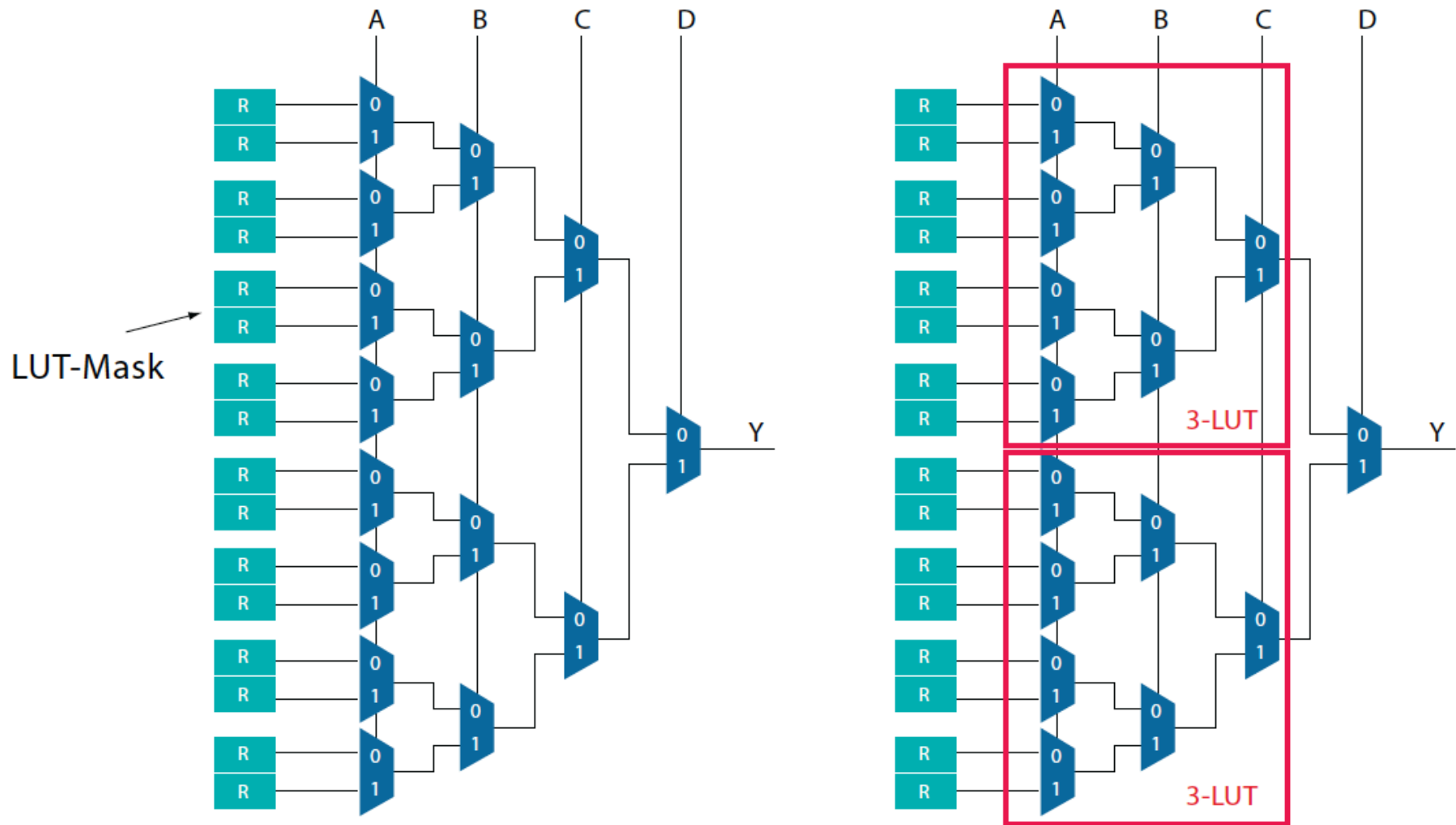8-Input Fracturable LUT
  Two Adders
  Two Registers



$$a'b'c'd' + abcd + abc'd' = 1000\ 0000\ 0000\ 1001 = 0x8009$$

