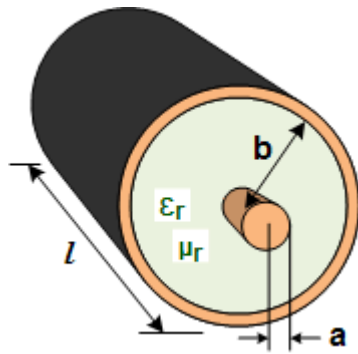


# Exercício 1 – Cabo Coaxial



Para

$a = 5 \text{ mm} \rightarrow \text{LineCalc (ADS)}$

$\epsilon_r = 2.1$

$Z_0 = 30 \Omega$


$l = 20 \text{ cm}$

$a = 2.42 \text{ mm}$

Teoria

$$L = \frac{\mu_0 \cdot \mu_r \cdot l}{2 \cdot \pi} \cdot \ln\left(\frac{b}{a}\right) \quad [\text{m,H}] \rightarrow L_{eq} = 0.145 \frac{\mu\text{H}}{\text{m}} \rightarrow L_{tot} = 29 \text{ nH}$$
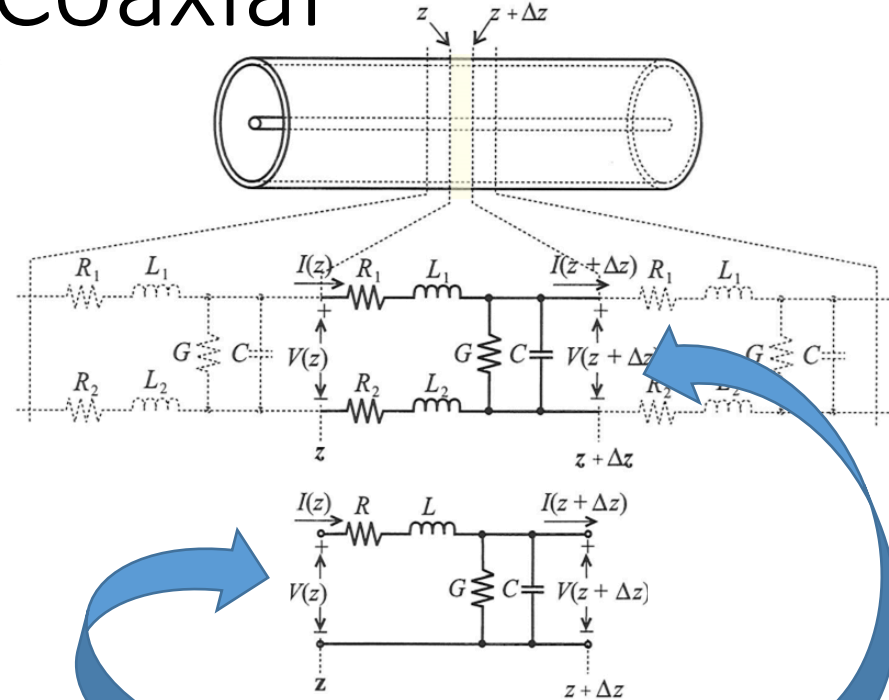
$$C = \frac{2 \cdot \pi \cdot \epsilon_0 \cdot \epsilon_r}{\ln\left(\frac{b}{a}\right)} \quad [\text{F/length}] \rightarrow C_{eq} = 0.0161 \frac{\text{nF}}{\text{m}} \rightarrow C_{tot} = 32.2 \text{ pF}$$





1) Calcule valor de  $Z_{in}$  em:

- a) 260 MHz
- b) 517 MHz

2) Calcule valor de  $\Gamma$ , VSWR e a potência Refletida

3) Calcule  $Z_{in}$  para:

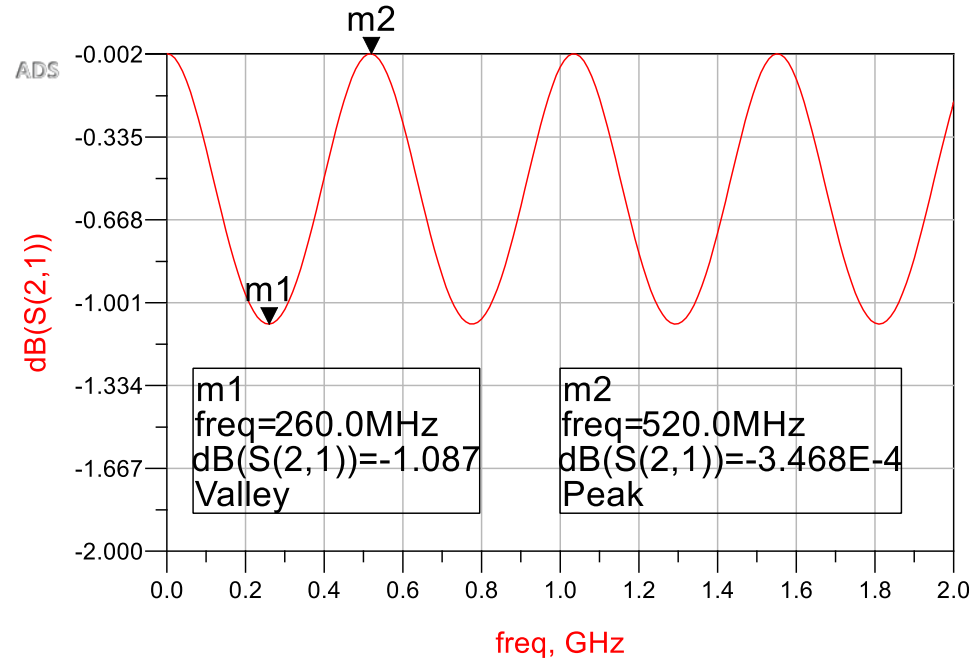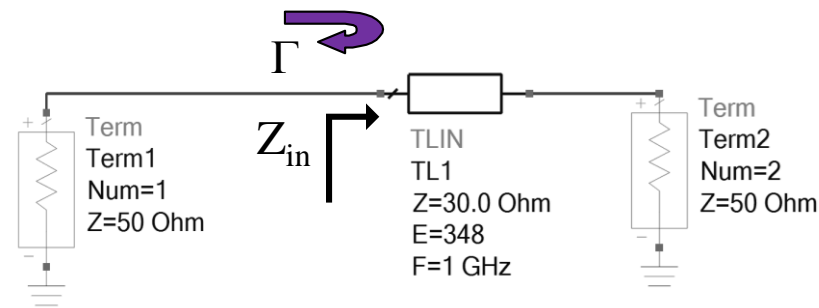- a)  $Z_L = Z_0$  (carga casada)
- b)  $l = \frac{\lambda}{4}$
- c)  $l = \frac{\lambda}{4}$  e  $Z_L = 0$
- d)  $l = \frac{\lambda}{4}$  e  $Z_L = \infty$
- e)  $l = \frac{\lambda}{2}$
- f)  $l \ll \lambda$



Apesar dos dois últimos itens darem a mesma resposta, os fenômenos envolvidos são diferentes. Explique-os