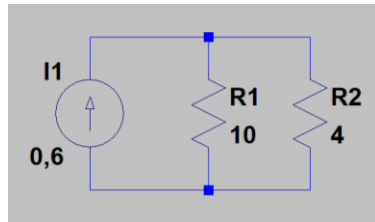



SEL0452 – MEDIDAS E CIRCUITOS ELÉTRICOS

GABARITO - LISTA DE EXERCÍCIOS 4


1. A)



B)

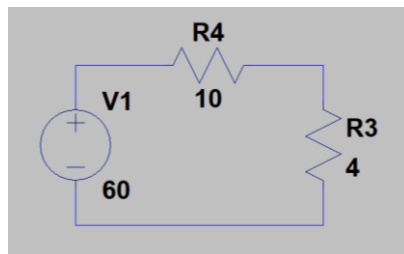

C)

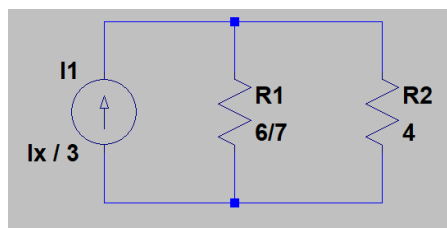

2. $I_5 = 2,625 \text{ A}$

3. $I = -0,577 \mu\text{A}$

4. $P = 5,22 \mu\text{W}$

5. $I_x = 0,0145 \text{ A}$

6. $V_x = -4,16 \text{ V}$

7. $V_3 = 0,067 \text{ V}$