

point was found to lie on the straight line obtained from Eq. 3.16. The curved parts of the characteristics were calculated by using Eqs. 3.9 and 3.11 to 3.14. The break points in Fig. 3.8 show that, except for operation at extreme values of  $\alpha$ , current is discontinuous for torques up to rated value.

The curves in Fig. 3.8 also show that no reasonable amount of approximation can produce a linear transfer function for the converter-motor combina-

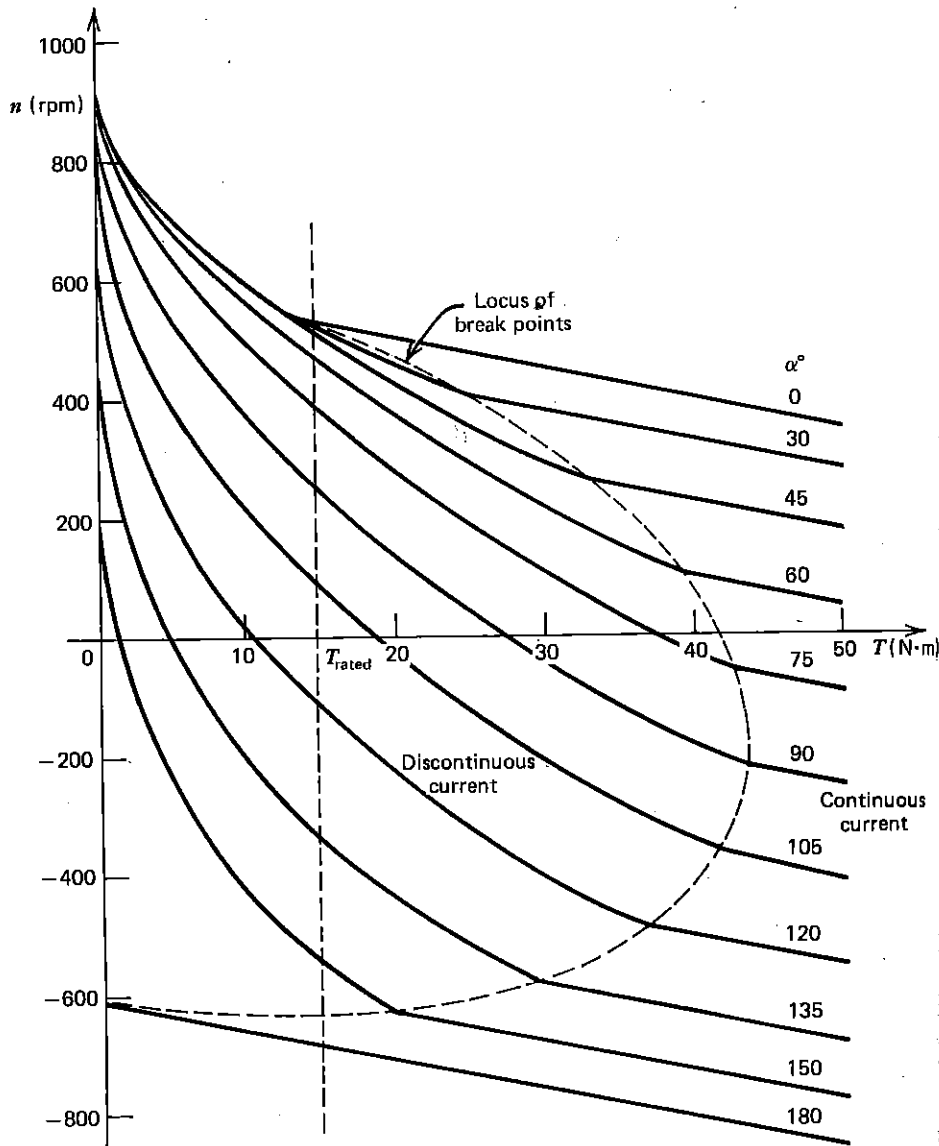


Fig. 3.8. Speed-torque characteristics for a single-phase rectifier drive.

tion. If a stability analysis is analog computer. When a simu behavior of the system for disc continuous current and that it will operate satisfactorily on b

Continuous-current operati inductance in the motor arm; ensure continuous-current ope Other converter configurations inductor considerably, even if

### 3.2.1

The converters in Fig. 3.1 car motor acting as a generator a current  $i_a$  cannot reverse, the invert without change of arm current or direction of rotat negative and, in effect, operat Fig. 3.8.

Figure 3.9 shows wavefor current and Fig. 3.10 illustrat gating signals are extended. Ex for all conditions of inverter o change in  $\bar{v}_i$  takes place on tra or conversely.<sup>3</sup> Figure 3.11 : continuous current in which t  $v_{AKA}$ . Time  $t_q$  is the time avai essential that  $\omega t_q \geq \omega t_{off} + \mu$ , of the converter and  $\mu$  is the continuous current when  $\alpha > \pi$  marked  $\alpha = 180^\circ$  in Fig. 3.8 is drive and should be replaced b

#### Example 3.1

The 230-V, 850-rpm, frame-si drive an antenna. The loss torq proportional to speed; that of motor armature is supplied fr and the ac supply of the rectif the value that gives rated speed

Determine  $i_a$ ,  $\bar{v}_i$ , and  $\alpha$  wh rated speed.

A family of speed-torque characteristics for a three-phase drive similar to those shown in Fig. 3.8 for a single-phase drive may be constructed by a procedure similar to that described at the end of Section 3.2.

Equations 3.5 and 3.9 may be applied to discontinuous-current operation of a three-phase, bridge-rectifier drive, provided that  $\alpha$  is replaced by  $\alpha + \pi/3$  in both equations, and, for the point of transition from continuous to discontinuous-current operation,  $\beta$  is replaced by  $\alpha + 2\pi/3$  in Eq. 3.9. This last equation may then be used to calculate  $\Omega_m$  at transition for a series of values

of  $\alpha$ . The corresponding value of  $\Omega_m$  is given by Eqs. 4.3 to 4.5. The point of transition is indicated in Eq. 4.7.

Once again, the point on the

$$\hat{v}_i = \sqrt{2} V \sin \alpha$$

$$\hat{v}_i = \sqrt{2} V \sin \alpha$$

and

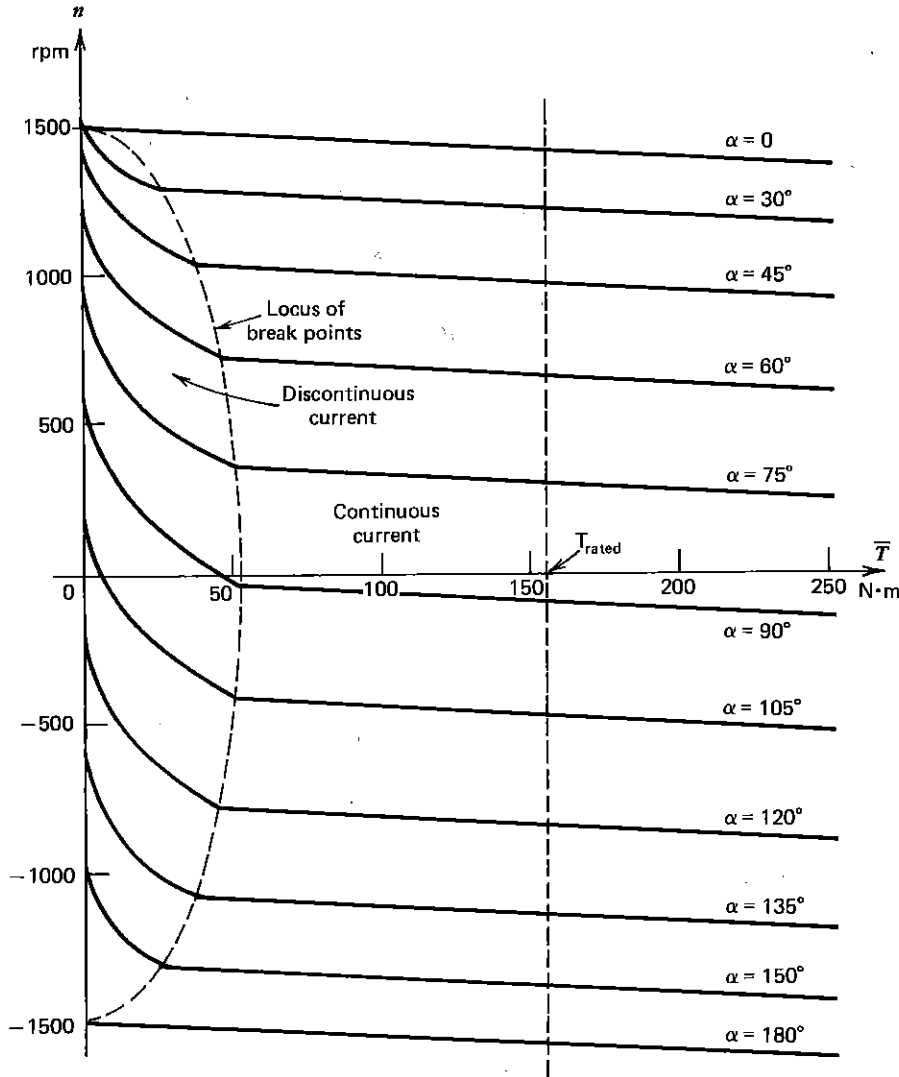


Fig. 4.4. Speed-torque characteristics for a three-phase rectifier drive.

Figure 4.4 shows a family of speed-torque characteristics for a 230-V, 25-hp, frame-size 366 motor excited by a three-phase bridge rectifier with a value of  $\alpha$ . The rectifier was set at the voltage of a dc source. These characteristics indicate that the range of current is continuous. The break-point torque indicates that break-point torque is at approximately  $\alpha =$

**Example 4.1**

For the motor in Fig. 4.4 determine the torque of doubling the armature

**Solution**

The motor parameters are  $n_r = 1150$  rpm,  $I_R = 92$  A and

$$\text{rated speed} = 1150 \text{ rpm}$$

$$k\Phi = \frac{230 - I_R R_a}{\omega_r}$$

$$Z = \frac{120\pi}{\omega_r}$$

$$\tan \phi = \frac{120\pi \times 92}{230 - 92 R_a}$$

$$\phi = 85.10^\circ$$