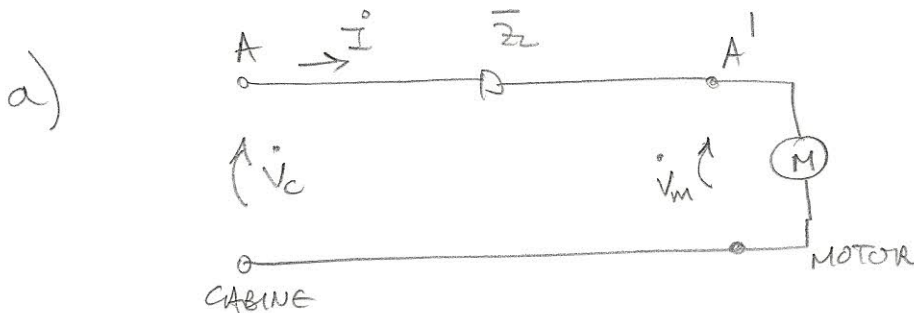


EXERCÍCIO 3.16



$$\begin{cases} \dot{V}_c = \frac{220}{\sqrt{3}} \angle 0^\circ \text{ V} & (\text{tensão de fase}) \\ \dot{V}_m = V_m \angle 0^\circ & (\text{tensão de fase com ângulo adotado}) \\ \bar{Z} = (0,1 + j0,05) \, \Omega \\ \dot{I} = 100 \angle 0 - \arccos 0,7 = 100 \angle -45,57^\circ \text{ A} \end{cases}$$

$$\begin{aligned} \dot{V}_c &= \dot{V}_m + \bar{Z} \cdot \dot{I} = V_m \angle 0^\circ + (0,1 + j0,05) \times 100 \angle -45,57^\circ \\ &= V_m + (10,571 - j3,641) = (V_m + 10,571) - j3,641 \\ &= \frac{220}{\sqrt{3}} \angle 0^\circ \end{aligned}$$

$$\therefore \sqrt{(V_m + 10,571)^2 + 3,641^2} = \frac{220}{\sqrt{3}} \Rightarrow V_m = 116,394 \text{ V}$$

$$\therefore \dot{V}_m = 116,394 \angle 0^\circ \text{ V}$$

$$\theta = \arctan \frac{-3,641}{116,394 + 10,571} = -1,64^\circ$$

$$\therefore V_c = 127,017 \angle -1,64^\circ \text{ V}$$

(2)

$$b) \quad \begin{cases} W_1 = (\sqrt{3} V_m) \cdot I \cdot \cos(\varphi + 30^\circ) \\ W_2 = (\sqrt{3} V_m) \cdot I \cdot \cos(\varphi - 30^\circ) \end{cases}$$

com $\varphi = 45,57^\circ$ (ângulo de potência do motor)

$$W_1 = \sqrt{3} \times 116,394 \times 100 \times \cos(45,57^\circ + 30^\circ) = 5024 \text{ W}$$

$$W_2 = \sqrt{3} \times 116,394 \times 100 \times \cos(45,57^\circ - 30^\circ) = 19420 \text{ W}$$

$$c) \quad \begin{cases} W_3 = \left(\sqrt{3} \times \frac{220}{\sqrt{3}} \right) \cdot I \cdot \cos(\varphi_c + 30^\circ) \\ W_4 = 220 \cdot I \cdot \cos(\varphi_c - 30^\circ) \end{cases}$$

$$\text{com } \varphi_c = -1,64^\circ - (-45,57^\circ) = 43,93^\circ$$

ângulo de potência na cabine

$$W_3 = 220 \times 100 \times \cos(43,93^\circ + 30^\circ) = 6090 \text{ W}$$

$$W_4 = 220 \times 100 \times \cos(43,93^\circ - 30^\circ) = 21353 \text{ W}$$

$$d) \quad \cos \varphi' = 0,9 \Rightarrow \varphi' = \arccos 0,9 = 25,84^\circ$$

Hipótese: a tensão no motor se mantém?

$$\boxed{\dot{V}'_m = 116,394 \angle 0^\circ \text{ V}}$$

$$P' = P = 5024 + 19420 = 24444 \text{ W}$$

$$Q = P \tan \varphi = 24444 \times \tan 45,57^\circ = 24935 \text{ VAR}$$

$$\text{e } Q' = Q - Q_{\text{cap}}$$

(3)

$$\begin{aligned} \tan \varphi' &= \frac{Q'}{P'} = \frac{Q - Q_{\text{cap}}}{P} = \frac{24935 - Q_{\text{cap}}}{24444} \\ &= \tan 25,84^\circ = 0,484 \end{aligned}$$

$$\therefore \boxed{Q_{\text{cap}} = 13097 \text{ VAR}}$$

$$\begin{aligned} C_{\Delta} &= \frac{\frac{Q_{\text{cap}}}{3}}{(\sqrt{3} \times 116,394)^2 \cdot \omega} \quad \text{1 fase!} \\ C_Y &= \frac{\frac{Q_{\text{cap}}}{3}}{116,394^2 \cdot \omega} \end{aligned}$$

$\omega = 2\pi \cdot 60 = 120\pi \text{ rad/s}$

$$\boxed{C_{\Delta} = 285 \mu\text{F}} \quad \boxed{C_Y = 855 \mu\text{F}}$$

e) $\boxed{Q_{\text{cap}} = 13097 \text{ VAR}} \quad (\text{trifásica})$

f)
$$I' = \frac{S'_m}{\sqrt{3} \cdot \underbrace{(\sqrt{3} V_m)}_{\text{Linha}}} = \frac{\sqrt{P'^2 + Q'^2}}{\sqrt{3} V_m} = \frac{\sqrt{24444^2 + (24935 - 13097)^2}}{3 \times 116,394}$$

$$I' = 77,781 \text{ A} \quad \left[< 100 \text{ A !!} \right]$$

perda ativa na linha: $P_{\text{at}} = 3 \times 0,1 \times 77,781^2 = 1815 \text{ W}$
 perda reativa na linha: $P_{\text{reat}} = 3 \times 0,05 \times 77,781^2 = 907 \text{ VAR}$

$\therefore$ novas potências na cabine:

$$\begin{aligned} P'_c &= P' + P_{\text{at}} = 24444 + 1815 = 26259 \text{ W} \\ Q'_c &= Q' + P_{\text{reat}} = (24935 - 13097) + 907 = 12745 \text{ VAR} \\ S'_c &= \sqrt{P_c'^2 + Q_c'^2} = 29189 \text{ VA} \end{aligned}$$

Verificação

nova tensão na cabine

$$\dot{V}'_c = \dot{V}'_m + \bar{Z}_L \cdot \dot{I}'$$

$$\text{com} \begin{cases} \dot{V}'_m = 116,394 \angle 0^\circ \text{ V (inalterada)} \\ \bar{Z}_L = (0,1 + j0,05) \Omega \\ \dot{I}' = 77,781 \angle 0 - (\arccos 0,9) \\ = 77,781 \angle -25,84^\circ \text{ A} \end{cases}$$

$$\therefore \boxed{\dot{V}'_c = 125,090 \angle 0,05^\circ \text{ V}}$$

novas potências na cabine

$$P'_c = \sqrt{3} V'_c I' \cos \varphi'_c$$

$$= \sqrt{3} \times (\underbrace{\sqrt{3} \times 125,090}_{\text{Linha}}) \times 77,781 \times \cos(0,05^\circ - (-25,84^\circ))$$

$$\boxed{P'_c = 26259 \text{ W}} \quad \underline{\underline{\text{OK}}}$$

$$\boxed{Q'_c = \sqrt{3} \cdot V'_c \cdot I' \cdot \sin \varphi'_c = 12745 \text{ VAR}} \quad \underline{\underline{\text{OK}}}$$
