

PSI3211 – CIRCUITOS ELÉTRICOS I

Solução da Lista 6: Redes de 1ª Ordem e Excitação Impulsiva

Redes de 1ª Ordem

1 – Temos que:
$$\begin{cases} -4e^{-4t} + 4e^{-4t} + 20 = f_1(t) \\ -4e^{-4t} + 10e^{-10t} + 4e^{-4t} - 4e^{-10t} = f_2(t) \end{cases}$$

$$\rightarrow f_1(t) = 20, t > 0, \quad f_2(t) = 6e^{-10t}, t > 0.$$

2 – $i(t) = i_0 e^{-t/\tau} \rightarrow i_0 = 10 \text{ A} \quad \tau = 0,2 \text{ s} = 200 \text{ ms}$

$$v(t) = Ri_0 e^{-t/\tau} \rightarrow R = \frac{400}{10} = 40 \Omega \quad \tau = \frac{L}{R} \rightarrow L = 40 \times 0,2 = 8 \text{ H}$$

Energia inicial: $\frac{1}{2} Li_0^2 = \frac{1}{2} \times 8 \times 100 = 400 \text{ J}$

Em $t = 50 \text{ ms} \rightarrow i = 7,788 \text{ A} \rightarrow W_L = \frac{1}{2} Li^2 = 242,61 \text{ J}$

Energia dissipada: $400 - 242,61 = 157,39 \text{ J}$

3 – a) $i_L(0_+) = i_L(0_-) = 0$ (admitido)



$$i_L(\infty) = I$$

$$\rightarrow i_L(t) = I(1 - e^{-t/\tau}), t \geq 0, \quad \tau = L/R$$


$$v(0_+) = RI$$

$$v(\infty) = 0$$
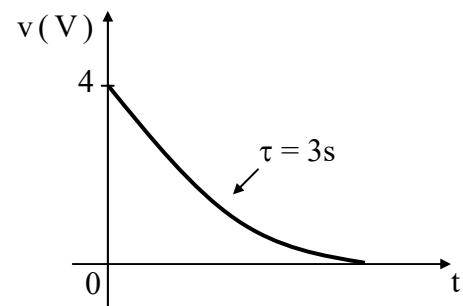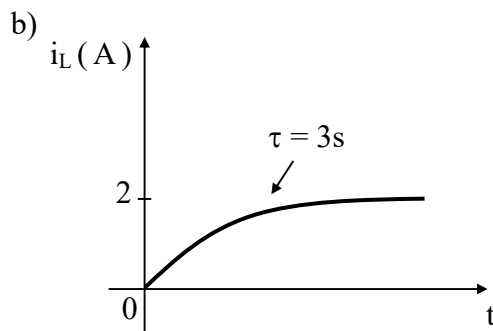
$$\rightarrow v(t) = RI e^{-t/\tau}, t > 0, \quad \tau = L/R$$



4 –

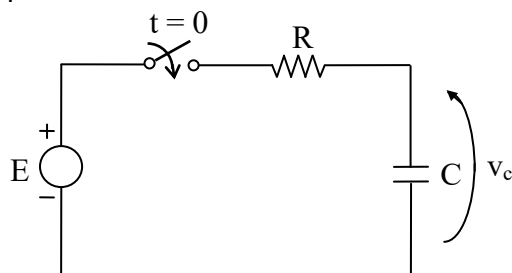


$$\begin{cases} v_c(0_+) = v_c(0_-) = 0 \text{ (admitido)} \\ v_c(\infty) = E \end{cases}$$


$$v_c(t) = E(1 - e^{-t/\tau}), t \geq 0, \quad \tau = RC$$

$$5 - \begin{cases} i(0_+) = i(0_-) = \frac{20}{4} = 5 \text{ A} \\ i(\infty) = \frac{20}{1} = 20 \text{ A} \end{cases} \quad \begin{cases} v(0_-) = 0 \\ v(0_+) = 20 - (5 \times 1) = 15 \text{ V} \\ v(\infty) = 0 \end{cases}$$
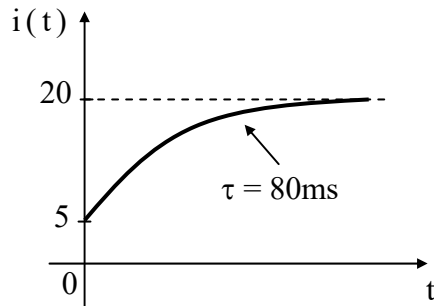
$$\tau = \frac{L}{R} = \frac{80 \times 10^{-3}}{1} = 80 \text{ ms}$$




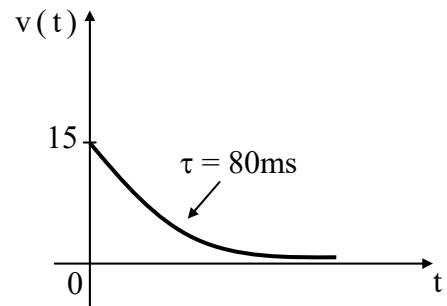
$$i(t) = (20 - 15e^{-12,5t}) \text{ (A, s)} \\ t \geq 0$$



$$v(t) = 15e^{-12,5t} \text{ (V, s)} \\ t > 0$$

6 –

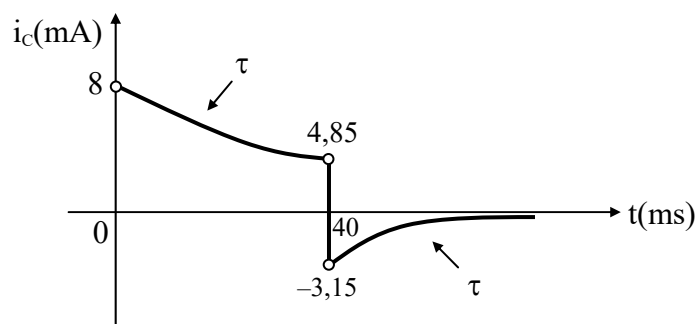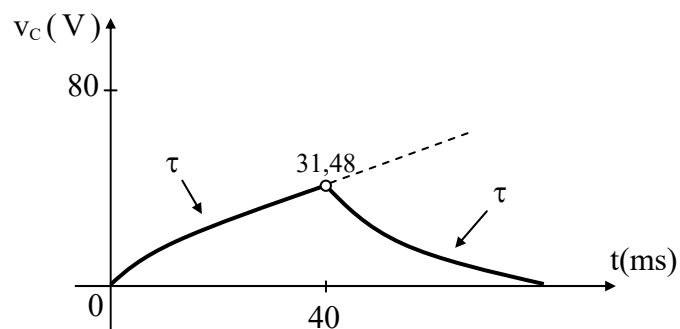

$$\tau = [(10 // 40)K + 2K] \cdot 8 \times 10^{-6} = 80 \text{ ms}$$

– Para $0 < t < 40 \text{ ms}$

$$v_c(0_+) = v_c(0_-) = 0$$

$$v_c(\infty) = (100 \times 40) / 50 = 80 \text{ V}$$

$$v_c(t) = -80e^{-t/80} + 80 \text{ (V, ms)}$$

$$i_c(0_+) = \frac{v_1(0_+)}{2\text{ K}} = \frac{100(40\text{ K} // 2\text{ K})}{10\text{ K} + (40\text{ K} // 2\text{ K})} \times \frac{1}{2\text{ K}} = 8\text{ mA}$$

$$i_c(\infty) = 0 \rightarrow i_c(t) = 8e^{-t/80} \text{ (mA, ms)}$$

– Para $t = 40\text{ ms}$


$$v_c(40_-) = 31,48\text{ V}$$

$$i_c(40_-) = 4,85\text{ mA}$$

$$v_c(40_+) = v_c(40_-)$$

$$i_c(40_+) = -31,48/10\text{ K} = -3,15\text{ mA}$$

(Thévenin equivalente): $t = 40_+$

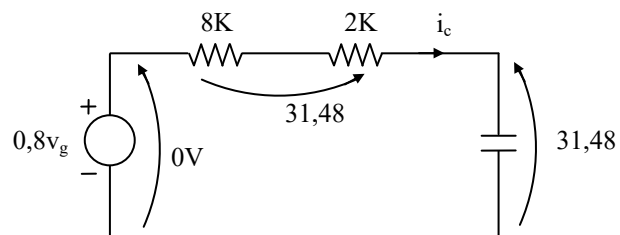

– Para $t > 40\text{ ms}$:

$$v_c(t) = 31,48e^{-(t-40)/80} \text{ (V, ms)}$$

$$i_c(t) = -3,15e^{-(t-40)/80} \text{ (mA, ms)}$$

Excitação Impulsiva

$$1 - a) \quad \dot{f}(t) = -e^{-t}H(t) + e^{-t}\delta(t) = -e^{-t}H(t) + \delta(t)$$

$$b) \quad \dot{f}(t) = \delta(t) + 2e^{-2t}H(t) - e^{-2t}\delta(t) = 2e^{-2t}H(t)$$

$$2 - a) \quad I = \int_{-2}^4 4\delta(t)dt + \int_{-2}^4 48\delta(t-2)dt \rightarrow I = 52$$

$$b) \quad I = \int_{-3}^4 t^2\delta(t)dt + \int_{-3}^4 t^2\delta(t+2,5)dt + \int_{-3}^4 t^2\delta(t-5)dt$$

$$I = 0 + 6,25 + 0 = 6,25$$

c) A integral $\int_{-1/2}^{1/2} (t^2+1)\cos(t)[\delta(t)-\delta(t-\pi/3)]dt$ pode ser calculada da seguinte forma:

$$\int_{-1/2}^{1/2} (t^2+1)\cos(t)[\delta(t)-\delta(t-\pi/3)]dt = \int_{-1/2}^{1/2} (t^2+1)\cos(t)\delta(t)dt - \int_{-1/2}^{1/2} (t^2+1)\cos(t)\delta(t-\pi/3)dt$$

Calculando cada uma das integrais da expressão anterior, temos:

$$\int_{-1/2}^{1/2} (t^2 + 1) \cos(t) \delta(t) dt = \underbrace{(t^2 + 1) \cos(t) \Big|_{t=0}}_{=1} \underbrace{\int_{-1/2}^{1/2} \delta(t) dt}_{=1} = 1$$

$$\int_{-1/2}^{1/2} (t^2 + 1) \cos(t) \delta(t - \pi/3) dt = 0. \text{ [Note que } t = \pi/3 \text{ está fora do intervalo de integração]}$$

Assim, a integral $\int_{-1/2}^{1/2} (t^2 + 1) \cos(t) [\delta(t) - \delta(t - \pi/3)] dt$ é igual a 1.

$$3 - \quad v(t) = -L \frac{di}{dt} \quad (\text{convenção do gerador})$$

$$\Rightarrow v(t) = -12 \delta(t) + 6 \delta(t - 2) \quad (\text{V, s})$$

4 – A tensão entre os terminais do capacitor é $e_s(t) = \cos(1000t) H(t)$ e a corrente que o atravessa é:

$$i(t) = C \frac{d}{dt} e_s(t) = 10^{-4} (-1000) \sin(1000t) H(t) + 10^{-4} \cos(1000t) \delta(t) =$$

$$= -0,1 \sin(1000t) H(t) + 10^{-4} \delta(t)$$

Assim, a potência instantânea recebida pelo capacitor é

$$p(t) = e_s(t) \cdot i(t) = -0,1 \sin(1000t) \cos(1000t) H(t) + 10^{-4} \cos(1000t) H(t) \delta(t)$$

$$= -\frac{0,1}{2} \sin(2000t) H(t) + 10^{-4} \delta(t)$$


Portanto,

$$p(t) = -0,05 \sin(2000t) H(t) + 10^{-4} \delta(t)$$

5 – A corrente i_R no resistor é dada por

$$i_R(t) = \frac{v_R(t)}{R} = \frac{2v_L(t)}{2} = v_L(t) \Rightarrow i_R(t) = L \frac{di_L(t)}{dt} = \frac{di_L(t)}{dt} = \frac{di_s(t)}{dt}$$

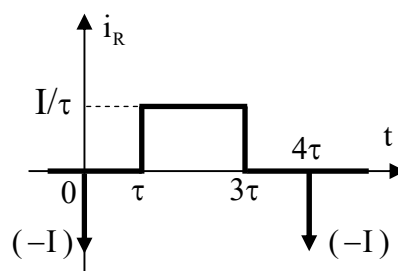Basta calcular a derivada de $i_s(t)$, que está representada no gráfico a seguir:



6 –

$$i(0_+) = \underset{\substack{\nearrow \\ \downarrow \\ 0}}{i(0_-)} + \frac{\psi}{L_{\text{eq}}} = \frac{\psi}{L_1 + L_2}$$

$$\tau = \frac{L_{\text{eq}}}{R_{\text{eq}}} = \frac{(L_1 + L_2)(R_1 + R_2)}{R_1 R_2}$$

$$i(t) = \frac{\psi}{(L_1 + L_2)} e^{-t/\tau} \quad t > 0$$