

EE320 Homework # 9

Synchronous Machines

SOLUTION

Problem 1: A 4-pole, 60Hz, Y-connected, 3-phase generator has a regulated terminal line-to-neutral voltage of $\tilde{V}_{as} = 260V_{rms} \angle 0^\circ$, a synchronous reactance of 0.06Ω , a stator resistance of 0.003Ω , and $L_{sf} = 0.02H$. The balanced 3-phase load draws 2MW at a lagging 0.8 power factor.

- Compute the 3-phase complex power of the load (magnitude and angle)
- Compute the generator phase current (magnitude and angle; hint: the angle of the current should be negative for the load to have a lagging power factor)
- Find the required excitation voltage (\tilde{E}_a)
- Calculate the required field current
- Calculate the required speed of the prime mover

Problem 2: Given the same machine as in problem 13.1. If the excitation voltage is $\tilde{E}_a = 360V_{rms} \angle 14^\circ$ and the field current is adjusted to maintain the same terminal voltage as in Problem 13.1,


- Find the new generator phase current
- Calculate the 3-phase real power consumed by the load and identify the new power factor
- Calculate the generator efficiency (consider stator winding losses as the only losses)

Problem 3: A 3-phase, Y-connected, 6-pole, 60Hz generator has $X_s = 1\Omega$, negligible r_s (stator resistance), and $L_{sf} = 0.2H$. The machine operates at a power angle of 31.48° with a field current of 100A. The line-to-neutral terminal voltage is 2400Vrms.

- Find the speed of the prime mover in rad/sec
- Determine the excitation voltage
- Find the line current
- Find the power consumed by the load and its power factor
- Find the developed torque

PROBLEM 1:

a)

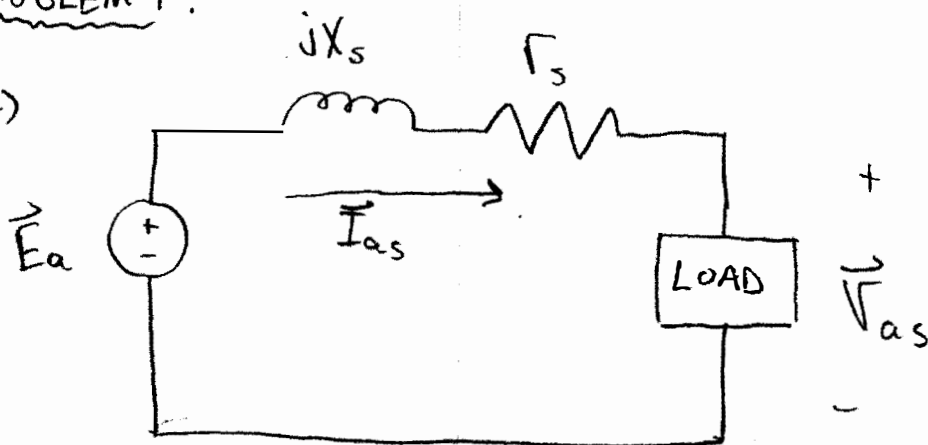


$$X_s = 0.06 \Omega$$

$$r_s = 0.003 \Omega$$

$$L_{sf} = 0.02 \text{ H}$$

$$S = 2.5 \text{ MVA}$$

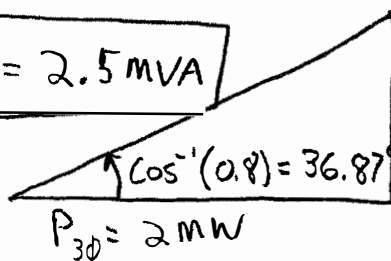

$$Q = P_{3\phi} \tan 36.87^\circ = 1.5 \text{ MVAR}$$

b) Generator phase current

$$S_{3\phi} = 3 \vec{V}_{as} \vec{I}_{as}^* \Rightarrow \vec{I}_{as}^* = \frac{S_{3\phi}}{3 \vec{V}_{as}} = \frac{2.5 \times 10^6 \angle 36.87^\circ}{3 (260 \angle 0^\circ)}$$

$$\vec{I}_{as}^* = 3205 \angle 36.87^\circ \text{ A}$$

$$\vec{I}_{as} = 3205 \angle -36.87^\circ \text{ A}$$

c) Find \vec{E}_a

KVL:

$$\vec{E}_a - \vec{I}_{as}(jX_s) - \vec{I}_{as}(r_s) - \vec{V}_{as} = 0$$

$$\vec{E}_a = (3205 \angle -36.87^\circ)(j0.06) + (3205 \angle -36.87^\circ)(0.003) + 260 \angle 0^\circ$$

$$\vec{E}_a = 410.7 \angle 21.1^\circ \text{ V}$$

Problem 1 (CONT'D)d) FIND I_f


$$\vec{E}_a = \frac{L_{sf} I_f \omega_e}{\sqrt{2}} \angle \delta$$

$$I_f = \frac{\sqrt{2} |\vec{E}_a|}{L_{sf} \omega_e} = \frac{\sqrt{2} (410.7)}{(0.02)(2\pi 60)} = \boxed{77.03 \text{ A}}$$

e) find ω_s

$$\omega_s = \omega_e = 2\pi 60 = 377 \frac{\text{rad}}{\text{sec}}$$

$$n_s = \frac{120 f_e}{p} = \frac{120 (60)}{4} = \boxed{1800 \text{ rpm}}$$

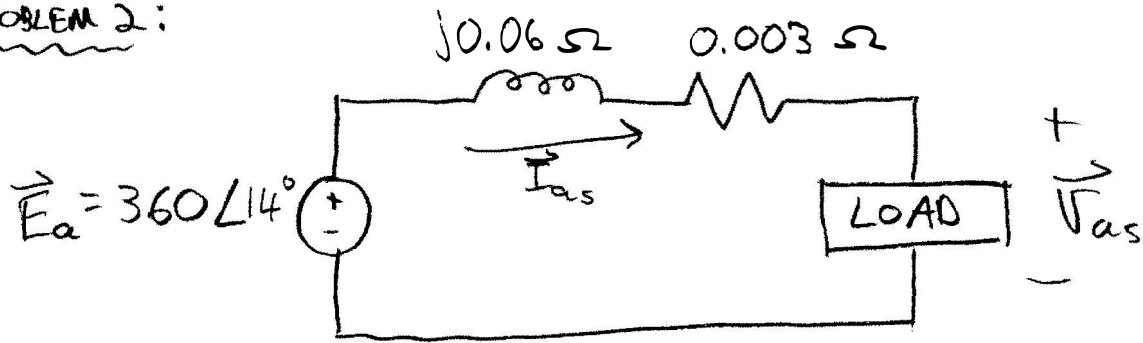PROBLEM 2:a) Find \vec{I}_{as}

$$\vec{E}_a - j0.06(\vec{I}_{as}) - 0.003(\vec{I}_{as}) - \vec{V}_{as} = 0$$


$$\vec{I}_{as} = \frac{\vec{E}_a - \vec{V}_{as}}{(0.003 + j0.06)} = \boxed{2076.4 \angle -42.86^\circ \text{ A}}$$

b) Find $P_{3\phi}$

$$S_{3\phi} = 3 \vec{V}_{as} \vec{I}_{as}^* = 3(260 \angle 0^\circ)(2076.4 \angle 42.86^\circ)$$

$$S_{3\phi} = 16.20 \angle 42.86^\circ$$

$$\text{pf} = \cos^{-1}(42.86^\circ) = \boxed{0.733}$$

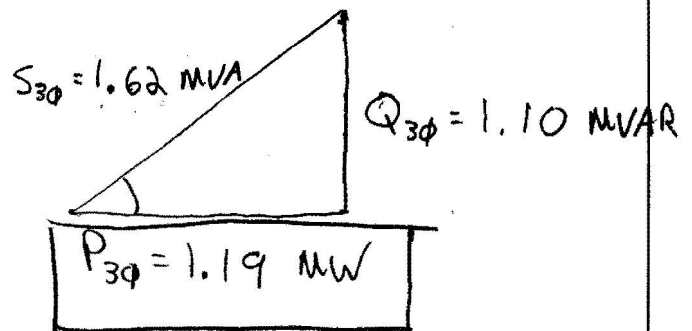c) Find η_{gen}


$$P_{\text{SCL}} = 3 |\vec{I}_{as}|^2 (0.003) = 38.8 \text{ kW}$$

↑
Stator
copper
losses

$$P_{\text{out}} = P_{\text{in}} - P_{\text{SCL}}$$

$$P_{\text{in}} = 1.19 \text{ MW} + 38.8 \text{ kW} = 1.23 \text{ MW}$$

$$\eta = \frac{1.19 \text{ MW}}{1.23 \text{ MW}} = \boxed{96.8\%}$$

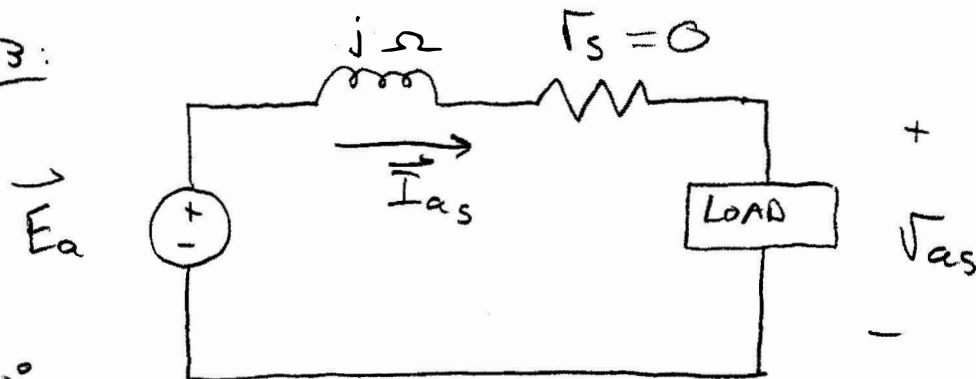PROBLEM 3:

$$\delta = 31.48^\circ$$

$$I_f = 100 \text{ A}$$

$$\vec{V}_{as} = 2400 \angle 0^\circ \text{ V}$$

$$L_{sf} = 0.2 \text{ H}$$

a) Find W_m

$$W_m = W_s = \frac{2}{P} W_e = \frac{2}{6} (2\pi 60) = 125.7 \frac{\text{rad}}{\text{sec}}$$

b) Find \vec{E}_a

$$|\vec{E}_a| = \frac{L_{sf} I_f W_e}{\sqrt{2}} = \frac{(0.2)(100)(2\pi 60)}{\sqrt{2}} = 5331.5 \text{ V}$$

$$\boxed{\vec{E}_a = 5331.5 \angle 31.48^\circ \text{ V}}$$

c) Find \vec{I}_{as}

$$\vec{I}_{as} = \frac{\vec{E}_a - \vec{V}_{as}}{j} = \frac{5331.5 \angle 31.48^\circ - 2400 \angle 0^\circ}{j}$$

$$\boxed{\vec{I}_{as} = 3515.7 \angle -37.6^\circ \text{ A}}$$

d) Find $P_{3\phi}$ and p.f.

$$\begin{aligned} \vec{S}_{3\phi} &= 3 \vec{V}_{as} \vec{I}_{as}^* = 3(2400 \angle 0^\circ)(3515.7 \angle 37.6^\circ) \\ &= 25.31 \angle 37.64^\circ \text{ MVA} \end{aligned}$$

Problem 3: (CONT'D)d) Find $P_{3\phi}$

$$P.F. = \cos^{-1}(37.64^\circ)$$

$$= 0.792$$

$$S_{3\phi} = 25.31 \text{ MVA}$$

$$Q_{3\phi} = 15.46 \text{ MVAR}$$

$$37.64^\circ$$

$$P_{3\phi} = 20.05 \text{ MW}$$

e) find $\tau_{dev} = \tau_{ind}$

no losses, $\Gamma_s = 0$

$$\tau_{dev} = \frac{P_{mech}}{W_m} = \frac{P_{3\phi}}{W_m} = \frac{20.05 \times 10^6}{125.7} = 159.5 \text{ kN}\cdot\text{m}$$

or you can solve

$$\tau_{dev} = \frac{3V_{as} E_a \sin \delta}{W_m X_s} = \frac{3(2400)(5331.5) \sin(31.48^\circ)}{125.7}$$

$$= 159.5 \text{ kN}\cdot\text{m}$$