

Física IV

14 setembro 2020


Circuitos de Corrente Alternada

Circuitos de corrente alternada

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = \mathcal{E}$$


$$Q(0) = Q_0$$

$$I(0) = I_0$$

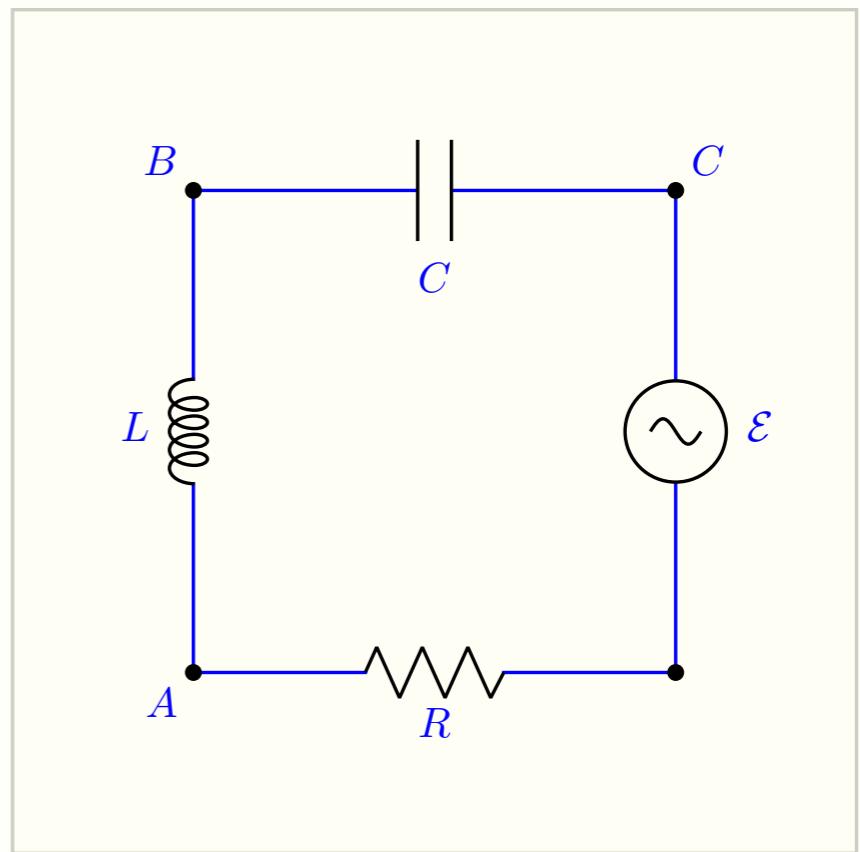

Circuitos de corrente alternada
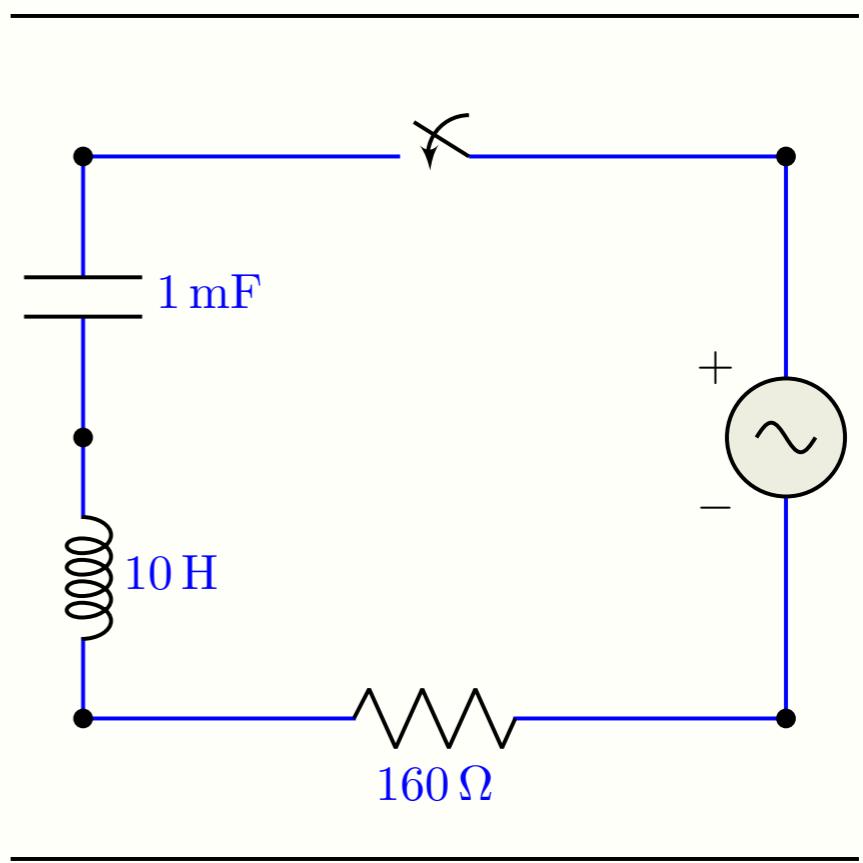
$$10 \frac{d^2Q}{dt^2} + 160 \frac{dQ}{dt} + 10^3 Q = 1.6 \cos(10t)$$



$$Q(0) = -10 \text{ mC}$$

$$I(0) = 0$$

Solução estacionária $Q(t) \Rightarrow q(t)$

$$10\frac{d^2q}{dt^2} + 160\frac{dq}{dt} + 10^3q = 1.6 \cos(10t)$$

$$10\frac{d^2q}{dt^2} + 160\frac{dq}{dt} + 10^3q = 1.6 \cos(10t)$$

$$10\frac{d^2z}{dt^2} + 160\frac{dz}{dt} + 10^3z = 1.6 \exp(i10t)$$

$$10\frac{d^2q}{dt^2} + 160\frac{dq}{dt} + 10^3q = 1.6 \cos(10t)$$

$$10\frac{d^2z}{dt^2} + 160\frac{dz}{dt} + 10^3z = 1.6 \exp(i10t)$$

$$z(t) = z_0 \exp(i10t)$$

$$10\frac{d^2q}{dt^2} + 160\frac{dq}{dt} + 10^3q = 1.6 \cos(10t)$$

$$10\frac{d^2z}{dt^2} + 160\frac{dz}{dt} + 10^3z = 1.6 \exp(i10t)$$

$$z(t) = z_0 \exp(i10t)$$

$$-10^3z_0 + 1600iz_0 + 10^3z_0 = 1.6$$

$$10 \frac{d^2q}{dt^2} + 160 \frac{dq}{dt} + 10^3 q = 1.6 \cos(10t)$$

$$10 \frac{d^2z}{dt^2} + 160 \frac{dz}{dt} + 10^3 z = 1.6 \exp(i10t)$$

$$z(t) = z_0 \exp(i10t)$$

$$\cancel{-10^3 z_0} + 1600iz_0 + \cancel{10^3 z_0} = 1.6 \exp(i10t)$$

$$10 \frac{d^2q}{dt^2} + 160 \frac{dq}{dt} + 10^3 q = 1.6 \cos(10t)$$

$$10 \frac{d^2z}{dt^2} + 160 \frac{dz}{dt} + 10^3 z = 1.6 \exp(i10t)$$

$$z(t) = z_0 \exp(i10t)$$

$$\cancel{-10^3 z_0} + 1600iz_0 + \cancel{10^3 z_0} = 1.6$$

$$z_0 = \frac{1}{10^3 i}$$

$$10 \frac{d^2q}{dt^2} + 160 \frac{dq}{dt} + 10^3 q = 1.6 \cos(10t)$$

$$10 \frac{d^2z}{dt^2} + 160 \frac{dz}{dt} + 10^3 z = 1.6 \exp(i10t)$$

$$z(t) = z_0 \exp(i10t)$$

$$\cancel{-10^3 z_0} + 1600iz_0 + \cancel{10^3 z_0} = 1.6$$

$$z_0 = \frac{1}{10^3 i} \quad \Rightarrow z = -10^{-3}i \left(\cos(10t) + i \sin(10t) \right)$$

$$10 \frac{d^2q}{dt^2} + 160 \frac{dq}{dt} + 10^3 q = 1.6 \cos(10t)$$

$$10 \frac{d^2z}{dt^2} + 160 \frac{dz}{dt} + 10^3 z = 1.6 \exp(i10t)$$

$$z(t) = z_0 \exp(i10t)$$


$$\cancel{-10^3 z_0} + 1600iz_0 + \cancel{10^3 z_0} = 1.6$$

$$z_0 = \frac{1}{10^3 i} \quad \Rightarrow z = -10^{-3}i \left(\cos(10t) + i \sin(10t) \right)$$
$$\Rightarrow q = 10^{-3} \sin(10t)$$

Circuitos de corrente alternada

$$10 \frac{d^2Q}{dt^2} + 160 \frac{dQ}{dt} + 10^3 Q = 1.6 \cos(10t)$$

$$Q(t) = q(t) + \Delta Q$$

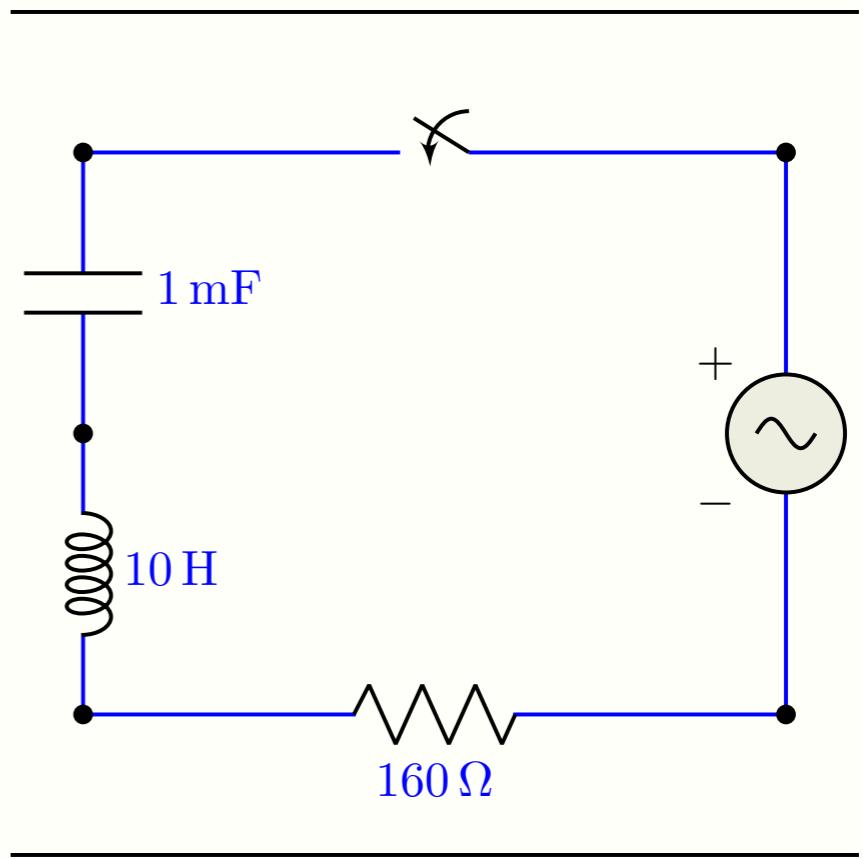

$$Q(0) = -10 \text{ mC}$$


$$I(0) = 0$$

Circuitos de corrente alternada

$$q(t) = \sin(10t) \text{ mC}$$

$$10\frac{d^2Q}{dt^2} + 160\frac{dQ}{dt} + 10^3Q = 1.6 \cos(10t)$$

$$Q(t) = q(t) + \Delta Q$$

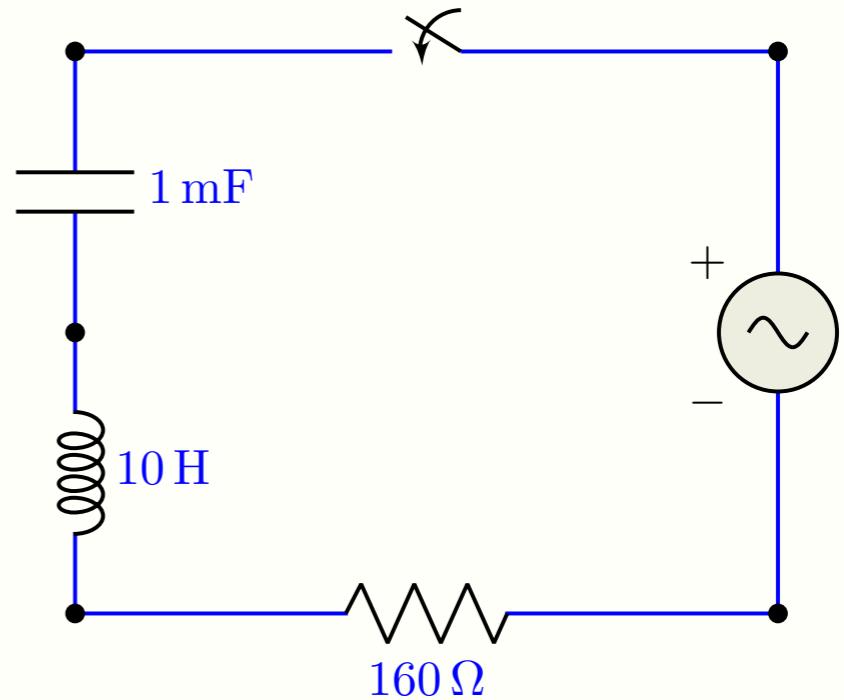

$$Q(0) = -10 \text{ mC}$$

$$I(0) = 0$$


Circuitos de corrente alternada

$$q(t) = \sin(10t) \text{ mC}$$

$$10 \frac{d^2Q}{dt^2} + 160 \frac{dQ}{dt} + 10^3 Q = 1.6 \cos(10t)$$

$$Q(t) = q(t) + \Delta Q$$
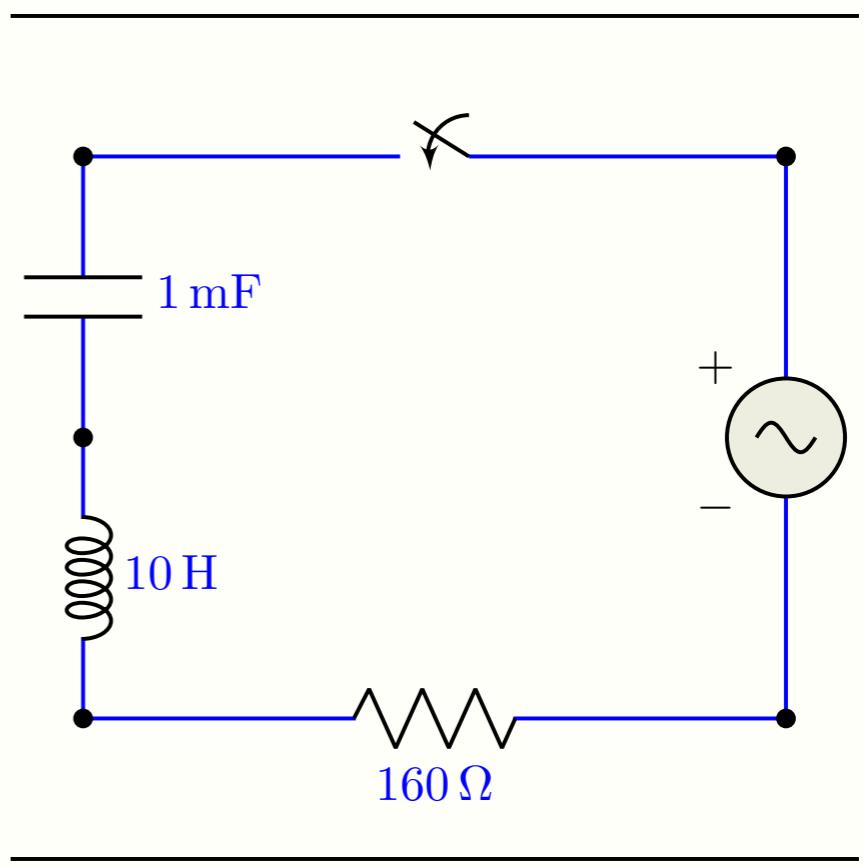
$$10 \frac{d^2\Delta Q}{dt^2} + 160 \frac{d\Delta Q}{dt} + 10^3 \Delta Q = 0$$



$$Q(0) = -10 \text{ mC}$$

$$I(0) = 0$$

$$10\frac{d^2\Delta Q}{dt^2}+160\frac{d\Delta Q}{dt}+10^3\Delta Q=0$$

$$10\frac{d^2\Delta Q}{dt^2}+160\frac{d\Delta Q}{dt}+10^3\Delta Q=0$$

$$\frac{d^2\Delta Q}{dt^2}+16\frac{d\Delta Q}{dt}+10^2\Delta Q=0$$

$$10\frac{d^2\Delta Q}{dt^2}+160\frac{d\Delta Q}{dt}+10^3\Delta Q=0$$

$$\frac{d^2\Delta Q}{dt^2}+\textcolor{red}{16}\frac{d\Delta Q}{dt}10^2\Delta Q=0$$

$$\tau = \frac{1}{8}\,\mathrm{s}$$

$$10 \frac{d^2 \Delta Q}{dt^2} + 160 \frac{d \Delta Q}{dt} + 10^3 \Delta Q = 0$$

$$\frac{d^2 \Delta Q}{dt^2} + 16 \frac{d \Delta Q}{dt} + 10^2 \Delta Q = 0$$

$$\tau = \frac{1}{8} \text{ s}$$

$$\omega_0 = 10 \text{ rad/s}$$

$$10 \frac{d^2 \Delta Q}{dt^2} + 160 \frac{d \Delta Q}{dt} + 10^3 \Delta Q = 0$$

$$\frac{d^2 \Delta Q}{dt^2} + 16 \frac{d \Delta Q}{dt} + 10^2 \Delta Q = 0$$

$$\left. \begin{array}{l} \tau = \frac{1}{8} \text{ s} \\ \omega_0 = 10 \text{ rad/s} \end{array} \right\} \omega_0 \tau > 1 \quad (\text{subamortecido})$$

$$10 \frac{d^2 \Delta Q}{dt^2} + 160 \frac{d \Delta Q}{dt} + 10^3 \Delta Q = 0$$

$$\frac{d^2 \Delta Q}{dt^2} + 16 \frac{d \Delta Q}{dt} + 10^2 \Delta Q = 0$$

$$\left. \begin{array}{l} \tau = \frac{1}{8} \text{ s} \\ \omega_0 = 10 \text{ rad/s} \end{array} \right\} \omega_1 = \sqrt{\omega_0^2 - \frac{1}{\tau^2}} = 6 \text{ rad/s}$$

$$\omega_1=\sqrt{\omega_0^2-\frac{1}{\tau^2}}=6\,\mathrm{rad/s}$$

$$\Delta Q = \alpha Q_x + \beta Q_y$$

$$\Delta Q = \alpha Q_x + \beta Q_y$$

$$\omega_1=\sqrt{\omega_0^2-\frac{1}{\tau^2}}=6\,\mathrm{rad/s}$$

$$Q_x=\exp(-8t)\cos(6t)$$

$$Q_y=\exp(-8t)\frac{\sin(6t)}{6}$$

$$\Delta Q = \alpha Q_x + \beta Q_y$$

$$\omega_1=\sqrt{\omega_0^2-\frac{1}{\tau^2}}=6\,\mathrm{rad/s}$$

$$Q(t)=q(t)+\alpha Q_x+\beta Q_y$$

$$Q_x=\exp(-8t)\cos(6t)$$

$$Q_y=\exp(-8t)\frac{\sin(6t)}{6}$$

$$q(t)=\sin(10t)\,\mathrm{mC}$$

$$\Delta Q = \alpha Q_x + \beta Q_y$$

$$\omega_1=\sqrt{\omega_0^2-\frac{1}{\tau^2}}=6\,\mathrm{rad/s}$$

$$Q(t)=q(t)+\alpha Q_x+\beta Q_y$$

$$Q_x=\exp(-8t)\cos(6t)$$

$$Q(0)=q(0)+\alpha Q_x(0)+\beta Q_y(0)$$

$$Q_y=\exp(-8t)\frac{\sin(6t)}{6}$$

$$q(t) = \sin(10t)\,\mathrm{mC}$$

$$\Delta Q = \alpha Q_x + \beta Q_y$$

$$\omega_1=\sqrt{\omega_0^2-\frac{1}{\tau^2}}=6\,\mathrm{rad/s}$$

$$Q(t) = q(t) + \alpha Q_x + \beta Q_y$$

$$Q_x = \exp(-8t)\cos(6t)$$

$$Q(0) = \cancel{q(0)} + \alpha Q_x(0) + \cancel{\beta Q_y(0)}$$

$$Q_y = \exp(-8t)\frac{\sin(6t)}{6}$$

$$q(t)=\sin(10t)\,\mathrm{mC}$$

$$\Rightarrow \color{red}\alpha = Q(0) = -10\,\mathrm{mC}$$

$$\Delta Q = \alpha Q_x + \beta Q_y$$

$$\omega_1=\sqrt{\omega_0^2-\frac{1}{\tau^2}}=6\,\mathrm{rad/s}$$

$$Q(t) = q(t) + \alpha Q_x + \beta Q_y$$

$$Q_x = \exp(-8t)\cos(6t)$$

$$Q(0) = \cancel{q(0)} + \alpha Q_x(0) + \cancel{\beta Q_y(0)}$$

$$Q_y = \exp(-8t)\frac{\sin(6t)}{6}$$

$$q(t)=\sin(10t)\,\mathrm{mC}$$

$$\alpha=-10\,\mathrm{mC}$$

$$\beta=-90\,\mathrm{mC/s}$$

$$\Delta Q = \alpha Q_x + \beta Q_y$$

$$\omega_1 = \sqrt{\omega_0^2 - \frac{1}{\tau^2}} = 6 \text{ rad/s}$$

$$Q(t) = q(t) + \alpha Q_x + \beta Q_y$$

$$Q_x = \exp(-8t)\cos(6t)$$

$$Q(0) = \cancel{q(0)} + \alpha \cancel{Q_x(0)} + \beta \cancel{Q_y(0)}$$



$$Q_y = \exp(-8t) \frac{\sin(6t)}{6}$$

$$q(t) = \sin(10t) \text{ mC}$$

$$Q(t) = \left(\sin(10t) - 10 \exp(-8t) \left(\cos(6t) + \frac{9}{6} \sin(6t) \right) \right) \text{ mC}$$

Transiente e regime estacionário

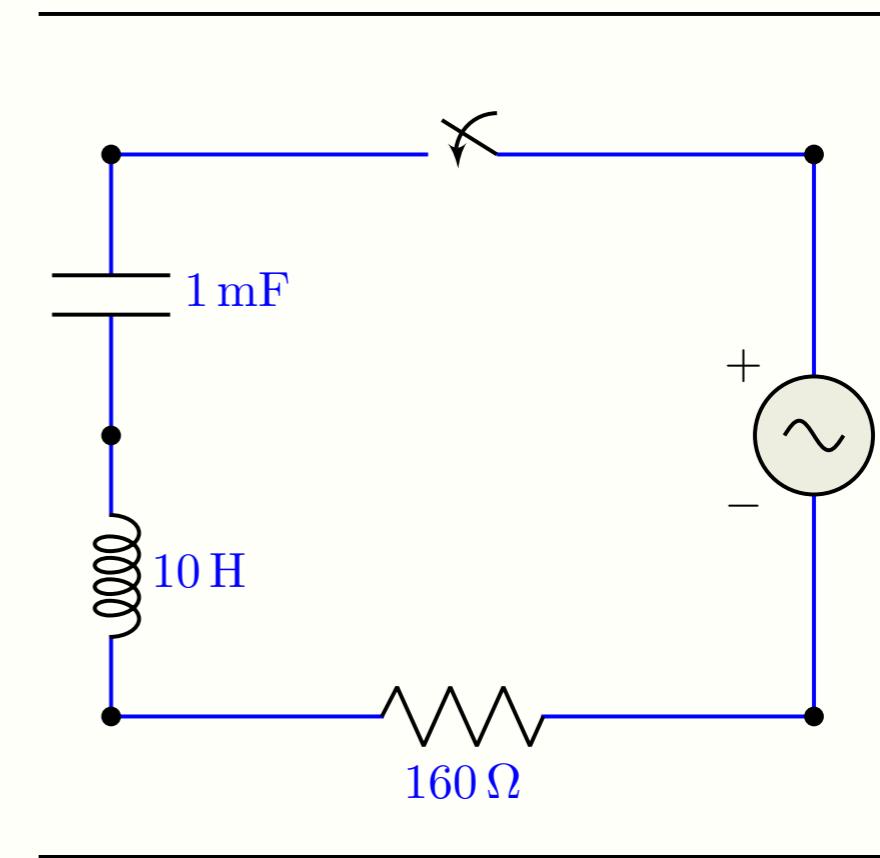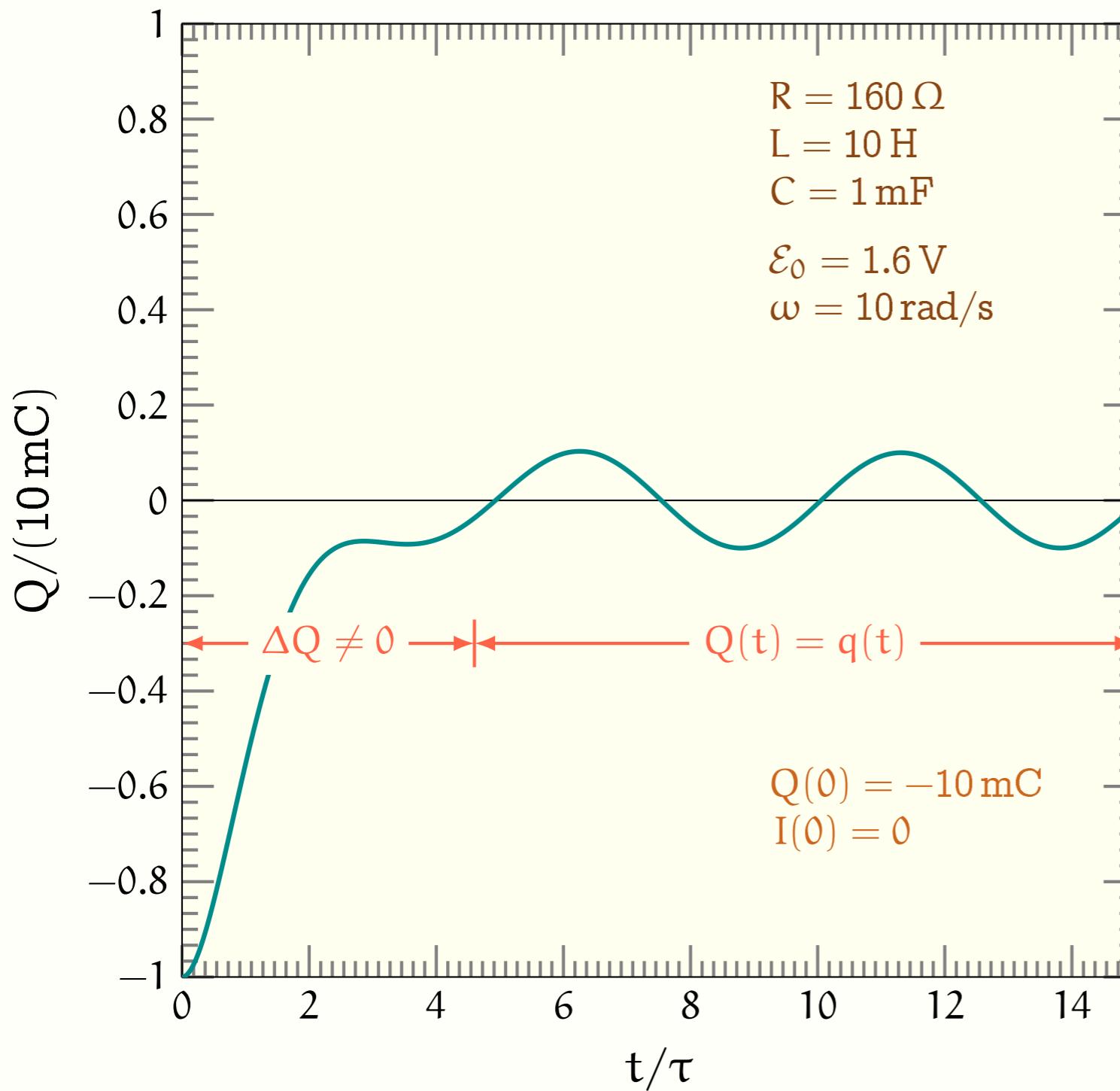
$$Q(t) = \left(\sin(10t) + 10 \exp(-8t) \left(\cos(6t) + \frac{7}{6} \sin(6t) \right) \right) \text{mC}$$



$$Q(0) = -10 \text{ mC}$$
$$I(0) = 0$$



João Evangelista Steiner

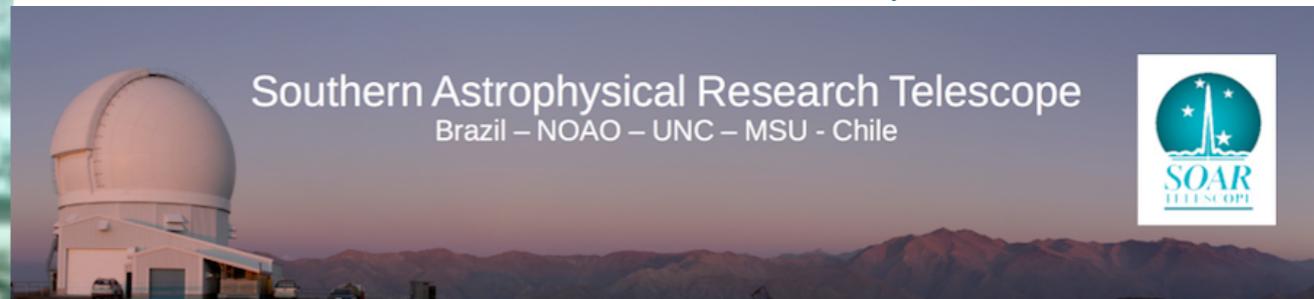


Southern Astrophysical Research Telescope
Brazil – NOAO – UNC – MSU - Chile



Circuitos de corrente alternada

Corrente estacionária
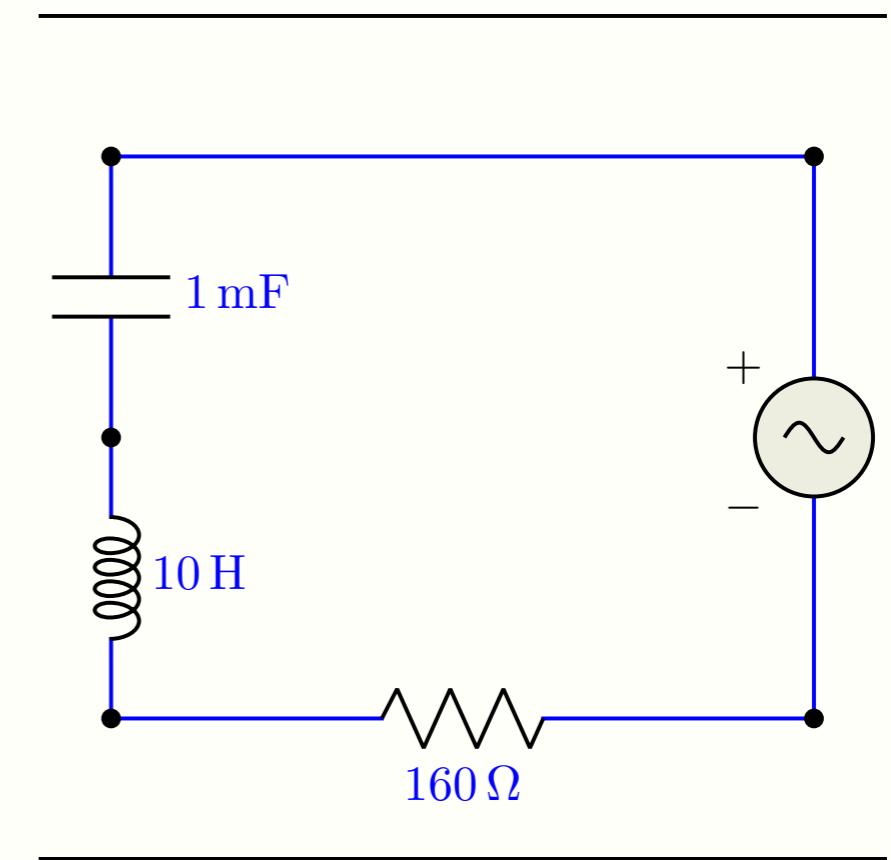
$$L \frac{d^2z}{dt^2} + R \frac{dz}{dt} + \frac{z}{C} = \mathcal{E}_0 \exp(i\omega t)$$




Circuitos de corrente alternada

Corrente estacionária

$$L \frac{d^2z}{dt^2} + R \frac{dz}{dt} + \frac{z}{C} = \mathcal{E}_0 \exp(i\omega t)$$
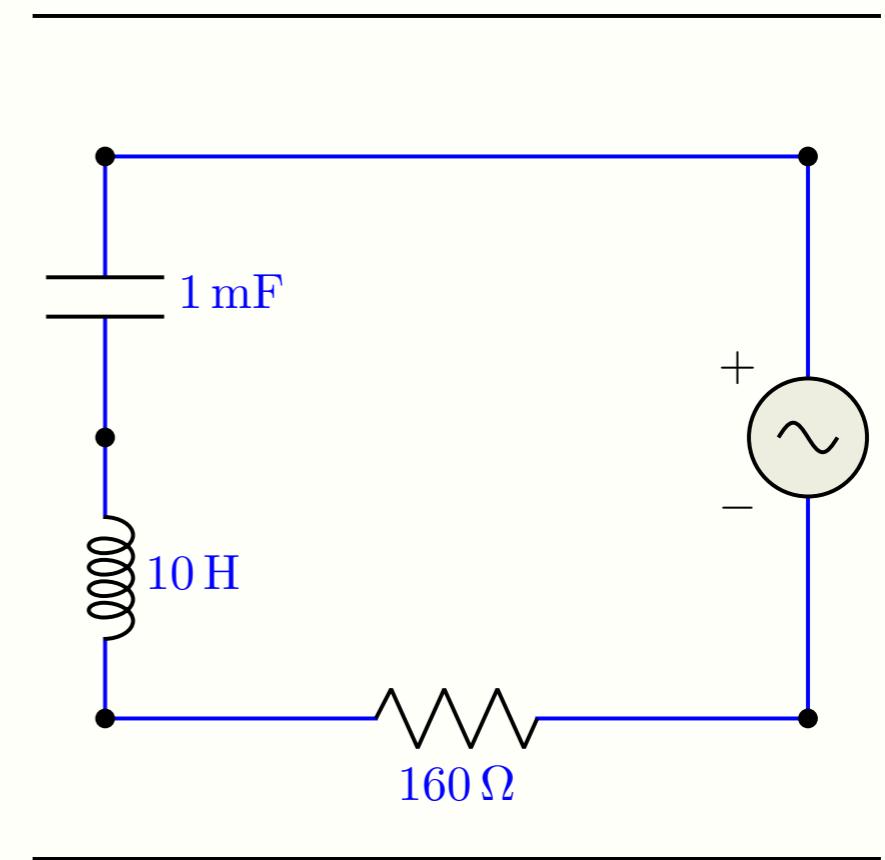
$$-L\omega^2 z + R i\omega z + \frac{z}{C} = \mathcal{E}_0 \exp(i\omega t)$$




Circuitos de corrente alternada

Corrente estacionária

$$L \frac{d^2 z}{dt^2} + R \frac{dz}{dt} + \frac{z}{C} = \mathcal{E}_0 \exp(i\omega t)$$

$$-L\omega^2 z + R i\omega z + \frac{z}{C} = \mathcal{E}_0 \exp(i\omega t)$$
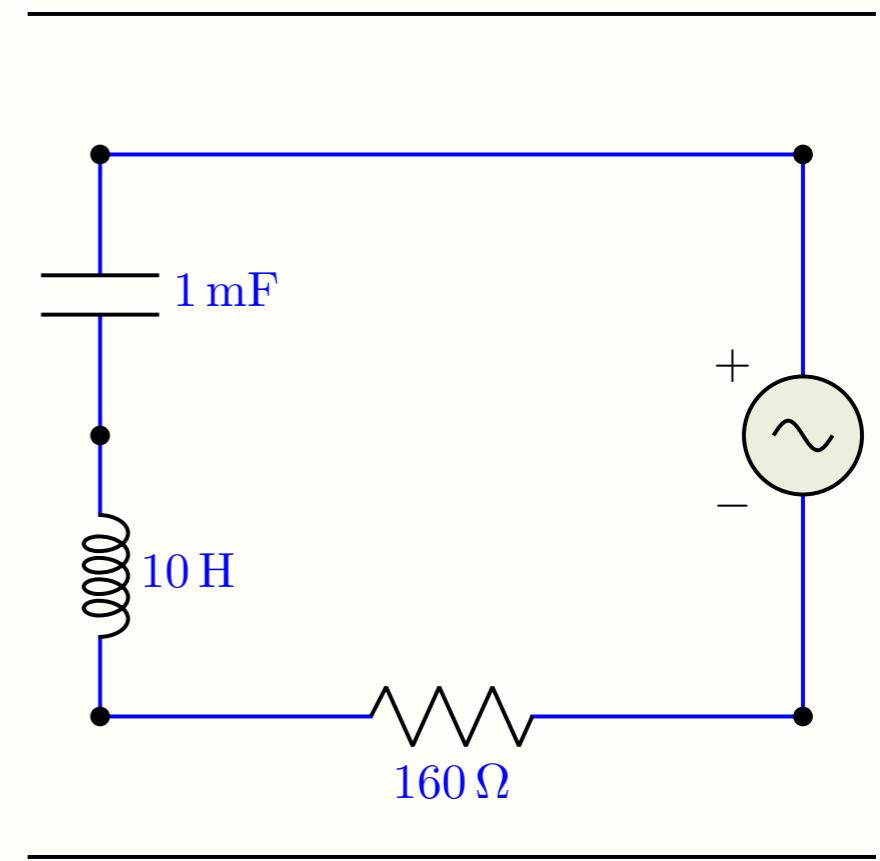
$$u \equiv \frac{dz}{dt} \Rightarrow I = \Re u$$




Circuitos de corrente alternada

Corrente estacionária

$$L \frac{d^2 z}{dt^2} + R \frac{dz}{dt} + \frac{z}{C} = \mathcal{E}_0 \exp(i\omega t)$$

$$-L\omega^2 z + R i\omega z + \frac{z}{C} = \mathcal{E}_0 \exp(i\omega t)$$
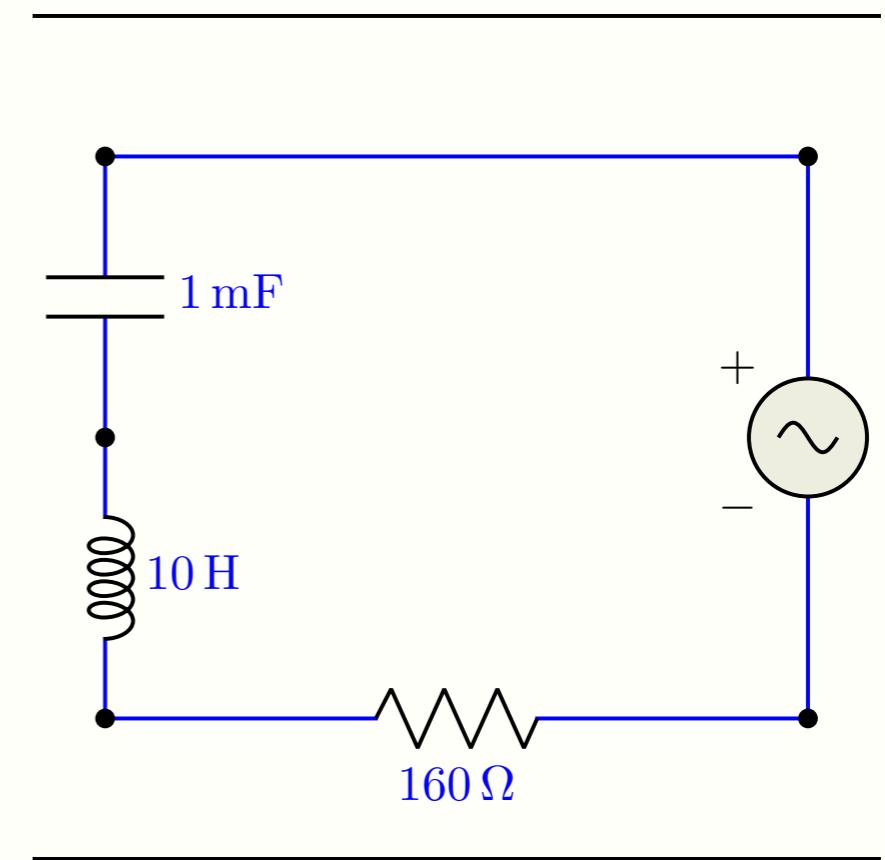
$$u \equiv \frac{dz}{dt} \Rightarrow u = i\omega z$$




Circuitos de corrente alternada

Corrente estacionária

$$L \frac{d^2 z}{dt^2} + R \frac{dz}{dt} + \frac{z}{C} = \mathcal{E}_0 \exp(i\omega t)$$

$$-L\omega^2 z + R i\omega z + \frac{z}{C} = \mathcal{E}_0 \exp(i\omega t)$$
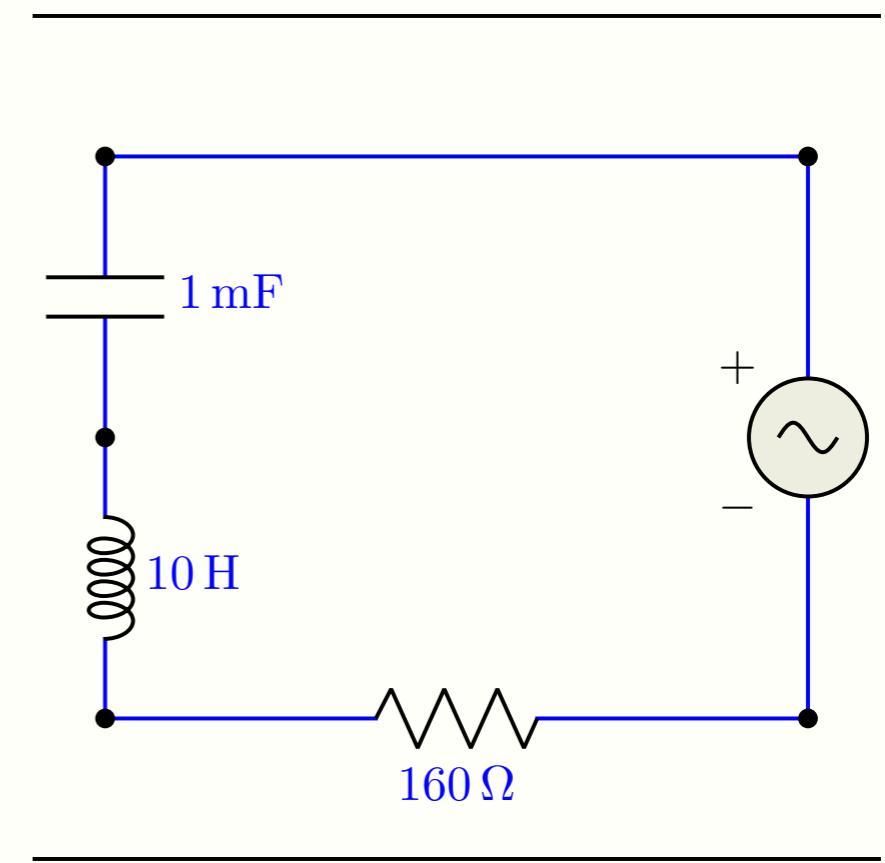
$$u \equiv \frac{dz}{dt} \Rightarrow u = i\omega z$$



Circuitos de corrente alternada


Corrente estacionária

$$L \frac{d^2 z}{dt^2} + R \frac{dz}{dt} + \frac{z}{C} = \mathcal{E}_0 \exp(i\omega t)$$

$$-L\omega^2 z + R i\omega z + \frac{z}{C} = \mathcal{E}_0 \exp(i\omega t)$$

$$u \equiv \frac{dz}{dt} \Rightarrow u = i\omega z$$

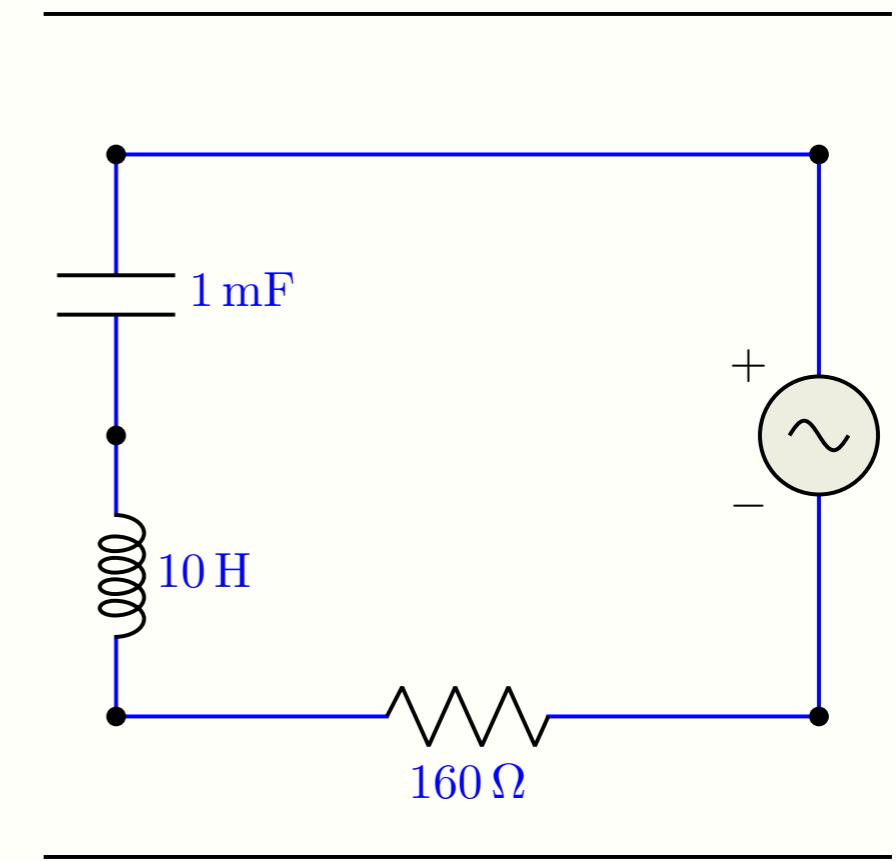
$$i\omega L u + R u + \frac{u}{i\omega C} = \mathcal{E}_0 \exp(i\omega t)$$



$$\left(i\omega L + R + \frac{1}{i\omega C} \right) u = \mathcal{E}_0 \exp(i\omega t)$$

Circuitos de corrente alternada

Corrente estacionária

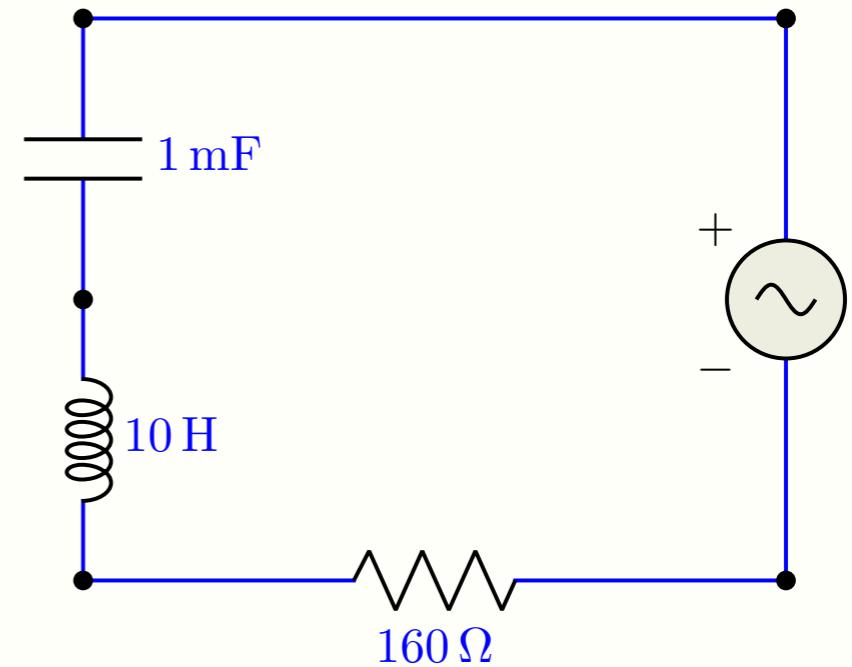

$$\left(i\omega L + R + \frac{1}{i\omega C} \right) u = \mathcal{E}_0 \exp(i\omega t)$$


Circuitos de corrente alternada

Corrente estacionária

Impedância

$$\underbrace{\left(i\omega L + R + \frac{1}{i\omega C} \right)}_Z u = \mathcal{E}_0 \exp(i\omega t)$$

$$\mathcal{E}_0 \exp(i\omega t) = Z u$$

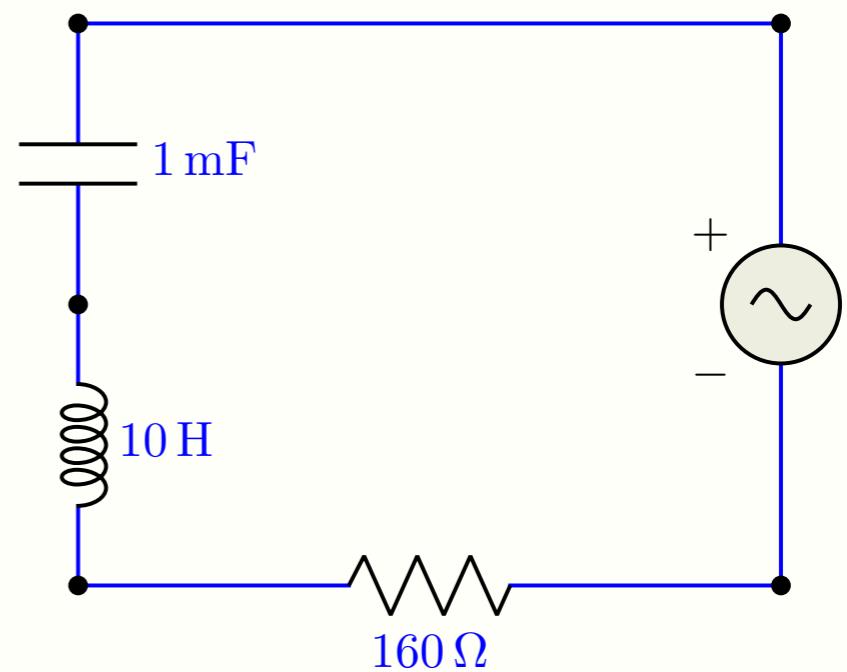

Circuitos de corrente alternada

Corrente estacionária

Impedância


$$\underbrace{\left(i\omega L + R + \frac{1}{i\omega C} \right)}_Z u = \mathcal{E}_0 \exp(i\omega t)$$

$$\mathcal{E}_0 \exp(i\omega t) = Z u$$

$$Z_R = R$$


$$Z_L = i\omega L$$

$$Z_C = \frac{1}{i\omega C}$$

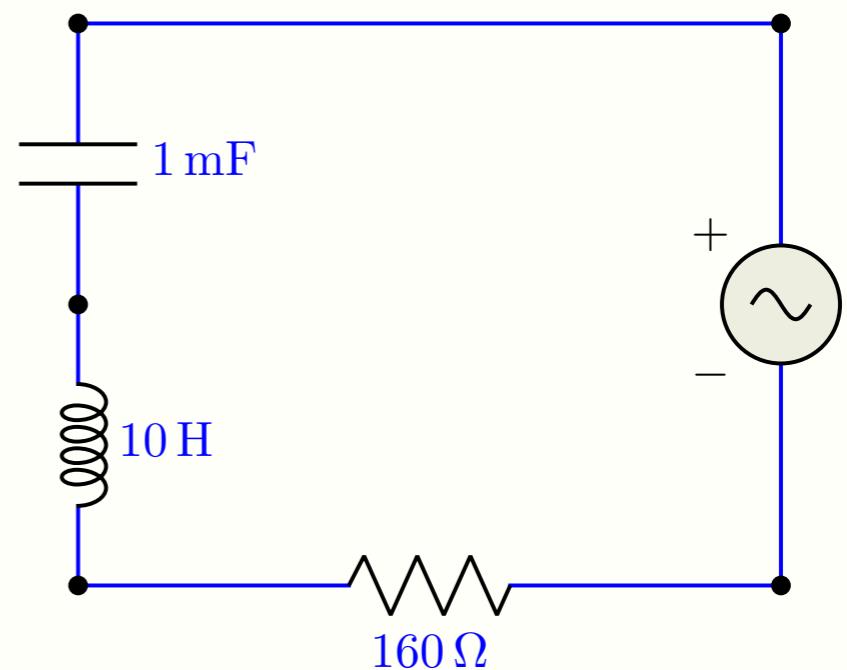

Pratique o que aprendeu

$$\mathcal{E}_0 \exp(i\omega t) = Z u$$

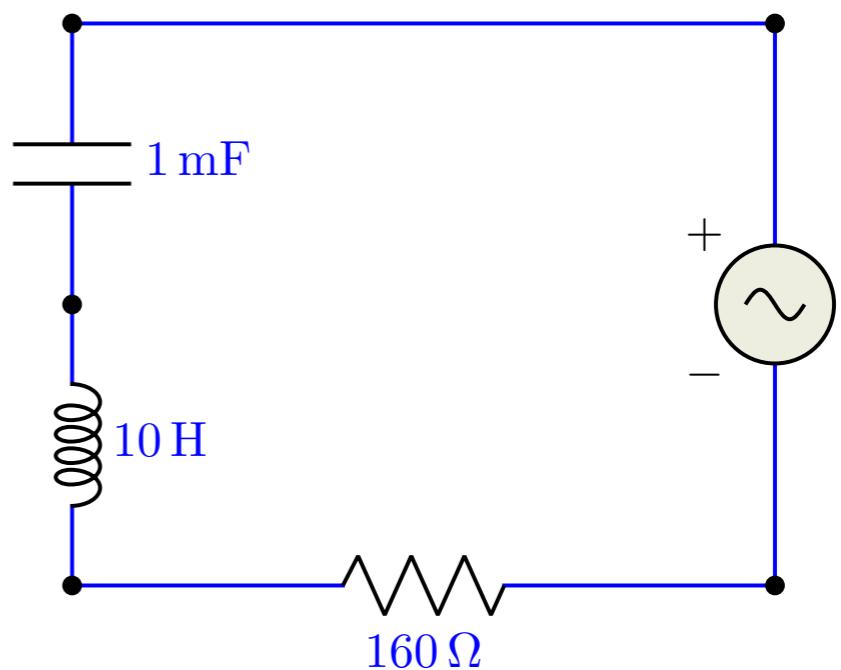

$$Z_R = R$$


$$Z_L = i\omega L$$

$$Z_C = \frac{1}{i\omega C}$$

Pratique o que aprendeu

$$\mathcal{E}_0 \exp(i\omega t) = Z u$$
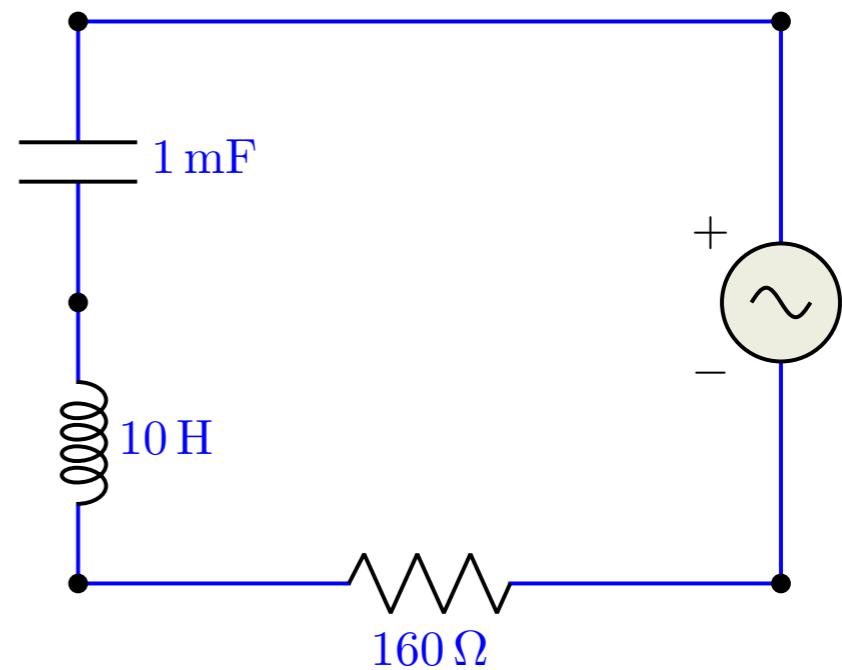
$$\left(10i\omega + 160 - i\frac{10^3}{\omega} \right) u = \mathcal{E}_0 \exp(i\omega t)$$



$$Z_R = R$$

$$Z_L = i\omega L$$

$$Z_C = \frac{1}{i\omega C}$$


Pratique o que aprendeu

$$\mathcal{E}_0 \exp(i\omega t) = Z u$$

$$\left(10i\omega + 160 - i\frac{10^3}{\omega} \right) u = \mathcal{E}_0 \exp(i\omega t)$$

$$\omega = 10 \quad \mathcal{E}_0 = 1.6$$

$$160u = 1.6 \exp(10it)$$

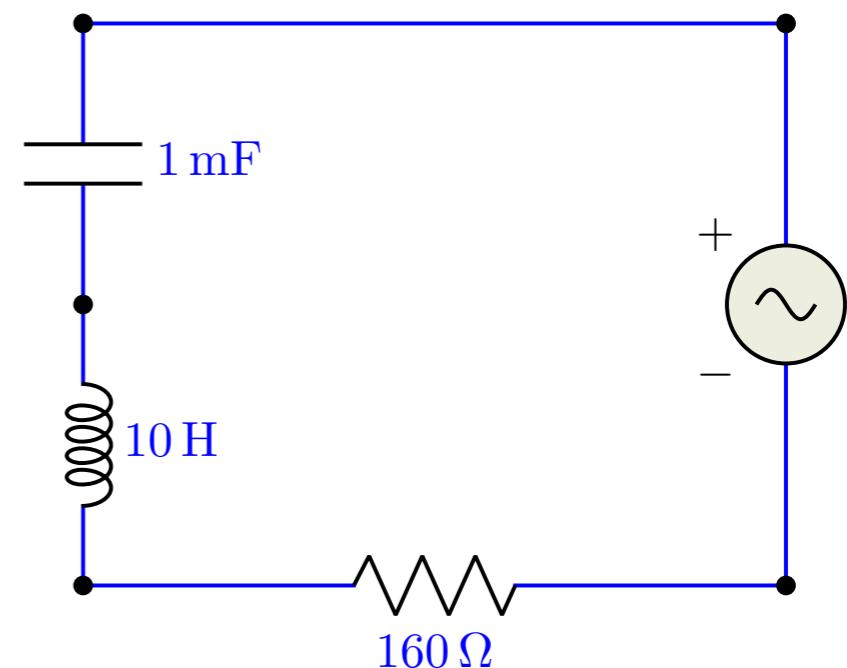

$$Z_R = R$$

$$Z_L = i\omega L$$

$$Z_C = \frac{1}{i\omega C}$$

Pratique o que aprendeu


$$\mathcal{E}_0 \exp(i\omega t) = Z u$$

$$\left(10i\omega + 160 - i\frac{10^3}{\omega} \right) u = \mathcal{E}_0 \exp(i\omega t)$$

$$\omega = 10 \quad \mathcal{E}_0 = 1.6$$

$$160u = 1.6 \exp(10it)$$

$$u = 10^{-2} \exp(10it)$$

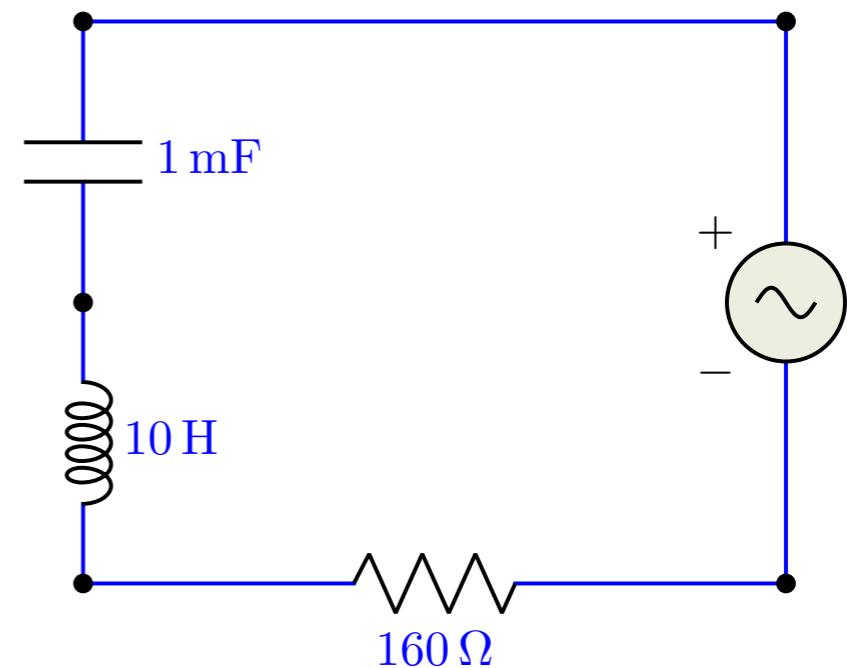

$$Z_R = R$$

$$Z_L = i\omega L$$

$$Z_C = \frac{1}{i\omega C}$$

Pratique o que aprendeu

$$\mathcal{E}_0 \exp(i\omega t) = Z u$$


$$\left(10i\omega + 160 - i\frac{10^3}{\omega} \right) u = \mathcal{E}_0 \exp(i\omega t)$$

$$\omega = 10 \quad \mathcal{E}_0 = 1.6$$

$$160u = 1.6 \exp(10it)$$

$$u = 10^{-2} \exp(10it)$$

$$I = 10^{-2} \cos(10t)$$

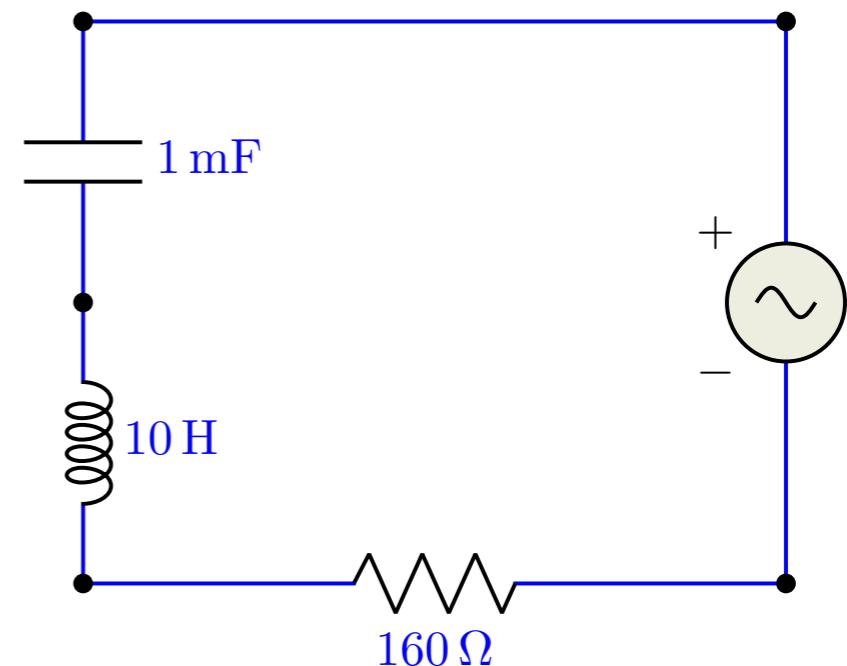

$$Z_R = R$$

$$Z_L = i\omega L$$

$$Z_C = \frac{1}{i\omega C}$$