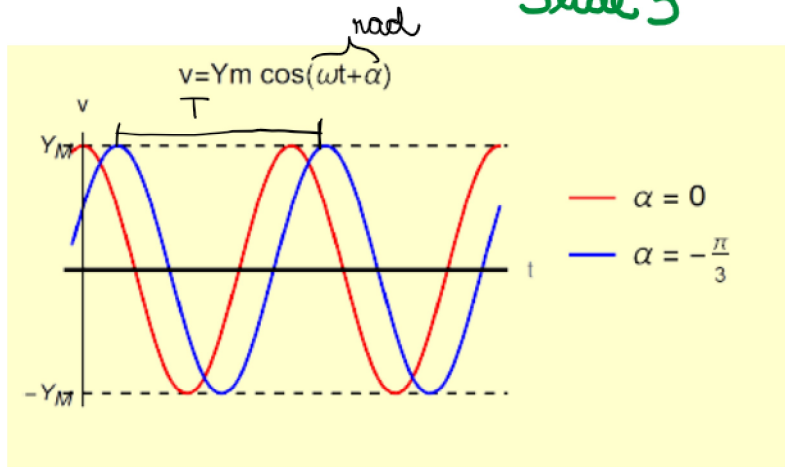


### Slide 3



Brasil:  $T = 16,66667 \text{ ms}$

$$f = \frac{1}{T} = 60 \text{ Hz}$$

$$\omega = 2\pi 60 \approx 376,99 \text{ rad/s}$$

### Slide 4

$$v(t) = \sqrt{2} V_m \cos(\omega t + \theta)$$

$$\vec{V} = V_m \cos(\omega t + \theta) - V_m \sin(\omega t + \theta) \cdot j$$

$$\sqrt{2} V_m e^{j(\omega t + \theta)} = \sqrt{2} V_m e^{j\omega t} e^{j\theta}$$

fasor

$$\vec{V} = \frac{V_m}{\sqrt{2}} e^{j\theta}$$

$i = j = \sqrt{-1}$


Slide 8 indutor,  $L$  (henry, H) = reator

$$\frac{V_m}{\sqrt{2}} \angle \theta \quad \text{ou} \quad \frac{V_m}{\sqrt{2}} e^{j\theta} \quad \text{ou} \quad \frac{V_m}{\sqrt{2}} e^{i\theta}$$

$$\begin{array}{ccc} \text{fluxo} (t) & = & L i(t) \\ \text{magnético} & \uparrow & \leftarrow \text{corrente} \\ (\text{Wb}) & \text{ind} & \end{array}$$

$$\left. \begin{array}{l} v_{\text{ind}} \\ e_{\text{ind}} \end{array} \right\} = \frac{d \text{fluxo}}{dt} \rightarrow v(t) = \frac{d}{dt} (L i(t)) = L \frac{di(t)}{dt}$$

# Slide 8 (última linha)

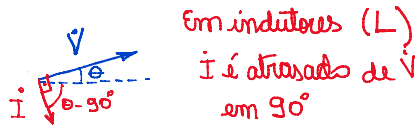

$$j = \sqrt{-1}$$

$$j^2 = -1$$

$$j^4 = 1$$

$$v = V \angle \theta \left[ \frac{V_M}{\sqrt{2}} \angle \theta \right] = V \cos \theta + j V \sin \theta$$


$$i = i \angle (\theta - 90^\circ) = \frac{V_M}{\omega L} \cos(\theta - 90^\circ) + j \frac{V_M}{\omega L} \sin(\theta - 90^\circ)$$

$$= \frac{V_M}{\omega L} \sin \theta + j \frac{V_M}{\omega L} (\sin \theta \cos(90^\circ) - \cos \theta \sin 90^\circ)$$

$$= \frac{V_M}{\omega L} \sin \theta + j \frac{V_M}{\omega L} (-\cos \theta)$$

$$= \frac{V_M}{\omega L} \sin \theta j^4 + j j^2 \frac{V_M}{\omega L} \cos \theta = \frac{V_M}{\omega L} j^3 (\cos \theta + j \sin \theta) = \frac{j^4}{j} \frac{1}{\omega L} [V_M \cos \theta + j V_M \sin \theta]$$
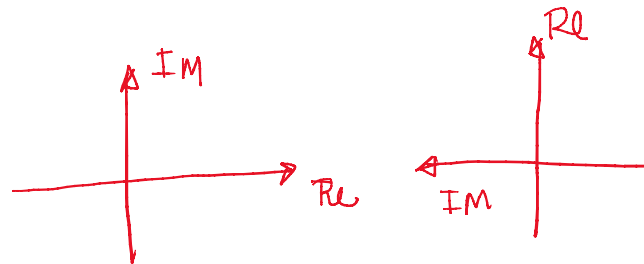
$$= \frac{1}{j \omega L} [V_M \angle \theta]$$



Real puro  $\rightarrow \bar{z} = a = a \angle 0^\circ$   
 Imag puro  $\rightarrow \bar{z} = j b = b \angle 90^\circ$   
 $\bar{z} = -j b = b \angle -90^\circ$

$$R \rightarrow \frac{V}{I} = R$$

$$L \rightarrow \frac{V}{I} = j \omega L$$

$$C \rightarrow \frac{V}{I} = \frac{-j}{\omega C}$$

Genericamente

$$\frac{V}{I} = \bar{Z} : \text{impedância}$$

$$\omega L = X_L : \text{reatância indutiva}$$

$$\frac{1}{\omega C} = X_C : \text{reatância capacitiva}$$

unidade  
 $\Omega$  (ohm)

ex: L tem  $j 20 \Omega$  ( $\bar{Z}$ )  
 ou tem  $20 \Omega$  ( $X_L, \bar{Z} = j X_L$ )  
 $0,15 H$  ( $L, \bar{Z} = j 2\pi 60 \cdot 0,15 \Omega$ )