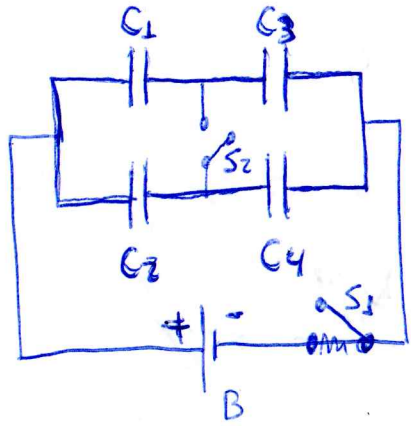


Cap. 25 Ex 27



12V

$$C_1 = 1,0 \mu\text{F}$$

$$C_2 = 2,0 \mu\text{F}$$


$$C_3 = 3,0 \mu\text{F}$$

$$C_4 = 4,0 \mu\text{F}$$

$S_1$  fechado  $q_1, q_2, q_3, q_4$ ?

$S_1$  e  $S_2$  fechado  $q_1, q_2, q_3, q_4$ ?

Quando  $S_1$  fechado

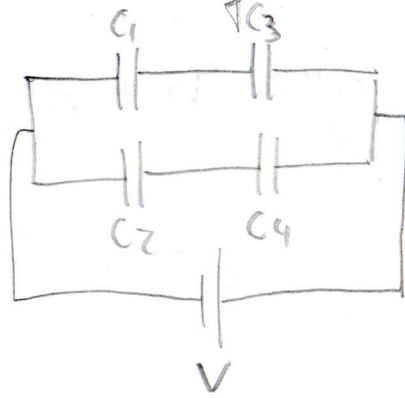

$C_1$  série com  $C_3$ , logo

$$q_1 = q_3$$

$$q_1 = C_1 V_1, \quad q_3 = C_3 V_3$$

$$V_1 + V_3 = V$$

$$\frac{q_1}{C_1} + \frac{q_3}{C_3} = V$$

$$\frac{q_1}{C_1} + \frac{q_1}{C_3} = V$$

$$\frac{q_1(C_1 + C_3)}{C_1 C_3} = V$$


$$q_1 = \frac{C_1 C_3 V}{C_1 + C_3}$$

$$q_1 = \frac{(1 \mu\text{F})(3 \mu\text{F})(12 \text{V})}{(1 \mu\text{F}) + (3 \mu\text{F})}$$

$$q_1 = q_3 = q_2 = q_4 = \frac{q_1}{2} = 9 \mu\text{C}$$

$$q_2 = \frac{C_2 C_4 V}{C_2 + C_4} = \frac{2 \mu\text{F} \cdot 4 \mu\text{F} \cdot 12 \text{V}}{2 \mu\text{F} + 4 \mu\text{F}} = 16 \mu\text{C} = q_4$$

Quando  $S_1$  e  $S_2$  fechados.

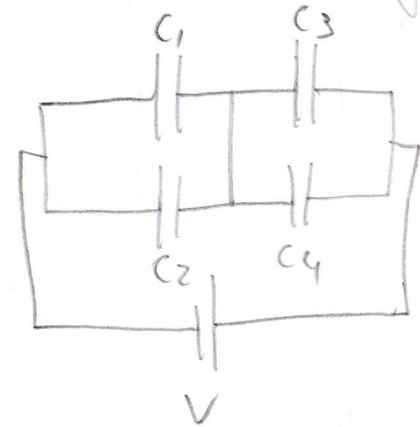

$C_1 // C_2$  e  $C_3 // C_4$

$$q_1 = C_1 V'$$

$$q_3 = C_3 V''$$


$$q_2 = C_2 V'$$

$$q_4 = C_4 V''$$

Portanto temos uma capacitância equivalente entre  $C_1$  e  $C_2$  e  $C_3$  e  $C_4$

$$C' = C_1 + C_2 \quad C'' = C_3 + C_4$$

O circuito pode ser reduzido a:

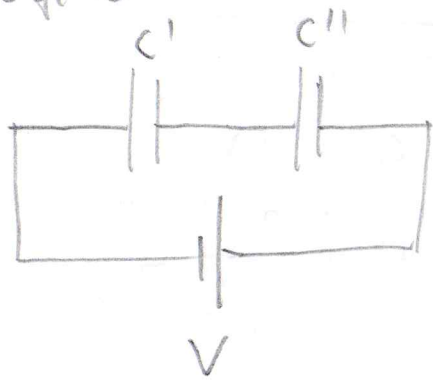

$C'$  série  $C''$

$$V' + V'' = V$$

$$\frac{q'}{C'} + \frac{q''}{C''} = V$$

Onde  $q' = q_1 + q_2$

$$q'' = q_3 + q_4$$

$$\frac{q_1 + q_2}{C'} + \frac{q_3 + q_4}{C''} = V$$

Mas  $q' = q''$ , logo

$$\frac{q_1 + q_2}{C'} + \frac{q_1 + q_2}{C''} = V$$

$$\frac{C_1 V' + C_2 V'}{C_1 + C_2} + \frac{C_3 V' + C_4 V'}{C_3 + C_4} = V$$

$$V' + V' \frac{(C_1 + C_2)}{C_3 + C_4} = V$$

$$\frac{C_3 V' + C_4 V' + C_1 V' + C_2 V'}{C_3 + C_4} = V$$

$$V' = \frac{(C_3 + C_4) V}{C_1 + C_2 + C_3 + C_4}$$

$$V' = \frac{(3 \mu\text{F} + 4 \mu\text{F}) 12 \text{V}}{1 \mu\text{F} + 2 \mu\text{F} + 3 \mu\text{F} + 4 \mu\text{F}}$$

$$V' = 8,4 \text{V}$$

$$q_1 = C_1 V' = 1 \mu\text{F} \cdot 8,4 \text{V}$$

$$q_1 = \underline{8,4 \mu\text{C}}$$

$$q_2 = C_2 V' = 2 \mu\text{F} \cdot 8,4 \text{V}$$

$$q_2 = \underline{16,8 \mu\text{C}}$$

$$q_3 = C_3 V'' = C_3 (V - V')$$

$$q_3 = 3 \mu\text{F} (12 - 8,4)$$

$$q_3 = 3 \mu\text{F} \cdot 3,6 \text{V} = \underline{10,8 \mu\text{C}}$$

$$q_4 = 4 \mu\text{F} \cdot 3,6 \text{V} = \underline{14,4 \mu\text{C}}$$