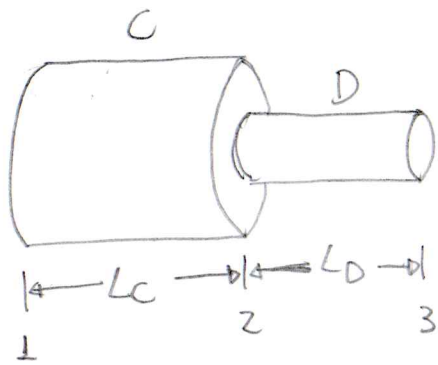


Cap 26 - Ex 53



$$L_C = L_D = 1,0 \text{ m}$$

$$\rho_C = 2 \times 10^{-6} \Omega \cdot \text{m}$$

$$d_C = 1,0 \text{ mm}$$

$$\rho_D = 1 \times 10^{-6} \Omega \cdot \text{m}$$

$$d_D = 0,5 \text{ mm}$$

$$i = 2 \text{ A}$$

- a) V entre 1 e 2
 b) V " 2 e 3
 c) P " 1 e 2
 d) P " 2 e 3

a) A diferença de potencial

V pode ser calculada por

$$V = R \cdot i$$

$$\therefore V_C = R_C \cdot i$$

$$R_C = \rho_C \cdot \frac{L_C}{A_C} = \rho_C \frac{L_C}{\pi r_C^2}$$

$$R_C = 2 \times 10^{-6} \Omega \cdot \text{m} \cdot \frac{1,0 \text{ m}}{\pi (0,0005 \text{ m})^2}$$

$$R_C = 2,546 \Omega$$

$$V_C = 2,546 \cdot \Omega \cdot 2 \cdot \text{A}$$

$$V_C \approx 5,093 \text{ V}$$

b) $V_D = R_D \cdot i$

$$R_D = \rho_D \cdot \frac{L_D}{\pi r_D^2} = \frac{1 \times 10^{-6} \cdot 1}{\pi (0,00025)^2}$$

$$R_D = 5,093 \Omega$$

$$V_D = 5,09 \times 2 \approx 10,2 \text{ V}$$

c) $P = iV = i^2 R = \frac{V^2}{R}$

$$P_C = 2 \cdot 5,093 \approx 10,2 \text{ W}$$

d) $P_D = 2 \cdot 10,2 \approx 20,4 \text{ W}$