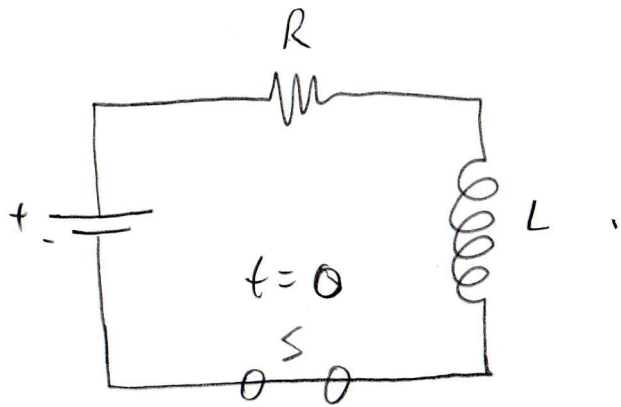


Cap 30 Ex 51



Valor de τ_L p/ 0,1% de i final.

Circuito de carga de Van editado:

$$i = \frac{\mathcal{E}}{R} \left(1 - e^{-t/\tau_L} \right)$$

$\underbrace{\hspace{2cm}}_{I_0}$

$$\text{Onde } \tau_L = \frac{L}{R}$$

Queremos calcular o tempo para que a corrente chegue ao valor 0,999 de I_0 (0,1%)

Partindo:

$$0,999 I_0 = I_0 (1 - e^{-t/\tau_L})$$

$$0,999 = 1 - e^{-t/\tau_L}$$

$$0,001 = e^{-t/\tau_L}$$

Aplicando \ln nos dois:

$$\ln(0,001) = \frac{-t}{\tau_L}$$

$$-6,907 = \frac{-t}{\tau_L}$$

$$t \approx 6,91 \tau_L$$

