

PSI3262 – Fundamentos de Circuitos Eletrônicos Digitais e Analógicos

Solução da Lista 7: Redes de 1ª Ordem

Redes de 1ª Ordem

$$1 - \text{Temos que: } \begin{cases} -4e^{-4t} + 4e^{-4t} + 20 = f_1(t) \\ -4e^{-4t} + 10e^{-10t} + 4e^{-4t} - 4e^{-10t} = f_2(t) \end{cases}$$

$$\rightarrow f_1(t) = 20 \quad f_2(2) = 6e^{-10t}$$

$$2 - i(t) = i_0 e^{-t/\tau} \rightarrow i_0 = 10 \text{ A} \quad \tau = 0,2 \text{ s} = 200 \text{ ms}$$

$$v(t) = Ri_0 e^{-t/\tau} \rightarrow R = \frac{400}{10} = 40\Omega \quad \tau = \frac{L}{R} \rightarrow L = 40 \times 0,2 = 8 \text{ H}$$

$$\text{Energia inicial: } \frac{1}{2} Li_0^2 = \frac{1}{2} \times 8 \times 100 = 400 \text{ J}$$

$$\text{Em } t = 50 \text{ ms} \rightarrow i = 7,788 \text{ A} \rightarrow W_L = \frac{1}{2} Li^2 = 242,61 \text{ J}$$

$$\text{Energia dissipada: } 400 - 242,61 = 157,39 \text{ J}$$

$$3 - a) i_L(0_+) = i_L(0_-) = 0 \quad (\text{admitido})$$

$$i_L(\infty) = I$$



$$i_L(t) = I(1 - e^{-t/\tau})$$

$$\tau = L/R$$


$$v(0_+) = RI$$

$$v(\infty) = 0$$

$$\rightarrow v(t) = RI e^{-t/\tau}$$

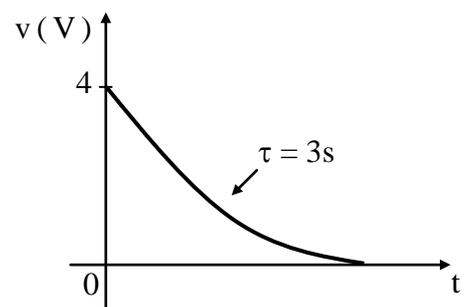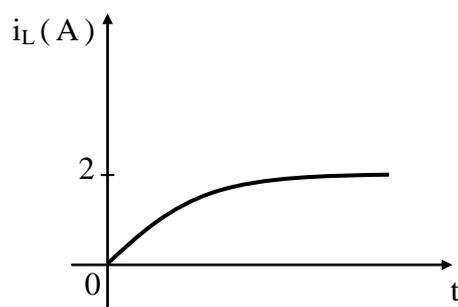

4 -

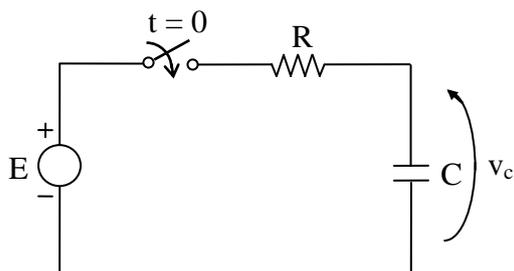


$$\begin{cases} v_c(0_+) = v_c(0_-) = 0 \quad (\text{admitido}) \\ v_c(\infty) = E \end{cases} \rightarrow v_c(t) = E(1 - e^{-t/\tau})$$

$$\tau = RC$$


$$5 - \begin{cases} i(0_+) = i(0_-) = \frac{20}{4} = 5\text{A} \\ i(\infty) = \frac{20}{1} = 20\text{A} \end{cases}$$

$$\begin{cases} v(0_-) = 0 \\ v(0_+) = 20 - (5 \times 1) = 15\text{V} \\ v(\infty) = 0 \end{cases}$$
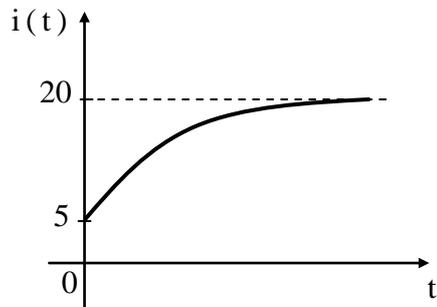
$$t \geq 0 \quad t = \frac{L}{R} = \frac{80 \times 10^{-3}}{1} = 80 \text{ ms}$$


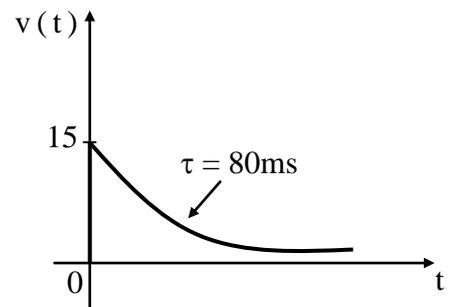
$$i(t) = (20 - 15e^{-12,5t}) \text{ (A)} \\ t \geq 0$$



$$v(t) = 15 e^{-12,5t} \text{ (V)} \\ t \geq 0$$