

ZAB0474 – Física Geral e Experimental III

Experimento 1 - Resistores

Tabela 1

	I (mA)	V_{BA} (V)	V_{CB} (V)	V_{DA} (V)
Circuito I	3,93	2,41	0,58	3,04
Circuito II	4,80	X	2,98	X
Circuito III	18,9	X	2,98	X

Tabela 2

	I (mA)	V_{BA} (V)	V_{CB} (V)	V_{DA} (V)
Circuito I	0,86	3,02	0,54	2,47
Circuito II	3,58	3,02	0,57	2,45

Tabela 3

	I (mA)	V_{BA} (V)	V_{CB} (V)	V_{DA} (V)
Circuito I	4,49	3,02	0,53	2,49