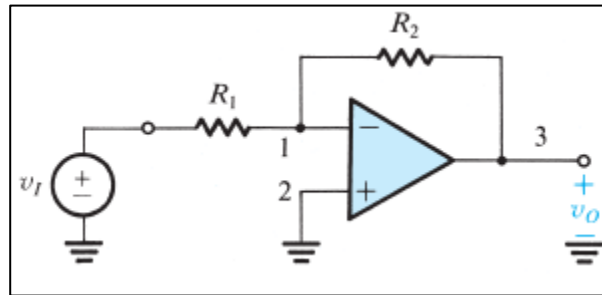


# **Inverting Amplifier**

## The Inverting Configuration


- 1 Op amps are not used alone; rather, the op amp is connected to passive components in a feedback circuit. There are two such basic circuit configurations employing an op amp and two resistors: the inverting configuration and the noninverting configuration.



- 2 Resistor  $R_2$  is connected from the output terminal of the op amp, terminal 3, back to the input terminal, terminal 1.

We speak of  $R_2$  as applying **negative feedback**.

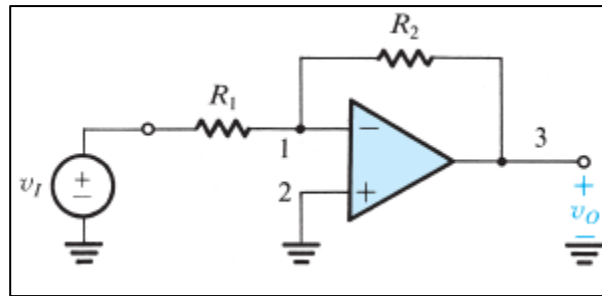If  $R_2$  were connected between terminals 3 and 2 we would have called this **positive feedback**.




- 3 We will do so assuming the op amp to be ideal. The gain  $A$  is very large (ideally infinite).

$$v_o = A(v_2 - v_1) \longrightarrow v_2 - v_1 = \frac{v_o}{A} = 0 \longrightarrow v_2 = v_1$$

- 4 It follows that the voltage at the inverting input terminal ( $v_1$ ) is given by  $v_1 = v_2$ . That is, because the gain  $A$  approaches infinity, the voltage  $v_1$  approaches and ideally equals  $v_2$ . We speak of this as the **two input terminals “tracking each other in potential.”** We also speak of a **“virtual short circuit”** that exists between the two input terminals. Here the word *virtual* should be emphasized, and one should *not* make the mistake of physically shorting terminals 1 and 2 together while analyzing a circuit. **A virtual short circuit means that whatever voltage is at 2 will automatically appear at 1 because of the infinite gain  $A$ .** But terminal 2 happens to be connected to ground; thus  $v_2 = 0$  and  $v_1 = 0$ . We speak of terminal 1 as being a **virtual ground**— that is, **having zero voltage but not physically connected to ground.**

$$Ganho = G = \frac{v_o}{v_I}$$

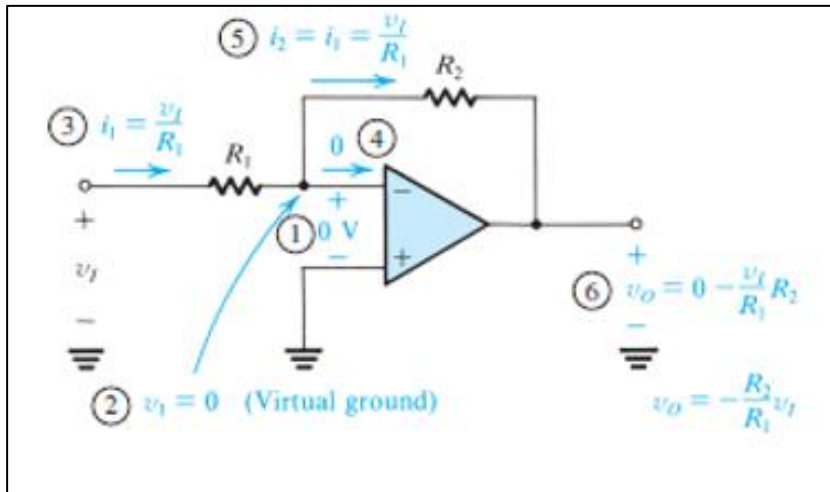

$$i_1 = \frac{v_I - v_1}{R_1} = \frac{v_i - 0}{R_1} = \frac{v_I}{R_1} \quad (1)$$

Where will this current go? It cannot go into the op amp, since the ideal op amp has an infinite input impedance and hence draws zero current. **It follows that  $i_1$  will have to flow through  $R_2$  to the low-impedance terminal 3.**

$$v_O = v_i - i_1 R_2 = 0 - \frac{v_I R_2}{R_1} \quad (2)$$

(1) e (2)  $\rightarrow$


$$G = \frac{v_O}{v_I} = -\frac{R_2}{R_1}$$

$$G = \frac{v_O}{v_I} = -\frac{R_2}{R_1}$$

We note that:

- 5.1 The fact that **the closed-loop gain depends entirely on external passive components (resistors  $R_1$  and  $R_2$ )** is very significant. It means that we can make the closed-loop gain as accurate as we want by selecting passive components of appropriate accuracy.
- 5.2 We started out with an amplifier having very large gain  $A$ , and through **applying negative feedback we have obtained a closed-loop gain that is much smaller than  $A$**  but is stable and predictable. That is, we are trading gain for accuracy.

## Effect of Finite Open-Loop Gain

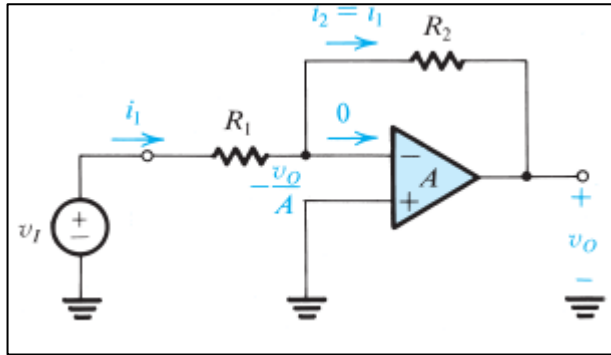

Analysis of the inverting configuration taking into account the finite open-loop gain of the op amp.

- 1 If we denote the output voltage  $v_o$  then the voltage between the two input terminals of the op amp will be  $v_o/A$ . Since the positive input terminal is grounded, the voltage at the negative input terminal must be  $-v_o/A$  (out of phase with respect the output). The current  $i_1$  through  $R_1$  can now be found:


$$i_1 = \frac{v_I - (-v_o/A)}{R_1} = \frac{v_I + v_o/A}{R_1} \quad (3)$$

- 2 The infinite input impedance of the op amp forces the current  $i_1$  to flow entirely through  $R_2$ . The output voltage  $v_o$  can thus be determined from:

$$v_o = -\frac{v_o}{A} - i_1 R_2 = -\frac{v_o}{A} - \left( \frac{v_I + v_o/A}{R_1} \right) R_2 \quad (4)$$

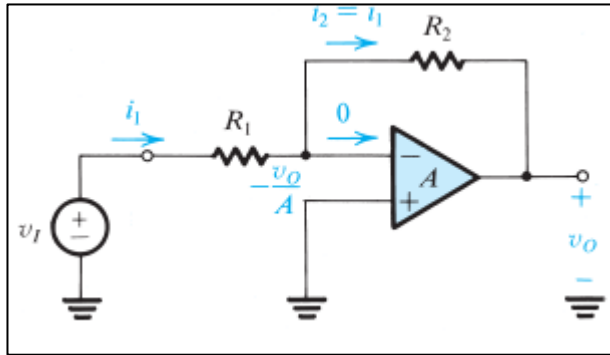(3) e (4)  $\longrightarrow$


$$G = -\frac{v_o}{v_I} = \frac{-R_2/R_1}{1 + \frac{(1+R_2/R_1)}{A}}$$



$$G = \frac{v_o}{v_i} = \frac{-R_2/R_1}{1 + (1 + R_2R_1)/A}$$

- 3 We note that:
- 3.1 As  $A$  approaches  $\infty$ ,  $G$  approaches the ideal value  $-R_2/R_1$ .
- 3.2 Also, we see that as  $A$  approaches  $\infty$ , the voltage at the inverting input ( $-v_o/A$ ) **terminal approaches zero**. This is the virtual-ground assumption we used in our earlier analysis when the op amp was assumed to be ideal.
- 3.3 Finally, note that the gain equation in fact indicates that **to minimize the dependence of the closed-loop gain  $G$  on the value of the open-loop gain  $A$ , we should make  $(1 + R_2R_1) \ll A$** .

## Input Resistance

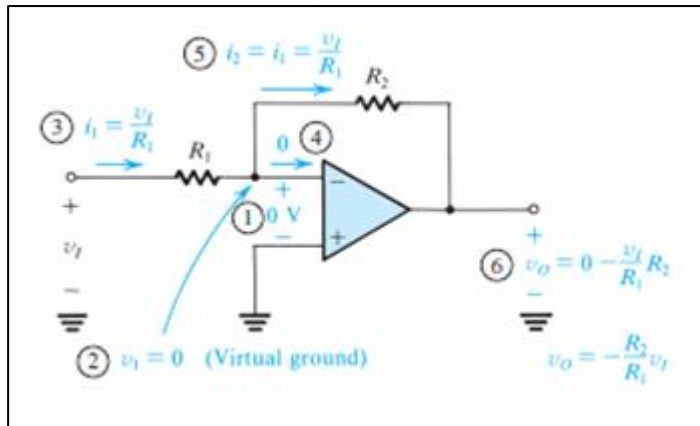

$$R_i = \frac{v_I}{i_I} = \frac{v_I}{v_I/R_1}$$



$$R_i = R_1$$

1


**Amplifier input resistance forms a voltage divider with the resistance of the source that feeds the amplifier. Thus, to avoid the loss of signal strength, voltage amplifiers are required to have high input resistance.**

In the case of the inverting op-amp configuration we are studying, to make  $R_i$  high we should select a high value for  $R_1$ . However, if the required gain is also high, then  $R_2$  could become impractically large (e.g., greater than a few megohms).

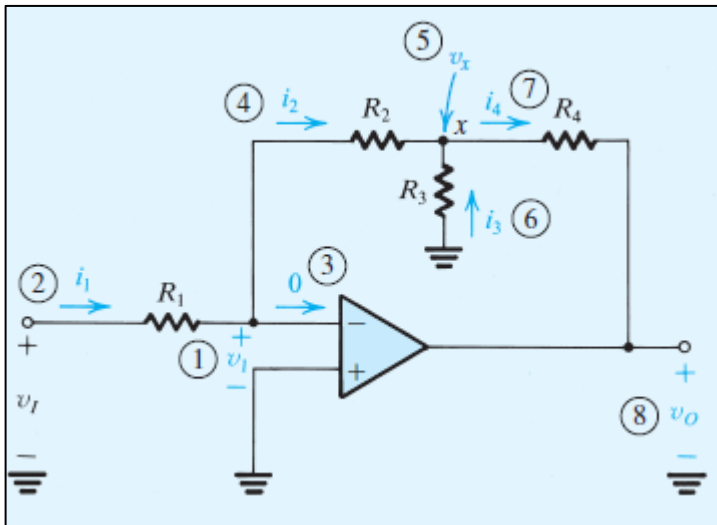**We may conclude that the inverting configuration suffers from a low input resistance.**



A solution to problem of low input resistance is discussed in this exercise !




Assuming the op amp to be ideal, derive an expression for the closed-loop gain of the circuit shown.

**Use this circuit to design an inverting amplifier with a gain of 100 and an input resistance of 1 M $\Omega$ .**

**Assume that for practical reasons it is required not to use resistors greater than 1 M $\Omega$ .**

$$Ganho = G = \frac{v_S}{v_I}$$

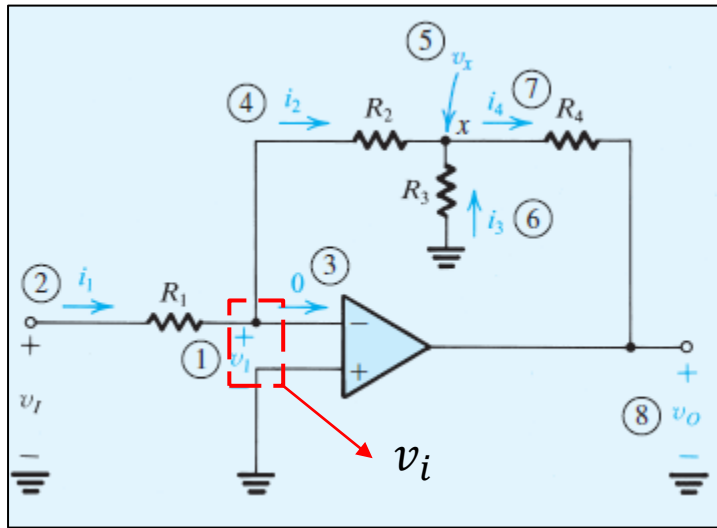

1 The analysis begins at the inverting input terminal of the op amp, where the voltage is:


$$v_i = 0 \quad (\text{virtual ground})$$

2 Knowing  $v_i$  we can determine the current  $i_1$  as follows:

$$i_1 = \frac{v_I - v_i}{R_1} = \frac{v_I - 0}{R_1} = \frac{v_I}{R_1}$$

3 Since zero current flows into the inverting input terminal, all of  $i_1$  will flow through  $R_2$ , and thus:

$$i_2 = i_1 = \frac{v_I}{R_1}$$

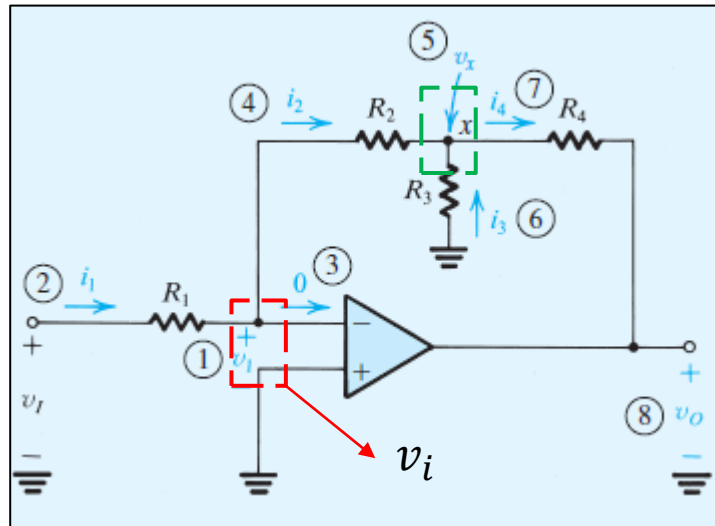

4 Now we can determine the voltage at **node x**:


$$v_x = v_i - i_2 R_2 = 0 - \frac{v_I}{R_1} R_2 = \frac{v_I}{R_1} R_2$$

5 This in turn enables us to find the current  $i_3$ :

$$i_3 = \frac{0 - v_x}{R_3} = \frac{R_2}{R_1 R_3} v_I$$

6 Next, a node equation at  $x$  yields  $i_4$ :
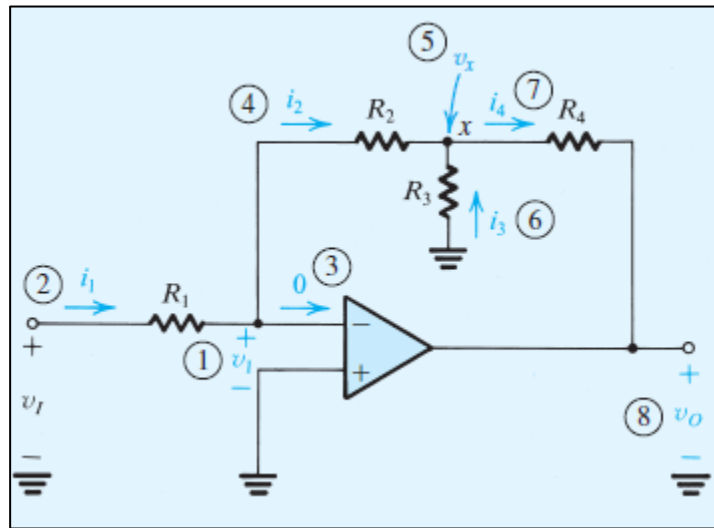
$$i_4 = i_2 + i_3 = \frac{v_I}{R_1} + \frac{R_2}{R_1 R_3} v_I$$



7 Finally, we can determine  $v_O$ :

$$v_O = v_x - i_4 R_4 = -\frac{R_2}{R_1} v_I - \left( \frac{v_I}{R_1} + \frac{R_2}{R_1 R_3} v_I \right) R_4$$

$$\rightarrow \frac{v_O}{v_I} = -\left[ \frac{R_2}{R_1} + \frac{R_4}{R_1} \left( 1 + \frac{R_2}{R_3} \right) \right] \rightarrow G = \frac{v_O}{v_I} = -\frac{R_2}{R_1} \left( 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right)$$

$$G = \frac{v_0}{v_I} = -\frac{R_2}{R_1} \left( 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right)$$

8


Now, since an input resistance of 1 M $\Omega$  is required, we select  $R_1 = 1 \text{ M}\Omega$ . Then, with the limitation of using resistors no greater than 1 M $\Omega$ , the maximum value possible for the first factor in the gain expression is 1 and is obtained by selecting  $R_2 = 1 \text{ M}\Omega$ .

To obtain a gain of -100,  $R_3$  and  $R_4$  must be selected so that the second factor in the gain expression is 100.

If we select the maximum allowed (in this example) value of 1 M $\Omega$  for  $R_4$ , then the required value of  $R_3$  can be calculated to be 10.2 k $\Omega$ .

**Thus this circuit utilizes three 1M $\Omega$  resistors and a 10.2k $\Omega$  resistor.**

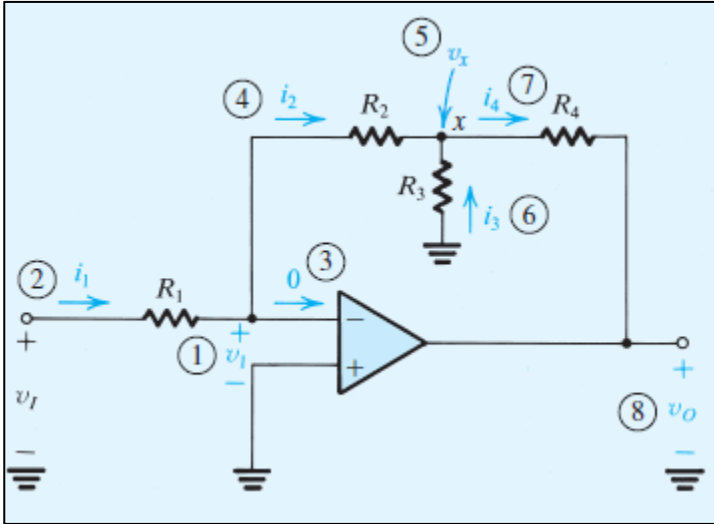**In comparison, if the inverting configuration were used with  $R_1 = 1 \text{ M}\Omega$  we would have required a feedback resistor of 100 M $\Omega$ , an impractically large value !**




$$\left\{ \begin{array}{l} i_3 R_3 = R_2 i_I \\ i_2 = i_I \\ i_4 = i_2 + i_3 \end{array} \right.$$

$$\rightarrow i_4 = \left( 1 + \frac{R_2}{R_3} \right) i_I$$


**$i_4$  não depende de  $R_4$  !**

## Output Resistance

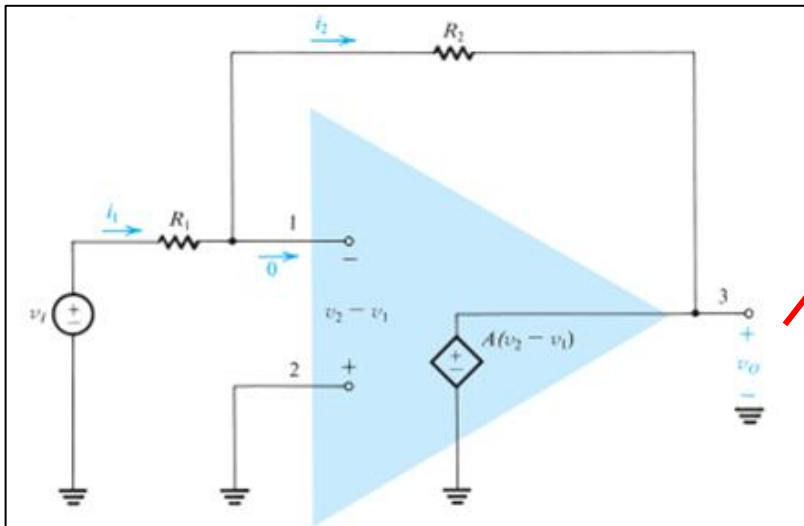

Since the output of the inverting configuration is taken at the terminals of the **ideal voltage source**  $A(v_2 - v_1)$ , it follows that the output resistance of the closed-loop amplifier is zero.

## The Weighted Summer

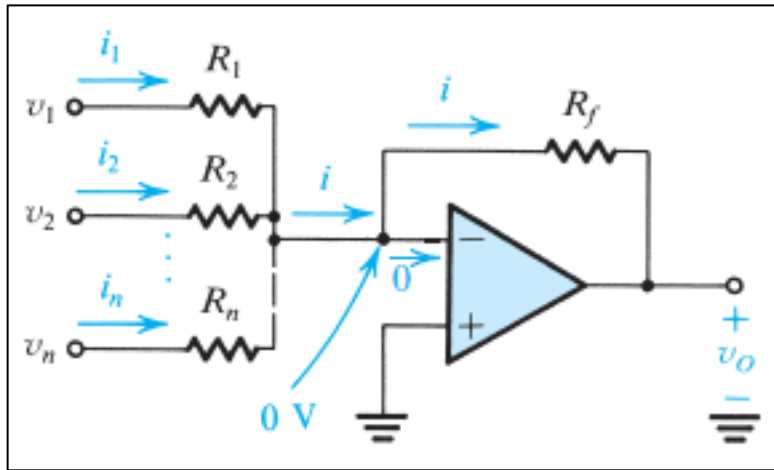

$$i_1 = \frac{v_1}{R_1}$$

$$i_2 = \frac{v_2}{R_2}$$

$$\dots i_n = \frac{v_n}{R_n}$$

$$i = i_1 + i_2 + \dots + i_n$$

$$v_o = 0 - iR_f$$

$$v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right)$$


1

That is, the output voltage is a weighted sum of the input signals  $v_1, v_2, \dots, v_n$ . This circuit is therefore called a **weighted summer**. Note that each summing coefficient may be independently adjusted by adjusting the corresponding “feed-in” resistor ( $R_1$  to  $R_n$ ). This nice property, which greatly simplifies circuit adjustment, is a direct consequence of the virtual ground that exists at the inverting op-amp terminal.



2

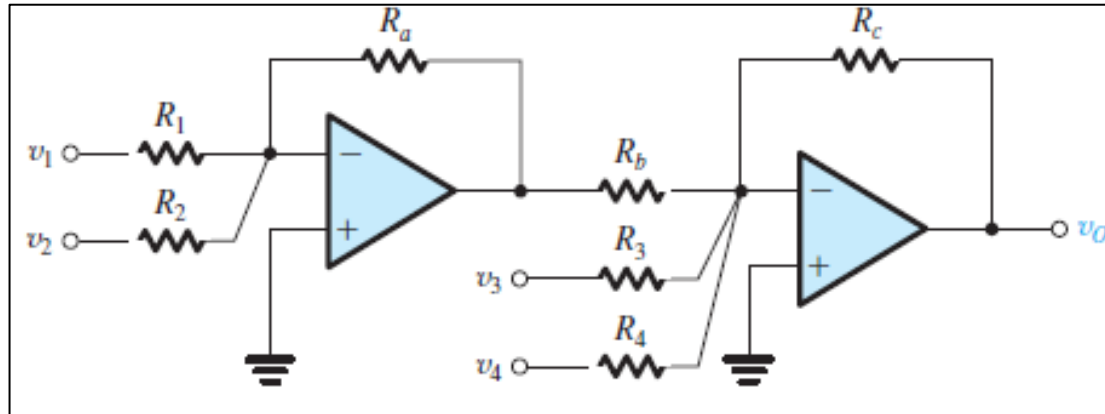
**In the weighted summer saw all the summing coefficients must be of the same sign. The need occasionally arises for summing signals with opposite signs.** Such a function can be implemented, however, using two op amps as shown below. Assuming ideal op amps, it can be easily shown that the output voltage is given by:



$$v_o = v_1 \left( \frac{R_a}{R_1} \right) \left( \frac{R_c}{R_b} \right) + v_2 \left( \frac{R_a}{R_2} \right) \left( \frac{R_c}{R_b} \right) - v_3 \left( \frac{R_c}{R_3} \right) - v_4 \left( \frac{R_c}{R_4} \right)$$

Weighted summers are utilized in a variety of applications including in **the design of audio systems** where they can be used in mixing signals originating from different musical instruments !


# Frequency Response

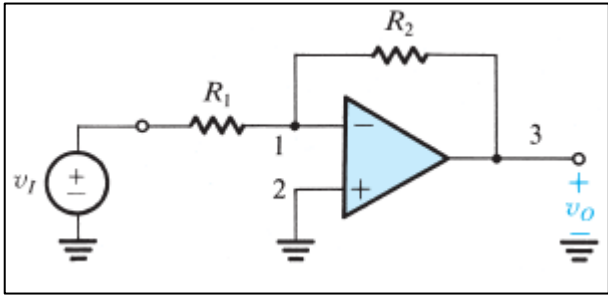

$$PGL = A_{vf} \times BW = f_T$$

$$A_{vf} = 10(20\text{dB})$$

$$BW = \frac{1\text{MHz}}{10} = 100\text{KHz}$$

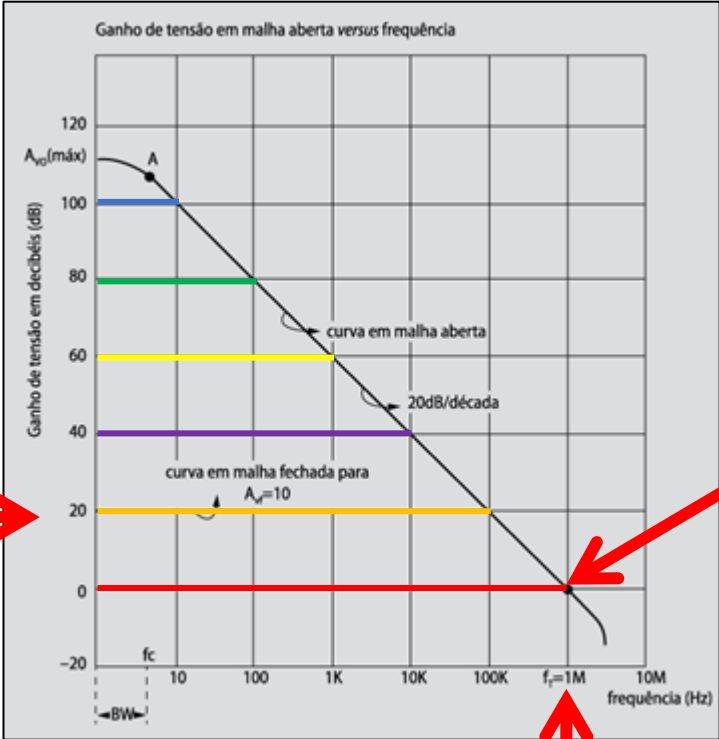


LM741 |  $f_T = 1\text{MHz}$   
 LF351 |  $f_T = 4\text{MHz}$

# **Noninverting Amplifier**
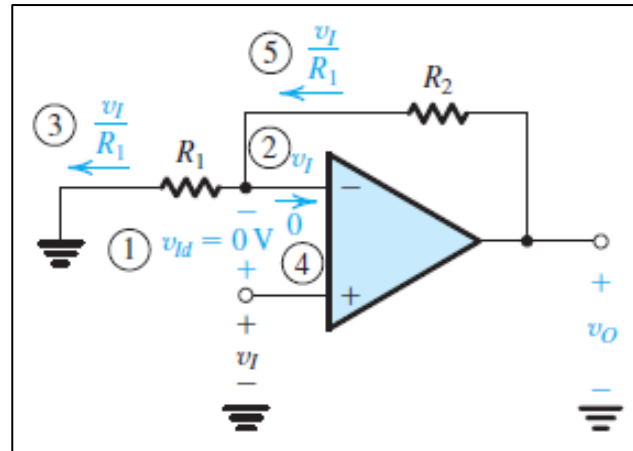
## The Noninverting Configuration

Here the input signal  $v_{Id}$  is applied directly to the positive input terminal of the op amp while one terminal of  $R_1$  is connected to ground.



$$v_{Id} = \frac{v_o}{A} = 0 \quad (5)$$

$$v_o = v_I + \left( \frac{v_I}{R_1} \right) R_2 \quad (6)$$

$$(5) \text{ e } (6) \longrightarrow G = \frac{v_o}{v_I} = 1 + \frac{R_2}{R_1}$$

## Effect of Finite Open-Loop Gain

it can be shown that the closed-loop gain of the noninverting amplifier circuit is given by

$$G = \frac{v_o}{v_i} = \frac{1 + (R_2/R_1)}{1 + (1 + R_2/R_1)/A}$$

$$\text{If } A \gg 1 + \frac{R_2}{R_1} \longrightarrow G = 1 + \frac{R_2}{R_1}$$


## Input and Output Resistance

The gain of the noninverting configuration is positive—hence the name noninverting.

**The input impedance of this closed-loop amplifier is ideally infinite**, since no current flows into the positive input terminal of the op amp.


The output of the noninverting amplifier is taken at the terminals of the ideal voltage source  $A(v_2 - v_1)$ , thus the **output resistance of the noninverting configuration is zero**.

## The Voltage Follower

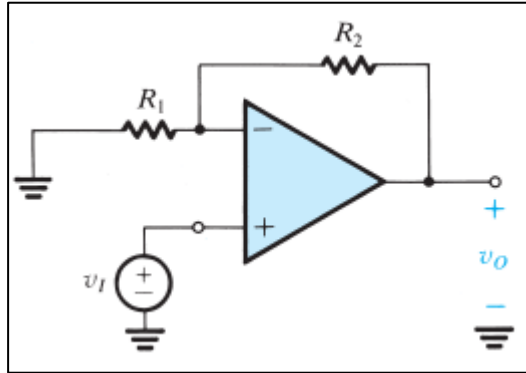

$$G = 1 + \frac{R_2}{R_1}$$


$$R_2 = 0 \text{ and } R_1 = \infty$$

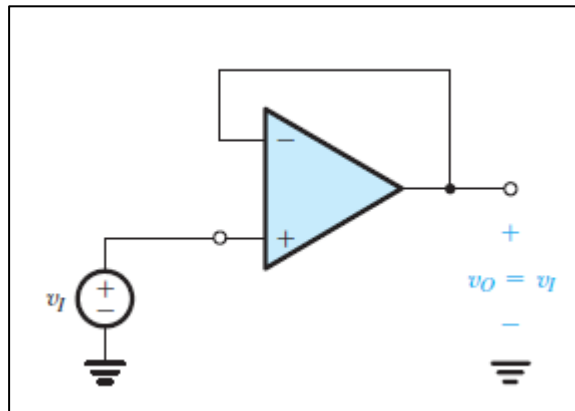

$$G = 1$$


There are situations in which one is interested not in voltage gain but only in a significant power gain. For instance, **the source signal can have a respectable voltage but a source resistance that is much greater than the load resistance. Connecting the source directly to the load would result in significant signal attenuation.** In such a case, one requires an amplifier with a high input resistance (much greater than the source resistance) and a low output resistance (much smaller than the load resistance) but with a modest voltage gain (or even unity gain). Such an amplifier is referred to as a **buffer amplifier**.

# Loading Effect - Op Amp Isolator

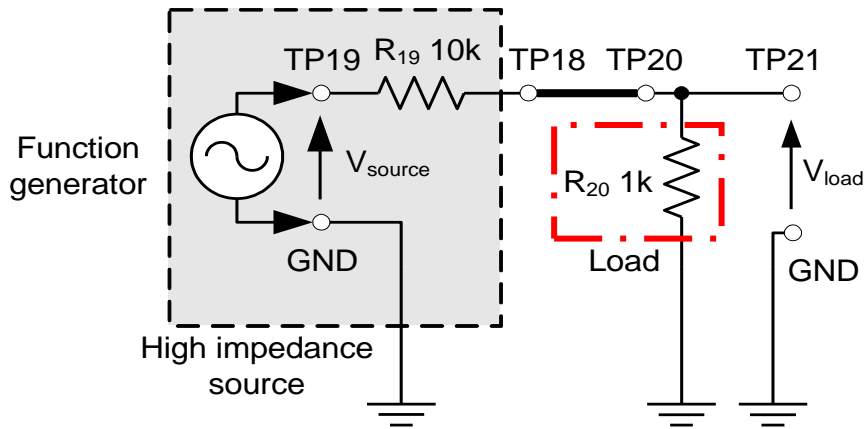

$$V_{load} = \frac{V_{source}}{10k + 1K} \cdot 1k$$

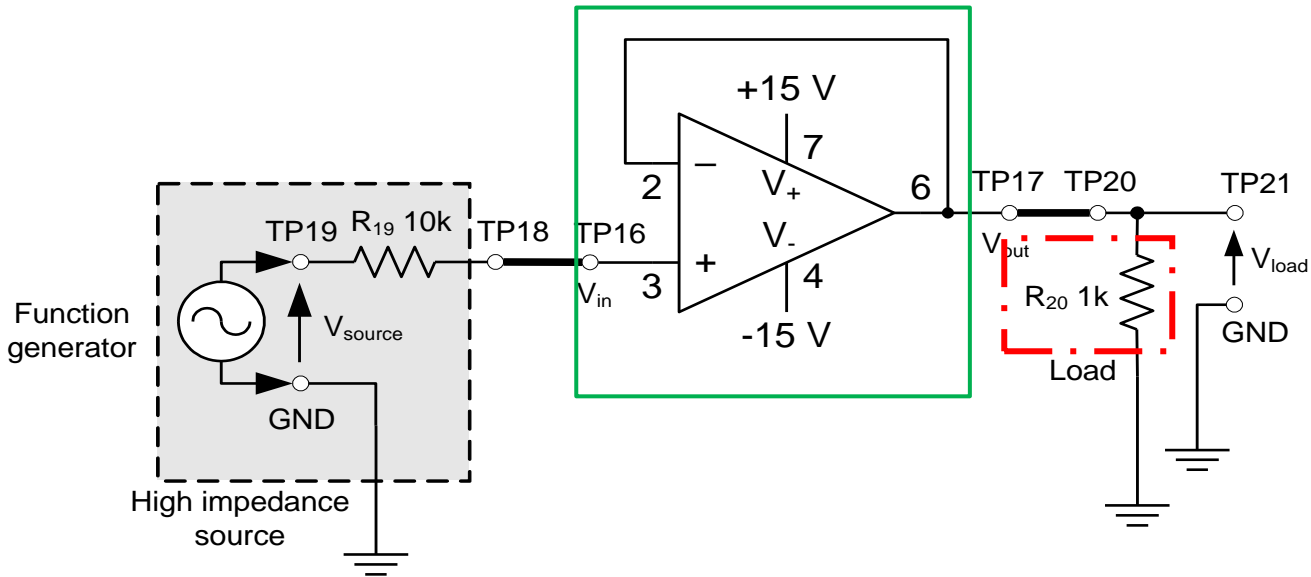**The resistive divider with 10kΩ e 1KΩ significantly reduces the voltage on the 1KΩ load !**



$$V_{load} = V_{source}$$