



**FIGURE 3.53** Capture schematic of the 5-V dc power supply in Example 3.10.

capacitor, and a zener voltage regulator. The only perhaps-puzzling component is  $R_{\text{isolation}}$ , the 100-M $\Omega$  resistor between the secondary winding of the transformer and ground. This resistor is included to provide dc continuity and thus “keep SPICE happy”; it has little effect on circuit operation.

Let it be required that the power supply (in Fig. 3.53) provide a nominal dc voltage of 5 V and be able to supply a load current  $I_{\text{load}}$  as large as 25 mA; that is,  $R_{\text{load}}$  can be as low as 200  $\Omega$ . The power supply is fed from a 120-V (rms) 60-Hz ac line. Note that in the PSpice schematic (Fig. 3.53), we use a sinusoidal voltage source with a 169-V peak amplitude to represent the 120-V rms supply (as 120-V rms = 169-V peak). Assume the availability of a 5.1-V zener diode having  $r_z = 10 \Omega$  at  $I_Z = 20$  mA (and thus  $V_{Z0} = 4.9$  V), and that the required minimum current through the zener diode is  $I_{Z\text{min}} = 5$  mA.

An approximate first-cut design can be obtained as follows: The 120-V (rms) supply is stepped down to provide 12-V (peak) sinusoids across each of the secondary windings using a 14:1 turns ratio for the center-tapped transformer. The choice of 12 V is a reasonable compromise between the need to allow for sufficient voltage (above the 5-V output) to operate the rectifier and the regulator, while keeping the PIV ratings of the diodes reasonably low. To determine a value for  $R$ , we can use the following expression:

$$R = \frac{V_{C\text{min}} - V_{Z0} - r_z I_{Z\text{min}}}{I_{Z\text{min}} + I_{L\text{max}}}$$

where an estimate for  $V_{C\text{min}}$ , the minimum voltage across the capacitor, can be obtained by subtracting a diode drop (say, 0.8 V) from 12 V and allowing for a ripple voltage across the capacitor of, say,  $V_r = 0.5$  V. Thus,  $V_{S\text{min}} = 10.7$  V. Furthermore, we note that  $I_{L\text{max}} = 25$  mA and  $I_{Z\text{min}} = 5$  mA, and that  $V_{Z0} = 4.9$  V and  $r_z = 10 \Omega$ . The result is that  $R = 191 \Omega$ .

Next, we determine  $C$  using a restatement of Eq. (3.33) with  $V_p/R$  replaced by the current through the 191- $\Omega$  resistor. This current can be estimated by noting that the voltage across  $C$  varies from 10.7 to 11.2 V, and thus has an average value of 10.95 V. Furthermore, the desired voltage across the zener is 5 V. The result is  $C = 520 \mu\text{F}$ .

Now, with an approximate design in hand, we can proceed with the SPICE simulation. For the zener diode, we use the model of Fig. 3.52, and assume (arbitrarily) that  $D_1$  has  $I_S = 100$  pA