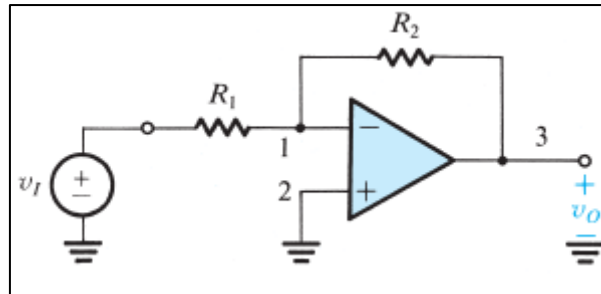


The Inverting Configuration with General Impedances

1


The op-amp circuit applications we have studied thus far utilized resistors in the op-amp feedback path and in connecting the signal source to the circuit (feed-in), that is, in the feed-in path. As a result, circuit operation has been (ideally) independent of frequency.



By allowing the use of capacitors together with resistors in the feedback and feed-in paths of op-amp circuits, a door is open to a very wide range of useful and exciting applications of the op amp.

The **op-amp-RC circuits** are considering two basic applications, namely, signal **integrators** and **differentiators**.

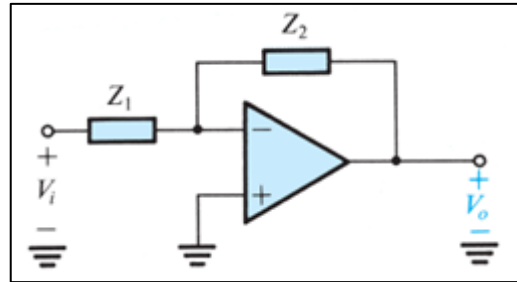- 2 The inverting closed-loop configuration with impedances $Z_1(s)$ and $Z_2(s)$ replacing resistors R_1 and R_2 , respectively is shown below.



$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)}$$


By replacing s by $j\omega$ provides the transfer function, that is, the transmission magnitude and phase for a sinusoidal input signal of frequency ω .

Note

A **single time constant network (STC)** is one that is composed of, or can be reduced to, one reactive component (capacitance or inductance) and one resistance.


Table 1.2 Frequency Response of STC Networks		
	Low-Pass (LP)	High-Pass (HP)
Transfer Function $T(s)$	$\frac{K}{1 + (s/\omega_0)}$	$\frac{Ks}{s + \omega_0}$
Transfer Function (for physical frequencies) $T(j\omega)$	$\frac{K}{1 + j(\omega/\omega_0)}$	$\frac{K}{1 - j(\omega_0/\omega)}$
Magnitude Response $ T(j\omega) $	$\frac{ K }{\sqrt{1 + (\omega/\omega_0)^2}}$	$\frac{ K }{\sqrt{1 + (\omega_0/\omega)^2}}$
Phase Response $\angle T(j\omega)$	$-\tan^{-1}(\omega/\omega_0)$	$\tan^{-1}(\omega_0/\omega)$
Transmission at $\omega = 0$ (dc)	K	0
Transmission at $\omega = \infty$	0	K
3-dB Frequency	$\omega_0 = 1/\tau$; $\tau \equiv$ time constant $\tau = CR$ or L/R	

STC

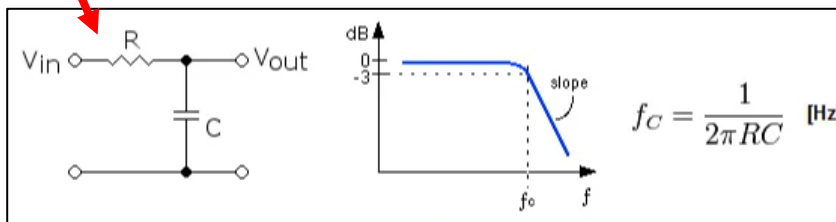

low-pass network

STC

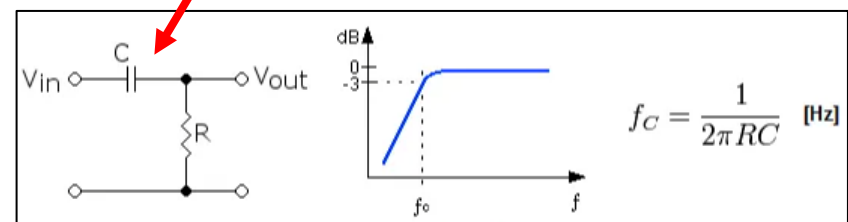



high-pass network

Exercise 1

For the circuit below:

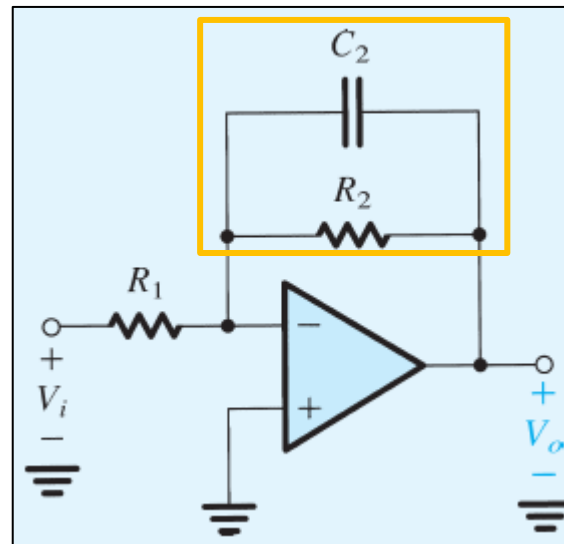- 1) Derive an expression for the transfer function. Show that the **transfer function** is that of a low-pass STC (single time constant) circuit.
- 2) By expressing the transfer function in the standard form shown find the **dc gain** and the 3-dB frequency.
- 3) Design the circuit to obtain a **dc gain of 40 dB**, a **3-dB frequency of 1 kHz**, and an **input resistance of 1 k Ω** .



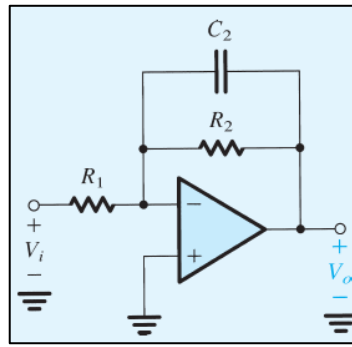

1

To obtain the transfer function of the circuit we substitute in the transfer function $Z_1 = R_1$ and since Z_2 is the parallel connection of two components, it is more convenient to work in terms of Y_2 . that is, we use the following alternative form of the transfer function:

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)}$$

$$\rightarrow \frac{V_o(s)}{V_i(s)} = -\frac{1}{Z_1(s)Y_2(s)}$$

$$Z_1 = R_1$$

$$Y_2(s) = (1/R_2) + sC_2$$

$$\rightarrow \frac{V_o(s)}{V_i(s)} = -\frac{1}{\frac{R_1}{R_2} + sC_2R_1}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{-R_2/R_1}{1 + sC_2R_2}$$

$$\omega_0 = \frac{1}{C_2R_2}$$

$$f_o = \frac{1}{2\pi R_2 C_2}$$


Table 1.2 Frequency Response of STC Networks

	Low-Pass (LP)	High-Pass (HP)
Transfer Function $T(s)$	$\frac{K}{1 + (s/\omega_0)}$	$\frac{Ks}{s + \omega_0}$
Transfer Function (for physical frequencies) $T(j\omega)$	$\frac{K}{1 + j(\omega/\omega_0)}$	$\frac{K}{1 - j(\omega_0/\omega)}$
Magnitude Response $ T(j\omega) $	$\frac{ K }{\sqrt{1 + (\omega/\omega_0)^2}}$	$\frac{ K }{\sqrt{1 + (\omega_0/\omega)^2}}$
Phase Response $\angle T(j\omega)$	$-\tan^{-1}(\omega/\omega_0)$	$\tan^{-1}(\omega_0/\omega)$
Transmission at $\omega = 0$ (dc)	K	0
Transmission at $\omega = \infty$	0	K
3-dB Frequency	$\omega_0 = 1/\tau$; $\tau \equiv$ time constant $\tau = CR$ or L/R	


$$\frac{V_o(s)}{V_i(s)} = \frac{-R_2/R_1}{1 + sC_2R_2}$$

$$\omega_0 = \frac{1}{C_2R_2}$$

$$f_0 = \frac{1}{2\pi R_2 C_2}$$

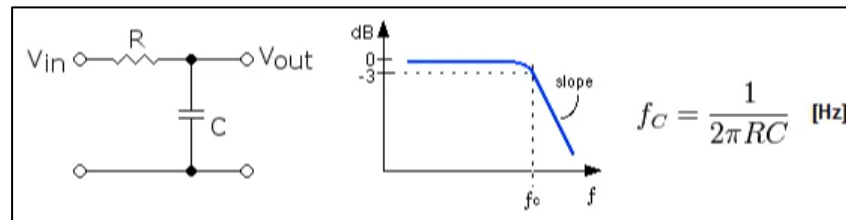

low-pass network

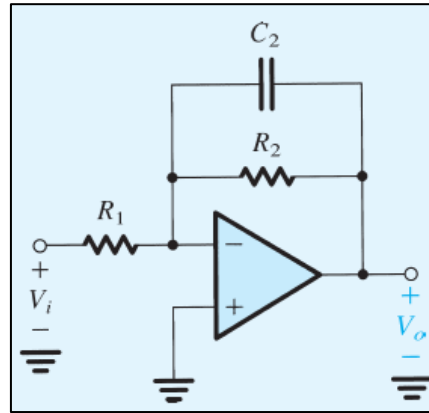

2 The capacitor behaves as an open circuit at dc. Thus at dc the gain is simply $(-R_2/R_1)$.

3 Now to obtain a dc gain of 40 dB, that is, 100 V/V, we select $R_2/R_1 = 100$.

For an input resistance of 1 k Ω , we select:

$$R_1 = 1 \text{ k}\Omega$$



$$R_2 = 100 \text{ k}\Omega$$

Finally, for a 3dB frequency at $f_0 = 1 \text{ kHz}$, we calculate C_2 :

$$\omega_0 = \frac{1}{C_2 R_2}$$



$$2\pi \times 1 \times 10^3 = \frac{1}{C_2 \times 100 \times 10^3}$$





$$C_2 = 1.59 \text{ nF}$$

The Integrator

The Inverting Integrator

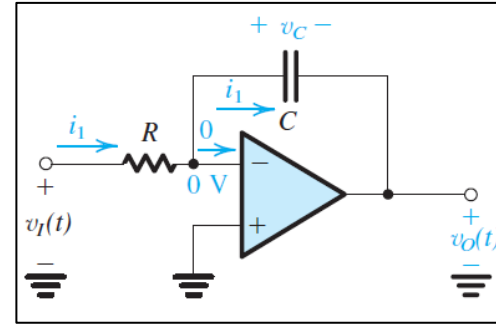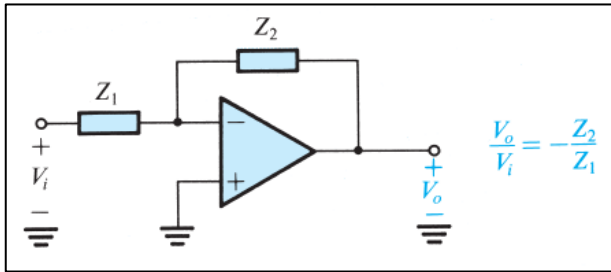- 1 By placing a capacitor in the feedback path and a resistor at the input, we obtain the circuit below. We shall now show that this circuit realizes the mathematical operation of integration.



- 2 Let the input be a time-varying function $v_i(t)$. The virtual ground at the inverting op-amp input causes $v_i(t)$ to appear in effect across R , and thus the current $i_1(t)$ will be $v_i(t)/R$

This current flows through the capacitor C , causing charge to accumulate on C . If we assume that the circuit begins operation at time $t = 0$, then at an arbitrary time t the current $i_1(t)$ will have deposited on C the following charge Q :


$$Q = \int_0^t i_1(t) dt$$

- 3 The capacitor voltage $v_c(t)$ will change by:

$$i_1(t) = C \frac{dv_c(t)}{dt} \quad \rightarrow \quad v_c(t) = \frac{1}{C} \int_0^t i_1(t) dt$$

4 If the initial voltage (at $t=0$) on C is V_c , thus
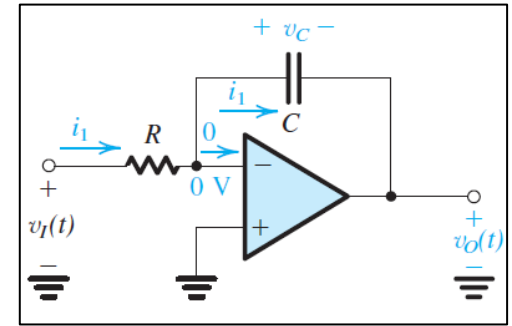
$$v_c(t) = V_c + \frac{1}{C} \int_0^t i_I(t) dt$$



5 The output voltage $v_o(t) = -v_c(t)$. Thus,


$$v_o(t) = -\frac{1}{RC} \int_0^t v_I(t) dt - V_c$$

Thus the circuit provides an output voltage that is proportional to the time integral of the input, with V_c being the initial condition of integration and **RC** is the **integrator time constant**.



6 Note that there is a negative sign attached to the output voltage, and thus this integrator circuit is said to be an **inverting integrator**. It is also known as a **Miller integrator**.

$$\left. \begin{array}{l} \frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)} \\ Z_1(s) = R \\ Z_2(s) = 1/sC \end{array} \right\} \rightarrow \frac{V_o(s)}{V_i(s)} = -\frac{1}{sCR} \rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{1}{j\omega CR} \rightarrow \begin{array}{l} \left| \frac{V_o}{V_i} \right| = \frac{1}{\omega CR} \\ \phi = +90^\circ \end{array}$$

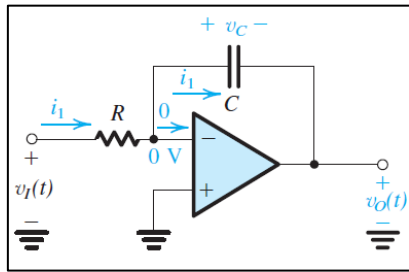
Comparison of the frequency response of the integrator to that of an STC low-pass network indicates that the integrator behaves as a low-pass filter.



Integrator

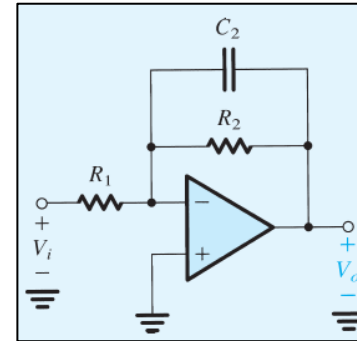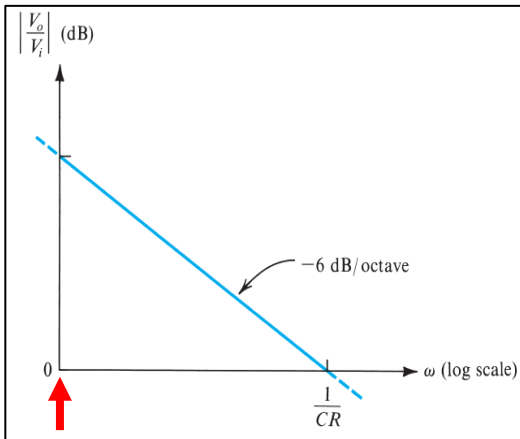

Low-pass STC network ($k=R_2/R_1$)

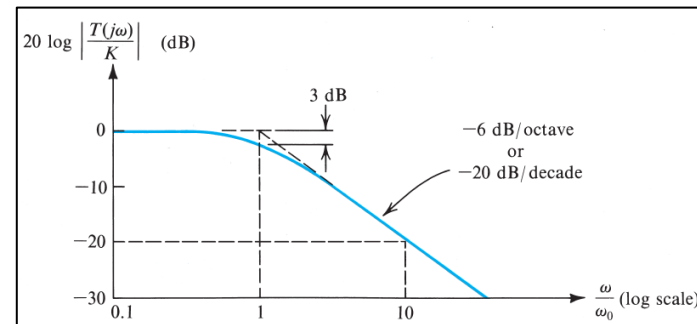

corner frequency (f_c)

$$f_c = \frac{1}{2\pi R_2 C_2}$$


Observe also that at $\omega = 0$, the magnitude of the integrator transfer function is infinite. This indicates that at dc the op amp is operating with an open loop.

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\omega CR}$$


R_2 causes the frequency of the integrator pole to move from its ideal location at $\omega = 0$ to one determined by the corner frequency of the STC network (R_F, C).

8

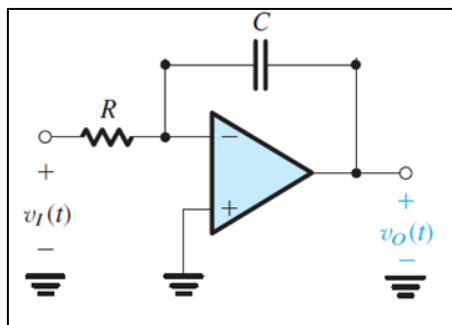The **dc problem of the integrator circuit can be alleviated by connecting a resistor R_F** across the integrator capacitor C , as shown below, and thus the **gain at dc will be $-R_F/R$** rather than infinite. Such a resistor provides a dc feedback path. Specifically, the integrator transfer function becomes:


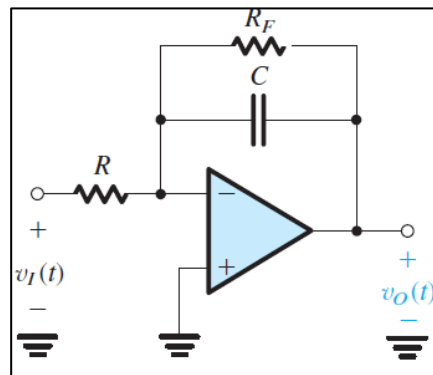
$$\frac{V_o(s)}{V_i(s)} = -\frac{1}{sCR}$$



$$\frac{V_o(s)}{V_i(s)} = -\frac{R_F/R}{1 + sCR_F}$$

9

Unfortunately, however, the integration is no longer ideal, and the lower the value of R_F , the less ideal the integrator circuit becomes. This is because R_F causes the frequency of the integrator pole to move from its ideal location at $\omega = 0$ to one determined by the corner frequency of the STC network (R_F, C).



The lower the value we select for R_F , the higher the corner frequency will be and the more nonideal the integrator becomes. Thus selecting a value for R_F presents the designer with a trade-off between dc performance and signal performance.

$$f_o = \frac{1}{2\pi CR_F}$$

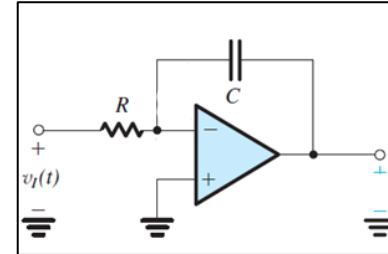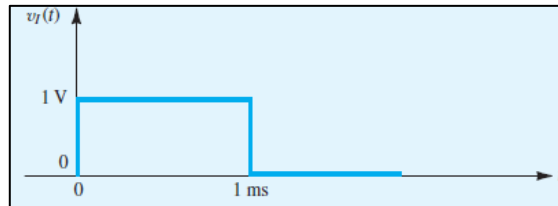Exercise 2

Find the output produced by a Miller integrator in response to an input pulse of 1V height and 1ms width as shown below. Let $R = 10 \text{ k}\Omega$ and $C = 10 \text{ nF}$.


If the integrator capacitor is shunted by a 1-M Ω resistor, how will the response be modified? The op amp is specified to saturate at $\pm 13\text{V}$.



1 In response to a 1V, 1ms input pulse, the integrator output, if $V_C = 0$, will be:

$$v_o(t) = -\frac{1}{RC} \int_0^t v_I(t) dt - V_C \rightarrow v_o(t) = -\frac{1}{RC} \int_0^t 1 dt \quad 0 \leq t \leq 1 \text{ ms}$$

$$\rightarrow v_o(t) = -10t$$

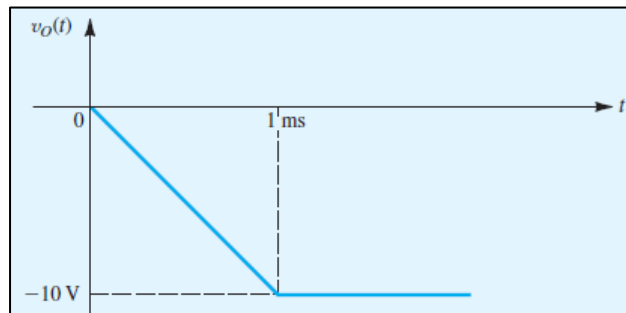

Charging a capacitor with a constant current produces a linear voltage across it !


2 The current in the resistor produces a constant current in the capacitor:

$$I_R = I_C = 1\text{V}/10\text{k}\Omega = 0,1\text{mA}$$

3

Next consider the situation with resistor connected $R_F = 1\text{M}\Omega$ across C .

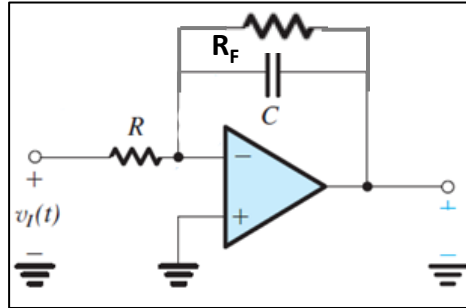As before, the 1V pulse will provide a constant current $I = 0.1\text{ mA}$. Now, however, this current is supplied to an STC network composed of R_F in parallel with C .



$$v_o(t) = v_{ofinal} - (v_{ofinal} - v_{oinitial})e^{-t/\tau}$$

$$v_{oinitial} = 0$$

$$v_{ofinal} = IR_f = 0.1 \times 10^{-3} \times 10^6 = 100$$

$$\tau = CR_f = 10 \times 10^{-9} \times 10^6 = 10\text{ms}$$

$$v_o(t) = -100(1 - e^{-t/0,01})$$



$$0 \leq t \leq 1\text{ms}$$

$$\rightarrow v_o(1\text{ms}) = -100(1 - e^{0,001/0,01}) = -9,5\text{V}$$

4

The output waveform is shown below, from which we see that including R_F causes the ramp to be slightly rounded such that the output reaches only -9.5 V , 0.5 V short of the ideal value of -10 V .

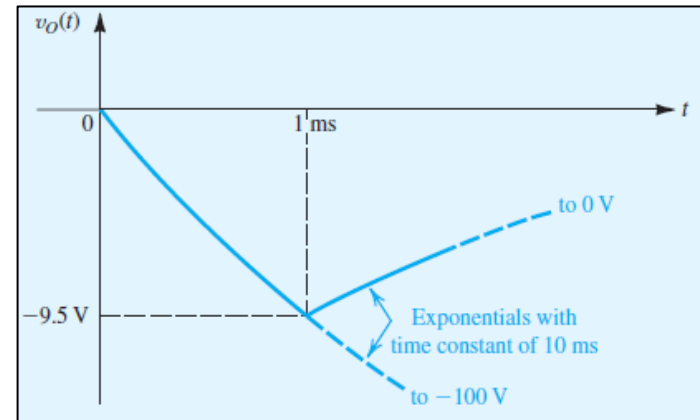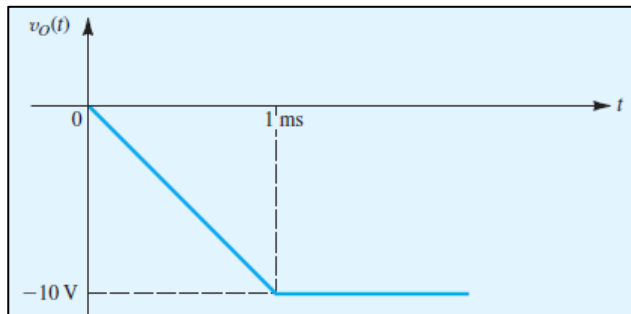Furthermore, for $t > 1\text{ ms}$, the capacitor discharges through R_F with the relatively long time-constant of 10 ms .



This example hints at an important application of integrators, namely, their use in providing triangular waveforms in response to square-wave inputs !


Integrators have many other applications, including their use in the design of active filters.

The Differentiator

The Op Amp Differentiator

1

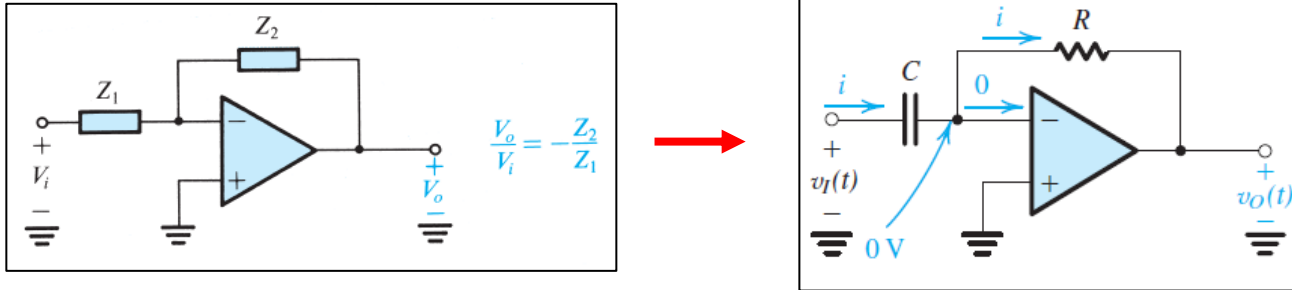Interchanging the location of the capacitor and the resistor of the integrator circuit results in the circuit that performs the mathematical function of differentiation.



2


To see how this comes about, let the input be the time-varying function, and note that the virtual ground at the inverting input terminal of the op amp causes to appear in effect across the capacitor C . Thus the current through C will be $C(dv_I/dt)$, and this current flows through the feedback resistor R providing at the op-amp output the following voltage:

$$\left. \begin{aligned} i &= C \frac{d(V_C)}{dt} \\ V_o &= -V_C \end{aligned} \right\} \rightarrow v_o(t) = -CR \frac{dv_I(t)}{dt}$$

3 The frequency-domain transfer function of the differentiator circuit can be found by substituting $Z_1(s)=1/sC$ and $Z_2(s)= R$ in the transfer function of an inverting configuration with general impedances:

$$\left. \begin{array}{l} \frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)} \\ Z_1(s) = R \\ Z_2(s) = 1/sC \end{array} \right\} \rightarrow \frac{V_o(s)}{V_i(s)} = -sCR \rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = -j\omega CR \rightarrow \left\{ \begin{array}{l} \left| \frac{V_o}{V_i} \right| = \omega CR \\ \phi = -90^\circ \end{array} \right.$$

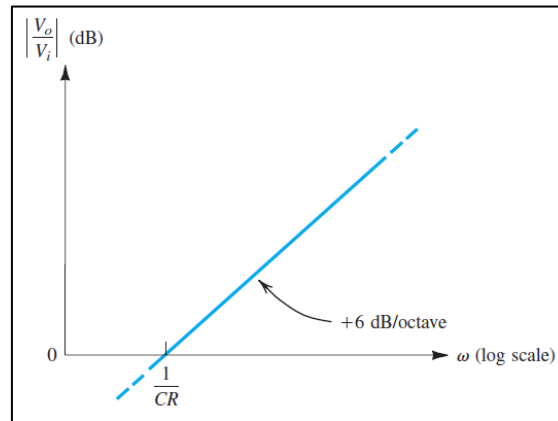4 The Bode plot of the magnitude response can be found by noting that for an octave increase in ω , the magnitude doubles (increases by 6 dB). Thus the plot is simply a straight line of slope +6 dB/octave (+20 dB/decade) intersecting the 0 dB line where RC is the **differentiator time-constant**.



5

The differentiator circuit suffer from stability problems and **are generally avoided in practice**. This is due to the spike introduced at the output every time there is sharp change in $v_i(t)$. Such a change could be interference coupled electromagnetically (“picked up”) from adjacent signal sources.

When the circuit is used, it is usually necessary to connect a small-valued resistor in series with the capacitor. This modification, unfortunately, turns the circuit into a nonideal differentiator.

For this reasons and because they suffer from stability problems, differentiator circuits are generally avoided in practice.