


Op Amp

DC Imperfections

- Input Bias Current
- Input Offset Current

- 1 The second dc problem encountered in op amps (ones constructed using BJTs) is illustrated below. **In order for the op amp to operate, its two input terminals have to be supplied with dc currents, termed the **input bias currents**.**

The op-amp
input bias currents

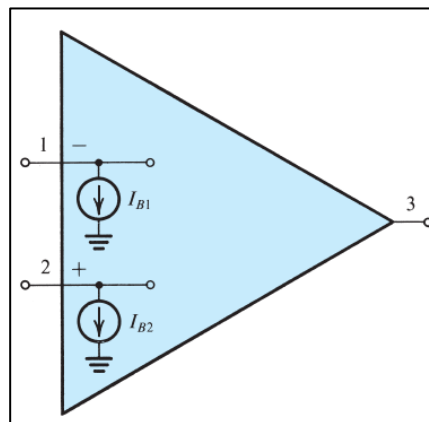

- 2 These two currents are represented by two current sources, I_{B1} and I_{B2} , connected to the two input terminals.

The op-amp manufacturer usually specifies the following currents:

Input Bias Current

$$I_B = \frac{I_{B1} + I_{B2}}{2}$$


(Typical value: $I_B = 100\text{nA}$)

Input Offset Current

$$I_{OS} = |I_{B1} - I_{B2}|$$

(Typical value: $I_{OS} = 10\text{nA}$)

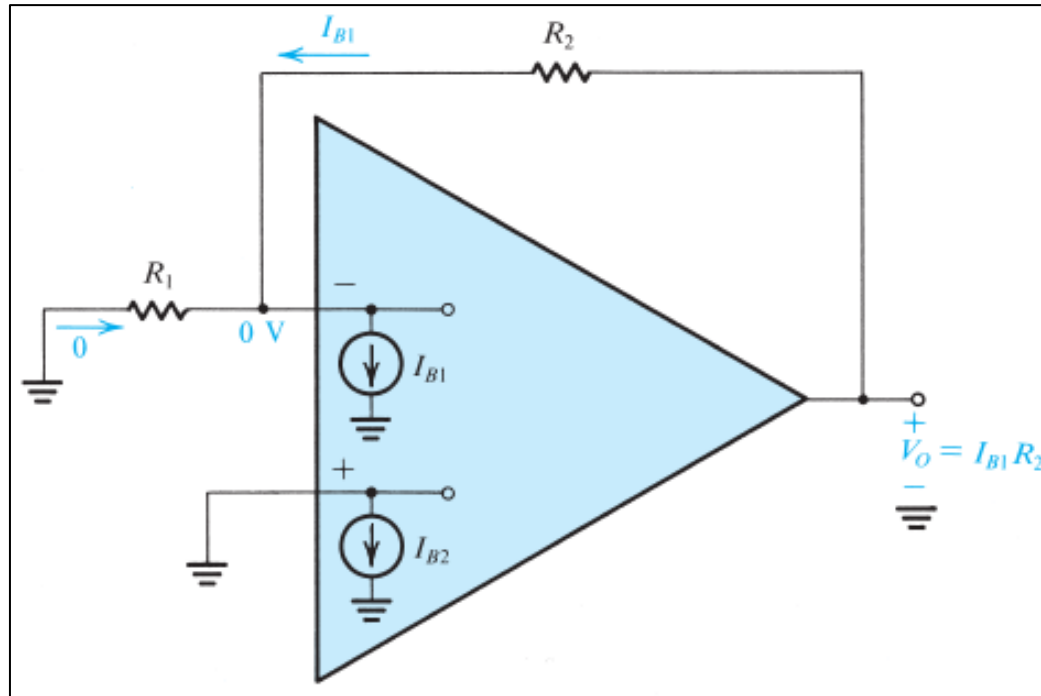- 3 We now wish to find the dc output voltage of the closed-loop amplifier due to the input bias currents. To do this we ground the signal source and obtain the circuit shown below for both the inverting and noninverting configurations.





The output dc voltage is given by:

$$V_O = I_{B1}R_2 \cong I_B R_2$$

$$I_B = \frac{I_{B1} + I_{B2}}{2}$$

4 Fortunately, however, a technique exists for reducing the value of the output dc voltage due to the input bias currents.

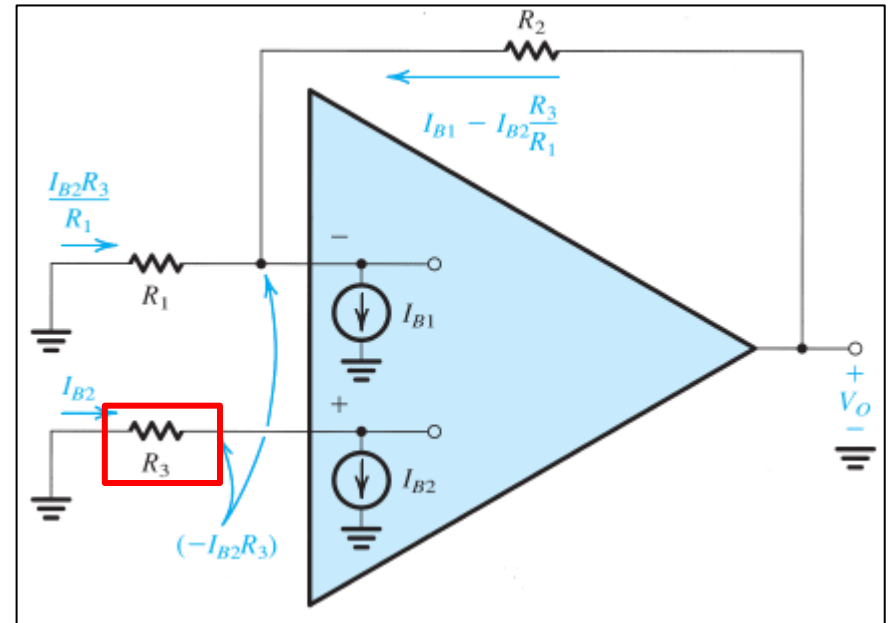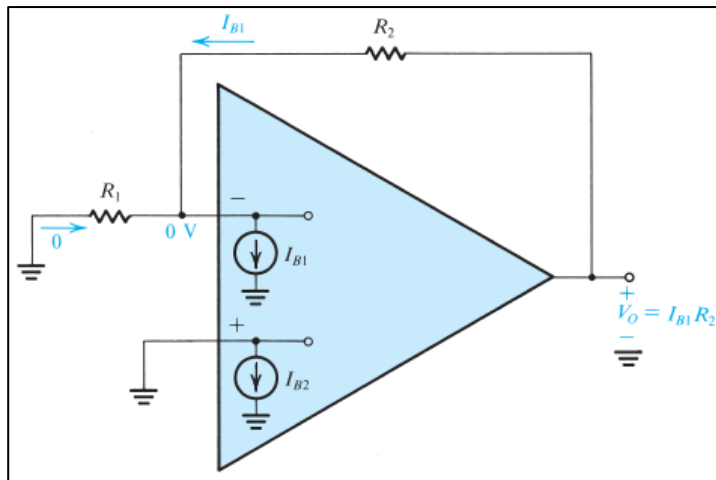The method consists of introducing a resistance R_3 in series with the noninverting input lead, as shown below.



The appropriate value for R_3 can be determined by analyzing the circuit, and the output voltage is given by:

$$V_O = -I_{B2}R_3 + R_2(I_{B1} - I_{B2}R_3/R_1)$$

$\underbrace{\quad}_{V_-}$ $\underbrace{\quad}_{V_{R2}}$ $\underbrace{\quad}_{I_{R1}}$

if $R_3 = 0 \rightarrow V_O = R_2 I_{B1}$

5

$$V_O = -I_{B2}R_3 + R_2(I_{B1} - I_{B2}R_3/R_1)$$

If $R_3 \neq 0$ 5.1 If $I_{B1} = I_{B2} = I_B$

$$V_O = I_B[R_2 - R_3(1 + R_2/R_1)]$$

$$R_3 = \frac{R_2}{1 + R_2/R_1} = \frac{R_1R_2}{R_1 + R_2}$$

$$V_O = 0$$

5.2 If $I_{B1} \neq I_{B2}$

$$I_{OS} = |I_{B1} - I_{B2}|$$

$$\begin{cases} I_{B1} = I_B + \frac{I_{OS}}{2} \\ I_{B2} = I_B - \frac{I_{OS}}{2} \end{cases}$$


$$R_3 = \frac{R_2}{1 + R_2/R_1} = \frac{R_1R_2}{R_1 + R_2}$$

$$V_O = I_{OS}R_2$$

It is usually about an order of magnitude smaller than the value obtained without R_3 !

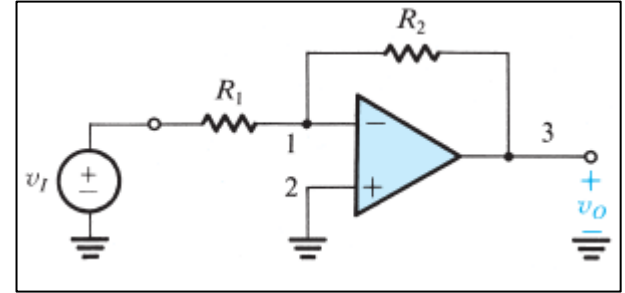Exercise

Consider an inverting amplifier circuit designed using an op amp and two resistors, $R_1 = 10 \text{ k}\Omega$ and $R_2 = 1 \text{ M}\Omega$. The op amp is specified to have an **input bias current of 100nA** and an **input offset current of 10 nA**.



1) Find the output dc offset voltage resulting.

$$\left. \begin{aligned} V_O &= -I_{B2}R_3 + R_2(I_{B1} - I_{B2}R_3/R_1) \\ R_3 &= 0 \end{aligned} \right\} V_O = I_{B1}R_2 = 100\text{nA} \times 1\text{M}\Omega \longrightarrow \boxed{V_O = 0.1\text{V}}$$

2) Find the value of a resistor R_3 to be placed in series with the positive input lead in order to minimize the output offset voltage. What is the new value of V_O ?

$$R_3 = \frac{R_1 R_2}{R_1 + R_2} = \frac{10\text{k}\Omega \times 1\text{M}\Omega}{10\text{k}\Omega + 1\text{M}\Omega} = 9.9\text{k}\Omega \longrightarrow \boxed{R_3 = 10\text{K}\Omega}$$

$$\longrightarrow V_O = I_{OS}R_2 = 10\text{nA} \times 1\text{M}\Omega \longrightarrow \boxed{V_O = 0.01\text{V}}$$

An order of magnitude smaller than the value obtained without R_3 !