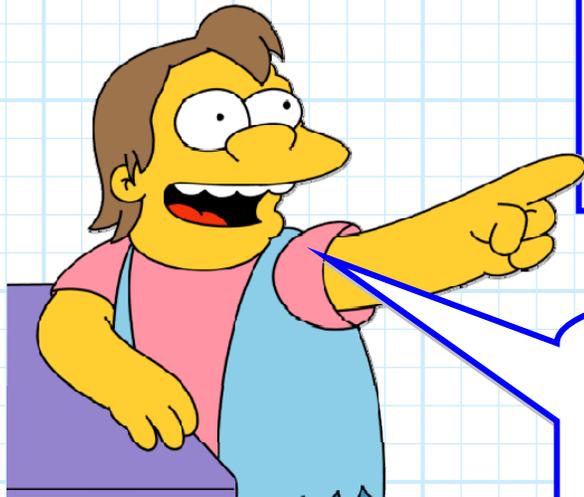


Line Impedance

Now let's define **line impedance** $Z(z)$, a **complex** function which is simply the ratio of the complex line **voltage** and complex line **current**:



$$Z(z) = \frac{V(z)}{I(z)}$$

Q: *Hey! I know what this is!*

The ratio of the voltage to current is simply the characteristic impedance Z_0 , right ???

A: **NO!** The line impedance $Z(z)$ is (generally speaking) **NOT** the transmission line **characteristic impedance** Z_0 !!!

→ It is unfathomably important that you understand this!!!! ←

Why Line Impedance is not Z_0

To see why line impedance $Z(z)$ is different than characteristic impedance Z_0 , recall that:

$$V(z) = V^+(z) + V^-(z) \quad \text{and that} \quad I(z) = \frac{V^+(z) - V^-(z)}{Z_0}$$

Therefore, line impedance is:

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \left(\frac{V^+(z) + V^-(z)}{V^+(z) - V^-(z)} \right) \neq Z_0$$

Or, more specifically, we can write:

$$Z(z) = Z_0 \left(\frac{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}} \right)$$

What then is Z_0 ?

Q: *I'm confused! Isn't:*

$$V^+(z)/I^+(z) = Z_0 ???$$



A: Yes! That is true! The ratio of the voltage to current for **each** of the two propagating waves is $\pm Z_0$.

However, the ratio of the **sum** of the two voltages, to the **sum** of the two currents, is **not** equal to Z_0 (generally speaking)!

→ This is actually confirmed by the expression of $Z(z)$ above.

Say that $V^-(z) = 0$, so that only **one** wave ($V^+(z)$) is propagating on the line.

In this case, the ratio of the **total** voltage to the total current is simply the ratio of the voltage and current of the **one** remaining wave—the **characteristic impedance** Z_0 !

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \left(\frac{V^+(z)}{I^+(z)} \right) = \frac{V^+(z)}{I^+(z)} = Z_0 \quad (\text{when } V^-(z) = 0)$$

Let's Summarize!!

Q: *So, it appears to me that characteristic impedance Z_0 is a transmission line parameter, depending **only** on the transmission line values L and C .*

*Whereas line impedance is $Z(z)$ depends the magnitude and phase of the two propagating waves $V^+(z)$ and $V^-(z)$ —values that depend **not only** on the transmission line, but also on the two things **attached** to either **end** of the transmission line!*

Right !?



A: Exactly!

Moreover, note that characteristic impedance Z_0 is simply a **number**, whereas line impedance $Z(z)$ is a **function** of position (z) on the transmission line.