

## 2.5 - The Quarter-Wave Transformer

Reading Assignment: pp. 73-76

By now you've noticed that a quarter-wave length of transmission line ( $l = \lambda/4$ ,  $2\beta l = \pi$ ) appears often in microwave engineering problems.

/


HO: The Quarter-Wave Transformer

Q: Why does the quarter-wave matching network work—after all, the quarter-wave line is mismatched at both ends?

A: HO: Multiple Reflection Viewpoint
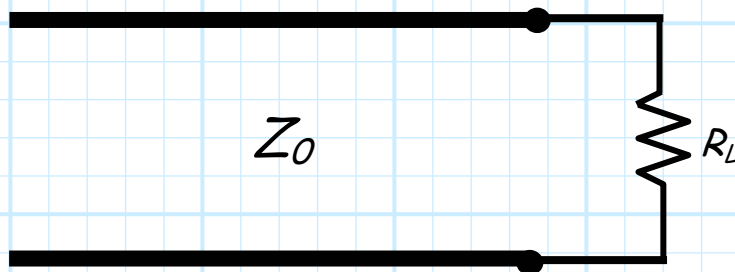
# The Quarter-Wave Transformer

Say the end of a transmission line with characteristic impedance  $Z_0$  is terminated with a **resistive** (i.e., real) load.




We typically would like **all** power traveling down the line to be **absorbed** by the load  $R_L$ .

But if  $R_L \neq Z_0$ , the line is **unmatched** and some of the incident power will be **reflected**.

**Q:** *Can all incident power be delivered to a resistive load if  $R_L \neq Z_0$ ??*

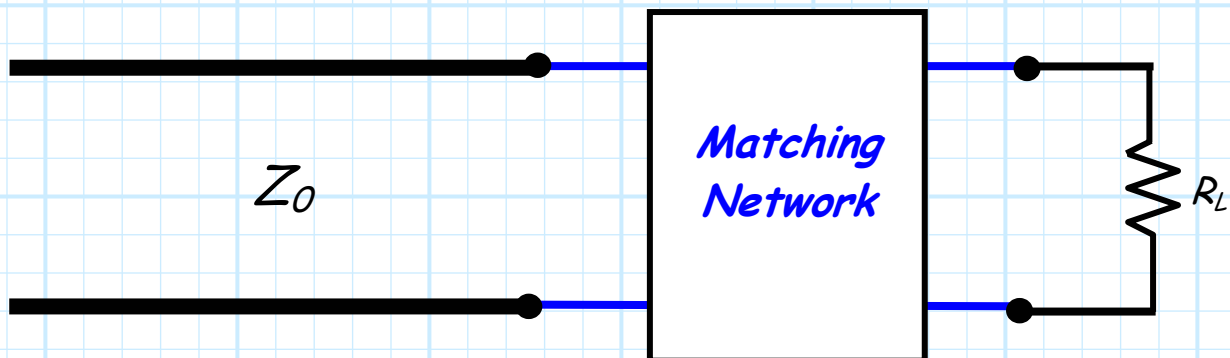**A:** **Yes!** We can insert a **matching network** between the transmission line and the load.



A matching network is a **lossless, 2-port** device. Its job is to **transform** the load  $R_L$  (or even  $Z_L$ ) to a value  $Z_0$ .


In other words, we want the **input** impedance of the matching network to be  $Z_{in} = Z_0$ , so that  $\Gamma_{in} = 0$  -- **no reflection!**

Since **none** of the incident power is **reflected**, and none is **absorbed** by the lossless matching network, it **all** must be absorbed by the **load  $R_L$ !**

**Q:** *These matching networks sound too good to be true. Exactly how do we **build** them?*

**A:** There are **many** methods and ways, but perhaps the easiest is the **quarter-wave transformer**.

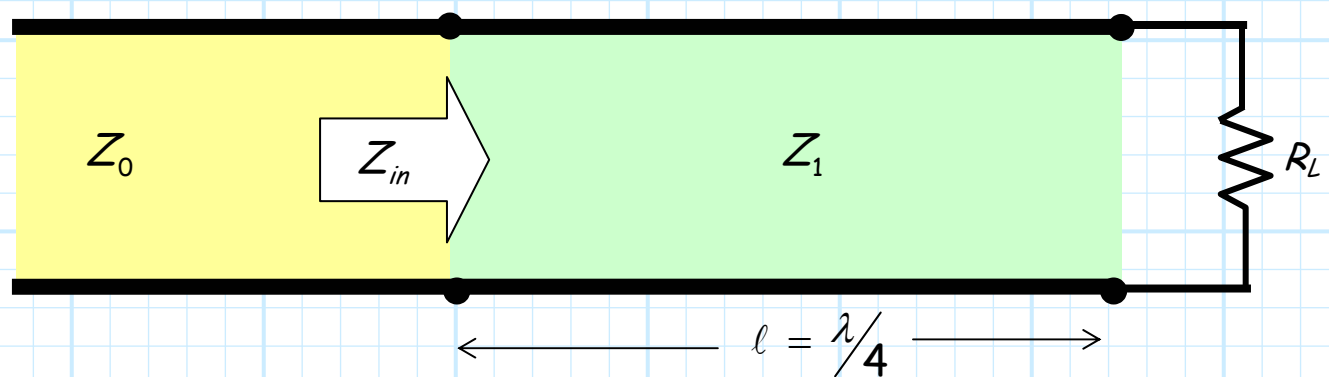First, insert a transmission line with characteristic impedance  $Z_1$  and length  $\ell = \lambda/4$  (i.e., a quarter-wave line) **between** the load and the  $Z_0$  transmission line.



The  $\lambda/4$  line is the **matching network!**

**Q:** *But what about the characteristic impedance  $Z_1$ ; what should its value be??*

**A:** Remember, the quarter wavelength case is one of the **special** cases that we studied. We know that the **input** impedance of the quarter wavelength line is:

$$Z_{in} = \frac{(Z_1)^2}{Z_L} = \frac{(Z_1)^2}{R_L}$$

Thus, if we wish for  $Z_{in}$  to be numerically equal to  $Z_0$ , we find:


$$Z_{in} = \frac{(Z_1)^2}{R_L} = Z_0$$

Solving for  $Z_1$ , we find its **required** value to be:

$$\begin{aligned}(Z_1)^2 / R_L &= Z_0 \\ (Z_1)^2 &= Z_0 R_L \\ Z_1 &= \sqrt{Z_0 R_L}\end{aligned}$$

In other words, the characteristic impedance of the quarter wave line is the **geometric average**  $Z_0$  and  $R_L$ !

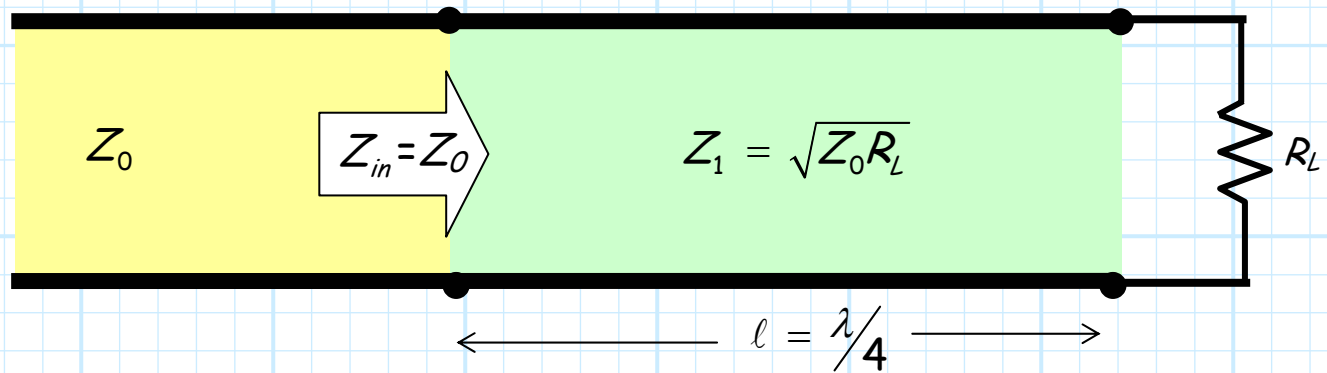Therefore, a  $\lambda/4$  line with characteristic impedance  $Z_1 = \sqrt{Z_0 R_L}$  will **match** a transmission line with characteristic impedance  $Z_0$  to a resistive load  $R_L$ .



Thus, **all power** is delivered to load  $R_L$ !

**Important Note:** We find that  $Z_{in} = Z_0$  **only** if the matching if the quarter-wave transmission line is **exactly** one-quarter wavelength in length  $l = \lambda/4$ .

The **problem** with this, of course, is that a physical length  $l$  of transmission line is exactly one-quarter wavelength at only **one** frequency  $f$ !

Remember, **wavelength** is related to **frequency** as:

$$\lambda = \frac{v_p}{f} = \frac{1}{f\sqrt{LC}}$$


where  $v_p$  is the **propagation velocity** of the wave.

For **example**, assuming that  $v_p = c$  ( $c$  = the speed of light in a vacuum), one wavelength at 1 GHz is 30 cm ( $\lambda = 0.3$  m), while one wavelength at 3 GHz is 10 cm ( $\lambda = 0.1$  m). As a result, a transmission line length  $\ell = 7.5$  cm is a quarter wavelength for a signal at 1GHz **only**.

Thus, a quarter-wave transformer provides a **perfect** match ( $\Gamma_{in} = 0$ ) at **one and only one** signal frequency!
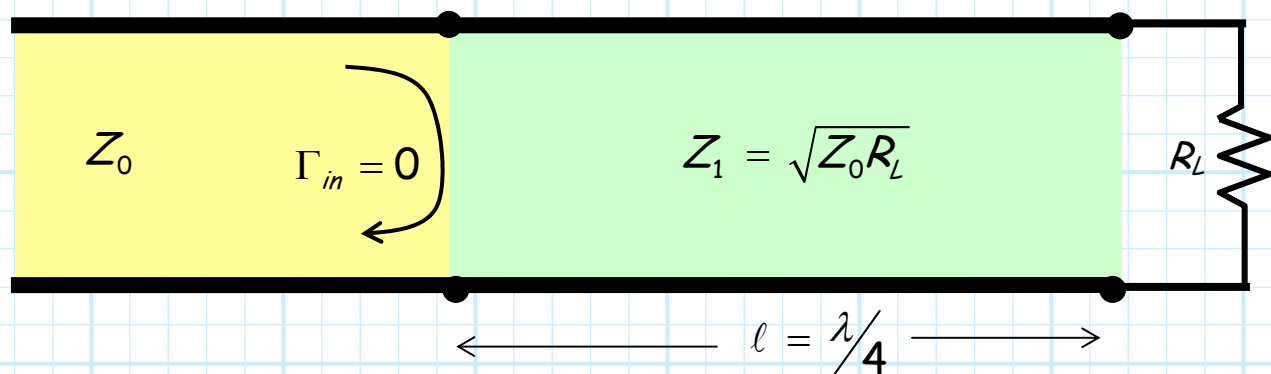
# Multiple Reflection Viewpoint


The **quarter-wave** transformer brings up an interesting question in  $\mu$ -wave engineering.



**Q:** *Why is there no reflection at  $z = -l$  ? It appears that the line is mismatched at both  $z = 0$  and  $z = -l$ .*


**A:** In fact there **are** reflections at these mismatched interfaces—an **infinite** number of them!

First, lets **define** a few terms:

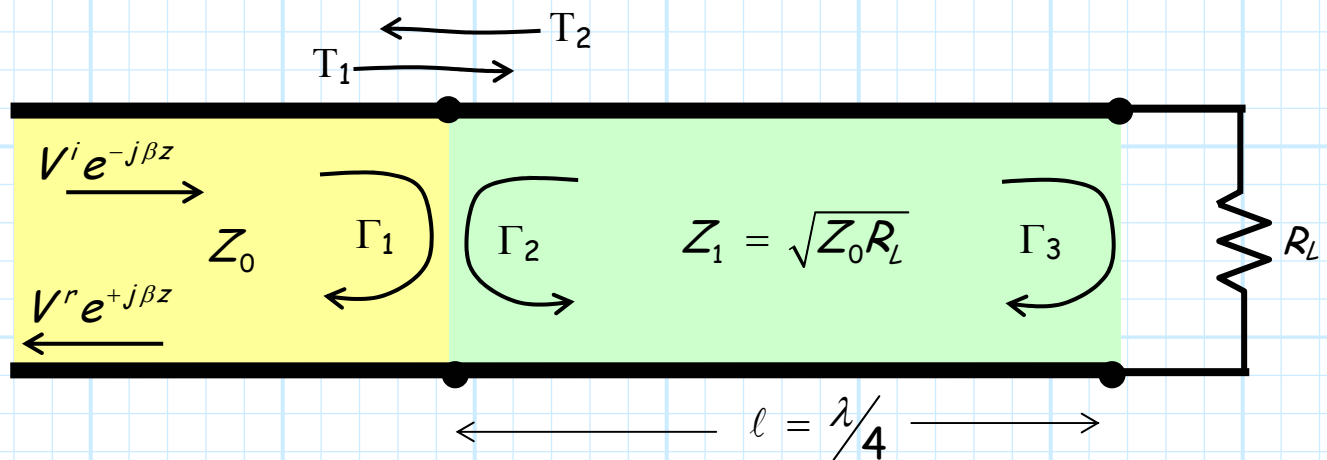


$\Gamma_1$  = **partial** reflection coefficient of a wave incident on the  $z = -l$  interface from the  $Z_0$  line:
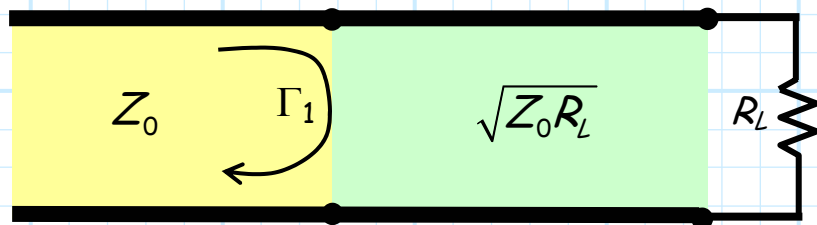
$$\Gamma_1 = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$




$\Gamma_2$  = **partial** reflection coefficient of a wave incident on the  $z = -l$  interface from the  $Z_1$  line:
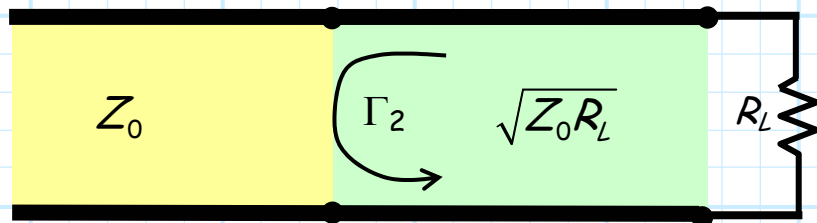
$$\Gamma_2 = \frac{Z_0 - Z_1}{Z_0 + Z_1} = -\Gamma_1$$



$\Gamma_3$  = **partial** reflection coefficient of a wave incident on the  $z = -0$  interface from the  $Z_1$  line:

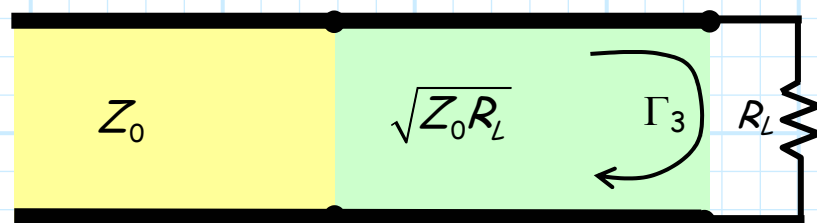
$$\Gamma_3 = \frac{R_L - Z_1}{R_L + Z_1}$$






$T_1 =$  **partial** transmission coefficient of a wave incident on the  $z = -\ell$  interface from the  $Z_0$  line:

$$T_1 = \frac{2Z_1}{Z_1 + Z_0}$$

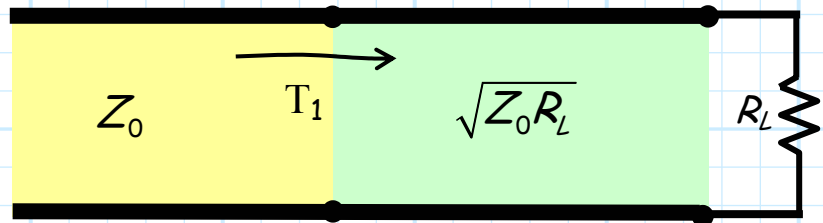


$T_2 =$  **partial** transmission coefficient of a wave incident on the  $z = -\ell$  interface from the  $Z_1$  line:

$$T_2 = \frac{2Z_0}{Z_0 + Z_1}$$

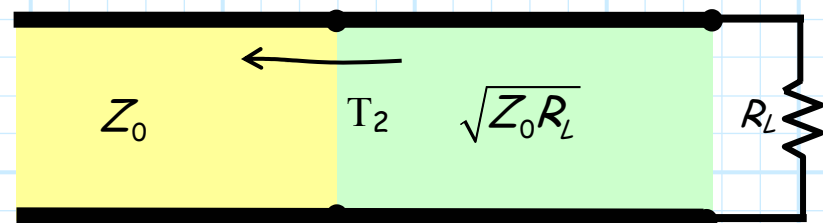


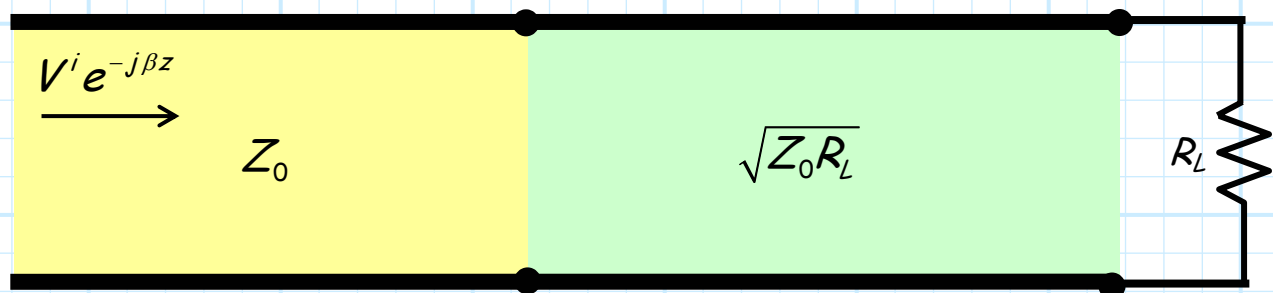Now let's try to interperate what **physically** happens when the **incident** voltage wave:




reaches the interface at  $z = -\ell$ .

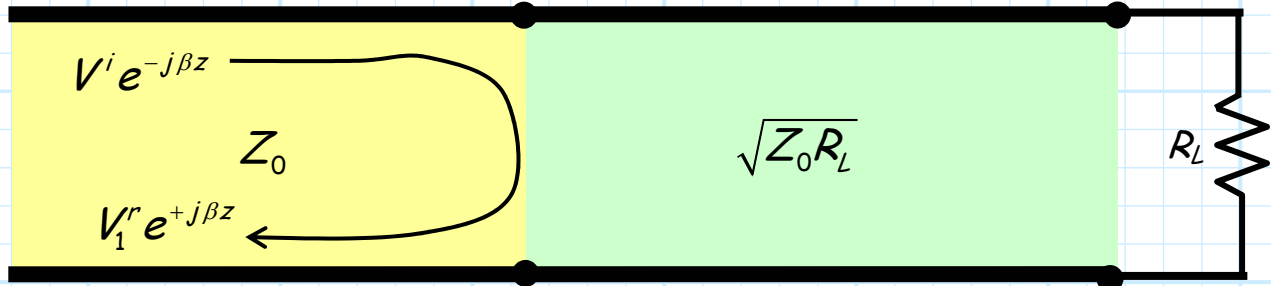1. At  $z = -\ell$ , the characteristic impedance of the transmission line changes from  $Z_0$  to  $Z_1$ . This mismatch creates a **reflected wave**:



where  $V_1^r = \Gamma_1 V^i$ .

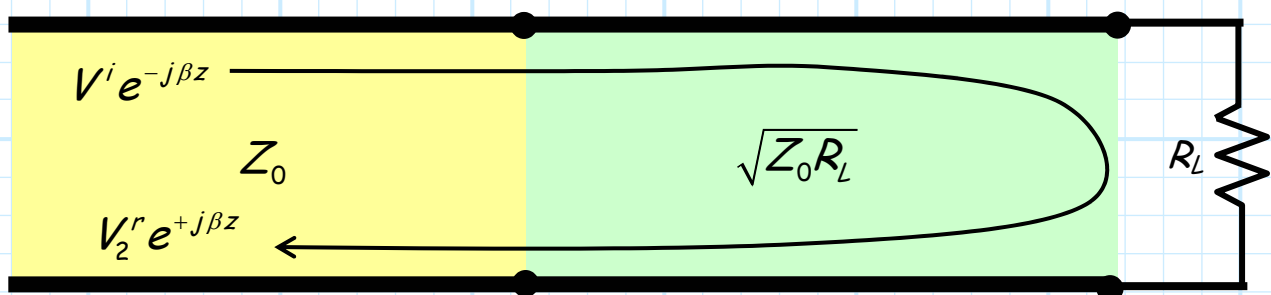
2. However, a **portion** of the incident wave is transmitted ( $T_1$ ) across the interface at  $z = -\ell$ , this wave travels a distance of  $\beta\ell = 90^\circ$  to the load at  $z = 0$ , where a portion of it is reflected ( $\Gamma_3$ ). This wave travels back  $\beta\ell = 90^\circ$  to the interface at  $z = -\ell$ , where a portion is again transmitted ( $T_2$ ) across into the  $Z_0$  transmission line—**another** reflected wave ( $V_2^r$ )!



where we have found that traveling  $2\beta\ell = 180^\circ$  has produced a **minus** sign in our result:

$$\begin{aligned} V_2^r &= T_2 e^{-j90^\circ} \Gamma_3 e^{-j90^\circ} T_1 V^i \\ &= -T_1 T_2 \Gamma_3 V^i \end{aligned}$$

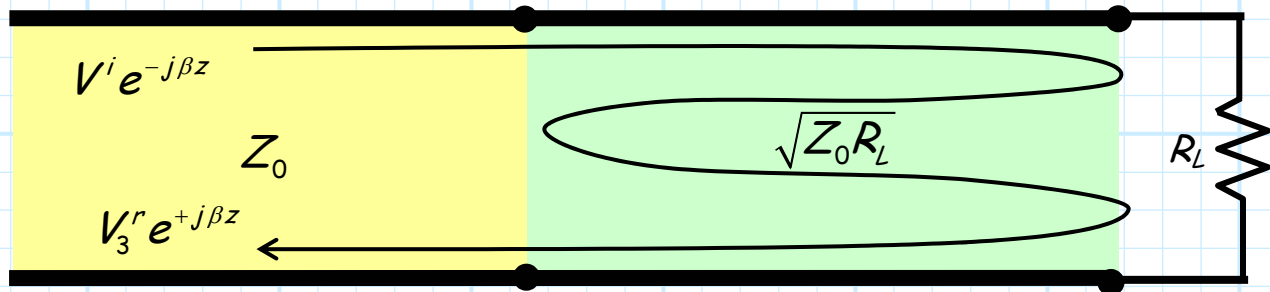3. However, a **portion** of this **second** wave is also **reflected** ( $\Gamma_2$ ) back into the  $Z_1$  transmission line at  $z = -\ell$ , where it again travels to  $\beta\ell = 90^\circ$  the load, is partially reflected ( $\Gamma_3$ ), travels  $\beta\ell = 90^\circ$  back to  $z = -\ell$ , and is partially transmitted into  $Z_0$  ( $T_2$ )—our **third** reflected wave!



where:

$$\begin{aligned} V_3^r &= T_2 e^{-j90^\circ} \Gamma_3 e^{-j90^\circ} \Gamma_2 e^{-j90^\circ} \Gamma_3 e^{-j90^\circ} T_1 V^i \\ &= T_1 T_2 (\Gamma_3)^2 \Gamma_2 V^i \end{aligned}$$

*n.* We can see that this “bouncing” back and forth can go on **forever**, with each trip launching a **new** reflected wave into the  $Z_0$  transmission line.

Note however, that the **power** associated with each successive reflected wave is **smaller** than the previous, and so eventually, the power associated with the reflected waves will **diminish** to insignificance!

**Q:** *But, why then is  $\Gamma = 0$  ?*

**A:** Each reflected wave  $V_n^r$  is a **coherent** wave. That is, they all oscillate at same frequency  $\omega$ ; the reflected waves differ only in terms of their **magnitude** and **phase**.

Therefore, to determine the **total** reflected wave, we must perform a **coherent summation** of each reflected wave—a operation easily performed since we have expressed our waves with **complex** notation:

$$V^r e^{+j\beta z} = \sum_{n=1}^{\infty} V_n^r e^{+j\beta z}$$

It can be shown that this infinite series **converges**, with the result:

$$V^r = \left( \frac{\Gamma_1 + \Gamma_1 \Gamma_2 \Gamma_3 - T_1 T_2 \Gamma_3}{1 + \Gamma_2 \Gamma_3} \right) V^i$$

Thus, the **total** reflection coefficient is:

$$\Gamma = \frac{V^r}{V^i} = \frac{\Gamma_1 + \Gamma_1 \Gamma_2 \Gamma_3 - T_1 T_2 \Gamma_3}{1 + \Gamma_2 \Gamma_3}$$

Using our definitions, it can likewise be shown that the **numerator** of the above expression is:

$$\Gamma_1 + \Gamma_1 \Gamma_2 \Gamma_3 - T_1 T_2 \Gamma_3 = \frac{2(Z_1^2 - Z_0 R_L)}{(Z_1 + Z_0)(R_L + Z_1)}$$

It is evident that the numerator (and therefore  $\Gamma$ ) will be **zero** if:

$$Z_1^2 - Z_0 R_L \Rightarrow Z_1 = \sqrt{Z_0 R_L}$$

Just as we expected!

Physically, this results insures that all the reflected waves add coherently together to produce a **zero value!**

A simple example of this phenomenon is the addition of **two** waves with **equal** magnitude and **opposite** phase (i.e., their phase difference is  $180^\circ$ ).

$$\cos(\omega t) + \cos(\omega t + 180^\circ) = \cos(\omega t) - \cos(\omega t) = 0$$

Note **all** of our transmission line analysis has been **steady-state** analysis. We assume our signals are **sinusoidal**, of the form  $\exp(j\omega t)$ . Note this signal exists for **all time**  $t$ —the signal is assumed to have been “on” **forever**, and assumed to continue on forever.

In other words, in steady-state analysis, **all** the multiple reflections have long since occurred, and thus have reached a steady state—the reflected wave is **zero!**