


Laboratório 3

Filtros Ativos Passa-Alta


Referência

OP AMPS for Everyone

Newnes, 2009

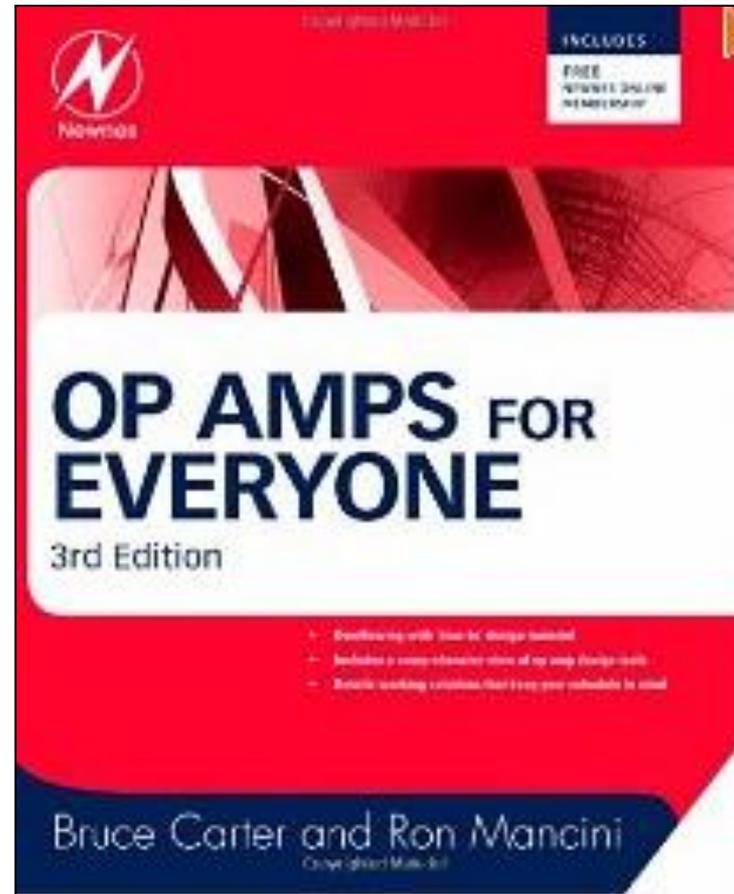


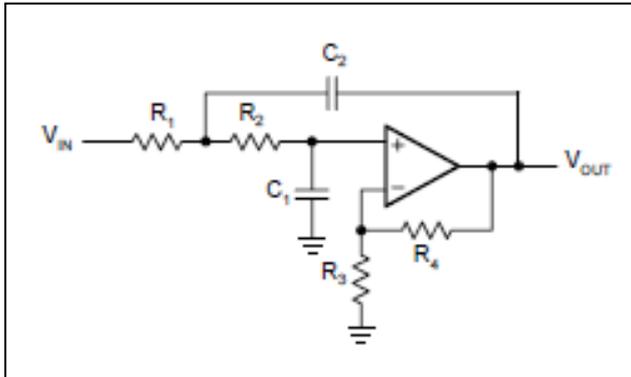1 By replacing the resistors of a low-pass filter with capacitors, and its capacitors with resistors a high-pass filter is created




General Sallen-Key **Low Pass** Topology

($G \neq 1$)

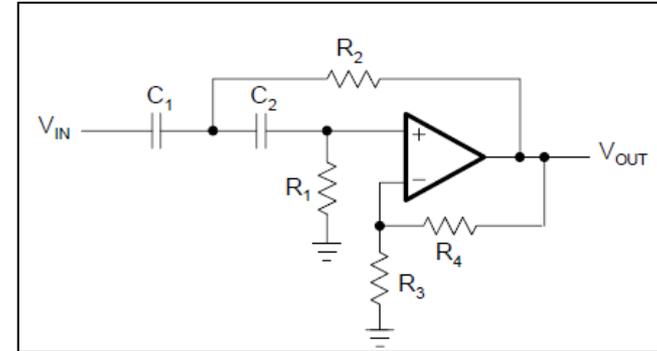


General Sallen-Key **High Pass** Topology

($G \neq 1$)

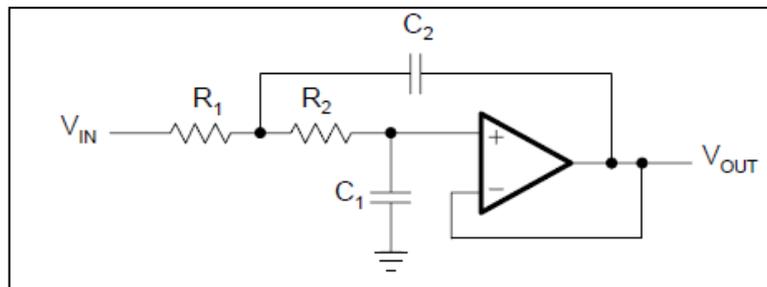

Unit Gain Sallen-Key **Low Pass** Topology

($G = 1$)

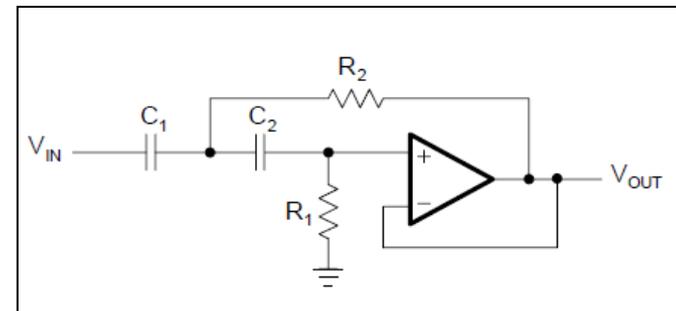


Unit Gain Sallen-Key **High Pass** Topology


($G = 1$)

2 To plot the gain response of a high-pass filter mirror the gain response of a low-pass filter **replacing Ω with $1/\Omega$ and s with $1/s$**
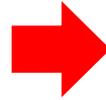
$$A(s) = \frac{A_0}{\prod_i (1 + a_i s + b_i s^2)}$$



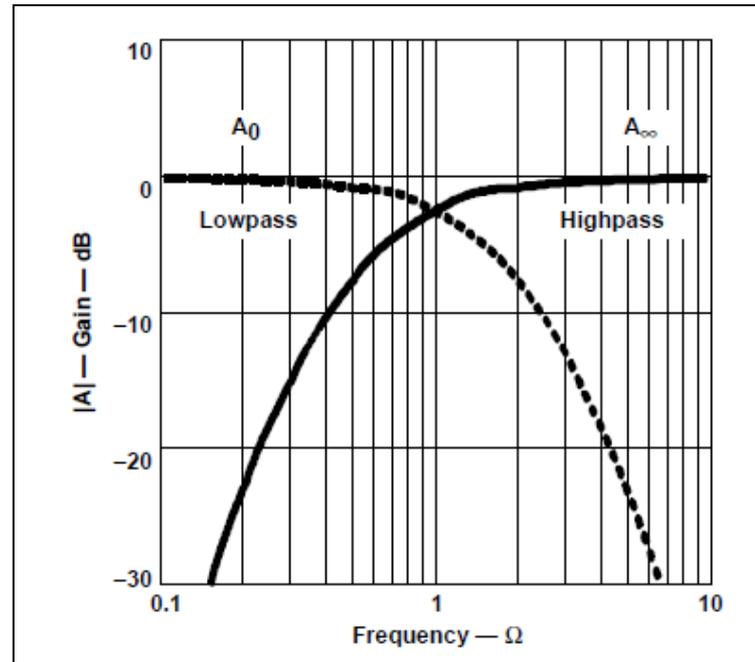
$$A(s) = \frac{A_\infty}{\prod_i \left(1 + \frac{a_i}{s} + \frac{b_i}{s^2}\right)}$$



High Pass Filters

First Order Topology


Inverting

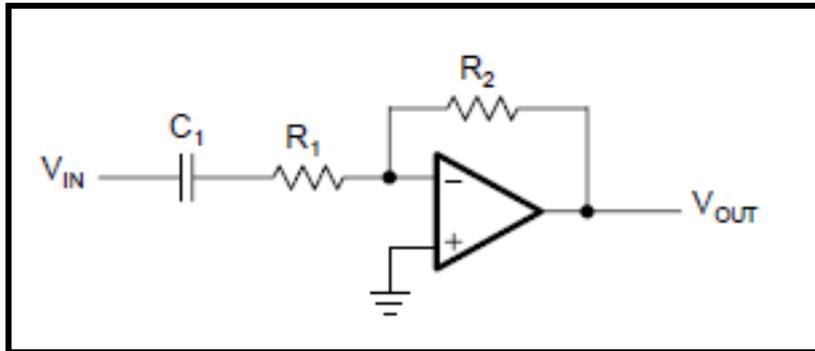

$$A(s) = - \frac{\frac{R_2}{R_1}}{1 + \frac{1}{\omega_c R_1 C_1} \cdot \frac{1}{s}}$$

$$A_\infty = - \frac{R_2}{R_1}$$

Noninverting

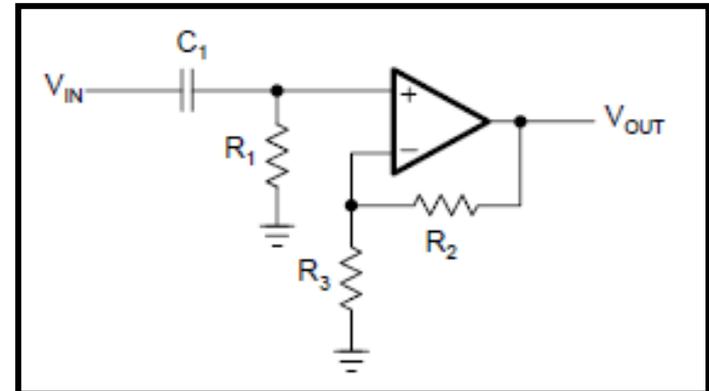


$$A(s) = \frac{1 + \frac{R_2}{R_3}}{1 + \frac{1}{\omega_c R_1 C_1} \cdot \frac{1}{s}}$$

$$A_\infty = 1 + \frac{R_2}{R_3}$$

**Designing
High Pass Filters
First Order Topology**

Inverting

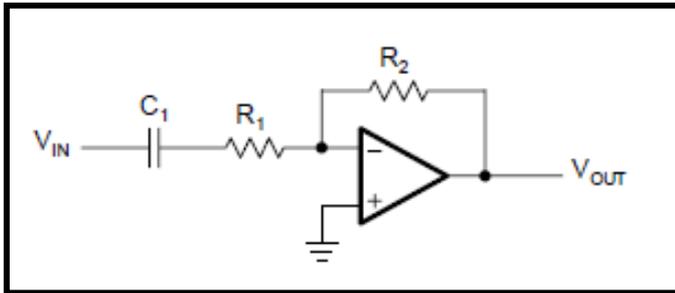


1 Specify f_c , A_∞ , C_1

2
$$R_1 = \frac{1}{2\pi f_c a_1 C_1}$$

3
$$R_2 = -R_1 A_\infty$$

Noninverting

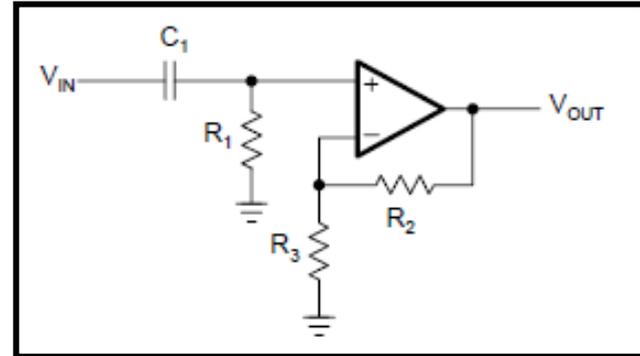

1 Specify f_c , A_∞ , C_1

2
$$R_1 = \frac{1}{2\pi f_c a_1 C_1}$$

3
$$R_2 = R_3(A_\infty - 1)$$


Pick R_2 and determine R_3

High Pass Filters

Second Order Topology

Sallen-Key Topology


General Sallen-Key Topology

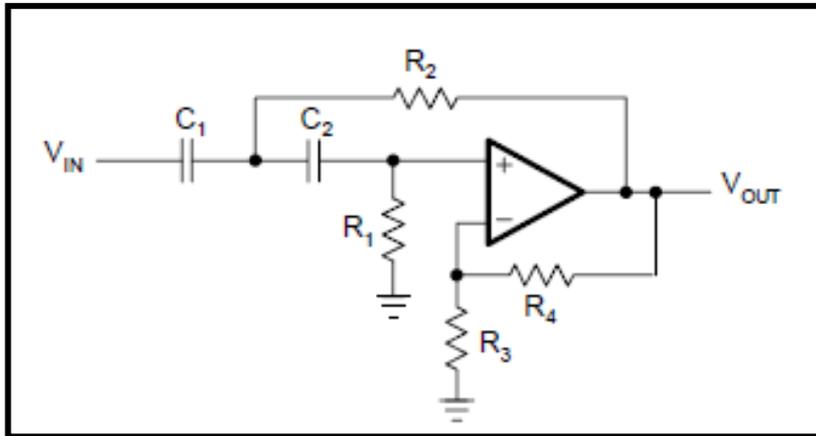

$$A(s) = \frac{\alpha}{1 + \frac{R_2(C_1 + C_2) + R_1 C_2(1 - \alpha)}{\omega_c R_1 R_2 C_1 C_2} \cdot \frac{1}{s} + \frac{1}{\omega_c^2 R_1 R_2 C_1 C_2} \cdot \frac{1}{s^2}}$$

$$\alpha = 1 + \frac{R_4}{R_3}$$

Unit Gain Sallen-Key Topology

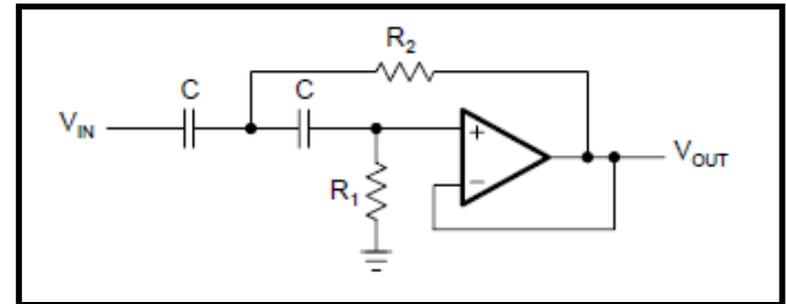


$$A(s) = \frac{1}{1 + \frac{2}{\omega_c R_1 C} \cdot \frac{1}{s} + \frac{1}{\omega_c^2 R_1 R_2 C^2} \cdot \frac{1}{s^2}}$$

$$\alpha = 1$$

Multiple Feedback Topology

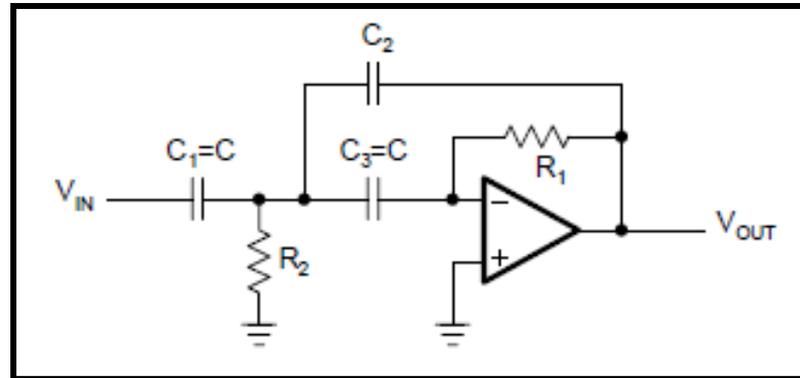The MFB topology is commonly used in filters that have high Qs and require a high gain




$$A(s) = - \frac{\frac{C}{C_2}}{1 + \frac{2C + C_2}{\omega_c R_1 C C_2} \cdot \frac{1}{s} + \frac{2C + C_2}{\omega_c R_1 C C_2} \cdot \frac{1}{s^2}}$$

$$A_\infty = \frac{C}{C_2}$$

**Designing
High Pass Filters
Second Order Topology**

Sallen-Key Topology (unit gain)

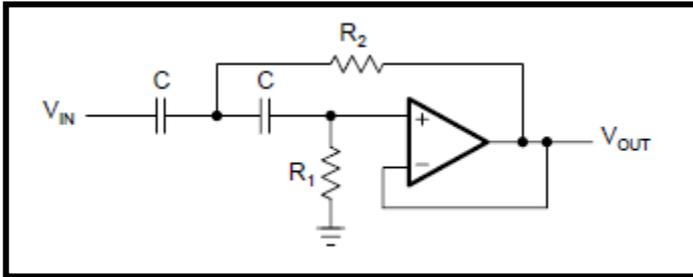

$$A(s) = \frac{1}{1 + \frac{2}{\omega_c R_1 C} \cdot \frac{1}{s} + \frac{1}{\omega_c^2 R_1 R_2 C^2} \cdot \frac{1}{s^2}}$$


1 Get the filter coefficients

2 Specify C

$$3 \quad R_1 = \frac{1}{\pi f_c C a_1}$$

$$4 \quad R_2 = \frac{a_1}{4\pi f_c C b_1}$$

Multiple Feedback Topology

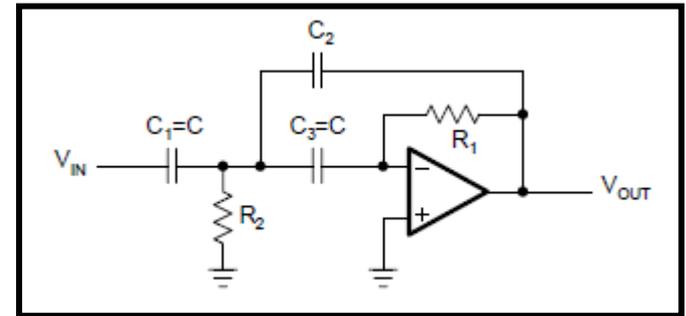

$$A(s) = - \frac{\frac{C}{C_2}}{1 + \frac{2C+C_2}{\omega_c R_1 C C_2} \cdot \frac{1}{s} + \frac{2C+C_2}{\omega_c R_1 C C_2} \cdot \frac{1}{s^2}}$$

$$A_\infty = \frac{C}{C_2}$$

1 Get the filter coefficients

2 Pick C and C₂

$$3 \quad R_1 = \frac{1 - 2A_\infty}{2\pi f_c \cdot C \cdot a_1}$$

$$4 \quad R_2 = \frac{a_1}{2\pi f_c \cdot b_1 C_2 (1 - 2A_\infty)}$$

**Designing
High Pass Filters
Higher Order Topology**

Example 1:

Design a third-order Sallen-Key unity-gain Bessel high-pass filter with the corner frequency $f_c = 1$ kHz.


1 Get the Bessel coefficients

Table 16-4. Bessel Coefficients

n	i	a_i	b_i	$k_i = f_{Ci} / f_c$	Q_i
1	1	1.0000	0.0000	1.000	—
2	1	1.3617	0.6180	1.000	0.58
3	1	0.7560	0.0000	1.323	—
	2	0.9996	0.4772	1.414	0.69
4	1	1.3397	0.4889	0.978	0.52
	2	0.7743	0.3890	1.797	0.81
5	1	0.6656	0.0000	1.502	—
	2	1.1402	0.4128	1.184	0.56
	3	0.6216	0.3245	2.138	0.92



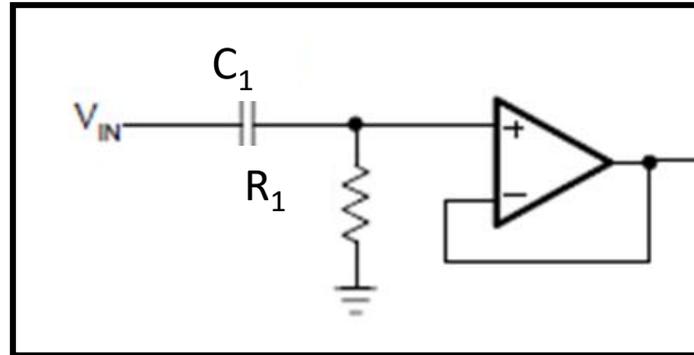First Filter: first order non-inverting with unit gain




2 Bessel coefficients: $a_1 = 0.756$, $b_1 = 0$

3 Pick $C_1 \rightarrow C_1 = 100\text{nF}$

4 Get $R_1 \rightarrow R_1 = \frac{1}{2\pi f_c a_1 C_1} = \frac{1}{2\pi \cdot 10^3 \text{Hz} \cdot 0.756 \cdot 100 \cdot 10^{-9} \text{F}} = 2.105 \text{ k}\Omega$

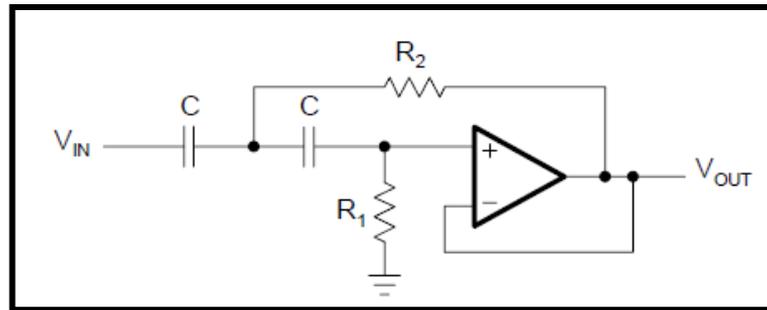Second Filter: second order SK with unit gain



5 Bessel coefficients: $a_2 = 0.996$, $b_2 = 0.4772$

6 Pick C \longrightarrow C = 100nF

7 $R_1 = \frac{1}{\pi f_c C a_1} \longrightarrow R_1 = \frac{1}{\pi f_c C a_1} = \frac{1}{\pi \cdot 10^3 \cdot 100 \cdot 10^{-9} \cdot 0.756} = 3.18 \text{ k}\Omega$

8 $R_2 = \frac{a_2}{4\pi f_c C a_2} \longrightarrow R_2 = \frac{a_1}{4\pi f_c C b_1} = \frac{0.9996}{4\pi \cdot 10^3 \cdot 100 \cdot 10^{-9} \cdot 0.4772} = 1.67 \text{ k}\Omega$

**Third-order Sallen Key unity-gain Bessel high-pass filter
with the corner frequency $f_c = 1$ kHz.**

