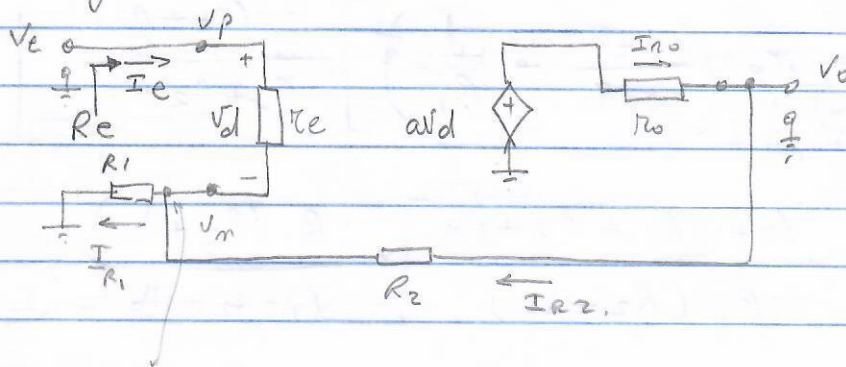


a) Configuração amplificada não inversor:



$R_e = ?$

$R_o = ?$

$A = ?$

$V_m = V_e - V_d$

$V_p = V_e$

$V_d = r_e I_e$

$I_e + I_{R2} = I_{R1}$

$I_{R1} = \frac{V_m}{R_1} = \frac{V_e - V_d}{R_1} = \frac{V_e - r_e I_e}{R_1}$

$I_{R2} = \frac{V_o - V_m}{R_2} = \frac{V_o - V_e + V_d}{R_2} = \frac{V_o - V_e + V_d}{R_2}$

$V_o = a V_d - r_o I_{R2}$

$I_{R2} = \frac{a V_d - r_o I_{R2} - V_e + r_e I_e}{R_2} = \frac{a r_e I_e - r_o I_{R2} - V_e + r_e I_e}{R_2}$

$I_{R2} + \frac{r_o}{R_2} I_{R2} = I_{R2} \left(1 + \frac{r_o}{R_2} \right) = \frac{a r_e I_e}{R_2} - \frac{V_e}{R_2} + \frac{r_e I_e}{R_2}$

$I_{R2} \left(1 + \frac{r_o}{R_2} \right) = \left(\frac{a r_e + r_e}{R_2} \right) I_e - \frac{V_e}{R_2}$

Atual: $I_e + \left[\frac{a r_e + r_e}{R_2} I_e - \frac{V_e}{R_2} \right] \frac{1}{\left(1 + \frac{r_o}{R_2} \right)} = \frac{V_e}{R_1} - \frac{r_e I_e}{R_1}$

$I_e + \frac{(a+1)r_e}{R_2} I_e \frac{R_2}{R_2 + r_o} + \frac{r_e}{R_1} I_e = \frac{V_e}{R_1} + \frac{R_2}{R_2(R_2 + r_o)} V_e$

$I_e \left[1 + \frac{(a+1)r_e}{R_2 + r_o} + \frac{r_e}{R_1} \right] = \left(\frac{1}{R_1} + \frac{1}{R_2 + r_o} \right) V_e = \frac{R_2 + r_o + R_1}{R_1(R_2 + r_o)} V_e$

$$\frac{V_e}{I_e} = R_e = \frac{1}{R_2 + R_1 + R_0} \times \left[1 + \frac{R_e (a+1)}{R_2 + R_0} + \frac{R_e}{R_1} \right]$$

$$R_e = \left[1 + R_e \left(\frac{a+1}{R_2 + R_0} + \frac{1}{R_1} \right) \right] \frac{R_1 (R_2 + R_0)}{R_2 + R_2 + R_0} =$$

$$= \left[1 + R_e \frac{(a+1)R_1 + R_2 + R_0}{R_1 (R_2 + R_0)} \right] \times \frac{R_1 (R_2 + R_0)}{R_1 + R_2 + R_0}$$

$$R_e = \frac{R_1 (R_2 + R_0)}{R_1 + R_2 + R_0} + \frac{R_1 (R_2 + R_0)}{R_1 + R_2 + R_0} \times \frac{(a+1)R_1 + R_2 + R_0}{R_1 (R_2 + R_0)} \times R_e$$

$$R_e = R_e \frac{(a+1)R_1 + R_2 + R_0}{R_1 + R_2 + R_0} + \frac{R_1 (R_2 + R_0)}{R_1 + R_2 + R_0}$$

$$R_e = R_e \frac{aR_1 + (R_1 + R_2 + R_0)}{R_1 + R_2 + R_0} + \frac{R_1 (R_2 + R_0)}{R_1 + R_2 + R_0} =$$

$$= R_e \left(\frac{aR_1}{R_1 + R_2 + R_0} + \frac{R_1 + R_2 + R_0}{R_1 + R_2 + R_0} \right) + \frac{R_1 (R_2 + R_0)}{R_1 + R_2 + R_0} =$$

$$= R_e \left(1 + \frac{aR_1}{R_1 + R_2 + R_0} \right) + \frac{R_1 (R_2 + R_0)}{R_1 + R_2 + R_0}$$

$$\text{Se } R_0 \ll R_d \quad \& \quad \ll R_1 + R_2 \Rightarrow$$

$$R_e = R_e \left(1 + \frac{aR_1}{R_1 + R_2} \right) + \frac{R_1 (R_2 + R_0)}{R_1 + R_2}$$


$$\& \text{ se } R_1, R_2 \gg R_0 \Rightarrow R_e = R_e \left(1 + \frac{aR_1}{R_1 + R_2} \right) + \frac{R_1 R_2}{R_1 + R_2}$$

$$\& \text{ se } R_1 // R_2 \ll R_d \quad \& \quad b = \frac{R_1}{R_1 + R_2} \Rightarrow \boxed{R_e = R_e (1 + ab)}$$

$$a \rightarrow \infty \Rightarrow ab \rightarrow \infty \Rightarrow \boxed{R_e \rightarrow \infty}$$

$$R_o = ?$$

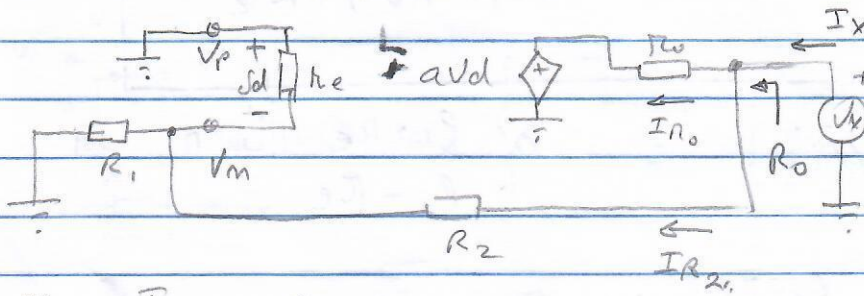Para se obter R_o , ative-se a entrada e aplica-se uma tensão de teste, v_x , aos terminais de saída:



$$I_x = I_{R_o} + I_{R_2}$$

$$I_{R_o} = \frac{v_x - a v_d}{r_o} \quad ; \quad I_{R_2} = \frac{v_x - v_m}{R_2}$$

$$I_x = \frac{v_x}{r_o} - \frac{a v_d}{r_o} + \frac{v_x - v_m}{R_2} \quad v_d = -v_m$$

$$v_m = \frac{(R_1 // r_e)}{(R_1 // r_e) + R_2} v_x \Rightarrow$$

$$I_x = \frac{v_x}{r_o} + \frac{a v_m}{r_o} + \frac{v_x - v_m}{R_2} =$$

$$= \frac{v_x}{r_o} + \frac{a (R_1 // r_e)}{[(R_1 // r_e) + R_2]} \frac{v_x}{r_o} + \frac{v_x}{R_2} - \frac{(R_1 // r_e)}{(R_1 // r_e) + R_2} \frac{v_x}{R_2}$$

$$\frac{1}{R_2} - \frac{(R_1 // r_e)}{(R_1 // r_e) + R_2} \times \frac{1}{R_2} = \frac{(R_1 // r_e) + R_2 - (R_1 // r_e)}{[(R_1 // r_e) + R_2] R_2} =$$

$$= \frac{R_2}{[(R_1 // r_e) + R_2] R_2} = \frac{1}{(R_1 // r_e) + R_2}$$

$$\therefore I_x = v_x \left[\frac{1}{r_o} + \frac{a (R_1 // r_e)}{[(R_1 // r_e) + R_2] r_o} + \frac{1}{(R_1 // r_e) + R_2} \right]$$

$$I_x = v_x \frac{1}{r_o} \left[1 + \frac{a (R_1 // r_e)}{(R_1 // r_e) + R_2} + \frac{r_o}{(R_1 // r_e) + R_2} \right]$$

$$I_x = v_x \frac{1}{r_o} \left[1 + \frac{a (R_1 // r_e) + r_o}{(R_1 // r_e) + R_2} \right]$$

$$\frac{V_x}{I_x} = R_0 = \frac{R_0}{1 + \frac{a(R_1 // R_e) + R_0}{(R_1 // R_e) + R_2}}$$

$$a(R_1 // R_e) + R_0 = a \frac{R_1 \times R_e}{R_1 + R_e} + R_0$$

$$\text{Se } a \frac{R_1 \times R_e}{R_1 + R_e} \gg R_0 \Rightarrow$$

$$R_0 = \frac{R_0}{1 + \frac{a(R_1 // R_e)}{(R_1 // R_e) + R_2}}$$

$$\text{Se } R_1 \ll R_e \Rightarrow R_0 = \frac{R_0}{1 + \frac{aR_1}{R_1 + R_2}}$$

$$\frac{R_1}{R_1 + R_2} = b$$


$$\Rightarrow \boxed{R_0 = \frac{R_0}{1 + ab}}$$

$$ab \rightarrow \infty \Rightarrow R_0 \rightarrow 0 \quad (R_0 = 0)$$

P2



A ?

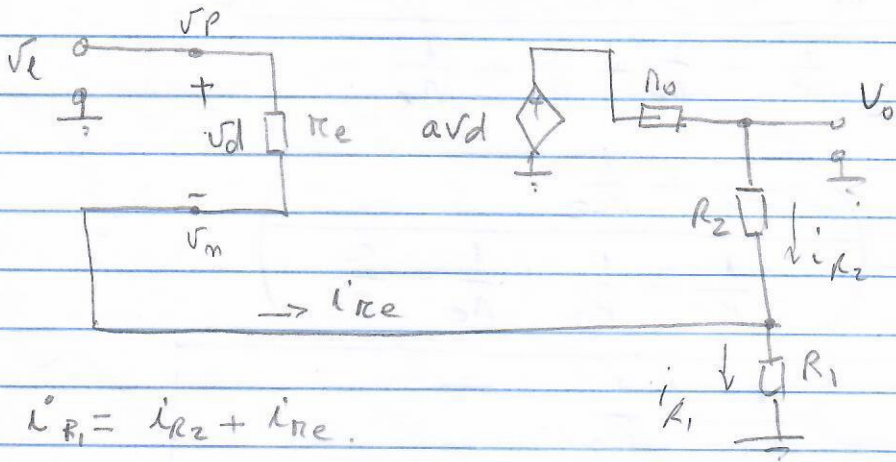

$$i_{R_1} = i_{R_2} + i_{r_e}$$

$$i_{R_1} = \frac{v_m}{R_1} \quad ; \quad i_{R_2} = \frac{v_o - v_m}{R_2} \quad ; \quad i_{r_e} = \frac{v_p - v_m}{r_e}$$

$$\frac{v_m}{R_1} = \frac{v_o - v_m}{R_2} + \frac{v_p - v_m}{r_e} \quad ; \quad v_p = v_e$$

$$\frac{v_m}{R_1} = \frac{v_o - v_m}{R_2} + \frac{v_e - v_m}{r_e}$$

$$v_m = \frac{a(v_p - v_m) - i_{R_2} R_o}{R_2} - \frac{v_m}{R_2}$$

base no $\ll R_2 \Rightarrow \frac{v_m}{R_1} = \frac{a v_e - a v_m}{R_2} + \frac{v_e - v_m}{r_e}$

$$v_m \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_e} + \frac{a}{R_2} \right) = v_e \left(\frac{1}{r_e} + \frac{a}{R_2} \right)$$

$$v_m = v_e \left(\frac{1}{r_e} + \frac{a}{R_2} \right) \times \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{a}{R_2} + \frac{1}{r_e}}$$

$$v_o = a(v_p - v_m) = a v_e - a v_e \left(\frac{1}{r_e} + \frac{a}{R_2} \right) \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{a}{R_2} + \frac{1}{r_e}}$$

$$A_v = \frac{v_o}{v_e} = a \left[1 - \left(\frac{1}{r_e} + \frac{a}{R_2} \right) \times \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{a}{R_2} + \frac{1}{r_e}} \right]$$

$$A_v = a \left[\frac{\frac{1}{R_1} + \frac{1}{R_2} + \frac{a}{R_2} + \frac{1}{R_e} - \frac{1}{R_e} - \frac{a}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{a}{R_2} + \frac{1}{R_e}} \right]$$

$$A_v = a \left(\frac{\frac{1}{R_2} + \frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_e} + \frac{a}{R_2}} \right)$$



$$A_v = \frac{\frac{1}{R_1} + \frac{1}{R_2}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_e} \right) \frac{1}{a} + \frac{1}{R_2}}$$

$$\text{Se } a \rightarrow \infty \Rightarrow A_v = \frac{\frac{1}{R_1} + \frac{1}{R_2}}{\frac{1}{R_2}} = \frac{R_1 + R_2}{\frac{R_1 R_2}{R_2}}$$

$$A_v = \frac{R_1 + R_2}{R_1 R_2} \times R_2 = \frac{R_1 + R_2}{R_1}$$

$$A_v = \left(1 + \frac{R_2}{R_1} \right)$$

b) Configuração amplificador inversor:

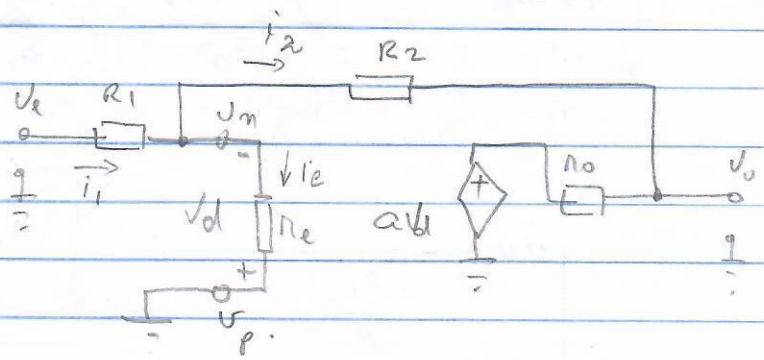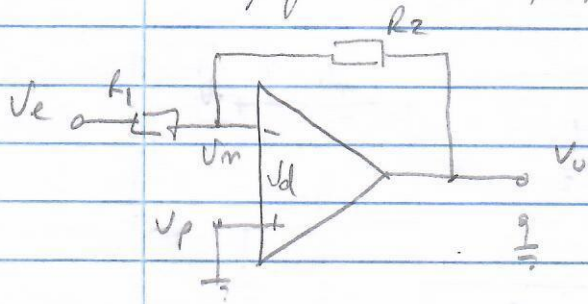

$$V_d = V_p - V_m = -V_m$$

$$A_v = ?$$

$$i_1 = i_2 + i_e \quad i_1 = \frac{V_e - V_m}{R_1} \quad ; \quad i_e = \frac{V_m}{R_e} \quad ;$$

$$i_2 = \frac{V_m - V_o}{R_2}$$

Para $R_o \ll R_2 \Rightarrow V_o = aV_d = a(V_p - V_m) = -aV_m$.

$$i_2 = \frac{V_m - (-aV_m)}{R_2} = \frac{V_m(1+a)}{R_2}$$

$$\frac{V_e - V_m}{R_1} = \frac{V_m(1+a)}{R_2} + \frac{V_m}{R_e} = \frac{V_e}{R_1} - \frac{V_m}{R_1}$$

$$V_m \left(\frac{1}{R_1} + \frac{1}{R_e} + \frac{(1+a)}{R_2} \right) = \frac{V_e}{R_1}$$

$$V_m = \frac{V_e}{R_1} \times \frac{1}{\frac{1}{R_1} + \frac{1}{R_e} + \frac{1+a}{R_2}} = V_e \frac{1}{1 + \frac{R_1}{R_e} + \frac{(1+a)R_1}{R_2}}$$

$$V_o = -aV_m = - \frac{aV_e}{1 + \frac{R_1}{R_e} + \frac{(1+a)R_1}{R_2}}$$

$$A_v = \frac{V_o}{V_e} = - \frac{a}{1 + \frac{R_1}{R_e} + \frac{(1+a)R_1}{R_2}}$$

Para $a \rightarrow \infty \Rightarrow$

$$A_v = - \frac{1}{\frac{1}{a} + \frac{R_1}{a\beta R_e} + \frac{(1+a)R_1}{a R_2}}$$

$$A_v = - \frac{1}{\frac{R_1}{R_2}} \quad \therefore \quad \boxed{A_v = - \frac{R_2}{R_1}}$$

$R_e = ?$ $R_e = \frac{V_e}{i_e} = \frac{V_e}{i_b}$

$i_b = \frac{V_e - V_{be}}{R_1} = i_e$

$$i_e = \frac{V_e - V_{be}}{R_1} = \frac{V_e}{R_1} \left[1 - \frac{1}{1 + \frac{R_1}{\beta R_e} + (1+a)\frac{R_1}{R_2}} \right]$$

$$i_e = \frac{V_e}{R_1} \left[\frac{1 + \frac{R_1}{\beta R_e} + (1+a)\frac{R_1}{R_2} - 1}{1 + \frac{R_1}{\beta R_e} + (1+a)\frac{R_1}{R_2}} \right] = \frac{V_e}{R_1} \frac{\frac{R_1}{\beta R_e} + \frac{(1+a)R_1}{R_2}}{1 + \frac{R_1}{\beta R_e} + (1+a)\frac{R_1}{R_2}}$$


$$R_e = \frac{V_e}{i_e} = \frac{V_e R_1 \left(1 + \frac{R_1}{\beta R_e} + \frac{(1+a)R_1}{R_2} \right)}{V_e \left(\frac{R_1}{\beta R_e} + \frac{(1+a)R_1}{R_2} \right)} = R_1 \frac{1 + \frac{R_1}{\beta R_e} + \frac{(1+a)R_1}{R_2}}{\frac{R_1}{\beta R_e} + \frac{(1+a)R_1}{R_2}}$$

$$R_e = \frac{\frac{1}{a} + \frac{R_1}{a\beta R_e} + \frac{(1+a)R_1}{a R_2}}{\frac{R_1}{a\beta R_e} + \frac{(1+a)R_1}{a R_2}} R_1$$

Para $a \rightarrow \infty \Rightarrow R_e = \frac{R_1}{\frac{R_1}{R_2}} R_1$

$\therefore \quad \boxed{R_e = R_1}$

R_0 ?

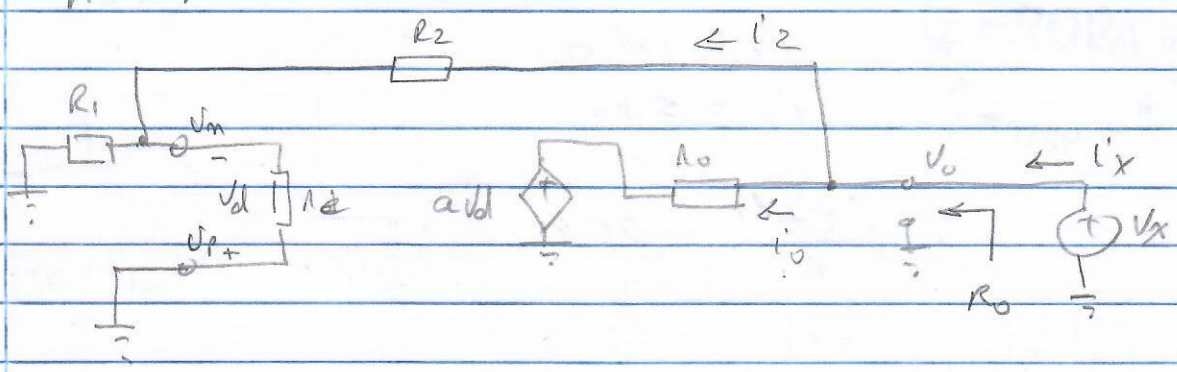

$V_e = 0$

$V_m = \frac{R_1}{R_1 + R_2} V_x$ and $i_x = i_2 + i_0$

$i_2 = \frac{V_x - V_m}{R_2}$ and $i_0 = \frac{V_x - aV_d}{R_0} = \frac{V_x - a(0 - V_m)}{R_0}$

$i_2 = \frac{V_x}{R_2} - \frac{1}{R_2} \frac{R_1}{R_1 + R_2} V_x$

$R_1 \gg R_2$

$i_x = \frac{V_x}{R_2} - \frac{1}{R_2} \frac{R_1}{R_1 + R_2} V_x + \frac{V_x}{R_0} - \frac{a}{R_0} (0 - V_m)$

$i_x = \frac{V_x}{R_2} - \frac{1}{R_2} \frac{R_1}{R_1 + R_2} V_x + \frac{V_x}{R_0} + \frac{a}{R_0} \frac{R_1}{R_1 + R_2} V_x$

$i_x = V_x \left(\frac{1}{R_2} - \frac{R_1}{R_2(R_1 + R_2)} + \frac{1}{R_0} + \frac{a}{R_0} \frac{R_1}{R_1 + R_2} \right)$

$R_0 = \frac{V_x}{i_x} = \frac{V_x}{\dots}$

$\frac{V_x}{V_x \left(\frac{1}{R_2} - \frac{R_1}{R_2(R_1 + R_2)} + \frac{1}{R_0} + \frac{a}{R_0} \frac{R_1}{R_1 + R_2} \right)} =$

$= \frac{1}{\frac{R_1}{R_1 + R_2} \left(\frac{1}{R_2} - \frac{a}{R_0} \right) + \frac{1}{R_0} (1 - a) + \frac{1}{R_2}}$

Para $a \rightarrow \infty \Rightarrow R_0 \rightarrow 0$.