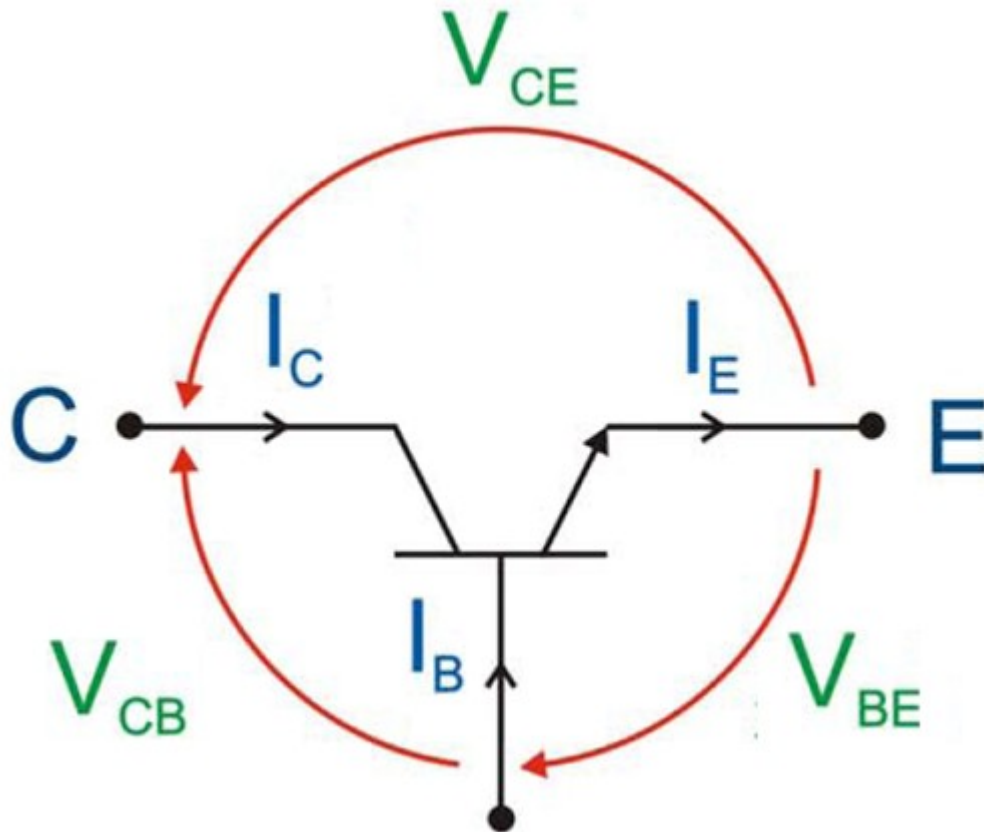


# Aula 19 - Transistor Bipolar




$$I_C = \beta I_B$$

$$\beta = 100-500$$


$$I_E = I_C + I_B \\ = (\beta + 1)I_B$$

$$V_{BE} = 0,7V$$

$$V_{CE} = V_{BE} + V_{CE}$$

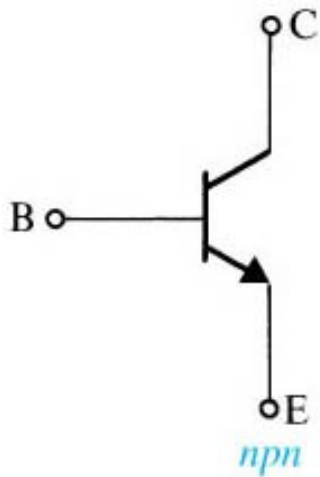

(a)

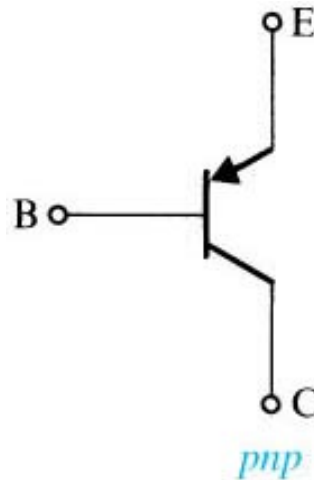

(b)

$$I_C = \beta I_B$$

$$\beta = 100-500$$

$$I_E = I_C + I_B$$



$$= (\beta + 1)I_B$$


$$V_{BE} = V_{EB} = 0,7V$$

$$V_{CE} = V_{BE} + V_{CB}$$


$$V_{EC} = V_{EB} + V_{BC}$$

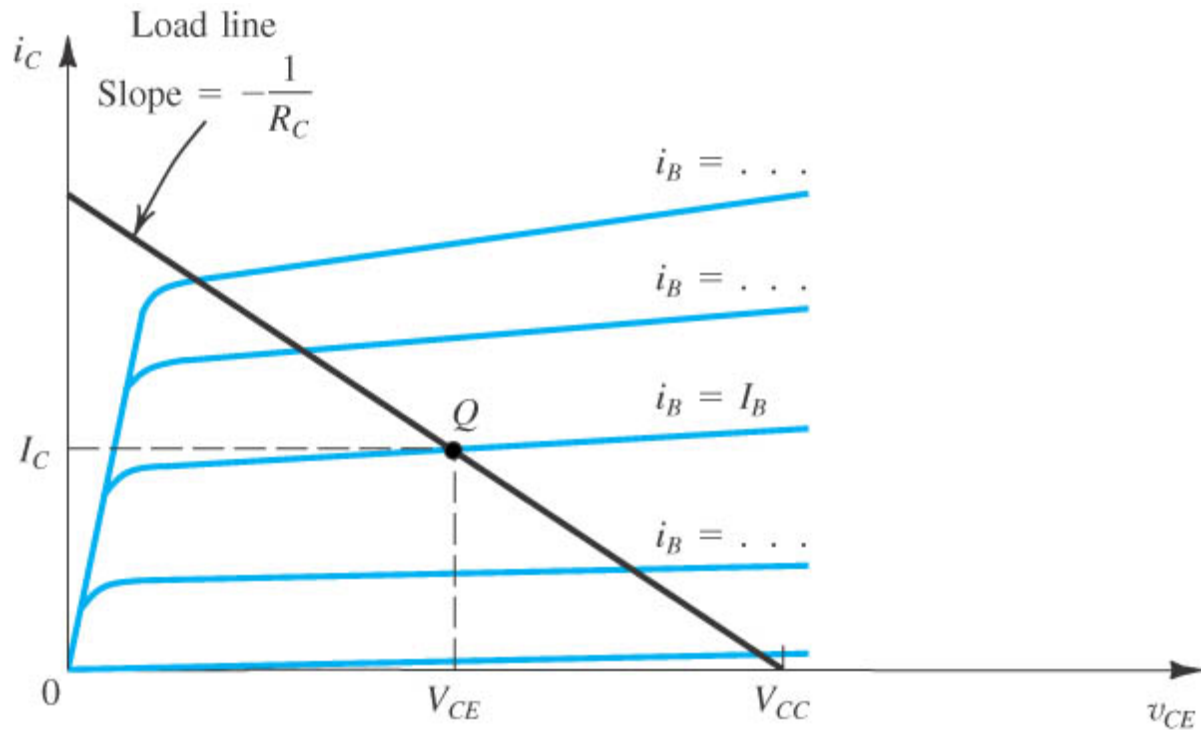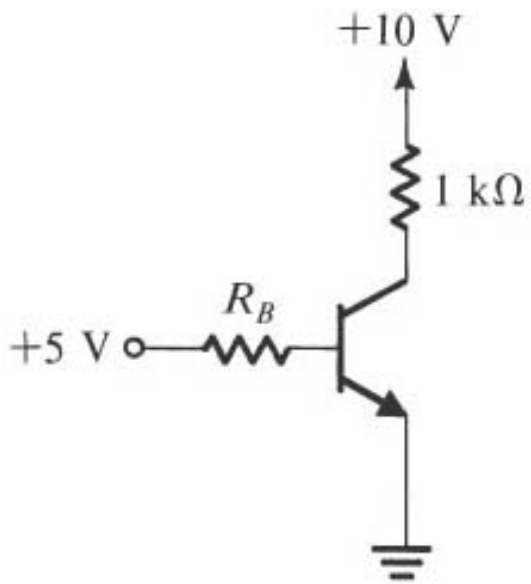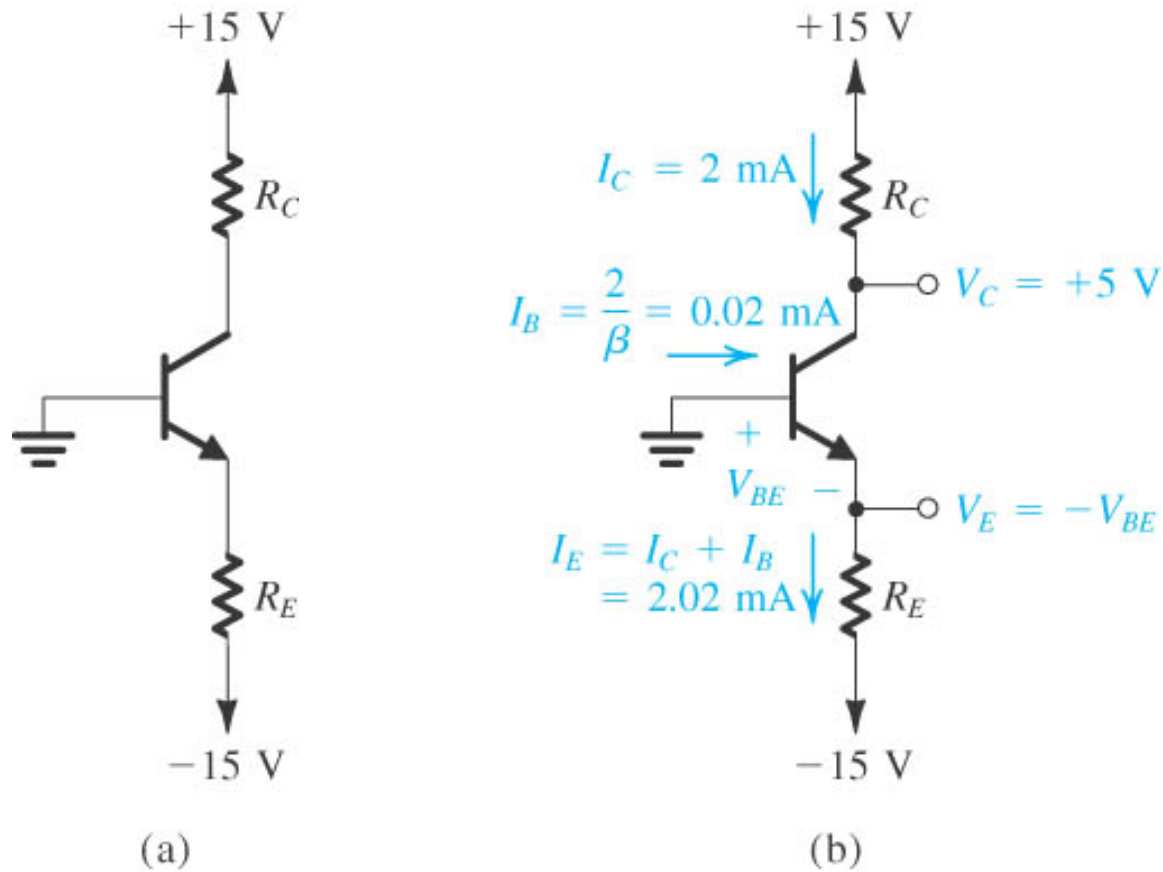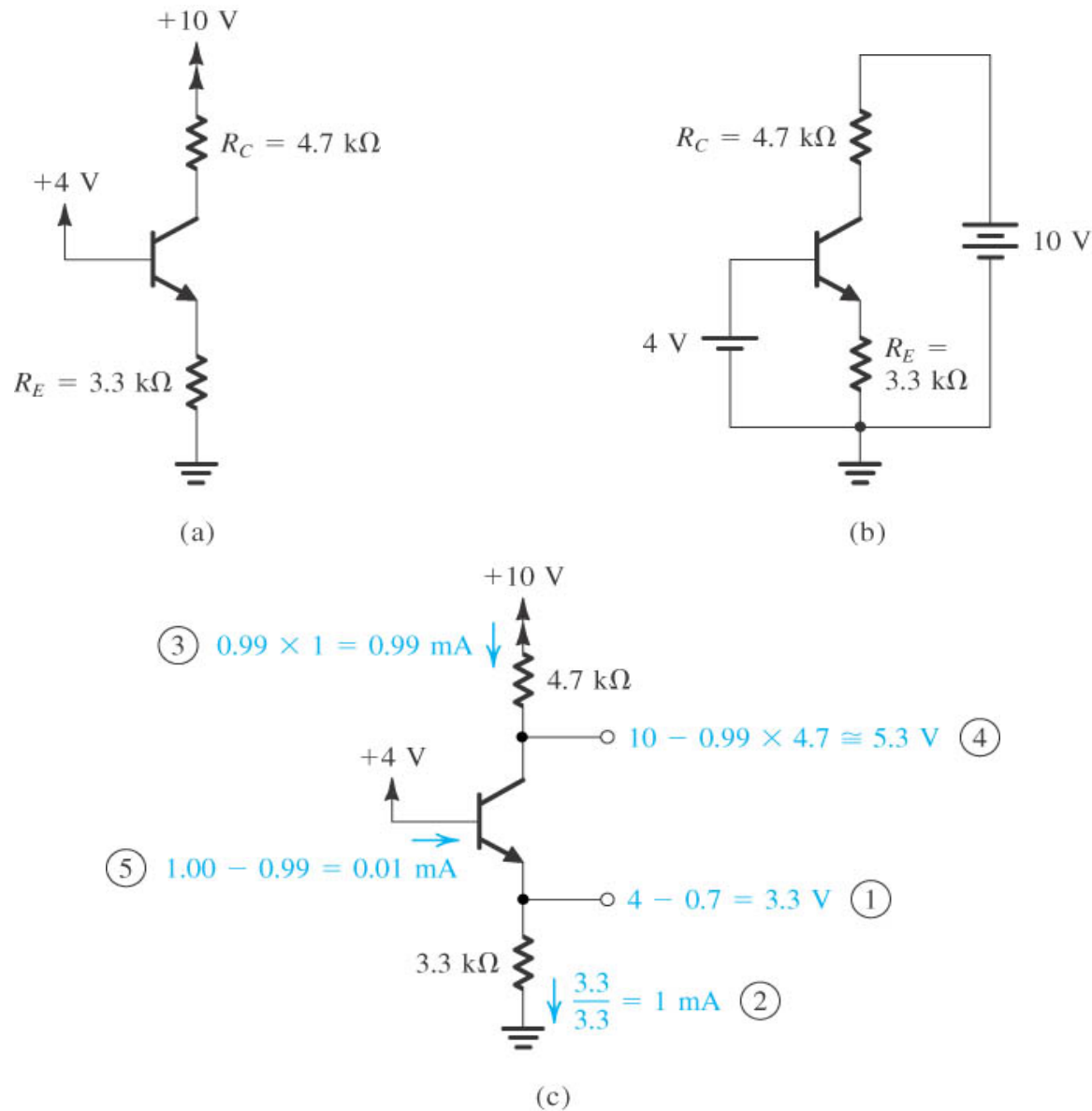**Figure 5.13** Circuit symbols for BJTs.

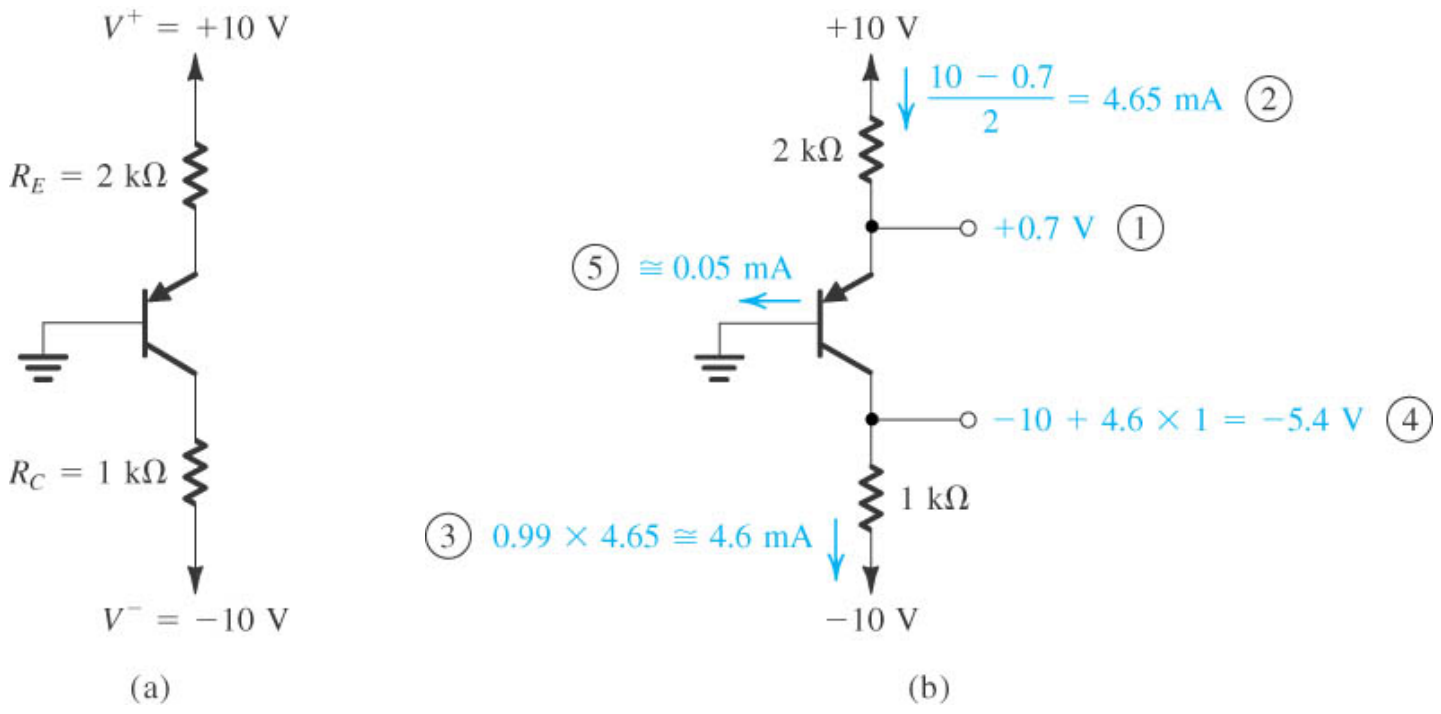





**Figure 5.15** Circuit for Example 5.1.




**Figure 5.34** Analysis of the circuit for Example 5.4: (a) circuit; (b) circuit redrawn to remind the reader of the convention used in this book to show connections to the power supply; (c) analysis with the steps numbered.



**Figure 5.37** Example 5.7: (a) circuit; (b) analysis with the steps indicated by circled numbers.

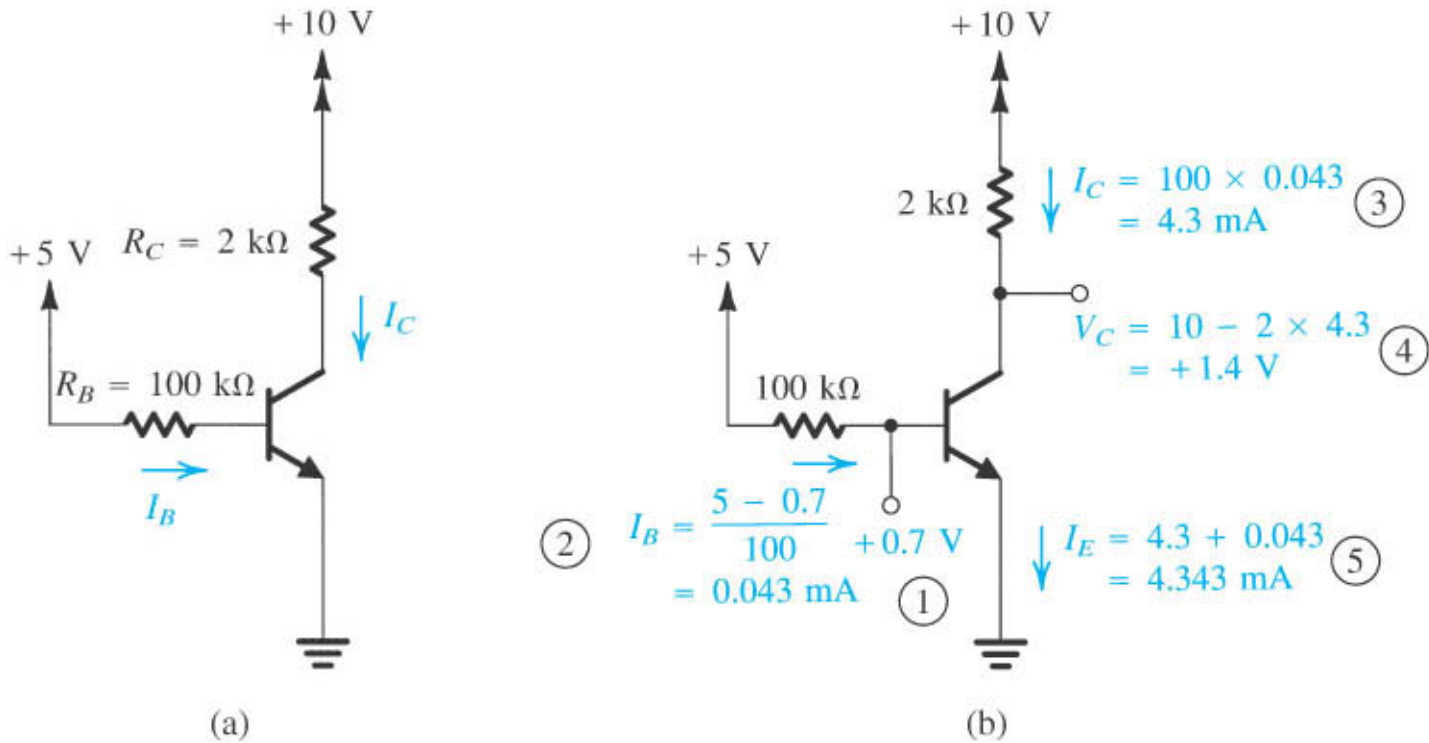


**Figure 5.38** Example 5.8: (a) circuit; (b) analysis with the steps indicated by the circled numbers.

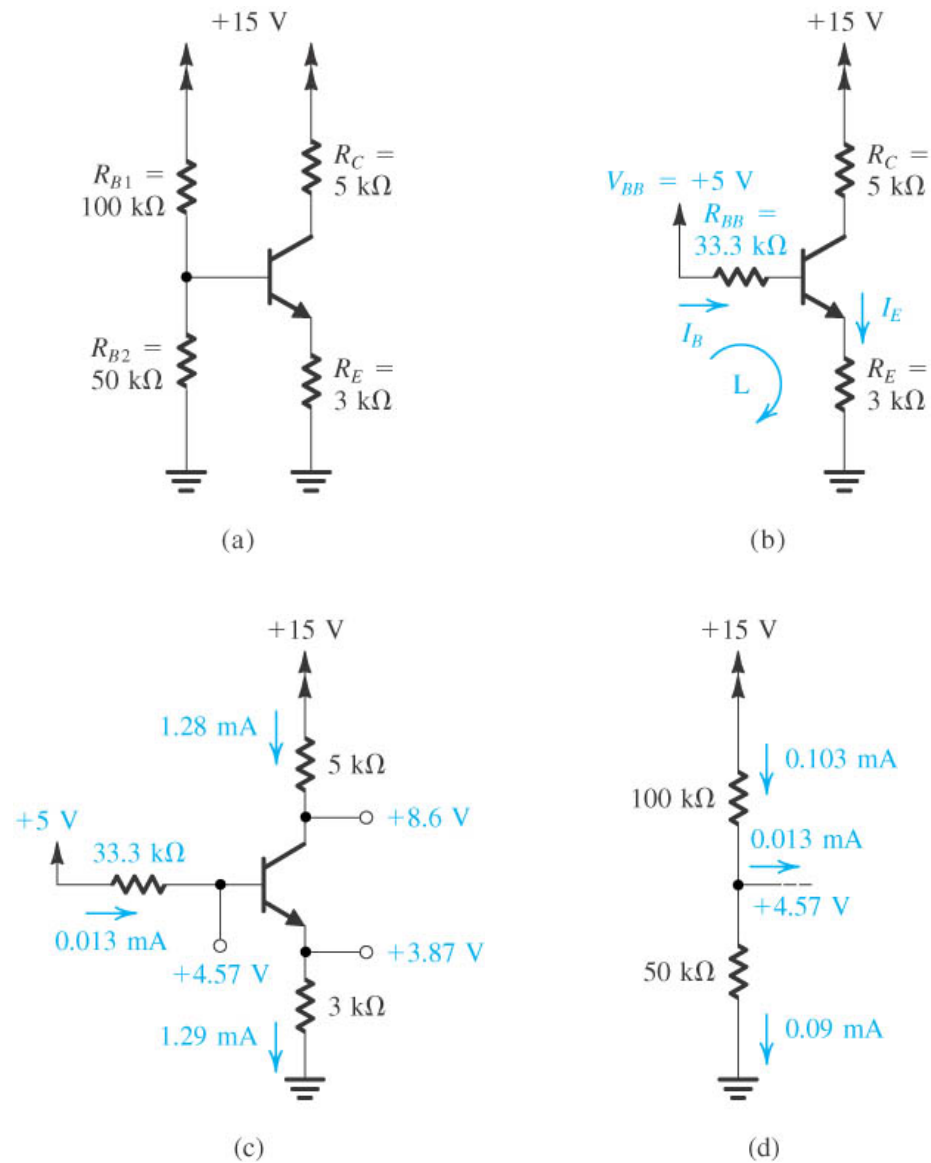

**Figure 5.40** Circuits for Example 5.10.



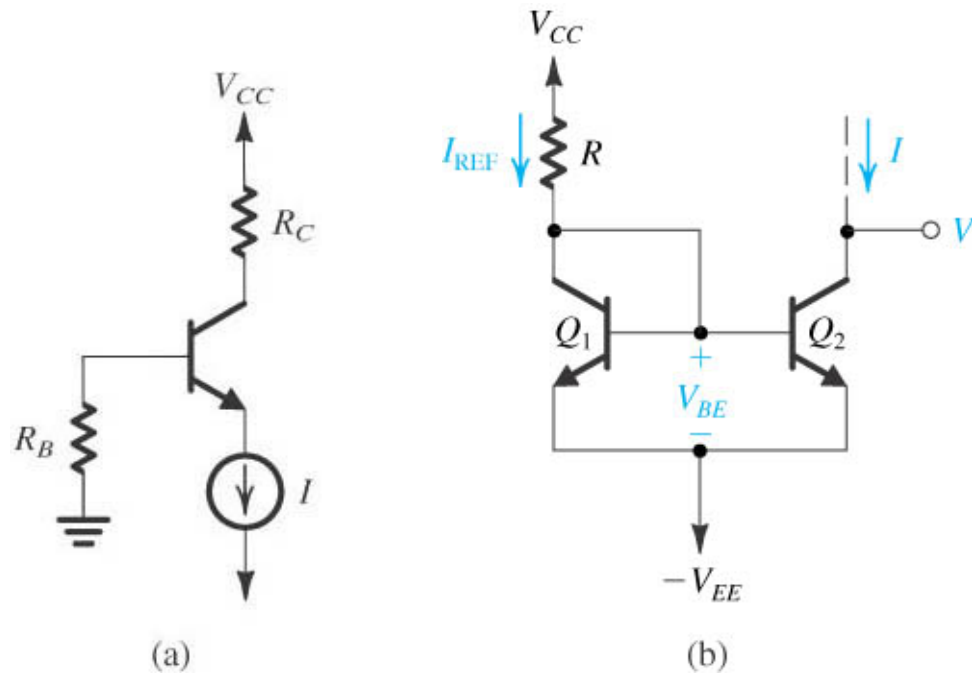

**Figure 5.47** (a) A BJT biased using a constant-current source  $I$ . (b) Circuit for implementing the current source  $I$ .