
 


# **PSI3024 – Eletrônica**

**Aulas 33 e 34**

**2023**

# Inversor pseudo-NMOS

 

### EXEMPLO 10.3

Considere o inversor pseudo-NMOS fabricado na tecnologia CMOS especificada no Exemplo 10.1, ou seja,  $\mu_n C_{ox} = 115 \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 30 \mu\text{A}/\text{V}^2$ ,  $V_{tn} = -V_{tp} = 0,4 \text{ V}$  e  $V_{DD} = 2,5 \text{ V}$ . Seja a razão  $W/L$  de  $Q_N$  de  $(0,375 \mu\text{m}/0,25 \mu\text{m})$  e  $r = 9$ . Obtenha:

- $V_{OH}$ ,  $V_{OL}$ ,  $V_{IL}$ ,  $V_{IH}$ ,  $V_M$ ,  $MR_H$  e  $MR_L$
- $(W/L)_p$
- $I_{\text{estat}}$  e  $P_D$
- $t_{PLH}$ ,  $t_{PHL}$  e  $t_p$ , supondo uma capacitância total na saída do inversor de  $7 \text{ fF}$

## Região II (segmento BC)

$$k_n = rk_p,$$


$$v_O = V_t + \sqrt{(V_{DD} - V_t)^2 - r(v_I - V_t)^2}$$

$$V_{IL} = V_t + \frac{V_{DD} - V_t}{\sqrt{r(r+1)}}$$

$$V_M = V_t + \frac{V_{DD} - V_t}{\sqrt{r+1}}$$

(ponto C)

$$v_O = v_I - V_t$$

 

## Região IV (segmento DE)

$$k_n = rk_p$$

## Região III (segmento CD)

ponto D  $v_O = V_t$


$$\frac{\partial v_O}{\partial v_I} = -1 \text{ e } v_I = V_{IH}$$


$$V_{IH} = V_t + \frac{2}{\sqrt{3r}} (V_{DD} - V_t)$$

$$v_I = V_{DD}$$


$$V_{OL} = (V_{DD} - V_t) \left[ 1 - \sqrt{1 - \frac{1}{r}} \right]$$
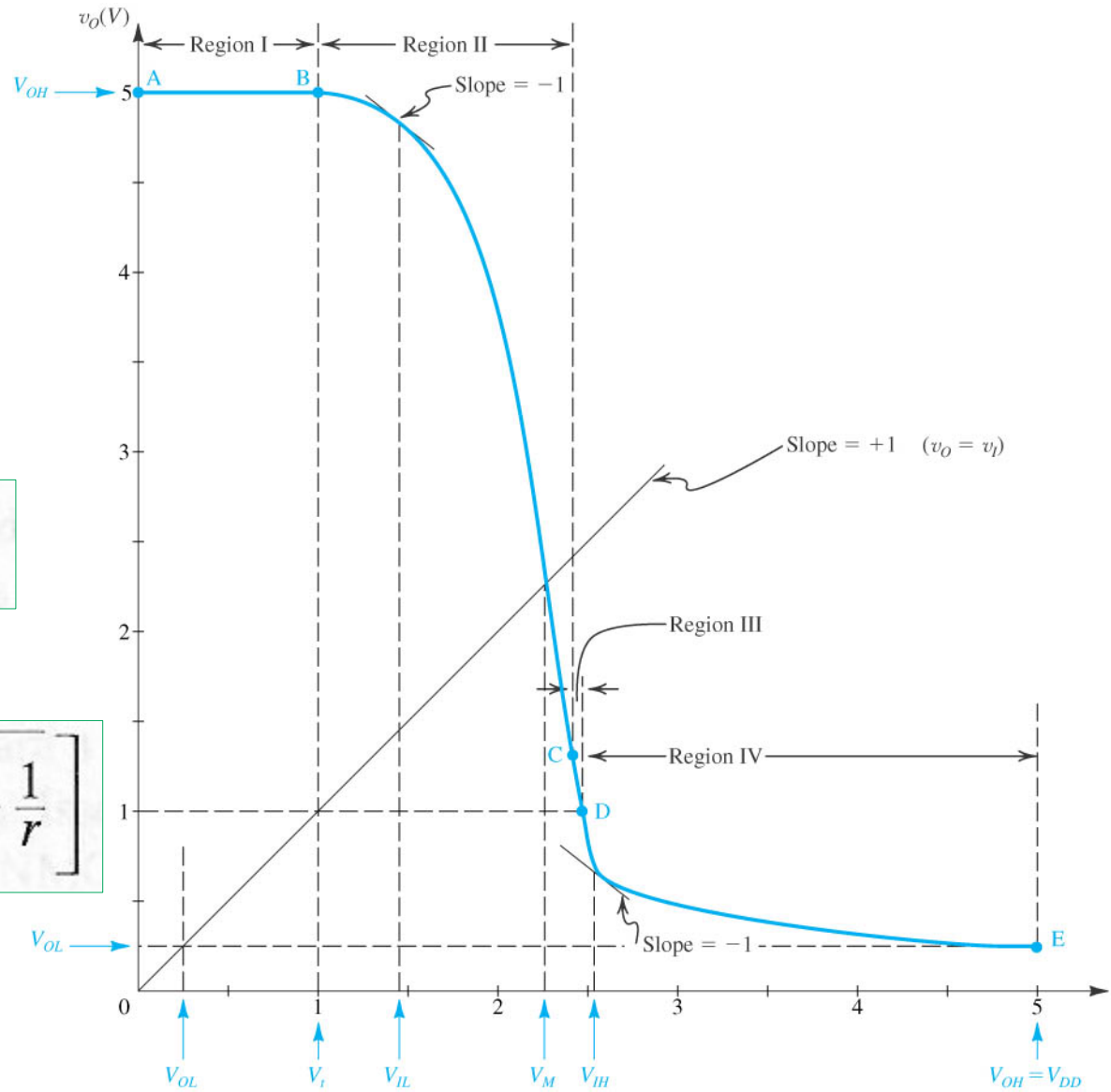
$$v_O = (v_I - V_t) - \sqrt{(v_I - V_t)^2 - \frac{1}{r} (V_{DD} - V_t)^2}$$



 

 
$$I_{estat} = \frac{1}{2} k_p (V_{DD} - V_t)^2$$





$$MR_H = (V_{DD} - V_t) \left( 1 - \frac{2}{\sqrt{3r}} \right)$$

$$MR_L = V_t - (V_{DD} - V_t) \left[ 1 - \sqrt{1 - \frac{1}{r}} - \frac{1}{\sqrt{r(r+1)}} \right]$$
 
# Portas Lógicas com transistores de passagem




- **Figure 10.23** Conceptual pass-transistor logic gates. **(a)** Two switches, controlled by the input variables  $B$  and  $C$ , when connected in series in the path between the input node to which an input variable  $A$  is applied and the output node (with an implied load to ground) realize the function  $Y = ABC$ . **(b)** When the two switches are connected in parallel, the function realized is  $Y = A(B + C)$ .

  

- Figure 10.27 e 10.28 – Transistor NMOS como chave de passagem .






# Efeito de corpo



 


$$V_t = V_{t0} + \gamma \left( \sqrt{V_{SB} + 2 \cdot \phi_F} - \sqrt{2 \cdot \phi_F} \right) \quad \text{CC}$$

 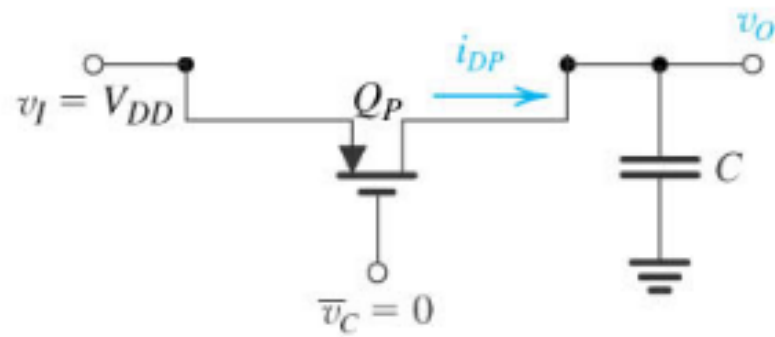 - **Figure 4.41** Small-signal equivalent-circuit model of a MOSFET in which the source is not connected to the body.





(a)

   


(b)


Transistor PMOS como chave de passagem .

 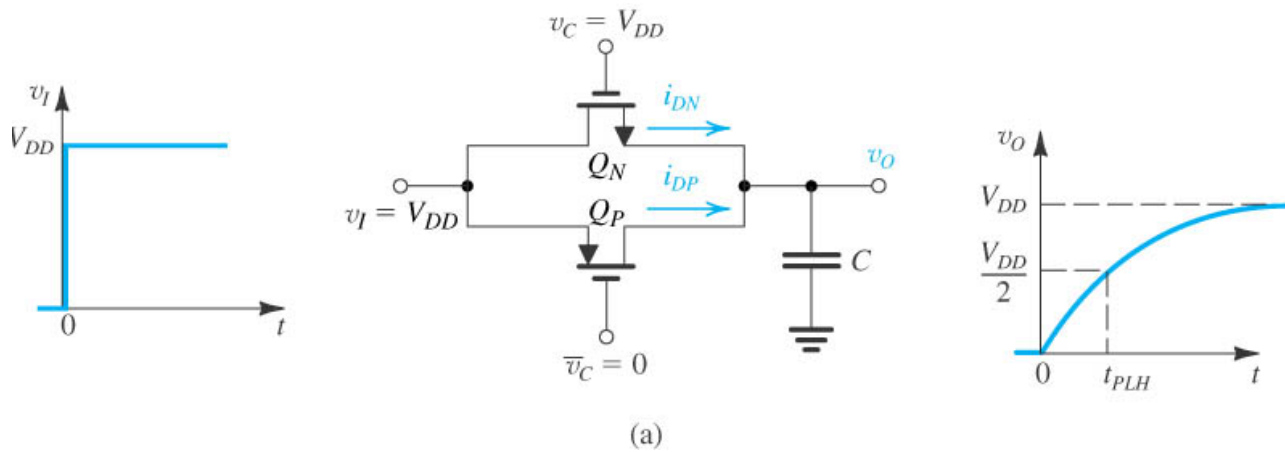


 
- **Figure 10.29** Operation of the transmission gate as a switch in PTL circuits with **(a)**  $v_I$  high and **(b)**  $v_I$  low.



 
- **Figure 10.32** An example of a pass-transistor logic gate utilizing both the input variables and their complements. This type of circuit is therefore known as complementary pass-transistor logic or CPL. Note that both the output function and its complement are generated.



 


 


(a)

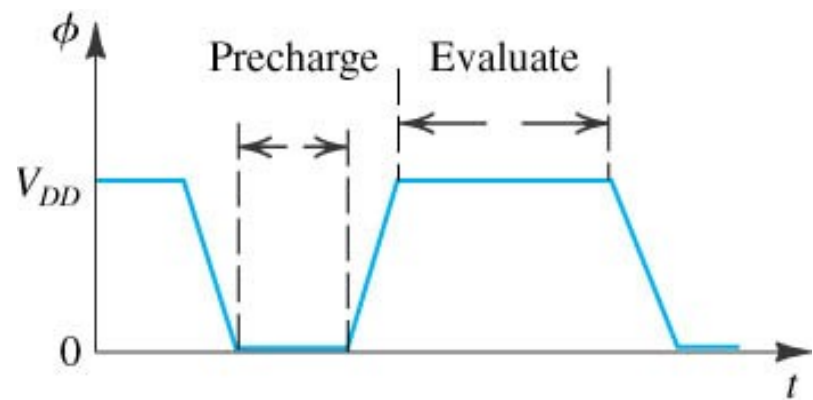



(b)

  - **Figure 10.33** (a) Basic structure of dynamic-MOS logic circuits. (b) Waveform of the clock needed to operate the dynamic logic circuit. (c) An example circuit.




  - **Figure 10.33** (a) Basic structure of dynamic-MOS logic circuits. (b) Waveform of the clock needed to operate the dynamic logic circuit. (c) An example circuit.







 - **Figure 10.34** (a) Charge sharing. (b) Adding a permanently turned-on transistor  $Q_L$  solves the charge-sharing problem at the expense of static power dissipation.




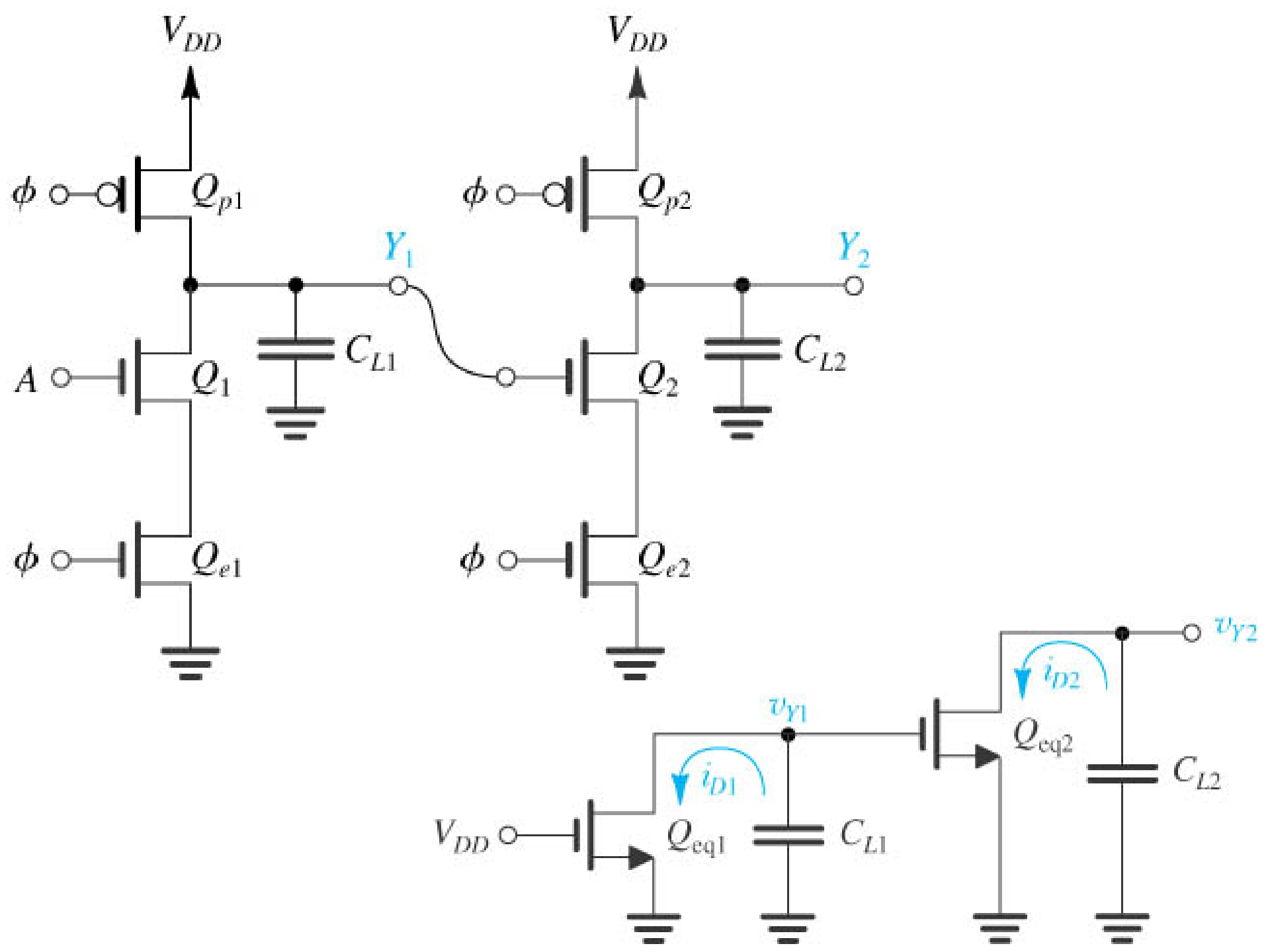- Figure 10.35** Two single-input dynamic logic gates connected in cascade. With the input  $A$  high, during the evaluation phase  $C_{L2}$  will partially discharge and the output at  $Y_2$  will fall lower than  $V_{DD}$ , which can cause logic malfunction.




 

 - **Figure 10.36** The Domino CMOS logic gate. The circuit consists of a dynamic-MOS logic gate with a static-CMOS inverter connected to the output. During evaluation,  $Y$  either will remain low (at 0 V) or will make one 0-to-1 transition (to  $V_{DD}$ ).





(a)

 

(b)

- **Figure 10.37** (a) Two single-input domino CMOS logic gates connected in cascade. (b) Waveforms during the evaluation phase.

 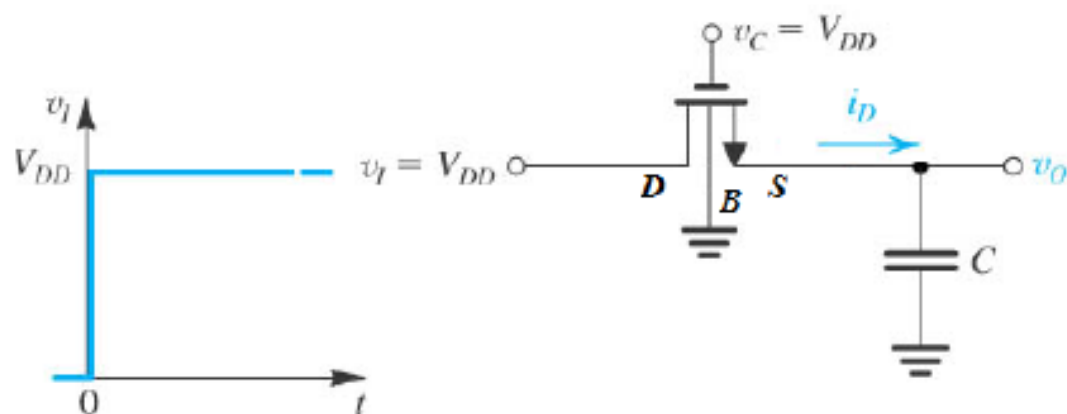Considere o transistor NMOS habilitado como porta de passagem ( $v_C = V_{DD}$ ), conforme indicado na figura a seguir. Sabendo-se que o substrato ( $B$ ) está aterrado, determine o valor numérico da tensão de saída sobre o capacitor  $C$  após sua carga completa.



### **Dados:**

$$V_{DD} = 5\text{V}$$

$$k_n' = 200\mu\text{A}/\text{V}^2$$

$$V_{t0} = 1,0\text{ V}$$

$$(W/L)_n = 1$$



$$\gamma = 0,5\text{ V}^{1/2}$$

$$2\phi_F = 0,6\text{V}$$
  
### **FORMULARIO**

$$V_t = V_{t0} \cdot \left( 1 + \gamma \left( \sqrt{V_{SB} + 2 \cdot \phi_F} - \sqrt{2 \cdot \phi_F} \right) \right)$$

Considere o transistor NMOS habilitado como porta de passagem ( $v_C = V_{DD}$ ), conforme indicado na figura a seguir. Sabendo-se que o substrato ( $B$ ) está aterrado, determine o valor numérico da tensão de saída sobre o capacitor  $C$  após sua carga completa.



### Dados:

$$V_{DD} = 5V$$

$$k_n' = 100 \mu A/V^2$$

$$V_{t0} = 1,5 V$$

$$(W/L)_n = 2$$


$$\gamma = 0,3 V^{1/2}$$

$$2\phi_F = 0,6V$$

### FORMULÁRIO


$$V_t = V_{t0} + \gamma \left( \sqrt{V_{SB} + 2 \cdot \phi_F} - \sqrt{2 \cdot \phi_F} \right)$$


# Célula de Memória SRAM CMOS

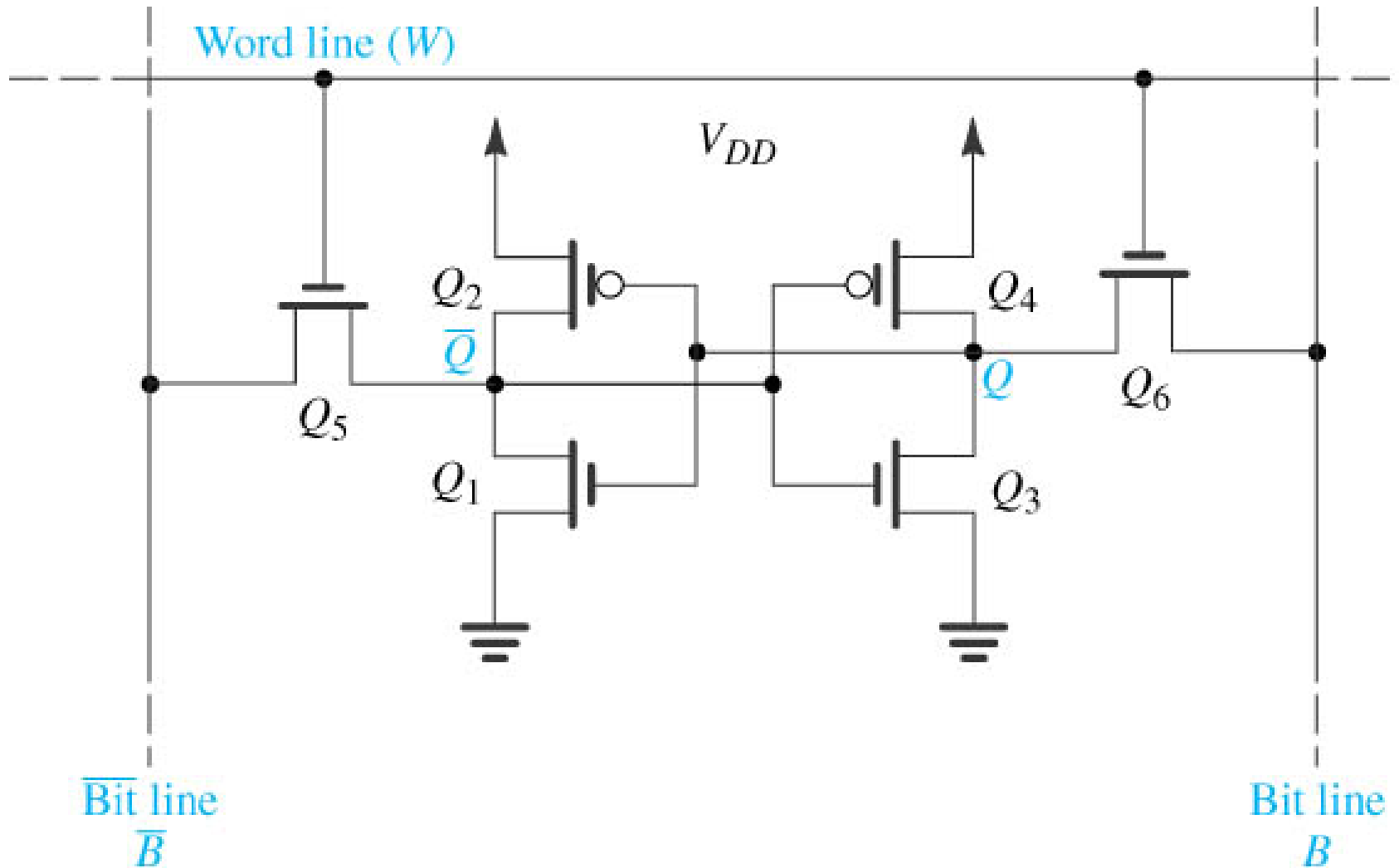




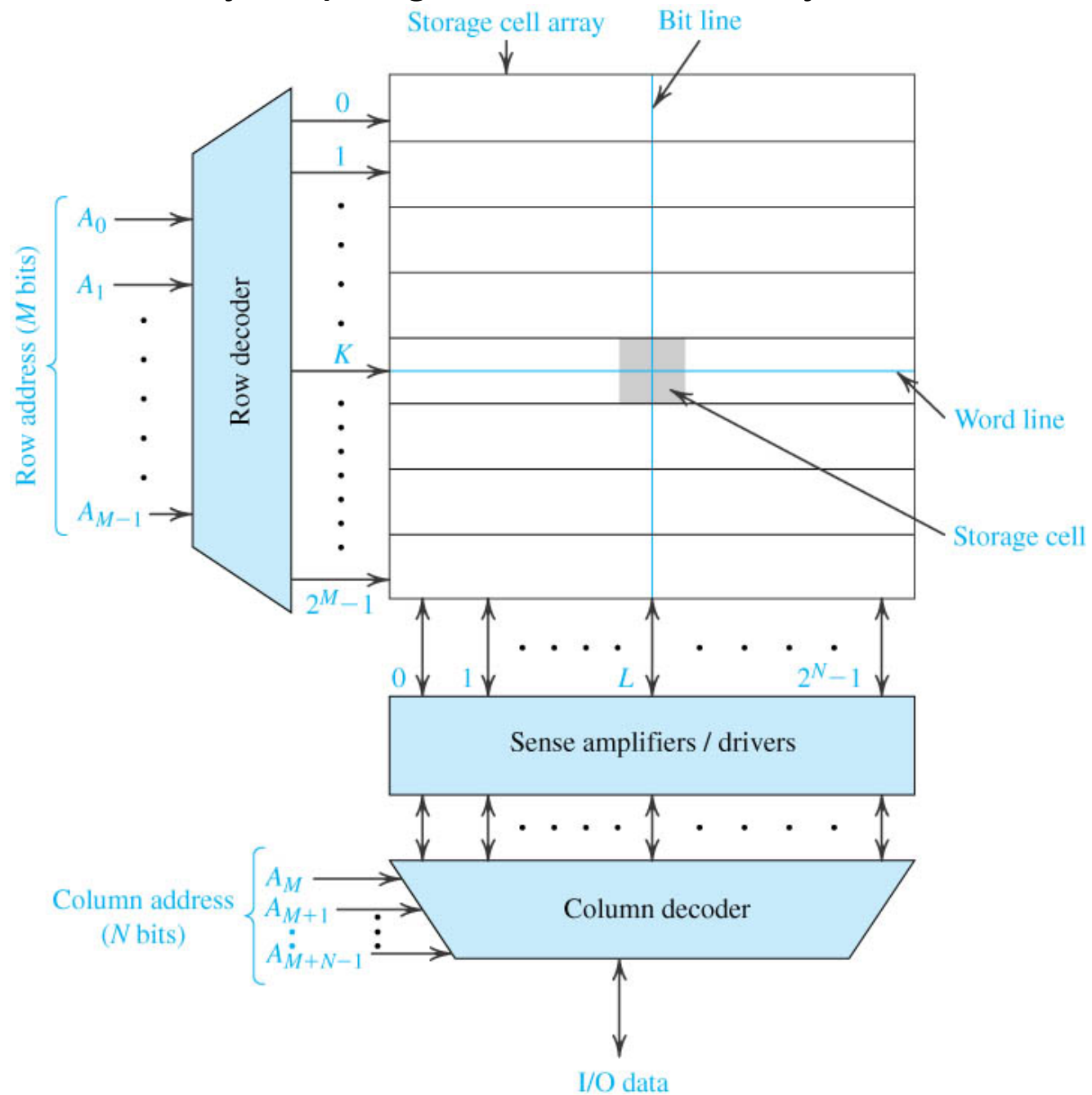- A  $2^{M+N}$ -bit memory chip organized as an array of  $2^M$  rows  $\times$   $2^N$  columns.



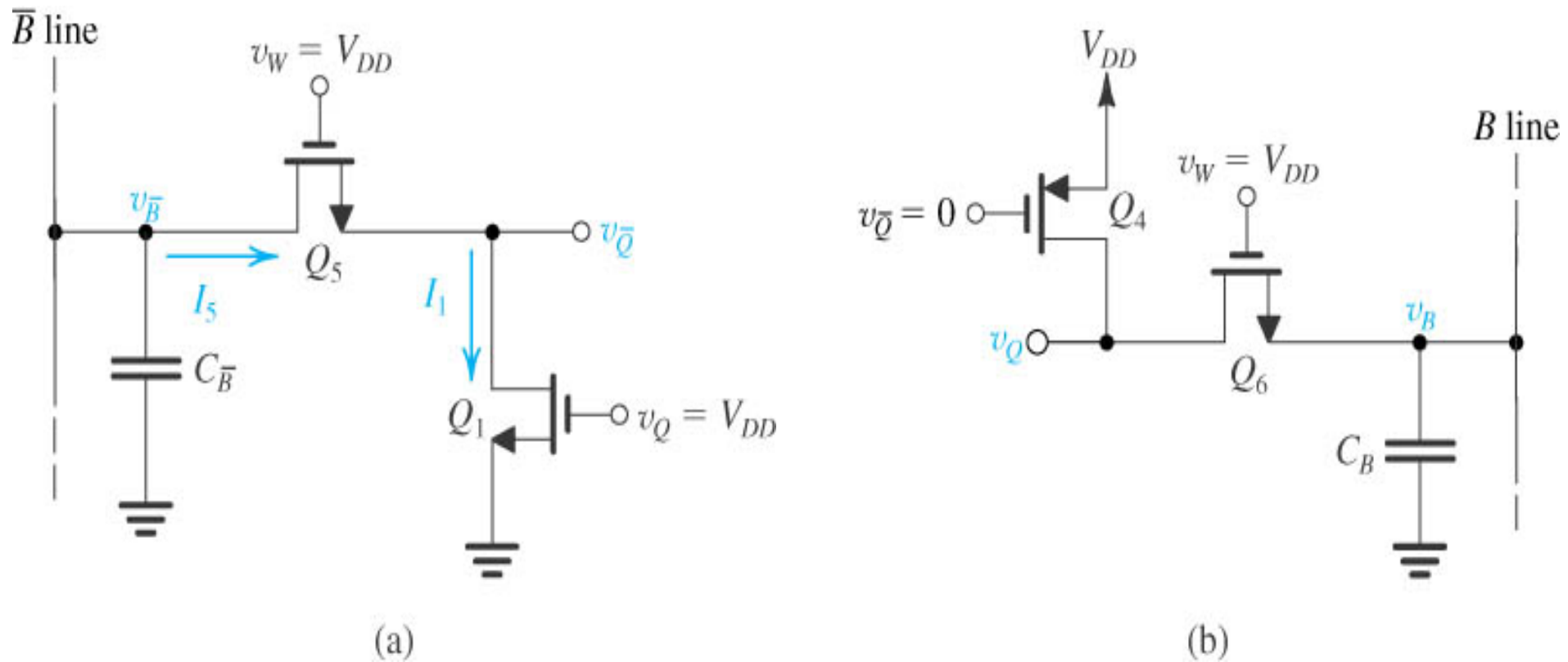

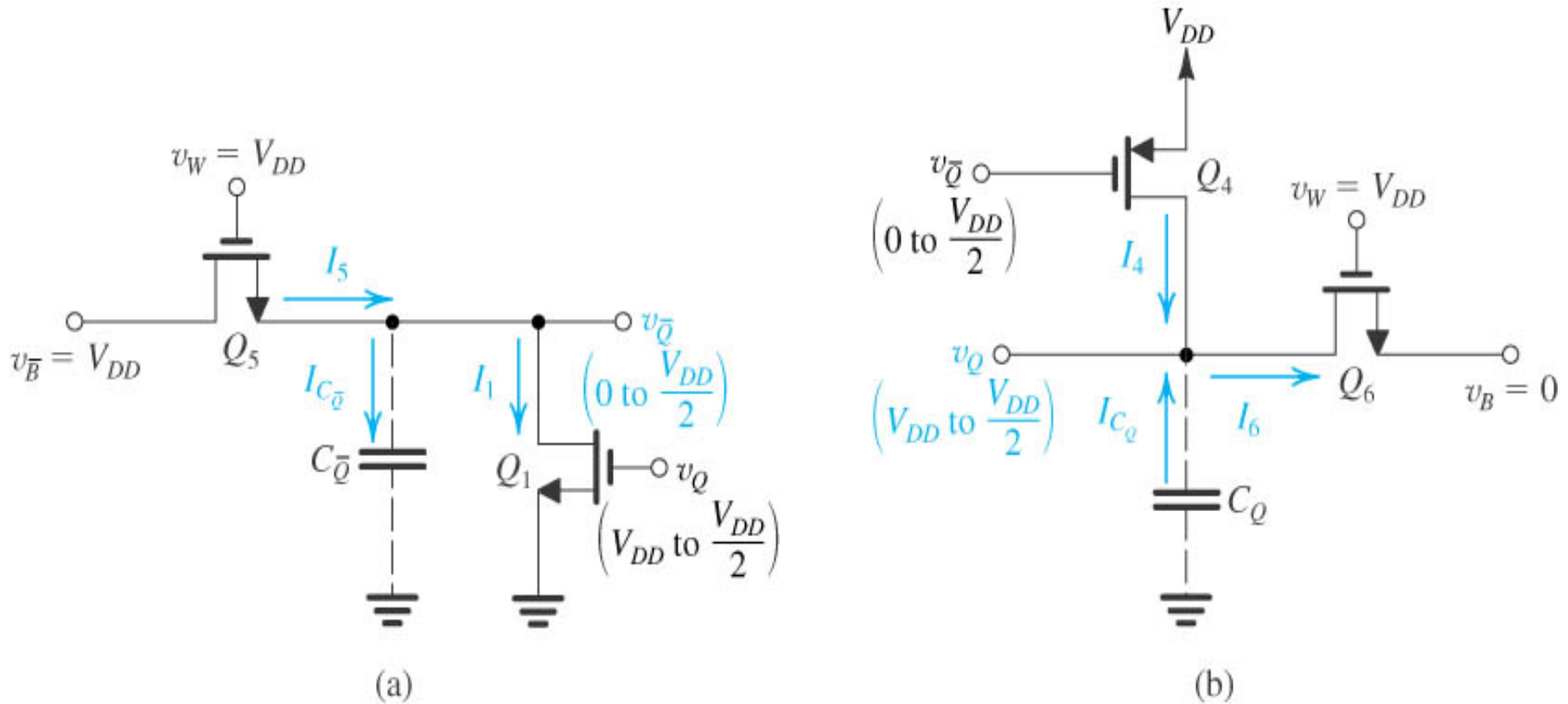- Figure 11.19** Relevant parts of the SRAM cell circuit during a read operation when the cell is storing a logic 1. Note that initially  $v_{\bar{Q}} = V_{DD}$  and  $v_Q = 0$ . Also note that the  $B$  and  $\bar{B}$  lines are usually precharged to a voltage of about  $V_{DD}/2$ . However, in Example 11.2, it is assumed for simplicity that the precharge voltage is  $V_{DD}$ .



- Figure 11.20** Relevant parts of the SRAM circuit during a write operation. Initially, the SRAM has a stored 1 and a 0 is being written. These equivalent circuits apply before switching takes place. **(a)** The circuit is pulling node  $Q$  up toward  $V_{DD}/2$ . **(b)** The circuit is pulling node  $Q$  down toward  $V_{DD}/2$ .