

PSI3024 – Eletrônica


Aula 35

2023

Teste 15 - 2º semestre de 2023

Para a porta lógica dinâmica mostrada na figura a seguir, determine o tempo de atraso máximo da mesma considerando as razões W/L fornecidas para os transistores Q_P , Q_A , Q_B e Q_C . Sabe-se que a razão W/L do transistor Q_e é elevada e que $V_e \cong 0$ V quando o mesmo está habilitado para $\phi = V_{DD}$.

 Calcule na condição de maior atraso o valor de $i_{DNmedio} = (i_{DN}(0) + i_{DN}(t_P))/2$.





Dados:

$V_{DD} = 5$ V
 $k_p' = 100$ nA/V²
 $k_n' = 200$ nA/V²
 $|V_{tp}| = |V_{tn}| = 1$ V
 $\lambda = 0$
 $V_e \cong 0$ V p/ $\phi = V_{DD}$
 $(W/L)_{Q_P} = 6$
 $(W/L)_{Q_A} = 3$
 $(W/L)_{Q_B} = 6$
 $(W/L)_{Q_C} = 6$
 $C_L = 446,25$ fF

Dados:

$V_{DD} = 5$ V
 $k_p' = 200$ nA/V²
 $k_n' = 400$ nA/V²
 $|V_{tp}| = |V_{tn}| = 1$ V
 $\lambda = 0$
 $V_e \cong 0$ V p/ $\phi = V_{DD}$
 $(W/L)_{Q_P} = 6$
 $(W/L)_{Q_A} = 3$
 $(W/L)_{Q_B} = 6$
 $(W/L)_{Q_C} = 6$
 $C_L = 446,25$ fF

  



- **Figure 10.33** (a) Basic structure of dynamic-MOS logic circuits. (b) Waveform of the clock needed to operate the dynamic logic circuit. (c) An example circuit.

EXEMPLO 10.3

Considere o inversor pseudo-NMOS fabricado na tecnologia CMOS especificada no Exemplo 10.1, ou seja, $\mu_n C_{ox} = 115 \mu\text{A/V}^2$, $\mu_p C_{ox} = 30 \mu\text{A/V}^2$, $V_{tn} = -V_{tp} = 0,4 \text{ V}$ e $V_{DD} = 2,5 \text{ V}$. Seja a razão W/L de Q_N de $(0,375 \mu\text{m}/0,25 \mu\text{m})$ e $r = 9$. Obtenha:

- (a) V_{OH} , V_{OL} , V_{IL} , V_{IH} , V_M , MR_H e MR_L
- (b) $(W/L)_p$
- (c) I_{estat} e P_D
- (d) t_{PLH} , t_{PHL} e t_P , supondo uma capacitância total na saída do inversor de 7 fF

Inversor pseudo-NMOS

  

Região II (segmento BC)

$$k_n = rk_p,$$


$$v_O = V_t + \sqrt{(V_{DD} - V_t)^2 - r(v_I - V_t)^2}$$

$$V_{IL} = V_t + \frac{V_{DD} - V_t}{\sqrt{r(r+1)}}$$

$$V_M = V_t + \frac{V_{DD} - V_t}{\sqrt{r+1}}$$

(ponto C)

$$v_O = v_I - V_t$$

 

Região IV (segmento DE)

$$k_n = rk_p$$

Região III (segmento CD)

ponto D $v_O = V_t$


$$\partial v_O / \partial v_I = -1 \text{ e } v_I = V_{IH}$$


$$V_{IH} = V_t + \frac{2}{\sqrt{3r}} (V_{DD} - V_t)$$

$$v_I = V_{DD}$$

$$V_{OL} = (V_{DD} - V_t) \left[1 - \sqrt{1 - \frac{1}{r}} \right]$$

 
$$v_O = (v_I - V_t) - \sqrt{(v_I - V_t)^2 - \frac{1}{r} (V_{DD} - V_t)^2}$$



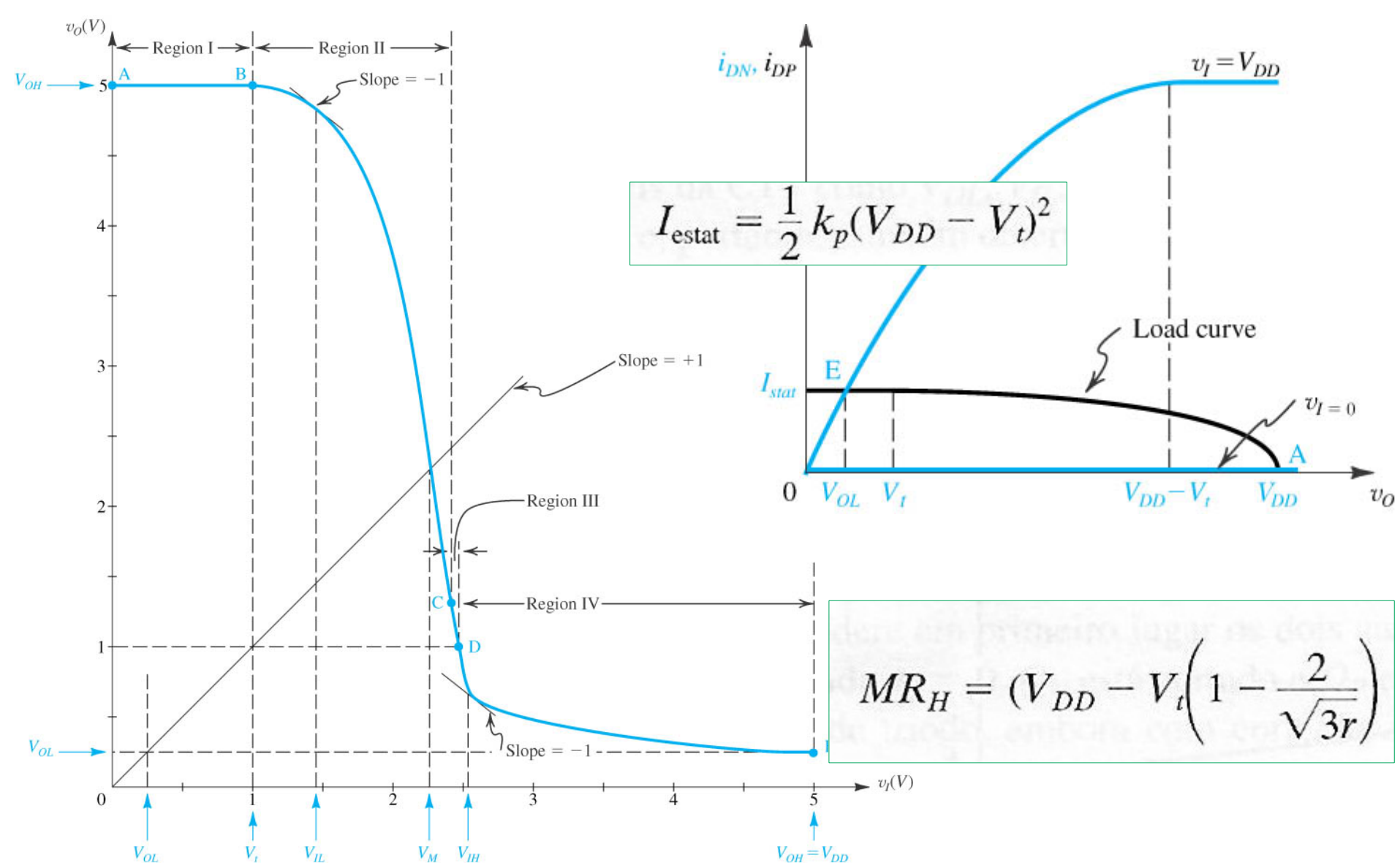



$$MR_L = V_t - (V_{DD} - V_t) \left[1 - \sqrt{1 - \frac{1}{r}} - \frac{1}{\sqrt{r(r+1)}} \right]$$

Célula de Memória SRAM CMOS

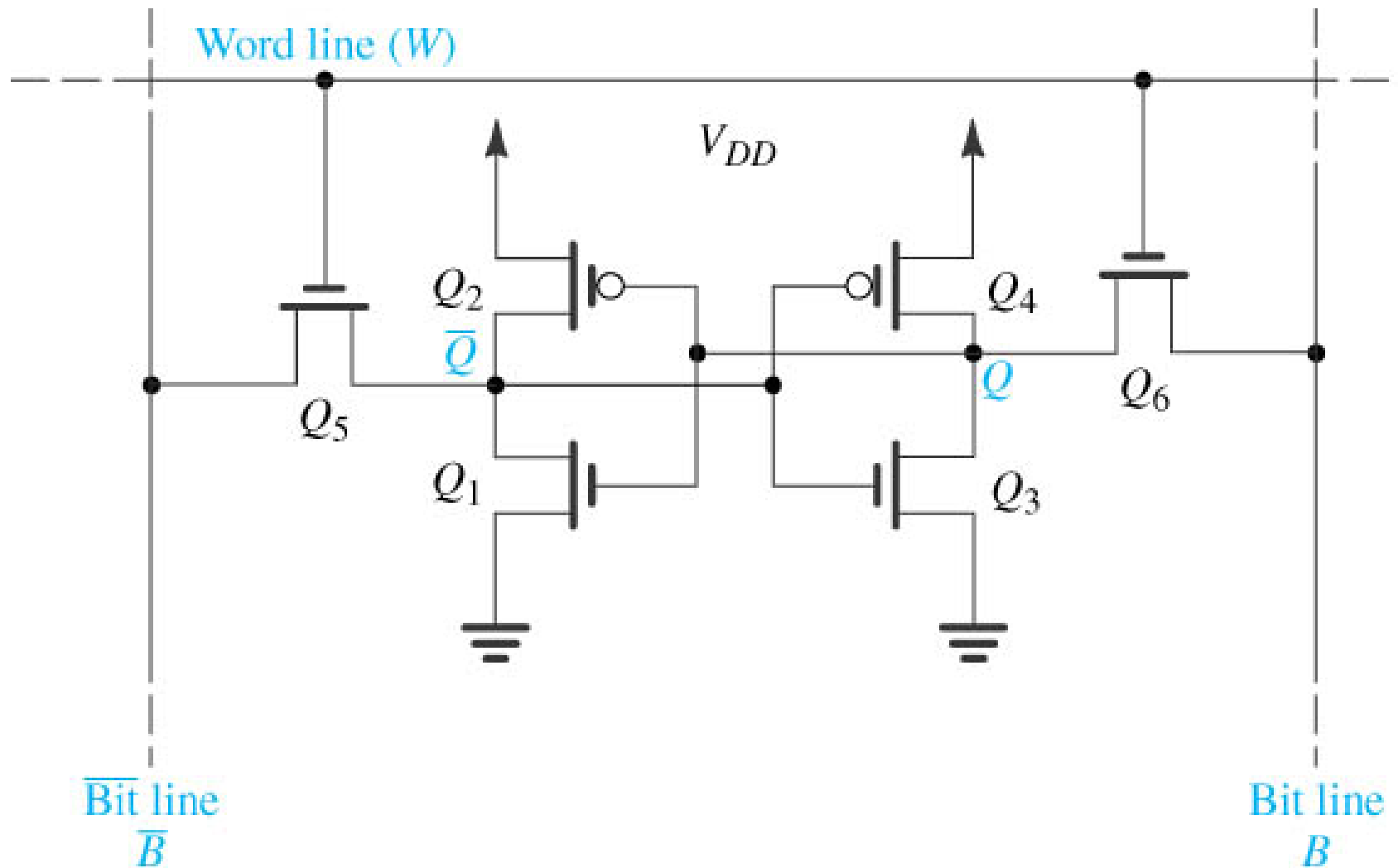


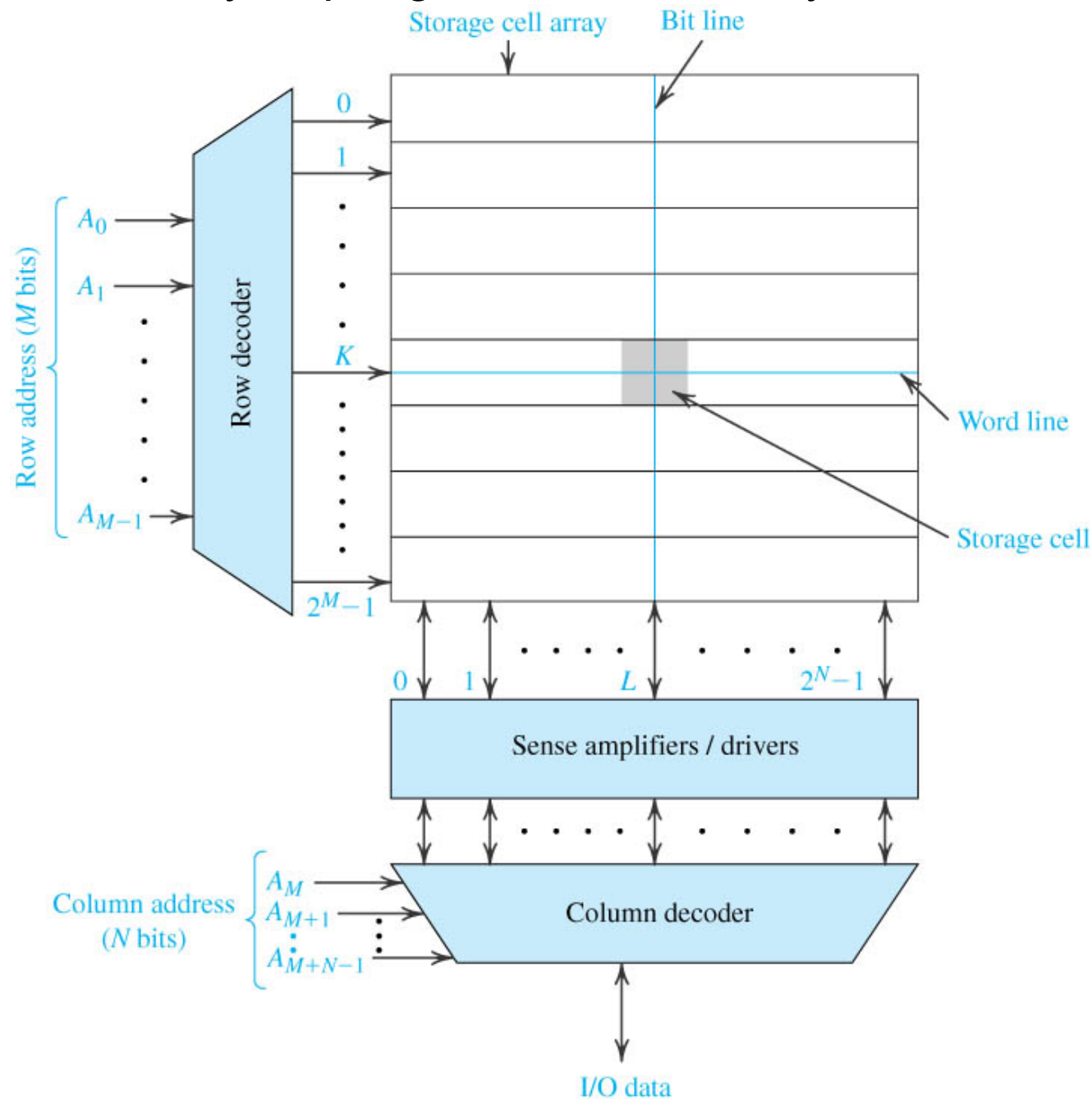- A 2^{M+N} -bit memory chip organized as an array of 2^M rows \times 2^N columns.



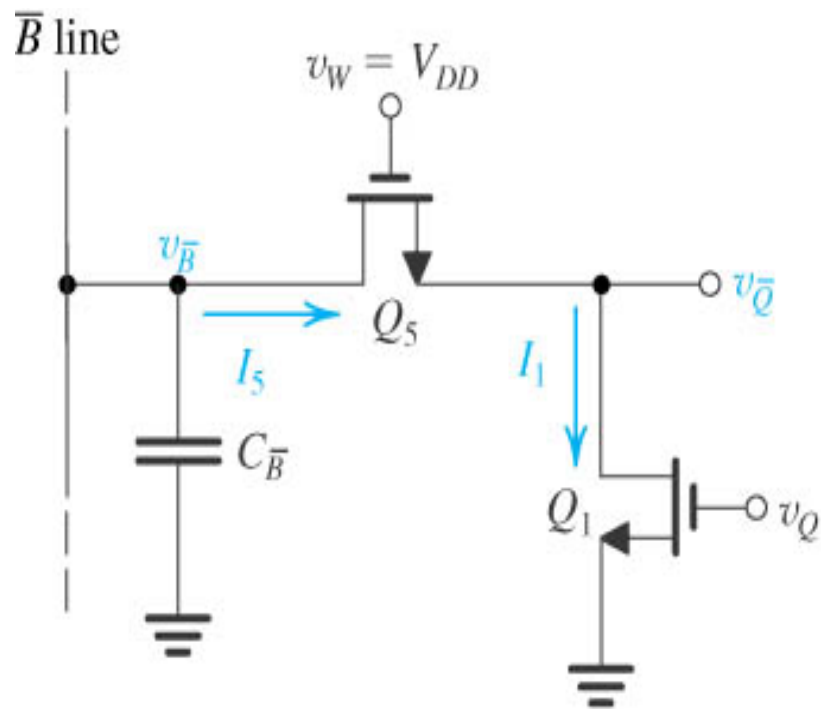

(a)

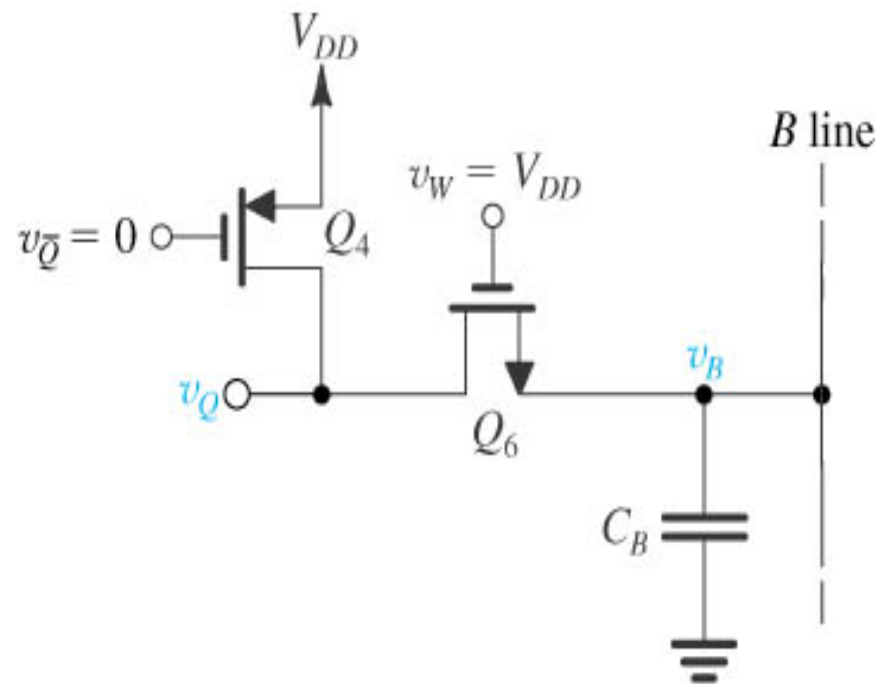

(b)

- Figure 11.19** Relevant parts of the SRAM cell circuit during a read operation when the cell is storing a logic 1. Note that initially $v_{\overline{Q}} = V_{DD}$ and $v_Q = 0$. Also note that the B and \overline{B} lines are usually precharged to a voltage of about $V_{DD}/2$. However, in Example 11.2, it is assumed for simplicity that the precharge voltage is V_{DD} .