
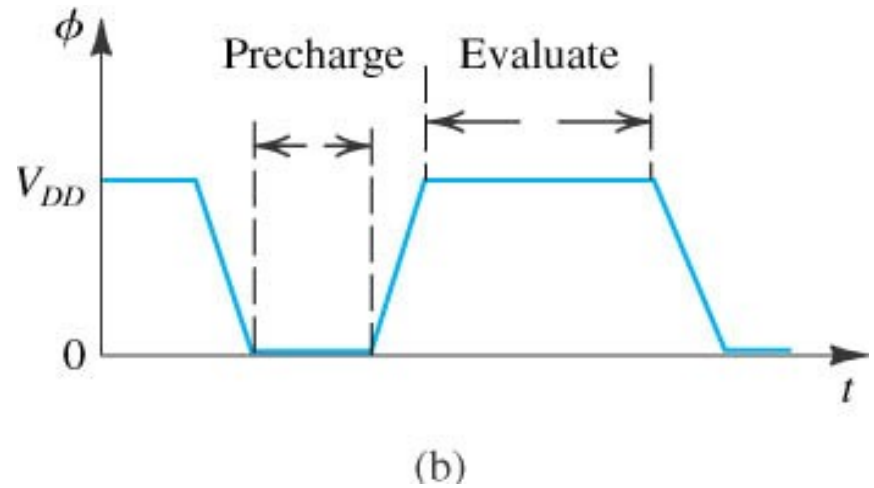


# **PSI3024 – Eletrônica**

**Aulas 36 e 37**

**2023**

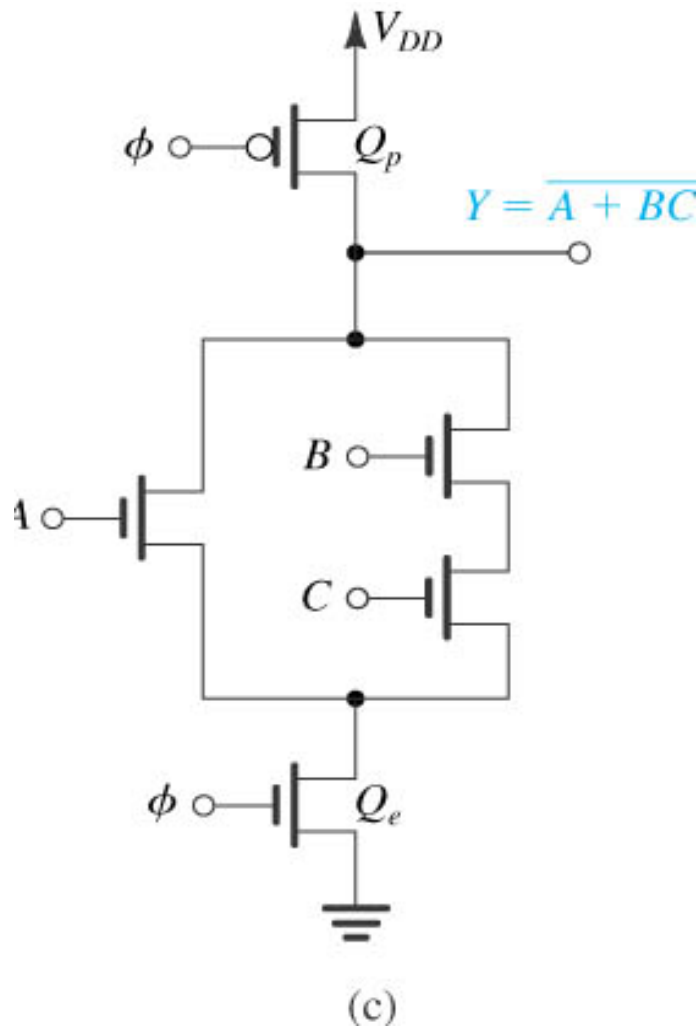



- **Figure 10.33** (a) Basic structure of dynamic-MOS logic circuits. (b) Waveform of the clock needed to operate the dynamic logic circuit. (c) An example circuit.

### EXEMPLO 10.3

Considere o inversor pseudo-NMOS fabricado na tecnologia CMOS especificada no Exemplo 10.1, ou seja,  $\mu_n C_{ox} = 115 \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 30 \mu\text{A}/\text{V}^2$ ,  $V_{tn} = -V_{tp} = 0,4 \text{ V}$  e  $V_{DD} = 2,5 \text{ V}$ . Seja a razão  $W/L$  de  $Q_N$  de  $(0,375 \mu\text{m}/0,25 \mu\text{m})$  e  $r = 9$ . Obtenha:

- (a)  $V_{OH}$ ,  $V_{OL}$ ,  $V_{IL}$ ,  $V_{IH}$ ,  $V_M$ ,  $MR_H$  e  $MR_L$
- (b)  $(W/L)_p$
- (c)  $I_{\text{estat}}$  e  $P_D$
- (d)  $t_{PLH}$ ,  $t_{PHL}$  e  $t_p$ , supondo uma capacitância total na saída do inversor de  $7 \text{ fF}$

# Inversor pseudo-NMOS

  

## Região II (segmento BC)

$$k_n = rk_p,$$


$$v_O = V_t + \sqrt{(V_{DD} - V_t)^2 - r(v_I - V_t)^2}$$

$$V_{IL} = V_t + \frac{V_{DD} - V_t}{\sqrt{r(r+1)}}$$

$$V_M = V_t + \frac{V_{DD} - V_t}{\sqrt{r+1}}$$

(ponto C)

$$v_O = v_I - V_t$$

 

## Região IV (segmento DE)

$$k_n = rk_p$$

## Região III (segmento CD)

ponto D  $v_O = V_t$


$$\frac{\partial v_O}{\partial v_I} = -1 \text{ e } v_I = V_{IH}$$


$$V_{IH} = V_t + \frac{2}{\sqrt{3r}} (V_{DD} - V_t)$$

$$v_I = V_{DD}$$

$$V_{OL} = (V_{DD} - V_t) \left[ 1 - \sqrt{1 - \frac{1}{r}} \right]$$
 
$$v_O = (v_I - V_t) - \sqrt{(v_I - V_t)^2 - \frac{1}{r} (V_{DD} - V_t)^2}$$



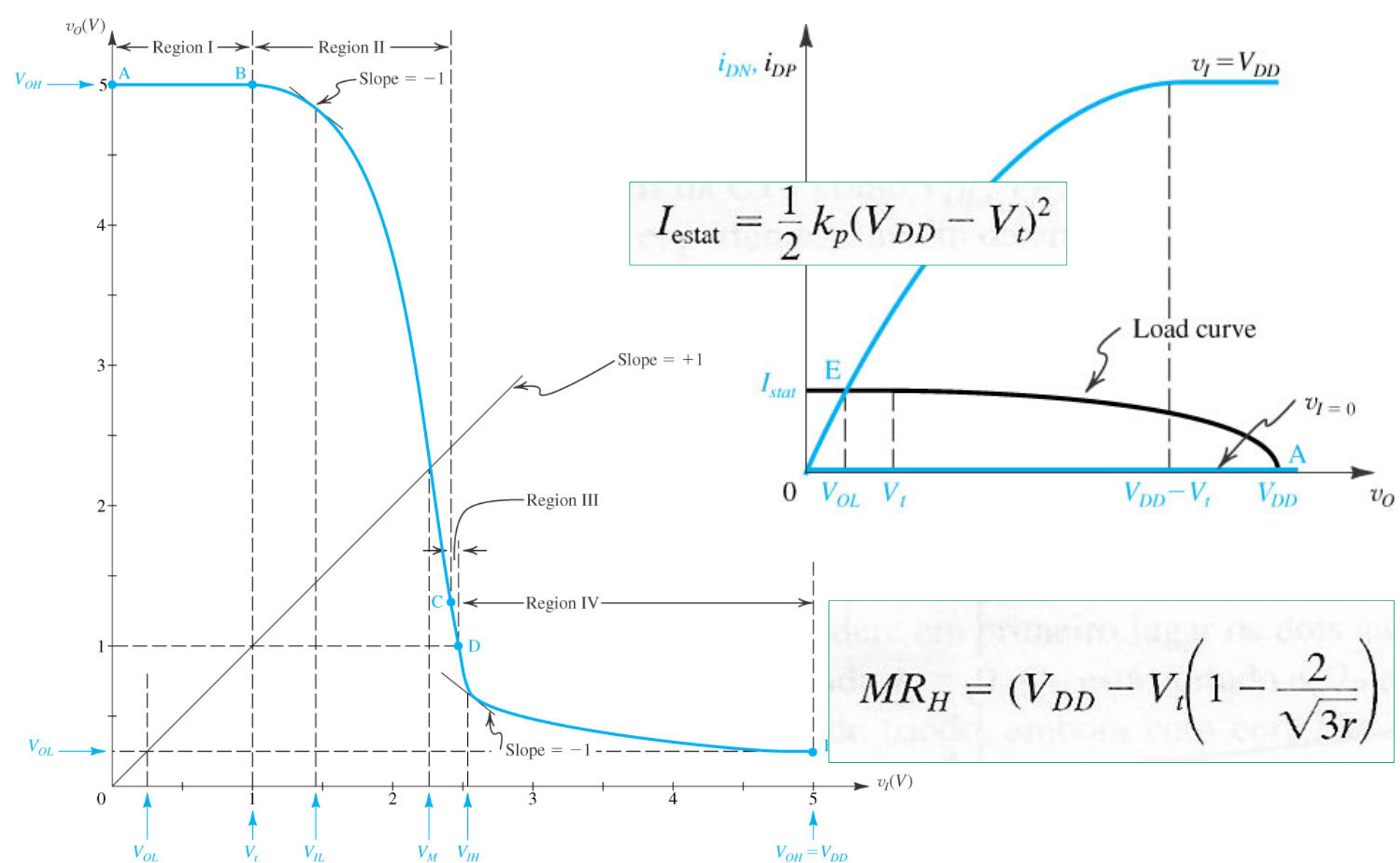


$$I_{estat} = \frac{1}{2} k_p (V_{DD} - V_t)^2$$

$$MR_H = (V_{DD} - V_t) \left( 1 - \frac{2}{\sqrt{3r}} \right)$$


$$MR_L = V_t - (V_{DD} - V_t) \left[ 1 - \sqrt{1 - \frac{1}{r}} - \frac{1}{\sqrt{r(r+1)}} \right]$$


# Célula de Memória SRAM CMOS

 



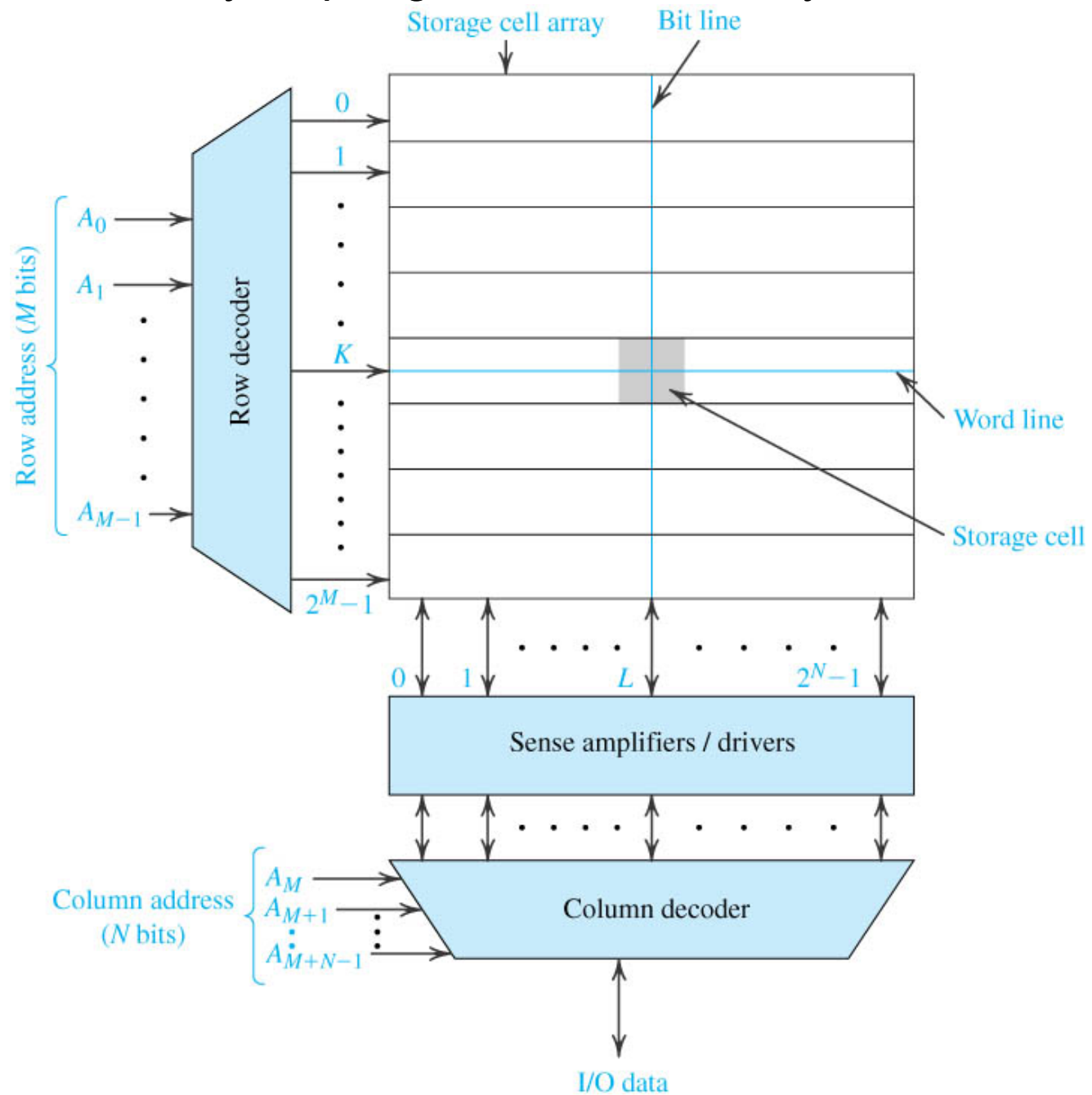- A  $2^{M+N}$ -bit memory chip organized as an array of  $2^M$  rows  $\times$   $2^N$  columns.



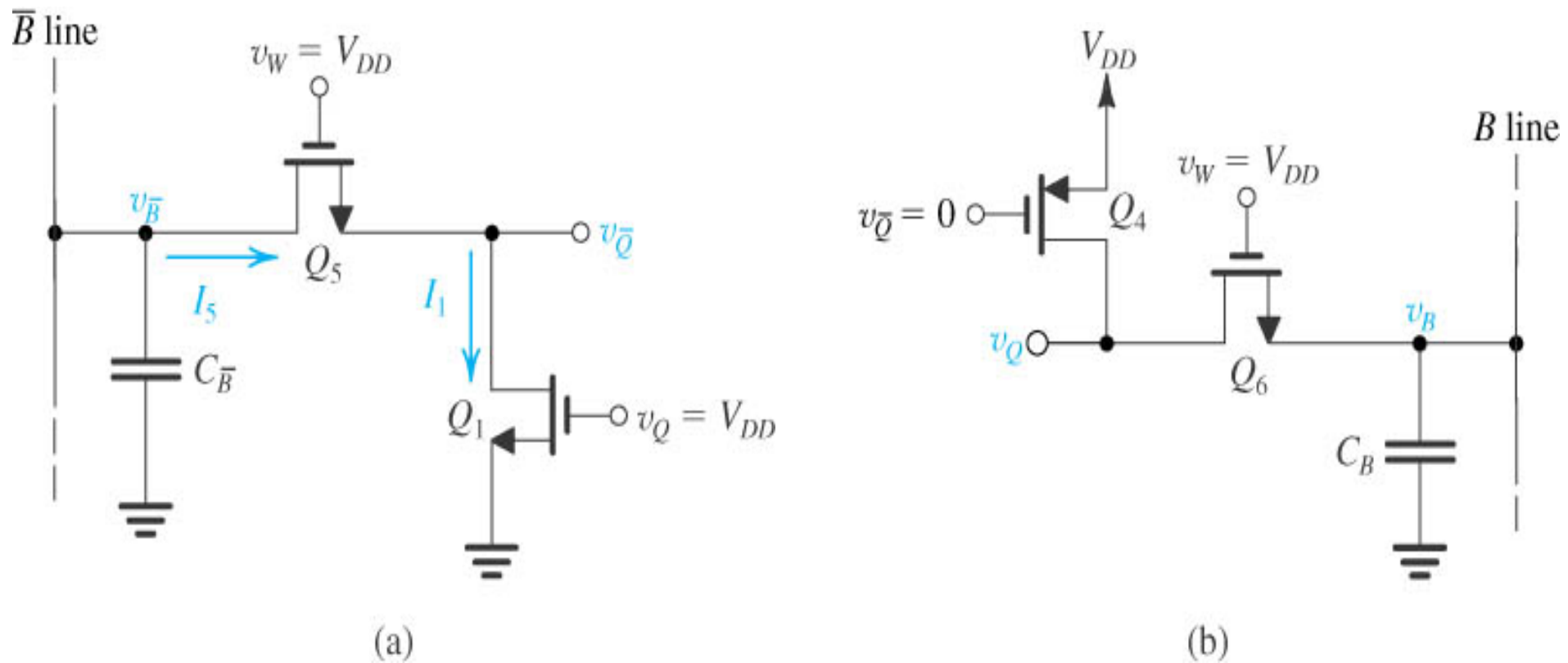

- Figure 11.19** Relevant parts of the SRAM cell circuit during a read operation when the cell is storing a logic 1. Note that initially  $v_Q = V_{DD}$  and  $v_{\bar{Q}} = 0$ . Also note that the  $B$  and  $\bar{B}$  lines are usually precharged to a voltage of about  $V_{DD}/2$ . However, in Example 11.2, it is assumed for simplicity that the precharge voltage is  $V_{DD}$ .

## EXEMPLO 11.2

A intenção deste exemplo é analisar a operação dinâmica da célula CMOS SRAM da Figura 11.18. Considere a célula sendo fabricada em uma tecnologia de processo para a qual  $\mu_n C_{ox} = 50 \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 20 \mu\text{A}/\text{V}^2$ ,  $V_{tn0} = -V_{tp0} = 1 \text{ V}$ ,  $2\phi_f = 0,6 \text{ V}$ ,  $\gamma = 0,5 \text{ V}^{1/2}$  e  $V_{DD} = 5 \text{ V}$ . Suponha que os transistores da célula tenham  $(W/L)_n = 4/2$ ,  $(W/L)_p = 10/2$  e suponha os transistores de acesso com  $(W/L) = 10/2$ . Supondo que a célula esteja armazenando um 1 e que a capacitância de cada linha de bit seja de 1 pF, determine o tempo necessário para surgir uma tensão de 0,2 V. Para simplificar a análise, suponha que as linhas  $B$  e  $\bar{B}$  estão pré-carregadas em  $V_{DD}$ .

$$I_1 = \mu_n C_{ox} \left( \frac{W}{L} \right)_1 \left[ (V_{DD} - V_{t1}) v_{\bar{Q}} - \frac{1}{2} v_{\bar{Q}}^2 \right]$$

$$I_1 = 50 \times \frac{4}{2} \left[ (5 - 1) v_{\bar{Q}} - \frac{1}{2} v_{\bar{Q}}^2 \right]$$

$$I_5 = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_5 (V_{DD} - v_{\bar{Q}} - V_{t5})^2$$

$$V_{t5} = 1 + 0,5 (\sqrt{v_{\bar{Q}} + 0,6} - \sqrt{0,6})$$

$V_{t5} = 1$  V e, portanto,  $I_5$  será

$$I_5 = \frac{1}{2} \times 50 \times \frac{10}{2} (5 - v_{\bar{Q}} - 1)^2$$

resolvendo para  $v_{\bar{Q}}$  resulta em  $v_{\bar{Q}} = 1,86$  V

segunda iteração,

O resultado é  $V_{t5} = 1,4 \text{ V}$ .


$$v_{\bar{Q}} = 1,6 \text{ V}$$

$$I_5 = 0,5 \text{ mA}$$

$v_{\bar{Q}}$  é menor que  $V_{DD}/2$


$$\Delta t = \frac{C_{\bar{B}} \Delta V}{I_5}$$
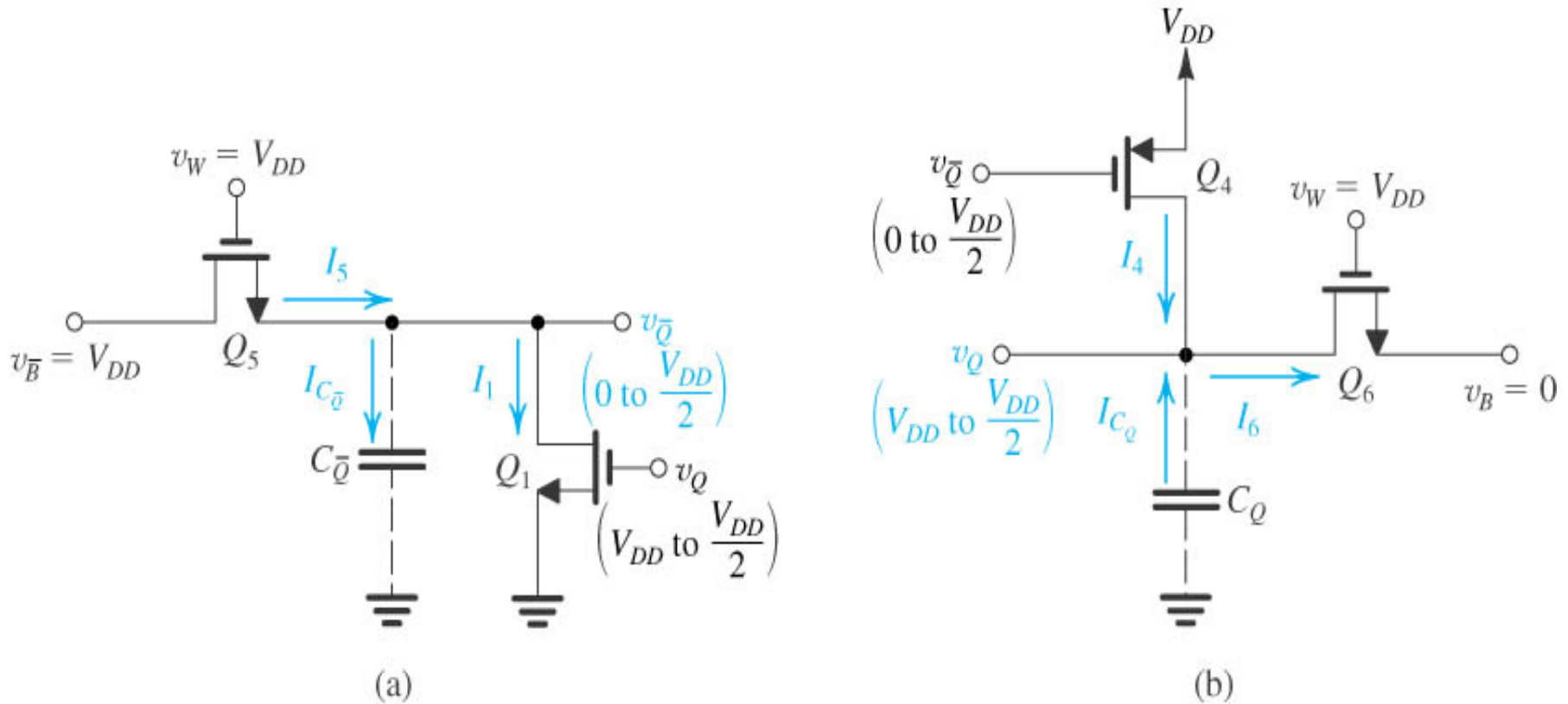
$$\Delta t = \frac{1 \times 10^{-12} \times 0,2}{0,5 \times 10^{-3}} = 0,4 \text{ ns}$$




- Figure 11.20** Relevant parts of the SRAM circuit during a write operation. Initially, the SRAM has a stored 1 and a 0 is being written. These equivalent circuits apply before switching takes place. **(a)** The circuit is pulling node  $Q$  up toward  $V_{DD}$ . **(b)** The circuit is pulling node  $Q$  down toward  $V_{DD}/2$ .

Para a célula de memória SRAM na figura a seguir, as linhas B e  $\bar{B}$  são energizadas com  $V_{DD}/2$  durante o ciclo de leitura e os transistores  $Q_5$  e  $Q_6$  são habilitados através da aplicação de uma tensão  $V_{DD}$  na Word line (W) quando passamos a ter  $v_Q = 3,75$  V e  $v_{\bar{Q}} = 1,25$  V. Determine as correntes  $I_5 = I_1$  e  $I_4 = I_6$  e obtenha o intervalo de tempo  $\Delta t$  necessário para que a diferença de potencial  $\Delta V$  entre as linhas B e  $\bar{B}$  seja de 0,2V a fim de ativar o amplificador sensor de leitura supondo que as correntes  $I_5 = I_1$  e  $I_4 = I_6$  permaneçam aproximadamente constantes. Suponha que o efeito de corpo nos transistores  $Q_5$  e  $Q_6$  seja desprezível, ou seja, a tensão de limiar não muda ( $V_m = 1$ V).

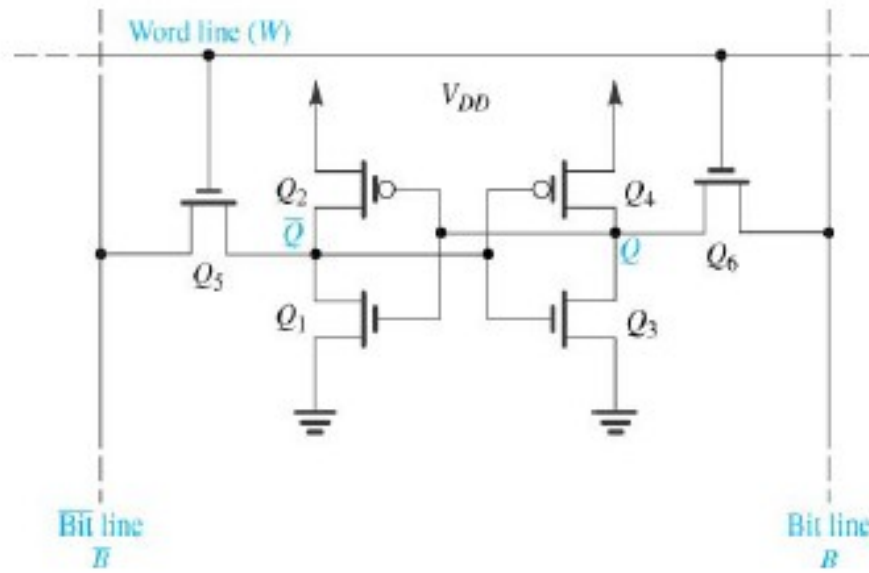


**Dados:**


- $V_{DD} = 5$  V
- $k_p' = 10 \mu\text{A/V}^2$  (20  $\mu\text{A/V}^2$ )
- $k_n' = 20 \mu\text{A/V}^2$  (40  $\mu\text{A/V}^2$ )
- $|V_{tp}| = |V_{tn}| = 1$  V
- $\lambda = 0$
- $(W/L)_{Q4} = 6$
- $(W/L)_{Q6} = 3$
- $(W/L)_{Q5} = 3$
- $(W/L)_{Q1} = 3$
- $C_B = C_{\bar{B}} = 1$  pF

 

(a)

 


(b)

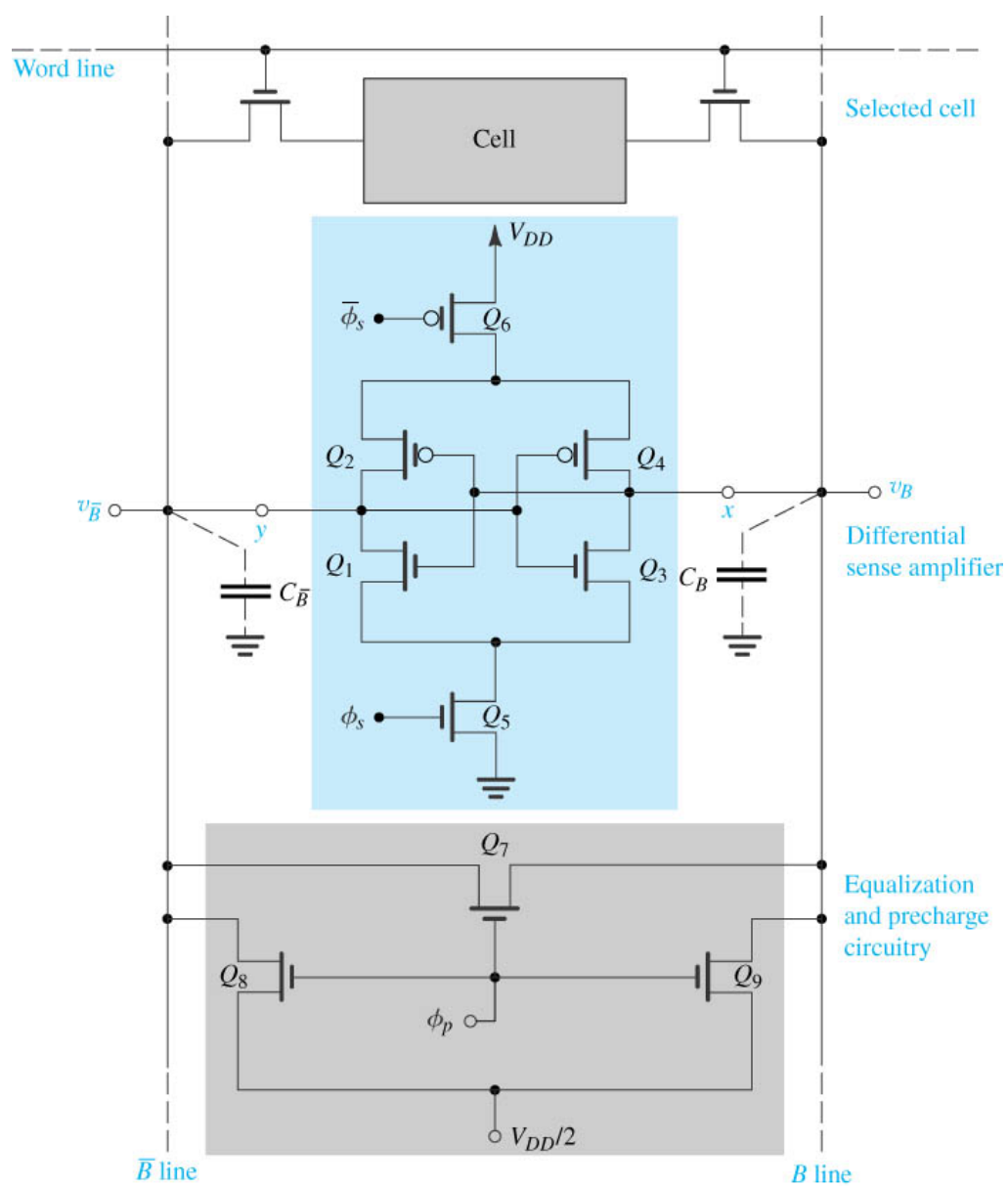


 - Figure 11.23** A differential sense amplifier connected to the bit lines of a particular column. This arrangement can be used directly for SRAMs (which utilize both the  $B$  and  $\bar{B}$  lines). DRAMs can be turned into differential circuits by using the “dummy cell” arrangement shown in Fig. 11.25.





 
- **Figure 11.24** Waveforms of  $v_B$  before and after the activation of the sense amplifier. In a read-1 operation, the sense amplifier causes the initial small increment  $\Delta V(1)$  to grow exponentially to  $V_{DD}$ . In a read-0 operation, the negative  $\Delta V(0)$  grows to 0. Complementary signal waveforms develop on the  $B$  line.



- **Figure 11.21** The one-transistor dynamic RAM cell.



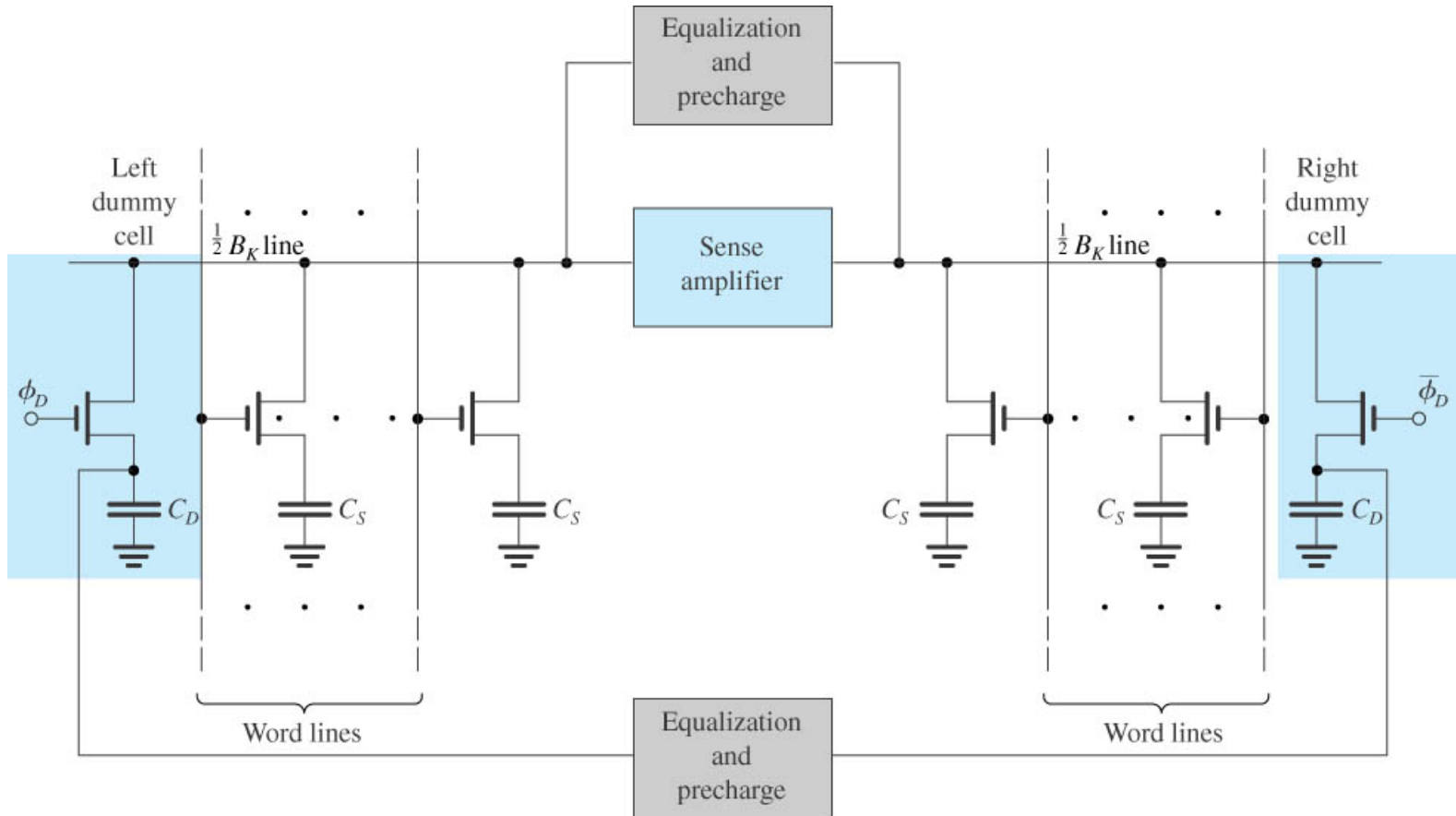- **Figure 11.22** When the voltage of the selected word line is raised, the transistor conducts, thus connecting the storage capacitor  $C_S$  to the bit-line capacitance  $C_B$ .



- **Figure 11.25** An arrangement for obtaining differential operation from the single-ended DRAM cell. Note the dummy cells at the far right and far left.