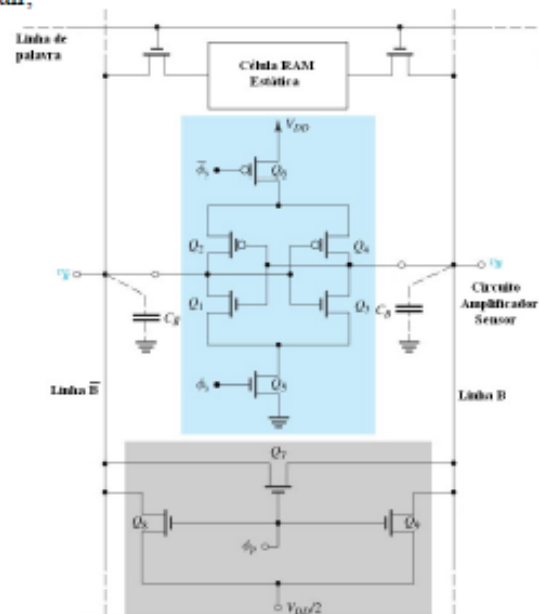


PSI3024 – Eletrônica

Aula 38

2023

Para o circuito a seguir,



- Explique a função do bloco formado pelos transistores Q_7, Q_8 e Q_9 .
- Explique o ciclo de leitura da célula de memória RAM estática, através do bloco amplificador sensor e do bloco formado pelos transistores Q_7, Q_8 e Q_9 . Inicie a explicação esboçando os perfis temporais das fases ϕ_s e ϕ_p , e “linha de palavra” nos diagramas a seguir.





EXEMPLO 10.3

Considere o inversor pseudo-NMOS fabricado na tecnologia CMOS especificada no Exemplo 10.1, ou seja, $\mu_n C_{ox} = 115 \mu\text{A/V}^2$, $\mu_p C_{ox} = 30 \mu\text{A/V}^2$, $V_{tn} = -V_{tp} = 0,4 \text{ V}$ e $V_{DD} = 2,5 \text{ V}$. Seja a razão W/L de Q_N de $(0,375 \mu\text{m}/0,25 \mu\text{m})$ e $r = 9$. Obtenha:

- (a) V_{OH} , V_{OL} , V_{IL} , V_{IH} , V_M , MR_H e MR_L
- (b) $(W/L)_p$
- (c) I_{estat} e P_D
- (d) t_{PLH} , t_{PHL} e t_P , supondo uma capacitância total na saída do inversor de 7 fF

Inversor pseudo-NMOS

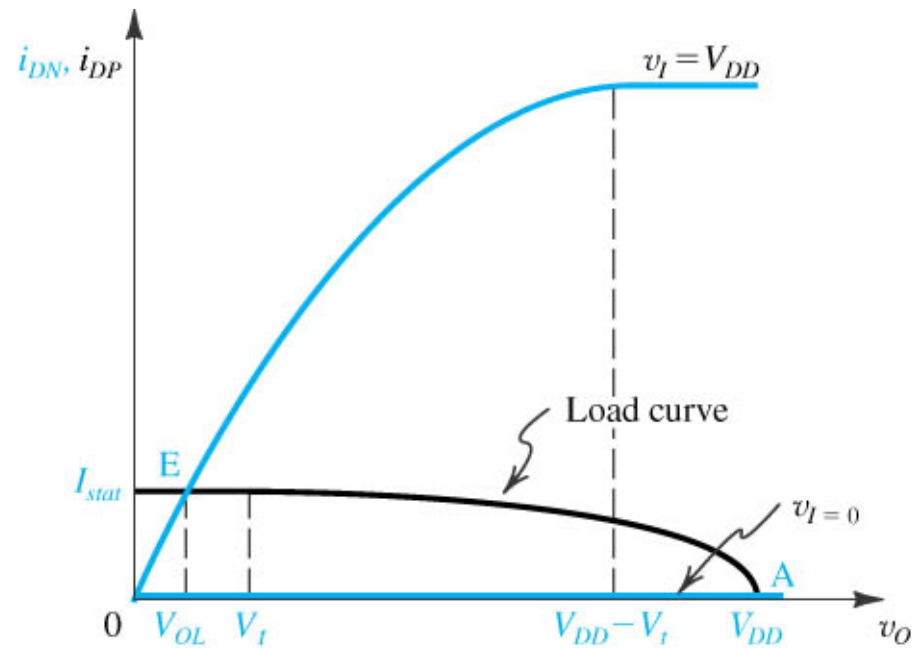 

Região II (segmento BC)

$$k_n = rk_p,$$


$$v_O = V_t + \sqrt{(V_{DD} - V_t)^2 - r(v_I - V_t)^2}$$

$$V_{IL} = V_t + \frac{V_{DD} - V_t}{\sqrt{r(r+1)}}$$

$$V_M = V_t + \frac{V_{DD} - V_t}{\sqrt{r+1}}$$

(ponto C)

$$v_O = v_I - V_t$$

 

Região IV (segmento DE)

$$k_n = rk_p$$

Região III (segmento CD)

ponto D $v_O = V_t$


$$\partial v_O / \partial v_I = -1 \text{ e } v_I = V_{IH}$$


$$V_{IH} = V_t + \frac{2}{\sqrt{3r}} (V_{DD} - V_t)$$

$$v_I = V_{DD}$$


$$V_{OL} = (V_{DD} - V_t) \left[1 - \sqrt{1 - \frac{1}{r}} \right]$$
 
$$v_O = (v_I - V_t) - \sqrt{(v_I - V_t)^2 - \frac{1}{r} (V_{DD} - V_t)^2}$$




 
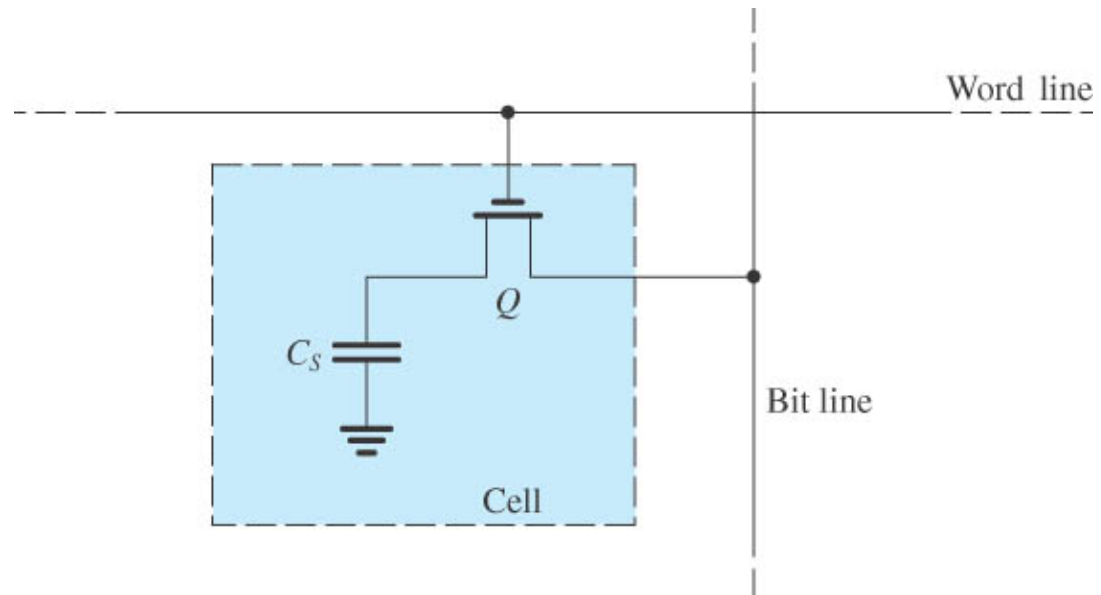
$$MR_L = V_t - (V_{DD} - V_t) \left[1 - \sqrt{1 - \frac{1}{r}} - \frac{1}{\sqrt{r(r+1)}} \right]$$




 
- **Figure 11.21** The one-transistor dynamic RAM cell.




- **Figure 11.25** An arrangement for obtaining differential operation from the single-ended DRAM cell. Note the dummy cells at the far right and far left.

 - A 2^{M+N} -bit memory chip organized as an array of 2^M rows $\times$ 2^N columns.




 

 
- Figure 11.24** Waveforms of v_B before and after the activation of the sense amplifier. In a read-1 operation, the sense amplifier causes the initial small increment $\Delta V(1)$ to grow exponentially to V_{DD} . In a read-0 operation, the negative $\Delta V(0)$ grows to 0. Complementary signal waveforms develop on the B line.



(a)

 


(b)


 


(c)

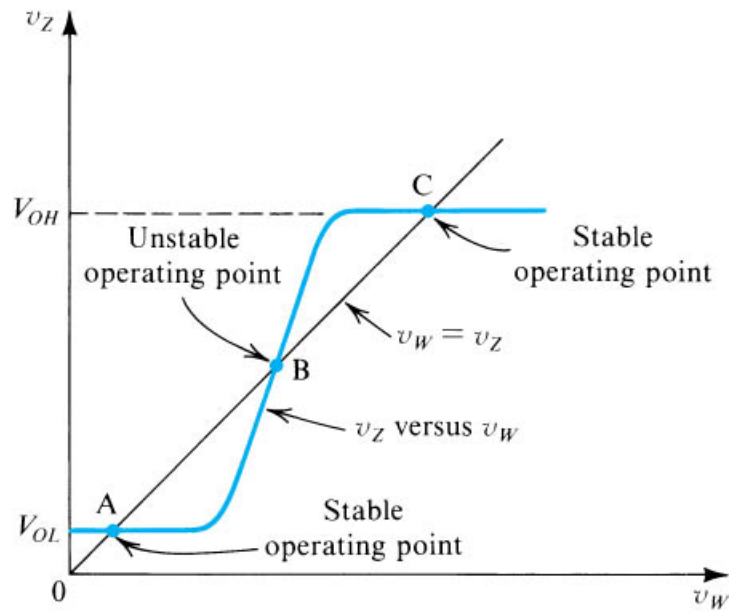
- **Figure 11.1** (a) Basic latch. (b) The latch with the feedback loop opened. (c) Determining the operating point(s) of the latch.



(c)

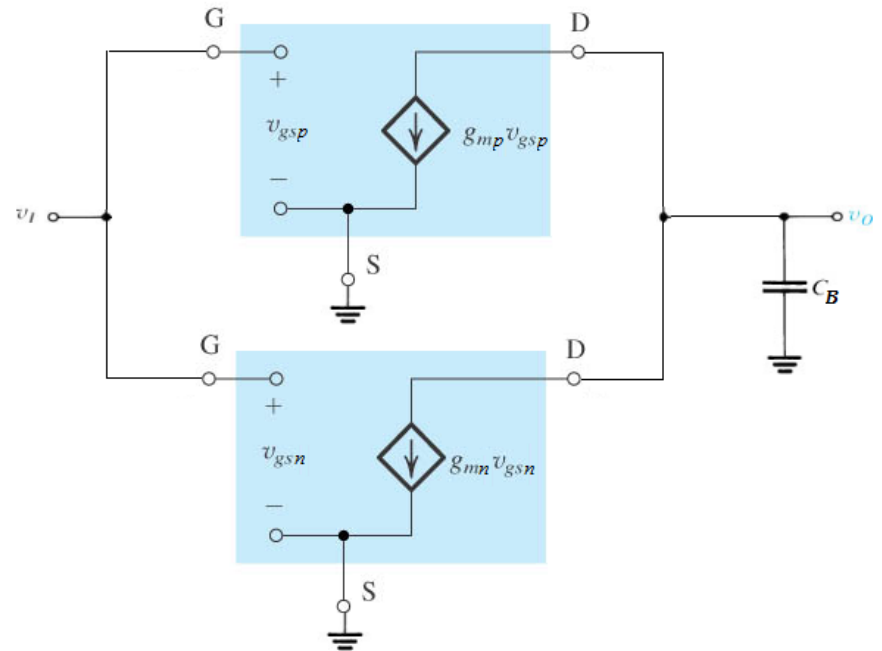 

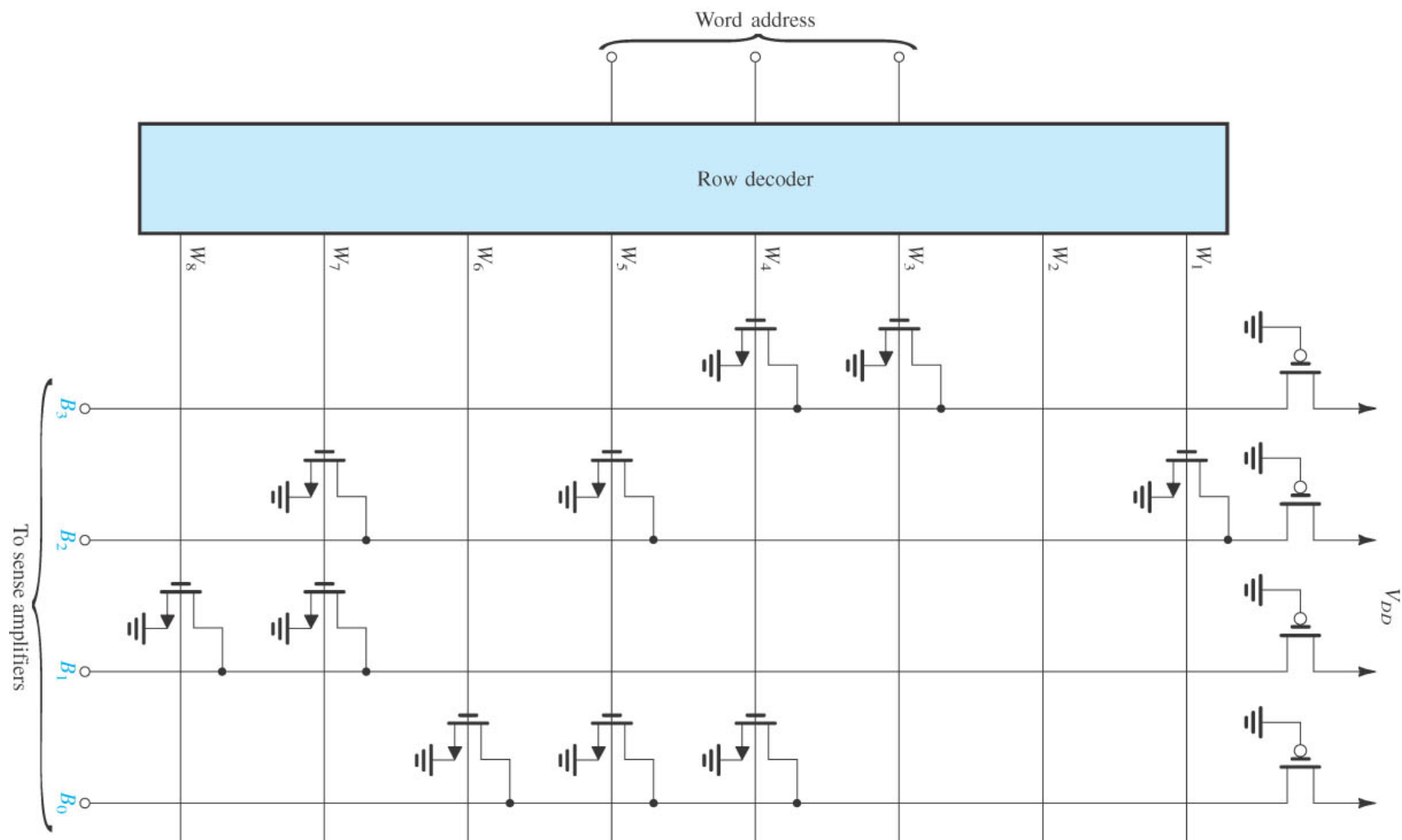- **Figure 11.1 (c)** Determining the operating point(s) of the latch.



- **Figure 11.29** A simple MOS ROM organized as 8 words $\times$ 4 bits.