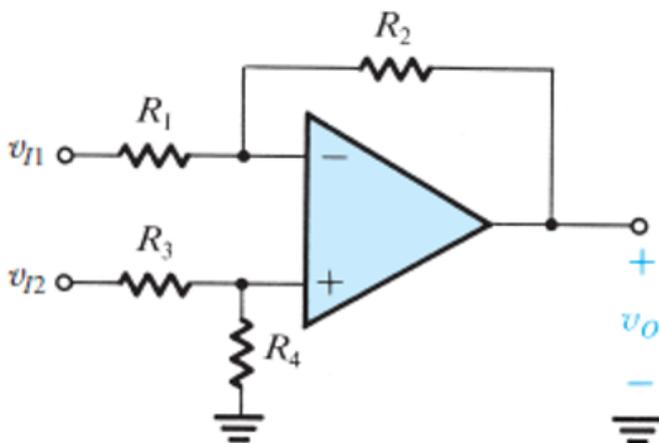


SEL0313 – Circuitos Eletrônicos I
Lista de Exercícios 1
(Amplificadores Operacionais)

Exercício 1

Consider the single op-amp difference-amplifier circuit for the case $R_1=R_3=2\text{k}\Omega$ and $R_2= R_4=200\text{ k}\Omega$. The resistors have 1% tolerance.

- a) Find the interval value of the differential gain A_d .
- b) Find the interval values of the differential input resistance R_{id} and the output resistance R_o .
- c) The best-case and worst-case common-mode gain A_{cm} and the corresponding value of CMRR.




$$A_d = \frac{R_2}{R_1}$$

$$R_{id} = 2 R_1$$

$$A_{cm} = \frac{R_4}{R_4 + R_3} \left(1 - \frac{R_2 R_3}{R_1 R_4} \right)$$

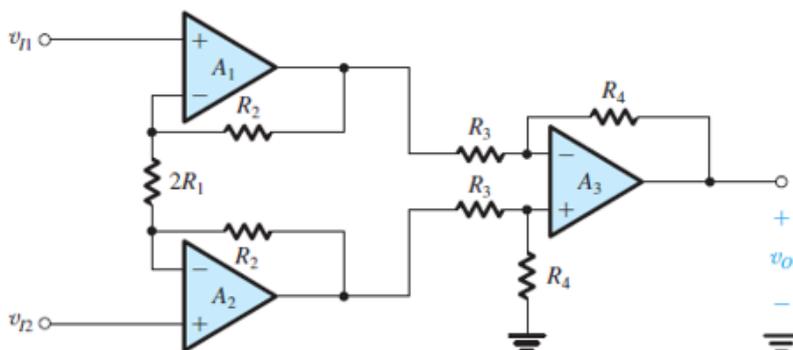Exercício 2

Design an instrumentation amplifier to provide a gain that can be varied over the range of 2 to 1000 utilizing a 100-k Ω variable resistance. Consider $R_3 = R_4$.



$$v_o = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{2R_1} \right) v_{Id}$$

Exercício 3


An op amp has a rated output voltage of $\pm 10\text{V}$. and a slew rate of $1\text{ V}/\mu\text{s}$.

a) What is its full-power bandwidth ?

b) If an input sinusoid with frequency $f = 5f_M$ is applied to a unity-gain follower constructed using this op amp, what is the maximum possible amplitude that can be accommodated at the output without incurring SR distortion?

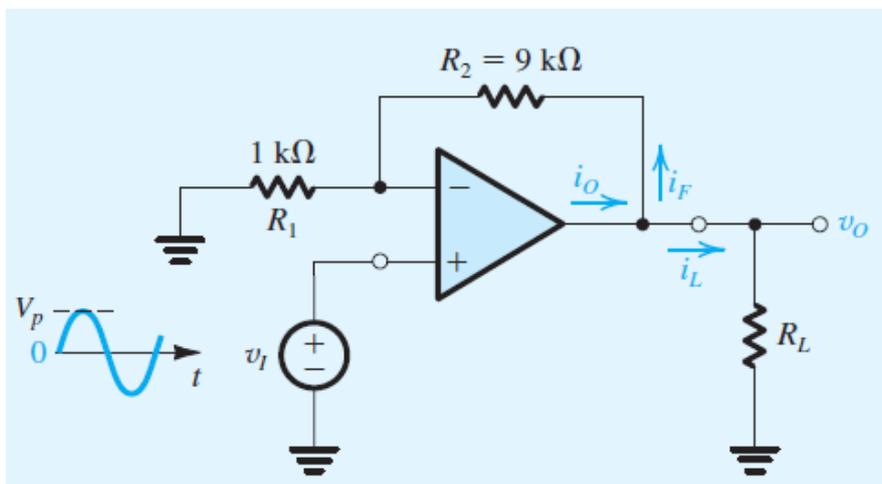Exercício 4

Consider the noninverting amplifier circuit shown below. The circuit is designed for a nominal gain $(1 + R_2/R_1) = 10\text{V}/\text{V}$. It is fed with a low-frequency sine-wave signal of peak voltage V_p and is connected to a load resistor R_L . The op amp is specified to have output saturation voltages $\pm 13\text{V}$ and output current limits of $\pm 20\text{mA}$.



Non-inverting Amplifier

a) For $V_p = 1\text{ V}$ and $R_L = 1\text{ k}\Omega$, specify the signal resulting at the output of the amplifier.

b) For $V_p = 1.5\text{ V}$ and $R_L = 1\text{ k}\Omega$, specify the signal resulting at the output of the amplifier.

c) For $R_L = 1\text{ k}\Omega$, what is the maximum value of V_p for which an undistorted sine-wave output is obtained ?

d) For $V_p = 1\text{ V}$, what is the lowest value of R_L for which an undistorted sine-wave output is obtained?