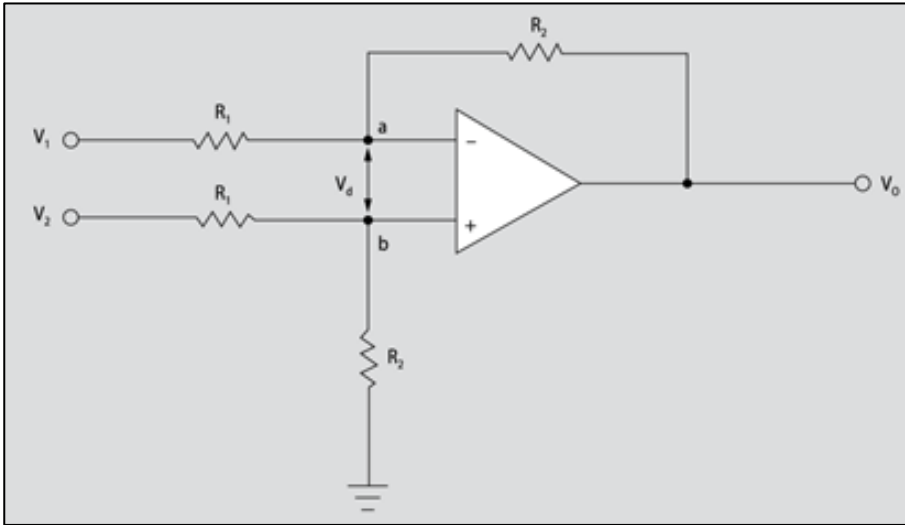


Single Op Amp Difference Amplifier

A Single Op-Amp Difference Amplifier



1 **Nó a:**


$$\frac{V_1 - V_a}{R_1} + \frac{V_o - V_a}{R_2} = 0$$

2 **Nó b:**

$$\frac{V_2 - V_b}{R_1} - \frac{V_b}{R_2} = 0$$

3 $V_a = V_b$ (virtual ground)

1 e **2** e **3**

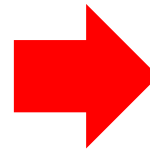

$$v_o = \frac{R_2}{R_1} (v_2 - v_1)$$

$\underbrace{\hspace{1.5cm}}_{A_d} \underbrace{\hspace{1.5cm}}_{V_{Id}}$

4

Although ideally the difference amplifier will amplify only the differential input signal v_{Id} and reject completely the common-mode input signal v_{Icm} , practical circuits will have an output voltage v_o given by

$$v_o = \frac{R_2}{R_1} (v_2 - v_1)$$

$$\underbrace{\quad}_{A_d} \underbrace{\quad}_{v_{Id}}$$

$$v_o = A_d v_{Id} + A_{cm} v_{Icm}$$

$$\left\{ \begin{array}{l} v_{Id} = v_2 - v_1 \\ v_{Icm} = \frac{v_1 + v_2}{2} \end{array} \right.$$

Where A_d denotes the amplifier differential gain and A_{cm} denotes its common-mode gain (ideally zero). The efficacy of a differential amplifier is measured by the degree of its rejection of common-mode signals in preference to differential signals. This is usually quantified by a measure known as the **common-mode rejection ratio (CMRR)**, defined as:

$$\text{CMRR} = \frac{|A_d|}{|A_{cm}|}$$




$$\text{CMRR} = 20 \log \frac{|A_d|}{|A_{cm}|} \quad (\text{dB})$$

Calculation of A_d and A_{cm}

A_d Calculation


1

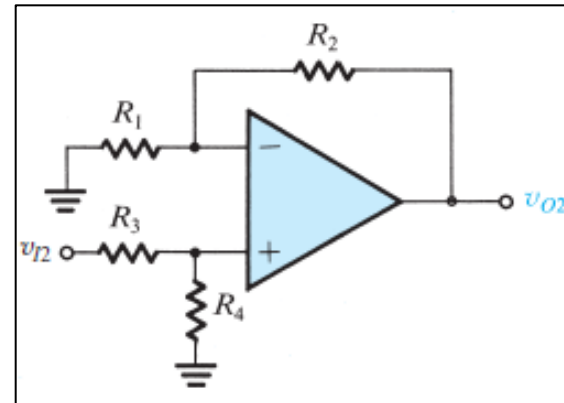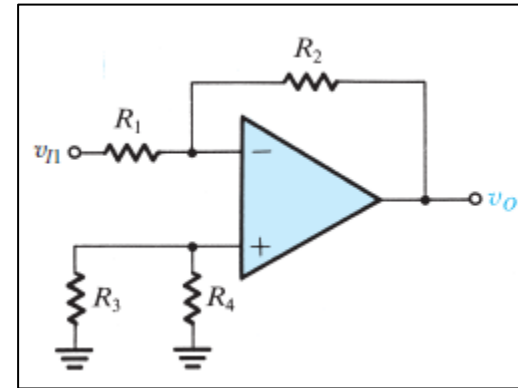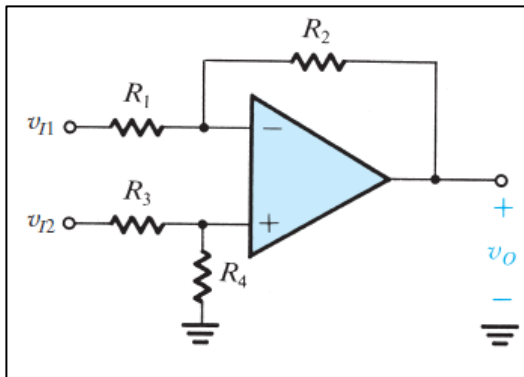Specifically, we wish to determine the output voltage v_O in terms of v_{I1} and v_{I2} . Toward that end, we observe that **the circuit is linear, and thus we can use superposition.**



2

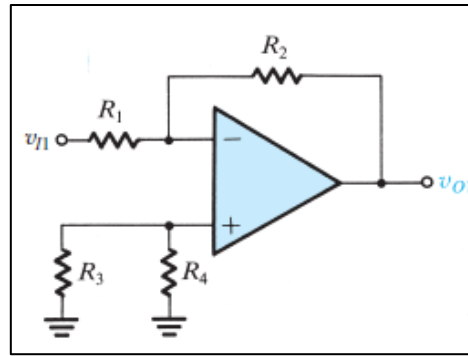
To apply superposition, we first **reduce v_{i2} to zero**, that is ground the terminal to which v_{i2} is applied, and then find the corresponding output voltage, which will be due entirely to v_{i1} . We denote this output voltage v_{o1} .



$$v_{o1} = -\frac{R_2}{R_1} v_{i1}$$


3

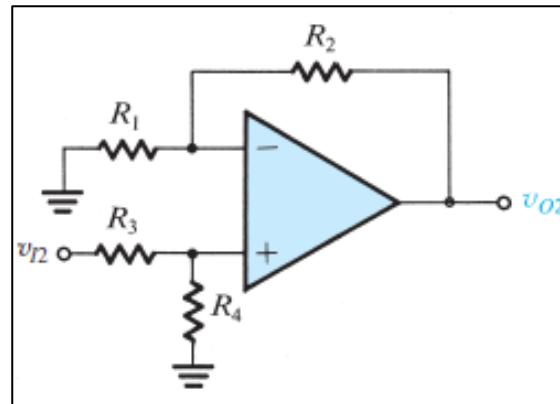Next, **we reduce v_{i1} to zero** and evaluate the corresponding output voltage v_{o2} . The circuit will now take the form shown which we recognize as the noninverting configuration with an additional voltage divider, made up of R_3 and R_4 , connected to the input v_{i2} .



$$v_{o2} = v_{i2} \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right)$$

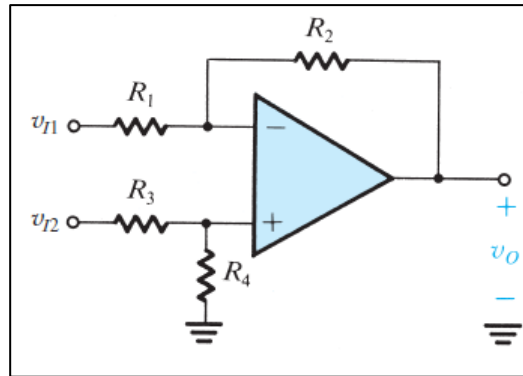If $\frac{R_4}{R_3} = \frac{R_2}{R_1} \rightarrow v_{o2} = v_{i2} \frac{R_2}{R_1}$



- 4** The superposition principle tells us that the output voltage v_o is equal to the sum of v_{o1} and v_{o2} . Thus we have:

$$v_{o1} = -\frac{R_2}{R_1} v_{I1}$$

+

$$v_{o2} = v_{I2} \frac{R_2}{R_1}$$




$$v_o = \frac{R_2}{R_1} (v_{I2} - v_{I1})$$

$$v_o = A_d v_{Id} + A_{cm} v_{Icm} \quad \longrightarrow \quad A_d = \frac{R_2}{R_1}$$

A_{cm} Calculation

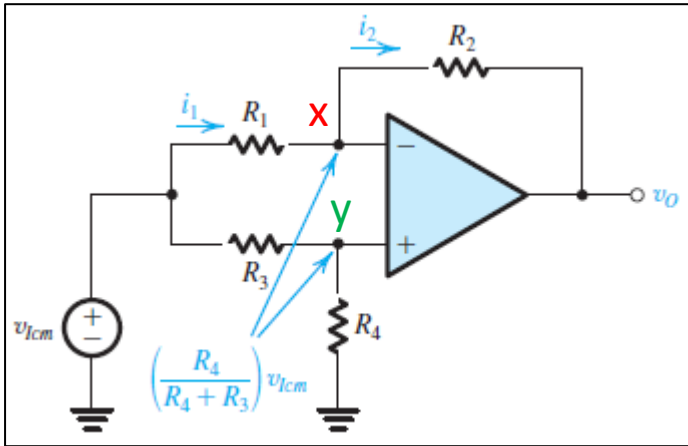5 Let's next consider the circuit with only a common-mode signal applied at the input, as shown in the circuit below:



5.1 $V_x = V_y$

5.2
$$i_1 = \frac{1}{R_1} \left[v_{Icm} - \frac{R_4}{R_4 + R_3} v_{Icm} \right] = v_{Icm} \frac{R_3}{R_4 + R_3} \frac{1}{R_1}$$

5.3
$$v_o = \frac{R_4}{R_4 + R_3} v_{Icm} - i_2 R_2$$

5.4 $i_2 = i_1$

Any mismatch in the resistance ratios can make A_{cm} nonzero and hence CMRR finite !

5.1 to **5.4**



$$v_o = \frac{R_4}{R_4 + R_3} \left(1 - \frac{R_2 R_3}{R_1 R_4} \right) v_{Icm}$$

$$v_o = A_d v_{Id} + A_{cm} v_{Icm}$$



$$A_{cm} = \frac{R_4}{R_4 + R_3} \left(1 - \frac{R_2 R_3}{R_1 R_4} \right)$$

$$\frac{R_4}{R_3} = \frac{R_2}{R_1}$$




$$A_{cm} = 0$$

Importance in Instrumentation


A Single-Op Difference Amplifier

A **difference amplifier** is one that responds to the difference between the two signals applied at its input and ideally rejects signals that are common to the two inputs.

Difference Amplifier

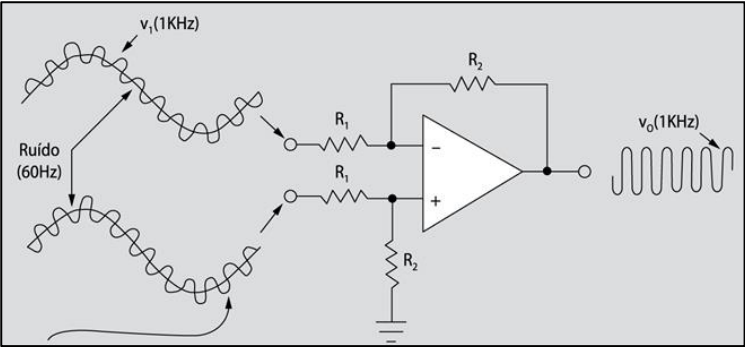

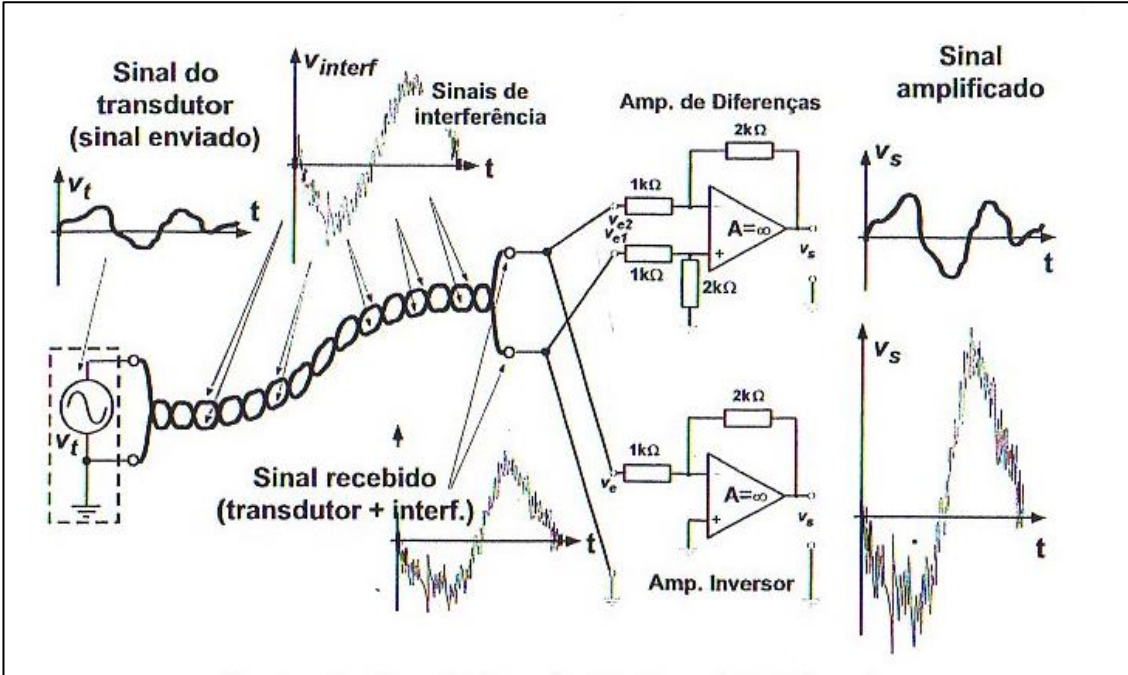**Difference Amplifier
X
Inversor Amplifier**




Input Resistance

Input Resistance


1

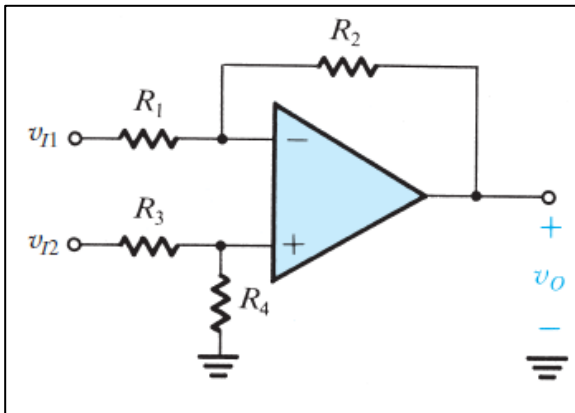In addition to rejecting common-mode signals, a difference amplifier is usually required to have a high input resistance. To find the input resistance between the two input terminals (i.e., the resistance seen by v_{id}), called the **differential input resistance** R_{id} , consider the circuit below. Here we have assumed that the resistors are selected so that:



$$R_3 = R_1$$

$$R_4 = R_2$$

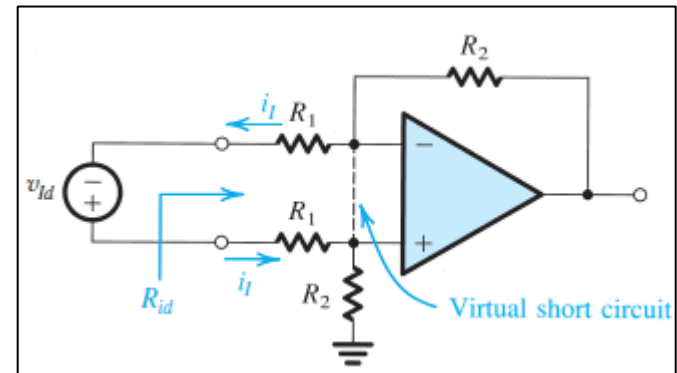

2

Since the two input terminals of the op amp track each other in potential, we may write a loop equation and obtain:

$$v_{id} = R_1 i_1 + R_1 i_2$$

$$R_{id} = \frac{v_{id}}{i_1}$$



$$R_{id} = 2R_1$$

Disadvantages

Disadvantages

1

$$v_o = \frac{R_2}{R_1} (v_{I2} - v_{I1})$$

$$R_{id} = 2R_1$$

If the amplifier is required to have a large differential gain, then R_1 will be relatively small and the input resistance will be correspondingly low.

if R_1 is chosen with a high value, let's say $1 \text{ M}\Omega$, it would require a higher R_2 value for getting a desirable gain which makes the circuit impractically !

2

Another drawback of the circuit is that it is not easy to vary the differential gain of the amplifier because there are two R_1 resistances.



Both of these drawbacks are overcome with another kind of difference amplifier named **instrumentation amplifier !**

CMRR Measurement

$$v_o = A_d v_d + A_c v_c$$

$$v_d = v_1 - v_2$$

$$v_c = \frac{v_1 + v_2}{2}$$

A_d - differential gain

A_c - common mode gain

1 If $v_c = 0$

$$A_d = \frac{v_o}{v_d}$$

$$\rightarrow v_1 = -v_2$$

$$v_d = v_1 - v_2 = 2v_1$$

$$A_d = \left| \frac{v_o}{2v_1} \right|$$

$$\text{If } v_1 = 0,5V$$

$$\rightarrow A_d = |v_{od}|$$

2 if $v_d = 0$

$$A_c = \frac{v_o}{v_c}$$

$$\rightarrow v_1 = v_2$$

$$v_c = v_2$$

$$A_c = \left| \frac{v_o}{v_1} \right|$$


$$\text{If } v_1 = 1V$$

$$\rightarrow A_c = |v_{oc}|$$

$$\rightarrow \text{CMRR} = \left| \frac{A_d}{A_c} \right|$$


A_d Measurement

3 A_d measurement using $|v_1^{\max}| = |v_2^{\max}| = 0,5V$.

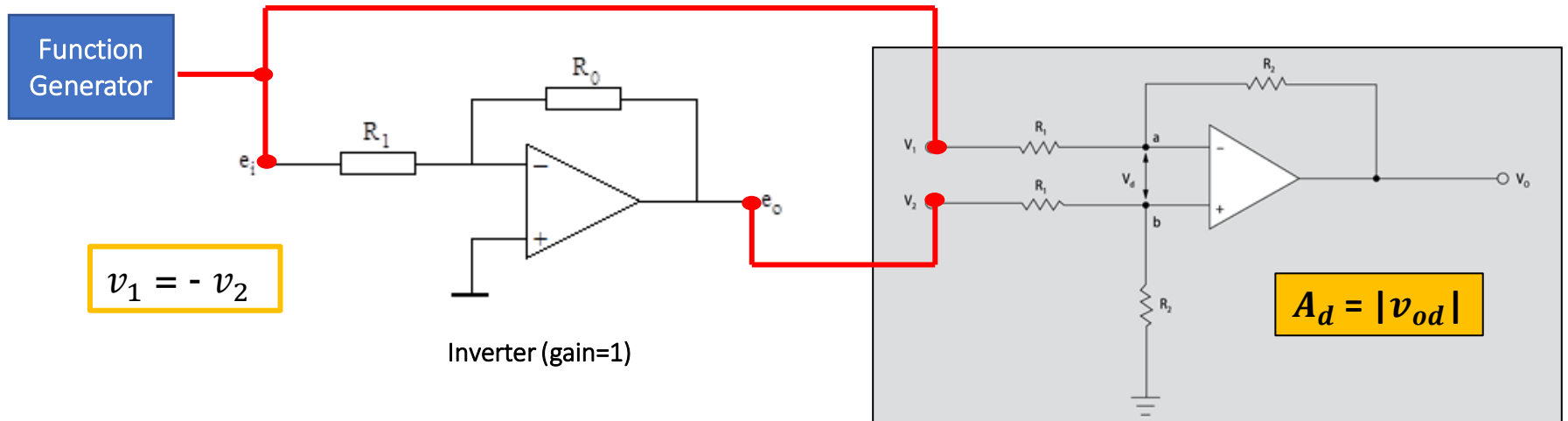

A_c Measurement

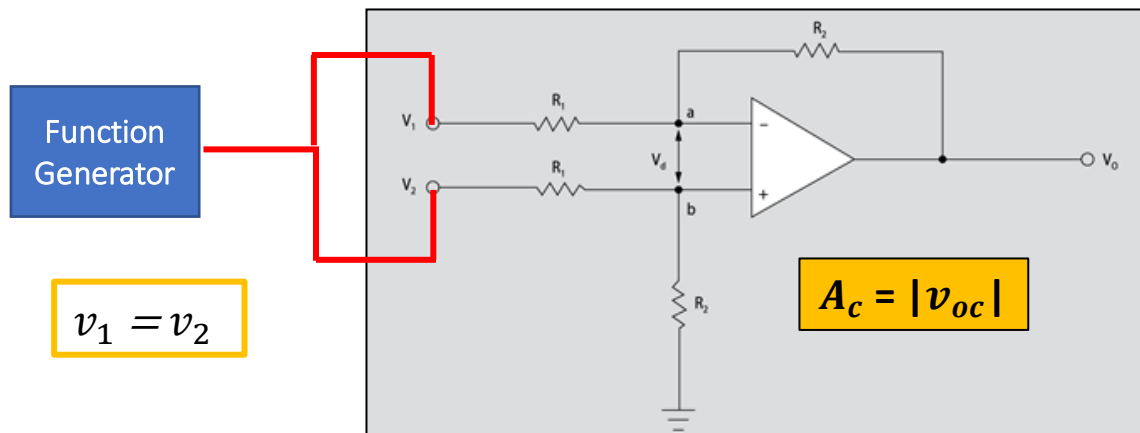4 A_c measurement using $v_1^{\max} = v_2^{\max} = 1V$.




$$CMRR = \left| \frac{A_d}{A_c} \right|$$

CMRR measurement is made in different frequencies !

$$\text{CMRR} = \left| \frac{A_d}{A_c} \right|$$

f (Hz)	$A_d = v_{od} $	$A_c = v_{oc} $	$\text{CMRR} = \frac{ A_d }{ A_c }$
60			
1K			
5K			
7K			
10K			

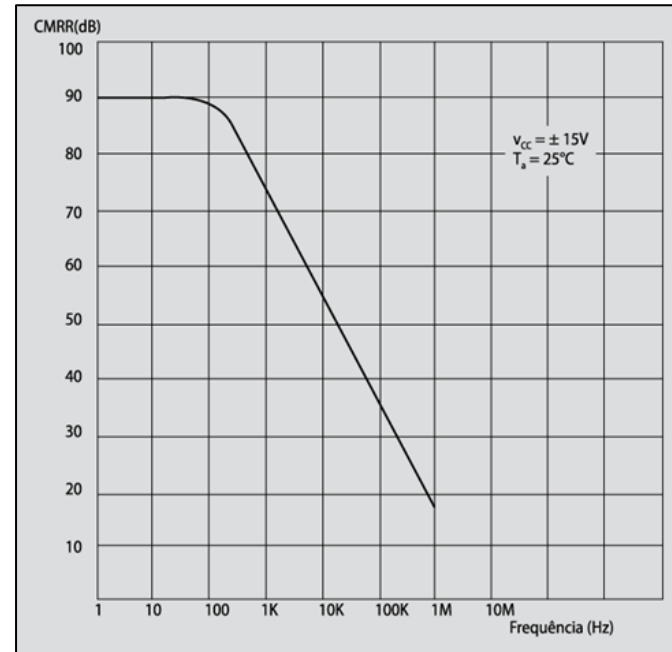

Typical CMRR Curve

CMRR Measurement in the LTSPice

CMRR measurement results in simulation are very close to the ones using integrated circuits!

$$CMRR = \left| \frac{A_d}{A_c} \right|$$

