

Architecting Speed

By Prof. Vanderlei Bonato

Estudo de caso – cálculo da potência de 3

- Código sequencial para X^3 :

$X = ?$

$XPower = 1;$

for($i=0; i<3; i++$)


$XPower = XPower * X;$

Cálculo sequencial em hw

```
module XPowerIterative(  
    output      reg[7:0] XPower,  
    output      finished,  
    input [7:0] X,  
    input clk, start);  
  
    reg [7:0] ncount;  
    assign finished = (ncount == 0);  
  
    always@(posedge clk)begin  
        if(start) begin  
            XPower <= X;  
            ncount <= 2;  
        end  
        else if(!finished) begin  
            ncount <= ncount -1;  
            XPower <= XPower * X;  
        end  
    end  
end  
endmodule
```

module XPowerIterative

Throughput?
Latency?
Timing?

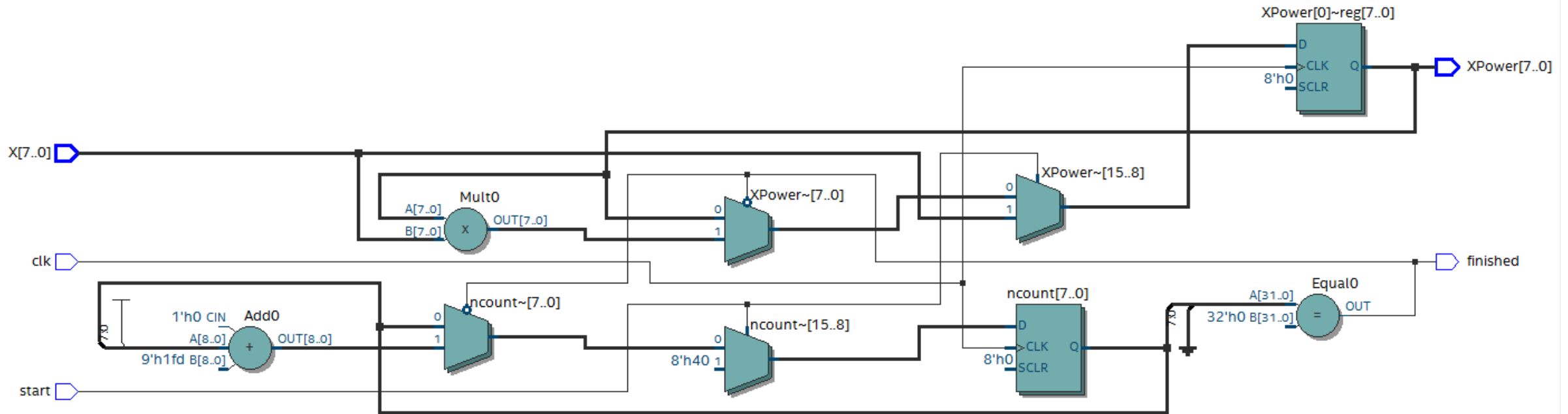


module XPowerPipelined


```
module XPowerPipelined(  
    output [7:0]XPower,  
    input [7:0]X,  
    input clk);  
  
    reg [7:0] XPower1, XPower2, XPower3;  
    reg [7:0] X1, X2;  
  
    assign XPower = XPower3;  
    always@(posedge clk)begin  
        //Load pipeline  
        X1 <= X;  
        XPower1 <=X;  
  
        //Pipeline stage 1  
        X2 <= X1;  
        XPower2 <= XPower1 * X1;  
  
        //Pipeline stage 2  
        XPower3 <= XPower2 * X2; //qual o efeito no pipeline se usar X1 no lugar de X2?  
  
    end  
endmodule
```

module XPowerPipelined

Throughput?
Latency?
Timing?

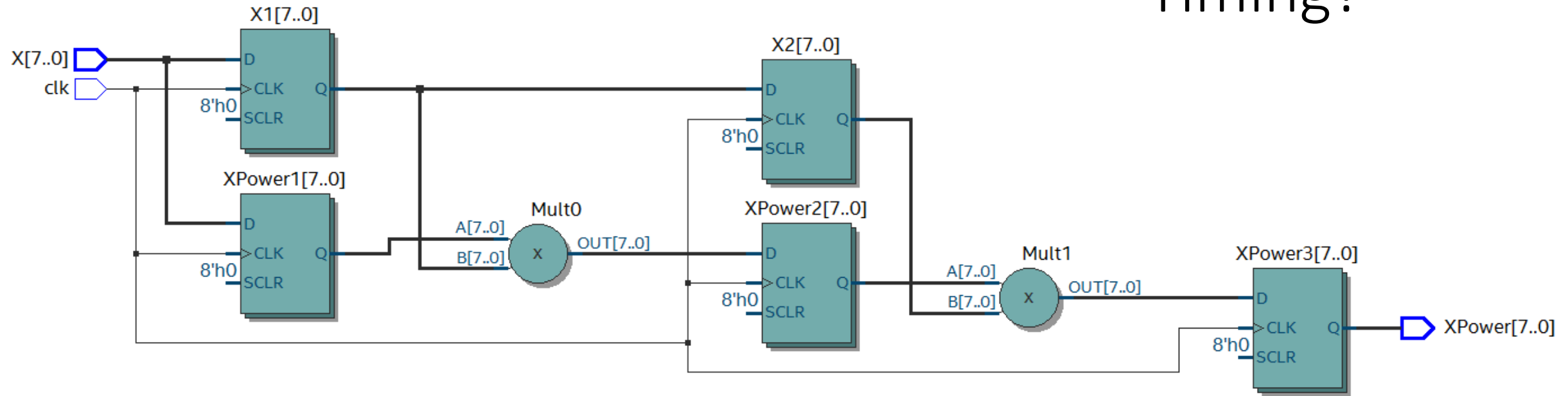

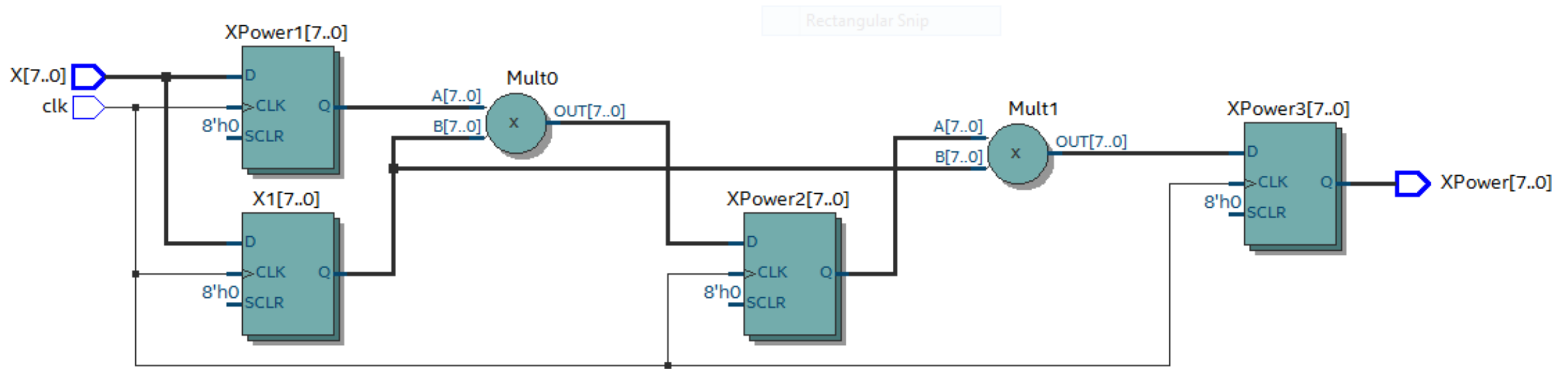Qual o efeito no pipeline se usar X1 no lugar de X2?



Throughput?
Latency?
Timing?

module combinatorial


```
module combinatorial(  
    output [7:0]XPower,  
    input [7:0]X  
);  
    reg [7:0] XPower1, XPower2;  
    reg [7:0] X1, X2;  
    assign XPower = XPower2 * X2; //mult 2  
    always @* begin  
        //Load data  
        X1 <= X;  
        XPower1 <=X;  
  
    end  
    always @* begin  
        //mult 1  
        X2 <= X1;  
        XPower2 <=XPower1 * X1;  
    end  
endmodule
```

Or


```
module combinatorial(  
    output [7:0]XPower,  
    input [7:0]X  
);  
  
    assign XPower = X * X * X; //x2  
  
endmodule
```

module combinatorial

Throughput?
Latency?
Timing?

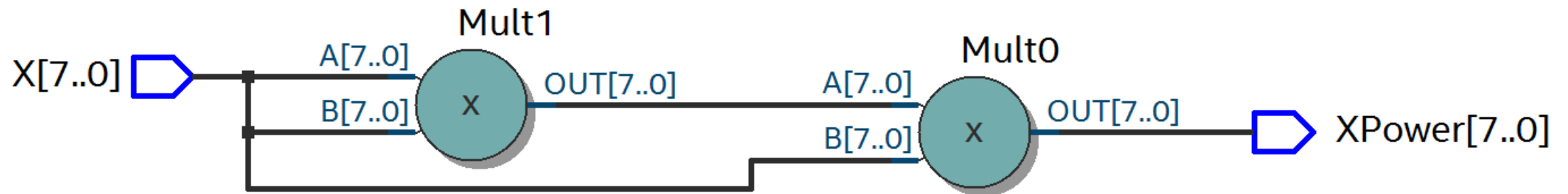

Or

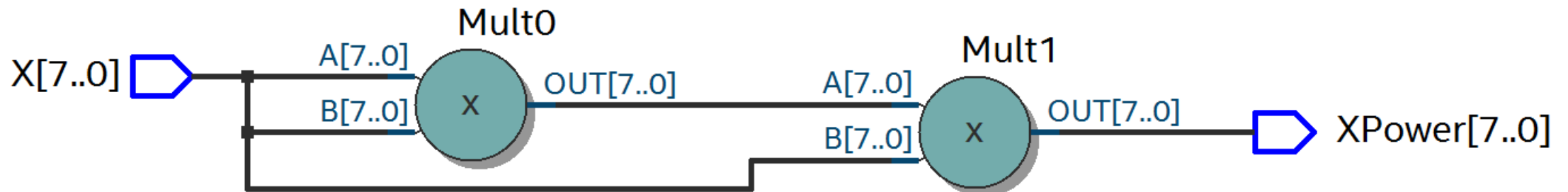

Exercício 1

- Simular todos esses circuitos
- Sintetizar para obter a frequência de operação
- Verificar para cada circuito
 - Throughput
 - Latency
 - Timing

Exercício 2

- Crie hardware para multiplicação de matriz nas três versões:
 - Iterativa,
 - Pipeline e
 - Combinacional;
- Tamanho da matriz $A_{5,3}$ e $B_{3,4}$;
- Números inteiros de 16 bits cada