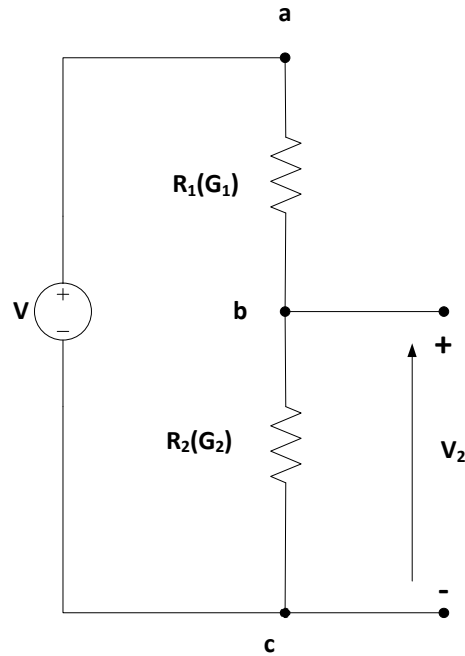



DIVISORES DE TENSÃO E CORRENTE

DIVISORES DE TENSÃO



$$V_2 = \frac{R_2}{R_1 + R_2} \cdot V = \frac{R_2}{R_{eqT}} \cdot V$$

$$V_2 = K \cdot V; \quad 0 < K < 1$$

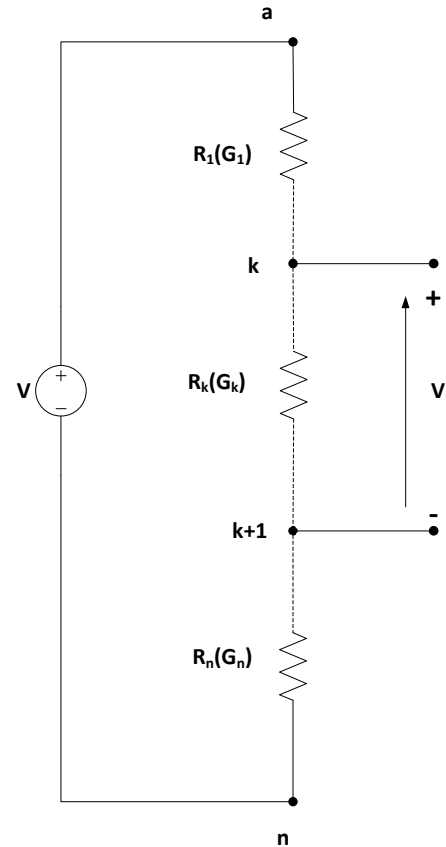


$$V_k = \frac{R_k}{\sum_{k=1}^n R_k} \cdot V = \frac{R_k}{R_{eqT}} \cdot V$$

$$V_k = K \cdot V; \quad 0 < K < 1$$

$$V_2 = \frac{G_{eqT}}{G_2} \cdot V = \frac{G_1}{G_1 + G_2} \cdot V$$

$$V_k = \frac{G_{eqT}}{G_k} \cdot V = \frac{\prod_{j \neq k} G_j}{\sum G_k} \cdot V$$

DIVISORES DE TENSÃO (EFEITO DE CARGA)

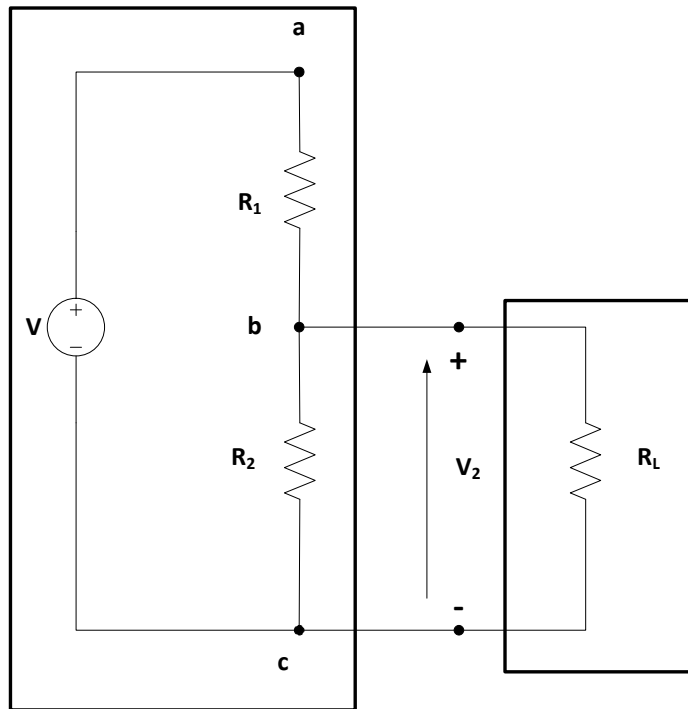

$$V_{2_{previsto}} = \frac{R_2}{R_1 + R_2} \cdot V = \frac{R_2}{R_{eqT}} \cdot V$$



$$V_{2_{previsto}} = K_1 \cdot V; \quad 0 < K_1 < 1$$

$$V_{2_{real}} = \frac{R_p}{R_1 + R_p} \cdot V = \frac{R_p}{R_{eqTnovo}} \cdot V$$

$$V_{2_{previsto}} = K_2 \cdot V; \quad 0 < K_1 < 1$$

$$V_{2_{previsto}} \leq V_{2_{real}}$$

DIVISORES DE TENSÃO (EFEITO DE CARGA)

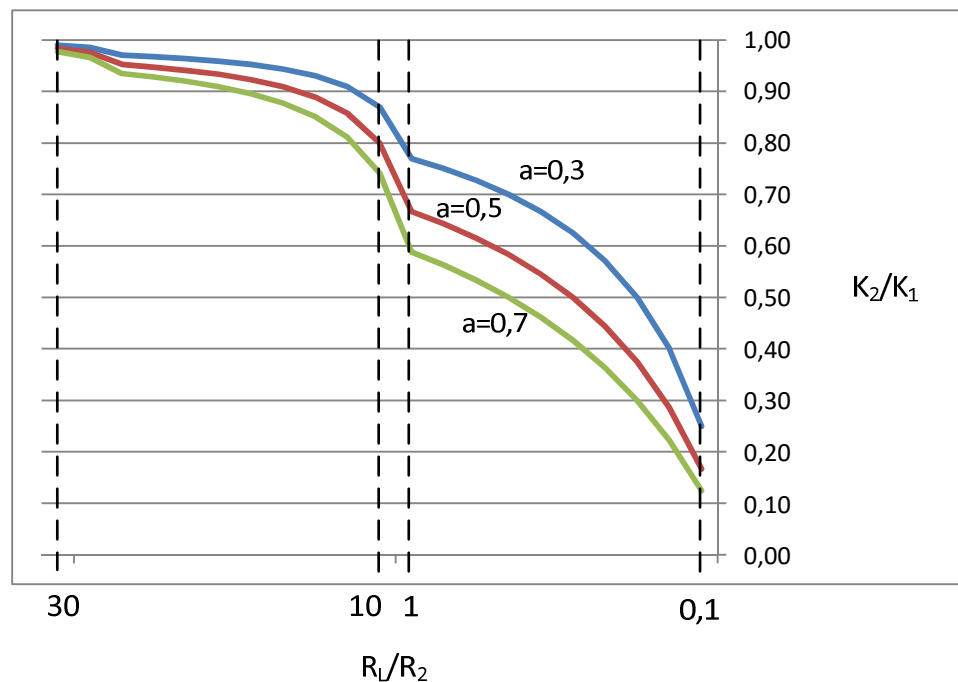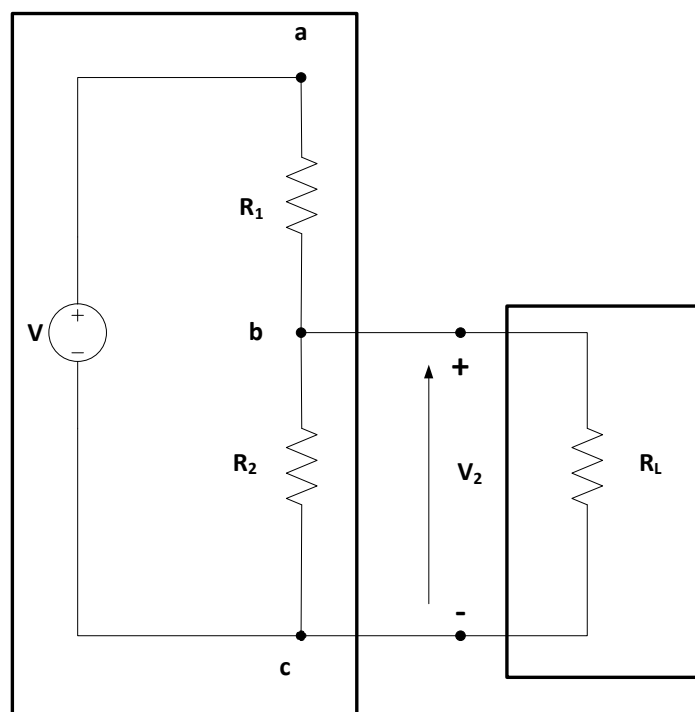


$$\frac{K_2}{K_1} = \frac{1}{1 + a/k}$$

$$a = \frac{R_1}{R_{eqT}}$$

$$R_{eqT} = R_1 + R_2$$


$$k = \frac{R_L}{R_2}$$

DIVISORES DE CORRENTE

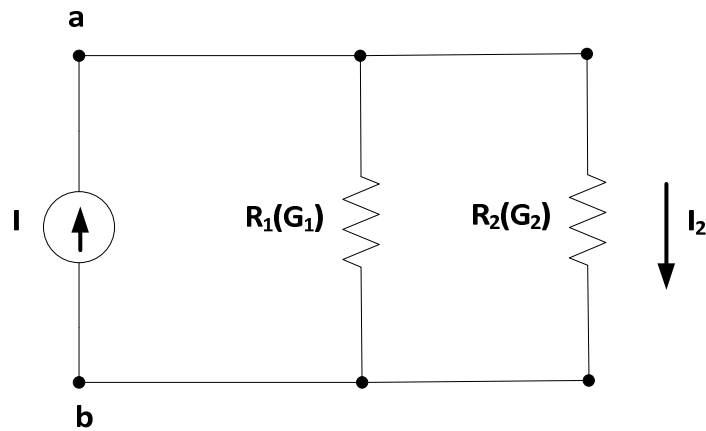

$$I_2 = \frac{G_2}{G_1 + G_2} \cdot I = \frac{G_2}{G_{eqT}} \cdot I$$

$$I_2 = K \cdot I; \quad 0 < K < 1$$

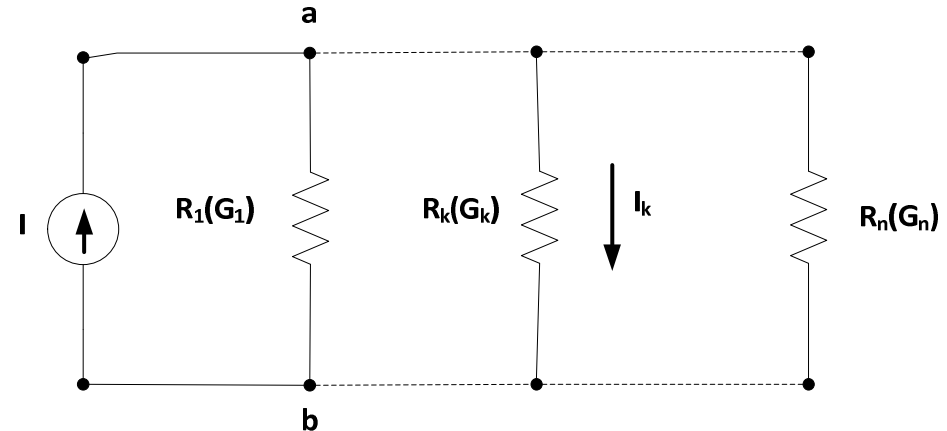

$$I_k = \frac{G_k}{\sum_{k=1}^n G_k} \cdot I = \frac{G_k}{G_{eqT}} \cdot I$$

$$I_k = K \cdot I; \quad 0 < K < 1$$

$$I_2 = \frac{R_{eqT}}{R_2} \cdot I = \frac{R_1}{R_1 + R_2} \cdot I$$

$$I_k = \frac{R_{eqT}}{R_k} \cdot I = \frac{\prod_{j \neq k} R_j}{\sum R_k} \cdot I$$