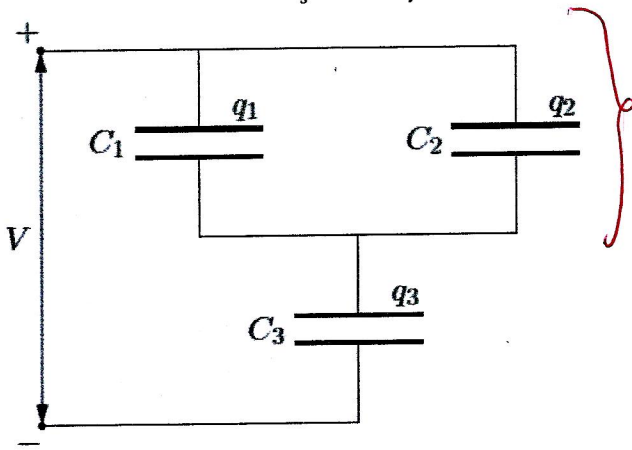


2) Considere o sistema esquematizado na figura.

(1,0): a) Determine a capacitância C equivalente do circuito em função de C_1, C_2, C_3 .


(1,0): b) Determine as cargas q_1, q_2 e q_3 considerando $C_1=C_2=C_3=C_0$.

$$Q=CV; C_p = \sum C_i; \frac{1}{C_s} = \sum \frac{1}{C_i}$$



Ligação em paralelo

$$C' = C_1 + C_2$$

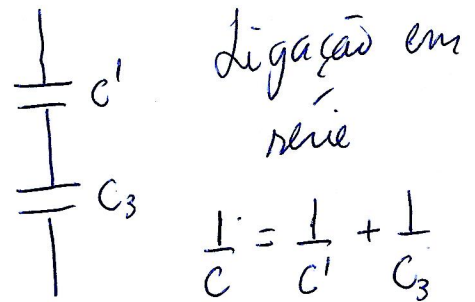

$$\frac{1}{C} = \frac{1}{C'} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{C_1 + C_2} + \frac{1}{C_3}$$


$$\frac{1}{C} = \frac{C_3 + C_1 + C_2}{C_3(C_1 + C_2)}$$

$$C = \frac{C_3(C_1 + C_2)}{C_1 + C_2 + C_3}$$

$$C = \frac{C_0(2C_0)}{3C_0} = \frac{2C_0}{3}$$

Quando $C_1=C_2=C_3=C_0$

$$C' = 2C_0$$

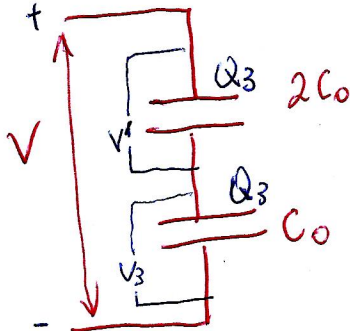

Mas capacitores em série tem a mesma carga

$$V = V' + V_3$$

$$V = \frac{Q_3}{2C_0} + \frac{Q_3}{C_0} = \frac{Q_3 + 2Q_3}{2C_0} = \frac{3Q_3}{2C_0}$$

$$Q_3 = \frac{2C_0 V}{3}$$

Os capacitores C_1 e C_2 estão no mesmo potencial V'

$$\frac{q_1}{C_0} = \frac{q_2}{C_0} = V' = \frac{Q_3}{2C_0} \Rightarrow$$

$$q_1 = q_2 = \frac{Q_3}{2} = \frac{C_0 V}{3}$$